


Semi-conductor

Logic Gates

① NOT Gate


Truth Table

A	$Y = \bar{A}$
0	1
1	0

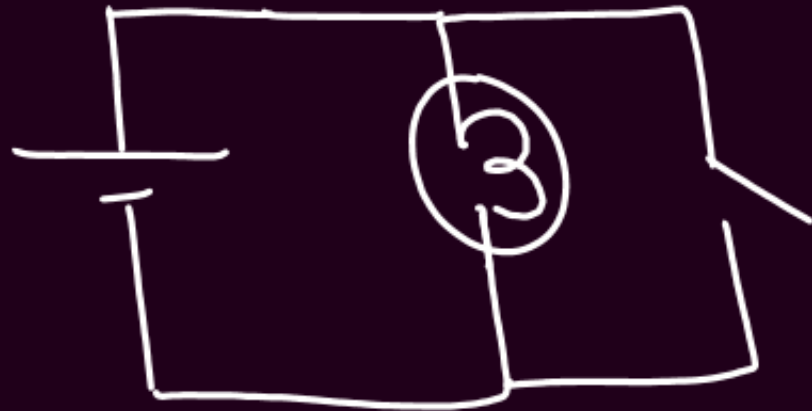

② OR Gate

A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

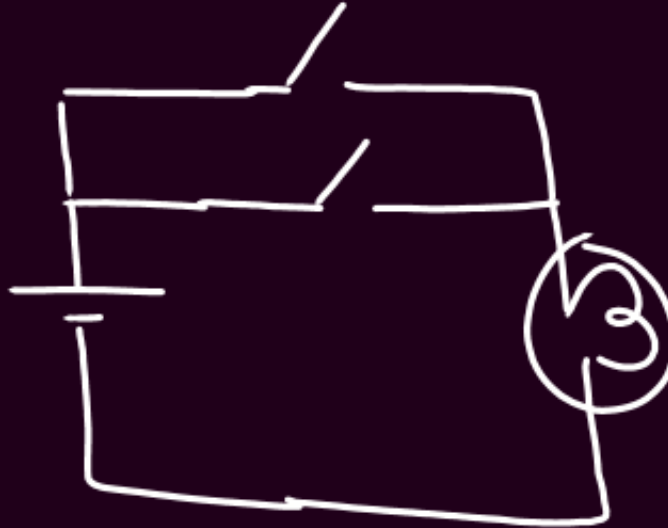

③ AND Gate



A	B	$Y = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1




④ NOR Gate $A \rightarrow$
 $B \rightarrow$  $\overline{A+B}$

A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

⑤ NAND Gate $A \rightarrow$
 $B \rightarrow$  $\overline{A.B}$

A	B	$\overline{A.B}$
0	0	1
0	1	1
1	0	1
1	1	0

⑥ XOR → Exclusive OR

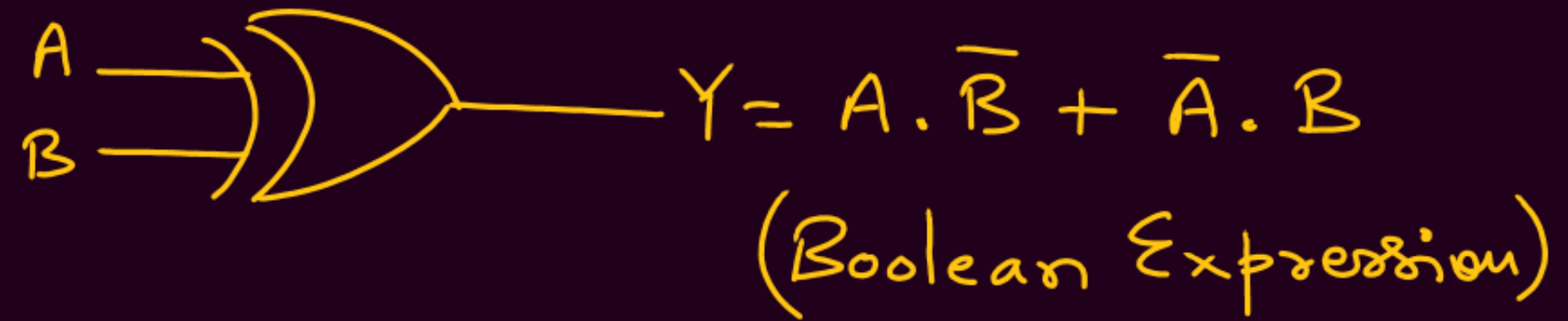


A	B	XOR
0	0	0
0	1	1
1	0	1
1	1	0

⑦ XNOR






A	B	XNOR
0	0	1
0	1	0
1	0	0
1	1	1

①

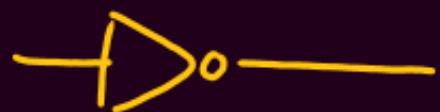


NOT

NOR

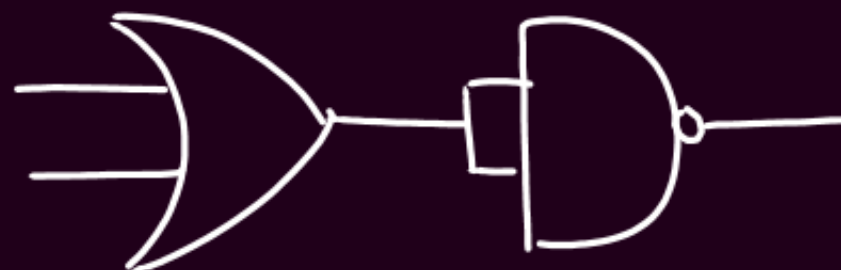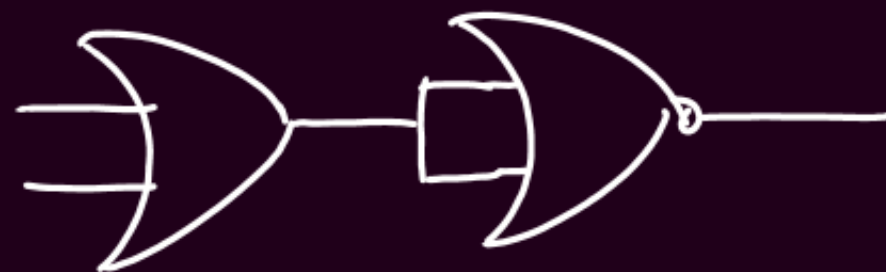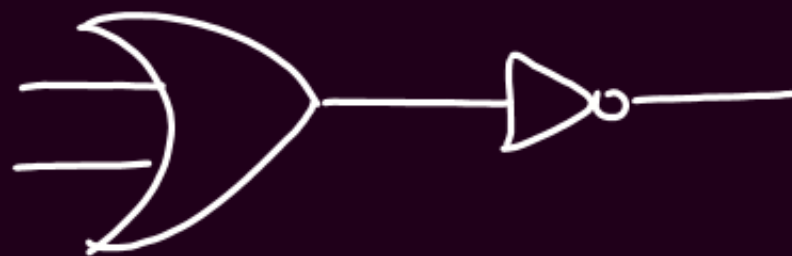

AND

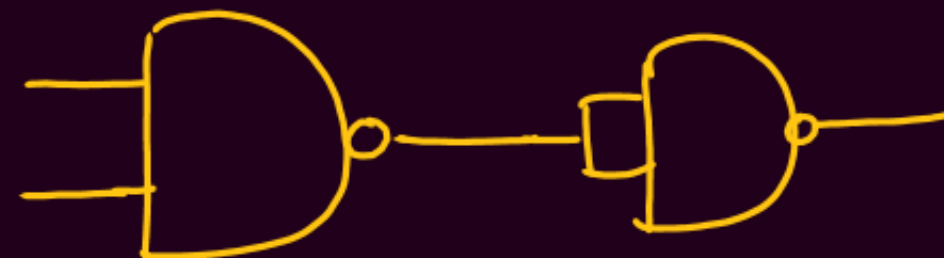



① AND



② NOR



A



B



① NAND



② XOR



Boolean Algebra

$$A \cdot A = A$$

$$A \cdot \bar{A} = 0$$

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A + A = A$$

$$A + \bar{A} = 1$$

$$A + 0 = A$$

$$A + 1 = 1$$

$$\textcircled{1} \quad \overline{A+B} = \bar{A} \cdot \bar{B}$$









$$\textcircled{2} \quad \overline{A \cdot B} = \bar{A} + \bar{B}$$

$$\textcircled{3} \quad A + AB = A$$

$$A(1+B) = A$$

$$\overline{\bar{A} + \bar{B}} = \overline{\bar{A}} \cdot \overline{\bar{B}} = A \cdot B$$
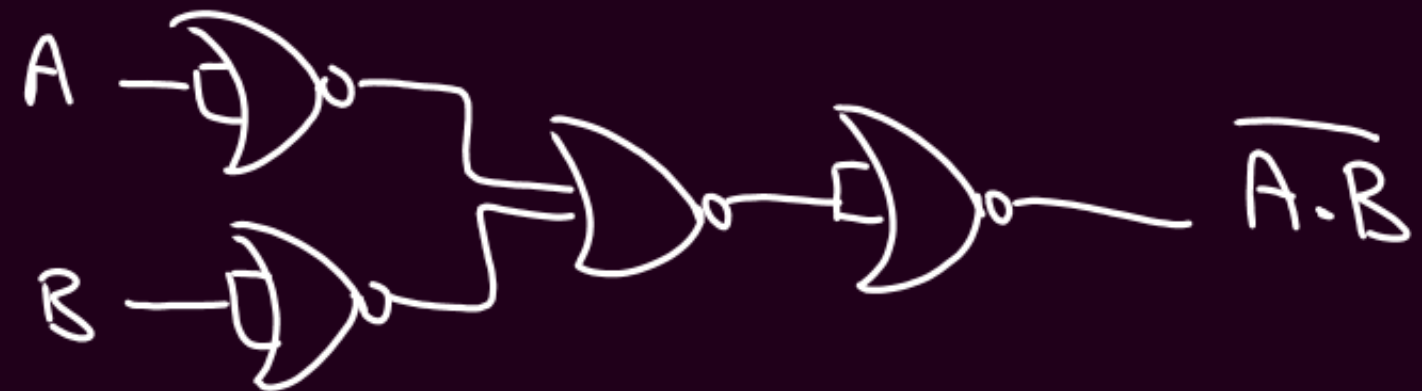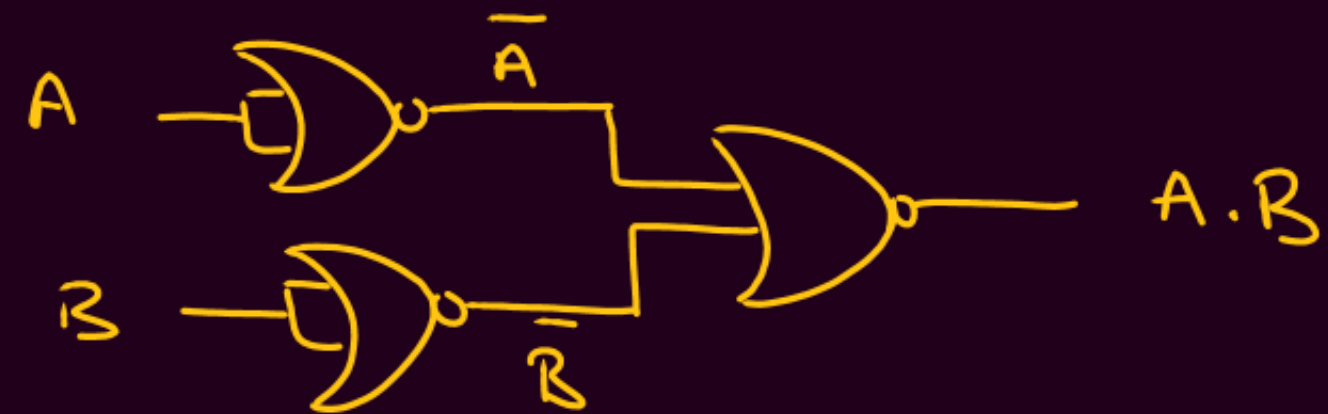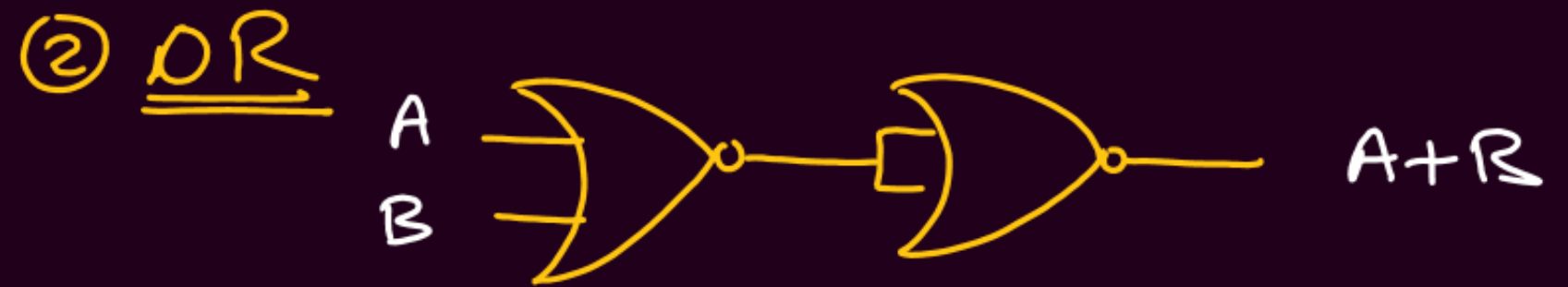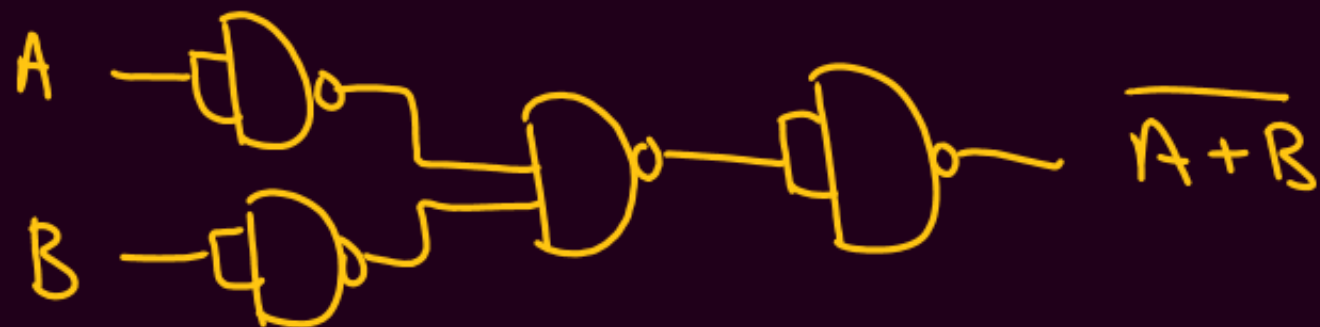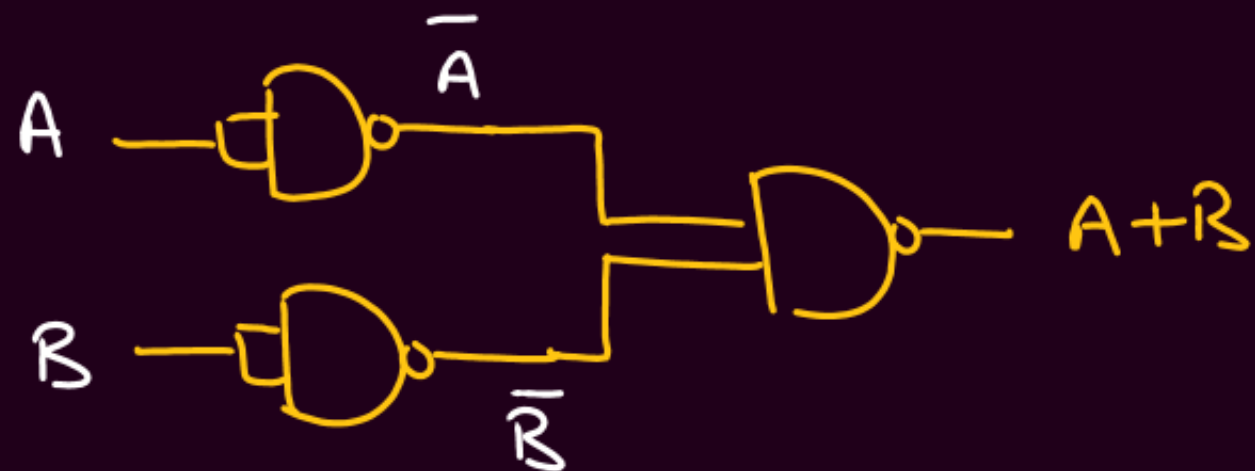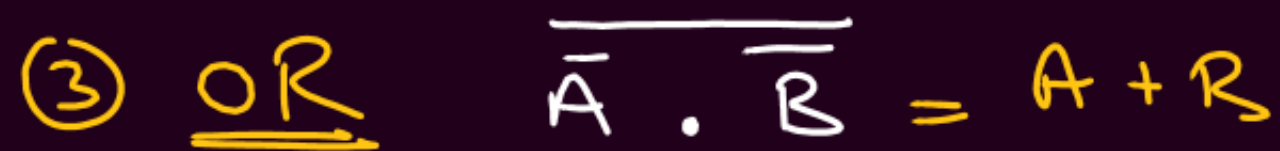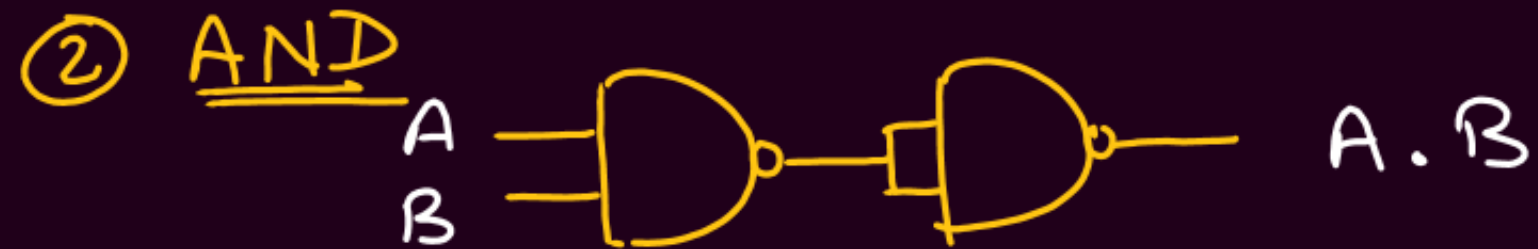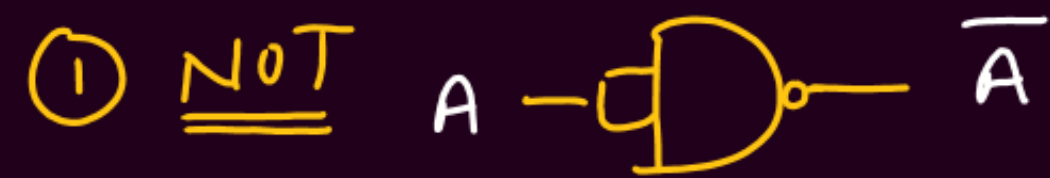
$$\overline{\bar{A} \cdot \bar{B}} = \overline{\bar{A}} + \overline{\bar{B}} = A + B$$




Min no. of Gates Req. to make

- ① NOT using NOR 1
- ② " " NAND 1
- ③ OR using NOR 2
- ④ AND using NAND 2
- ⑤ AND using NOR 3
- ⑥ NAND " " 4
- ⑦ OR using NAND 3
- ⑧ NOR " " 4

XOR


$$\bar{A} \cdot B + A \cdot \bar{B}$$


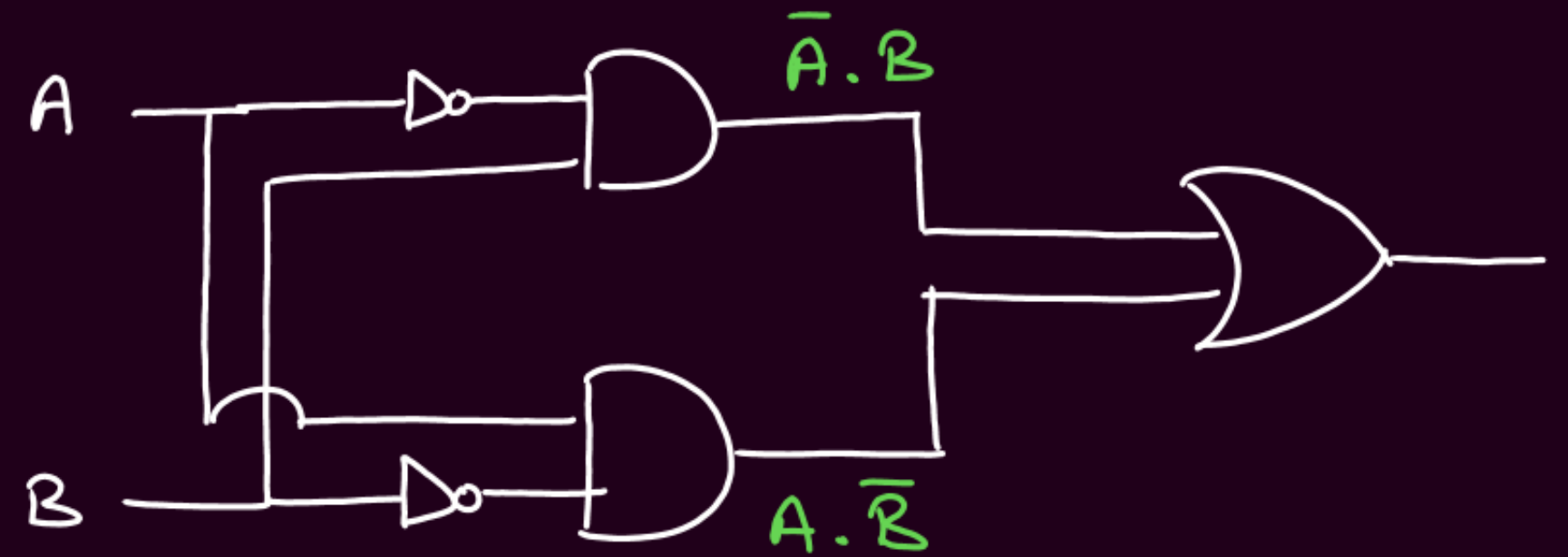


XNOR




$$A \cdot B + \bar{A} \cdot \bar{B}$$

$$\overline{A+B}$$

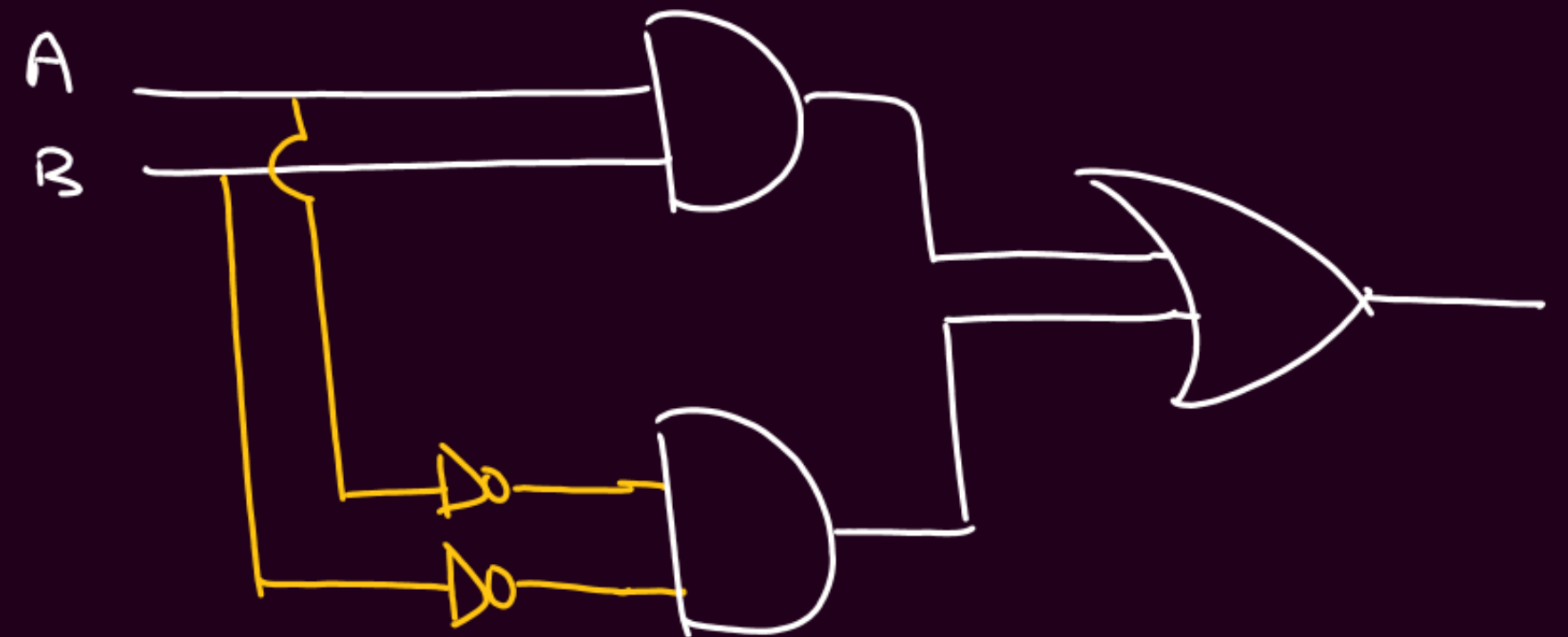

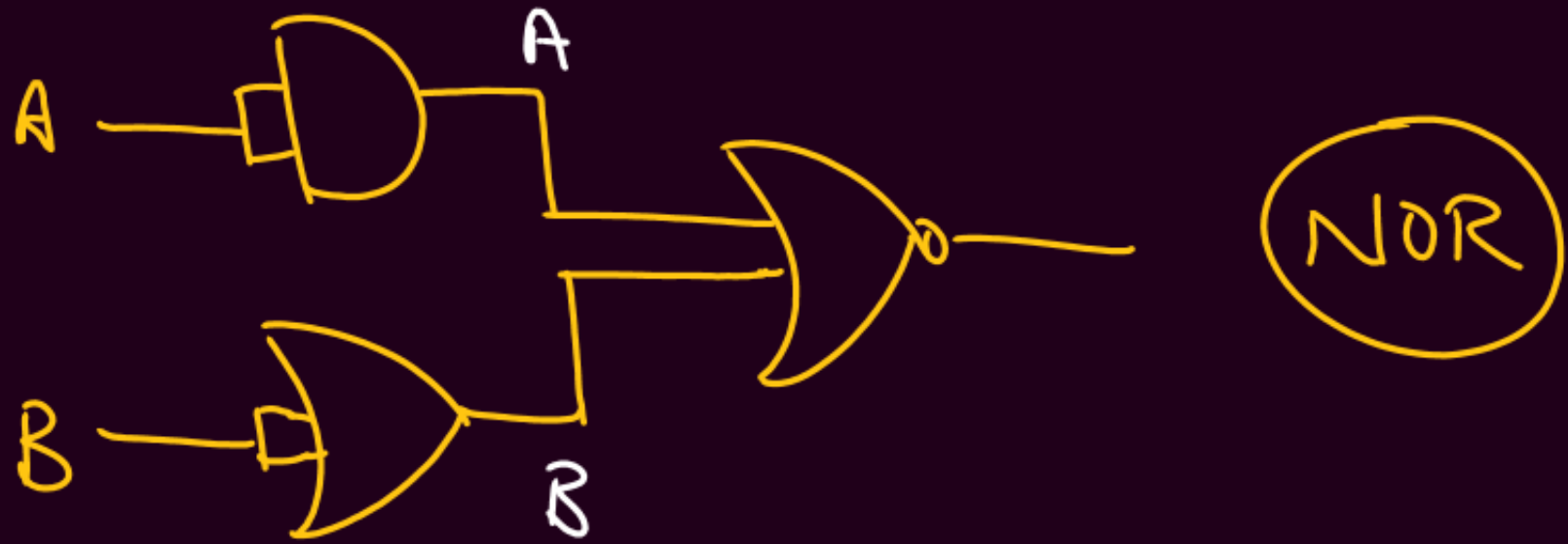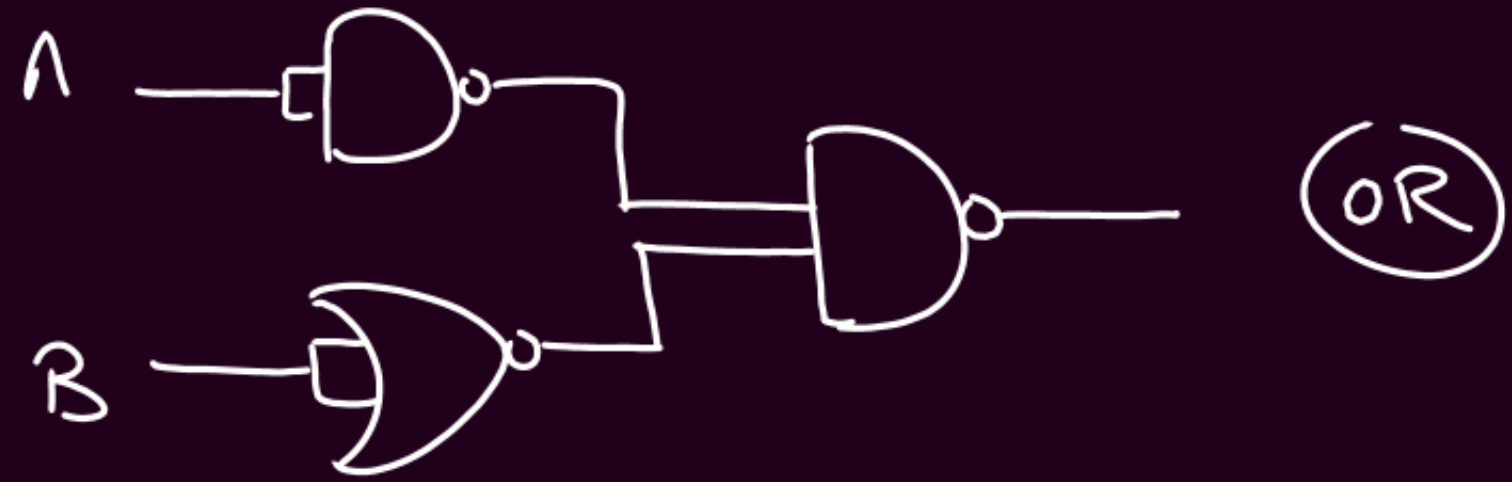

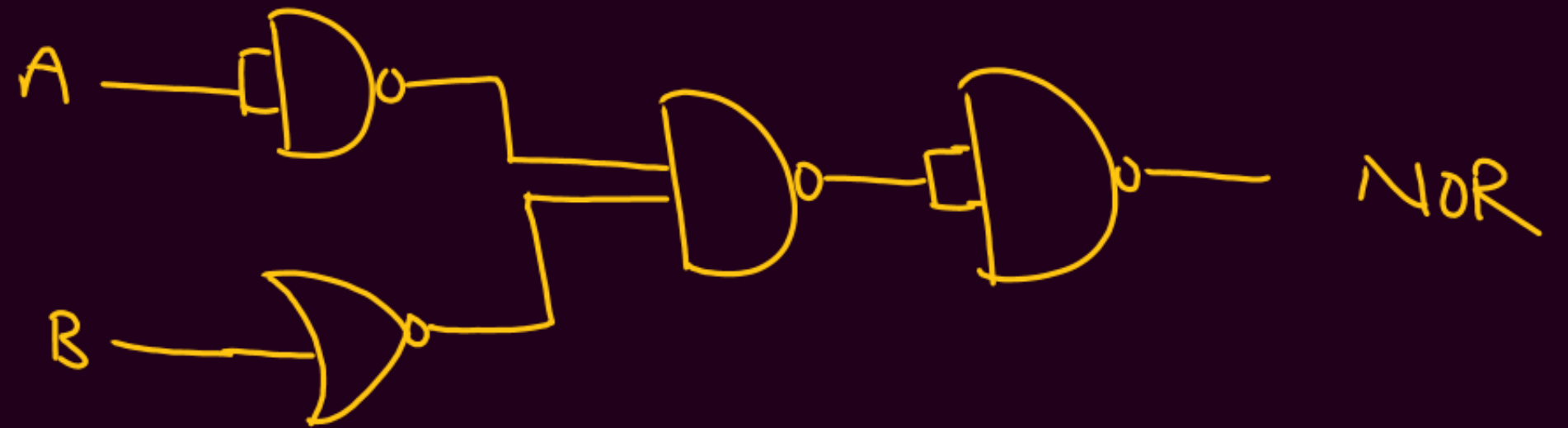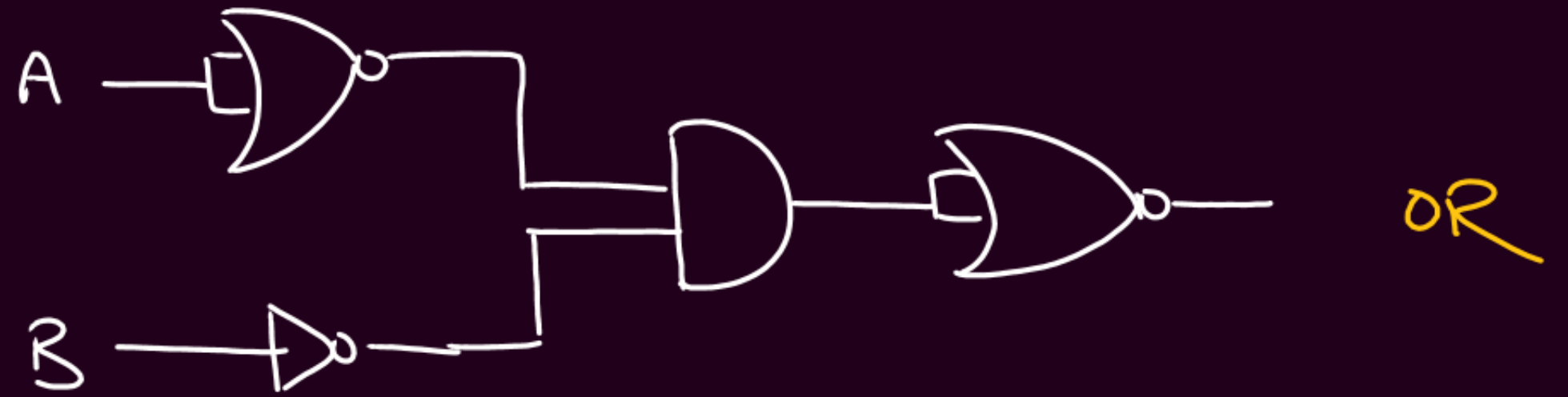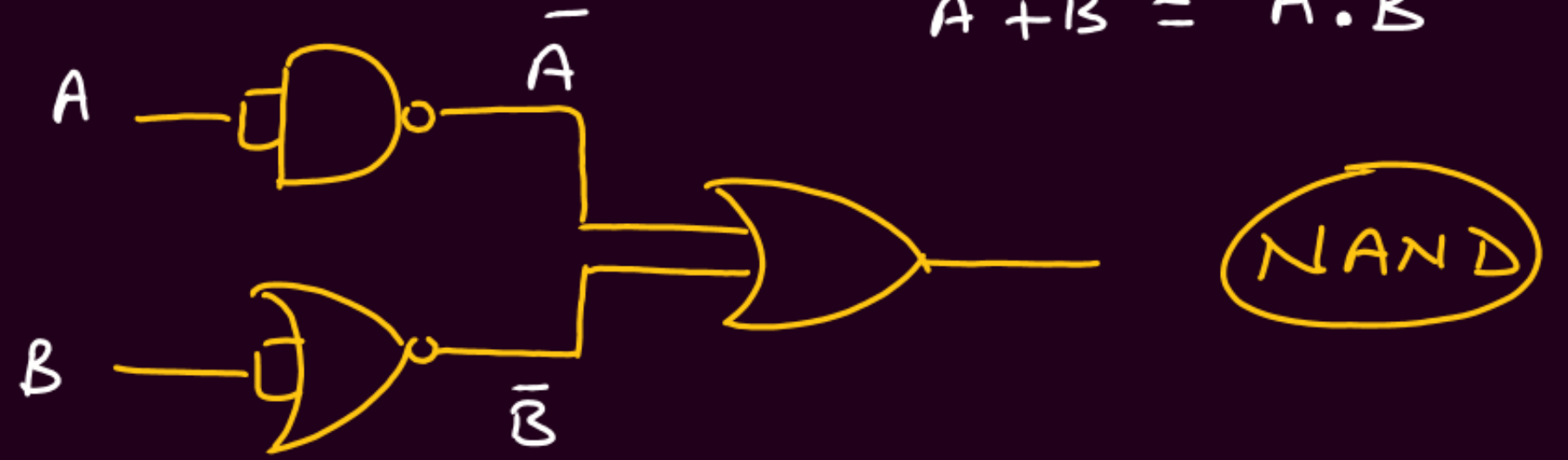
$$\bar{A} + \bar{B} = \overline{A \cdot B}$$





A	B	C	Y
0	0	0	1
1	1	1	0
0	1	0	1
1	0	1	0

A . B	C	OR	NOR = Y
0	0	0	1
1	1	1	0
0	0	0	1
0	1	1	0

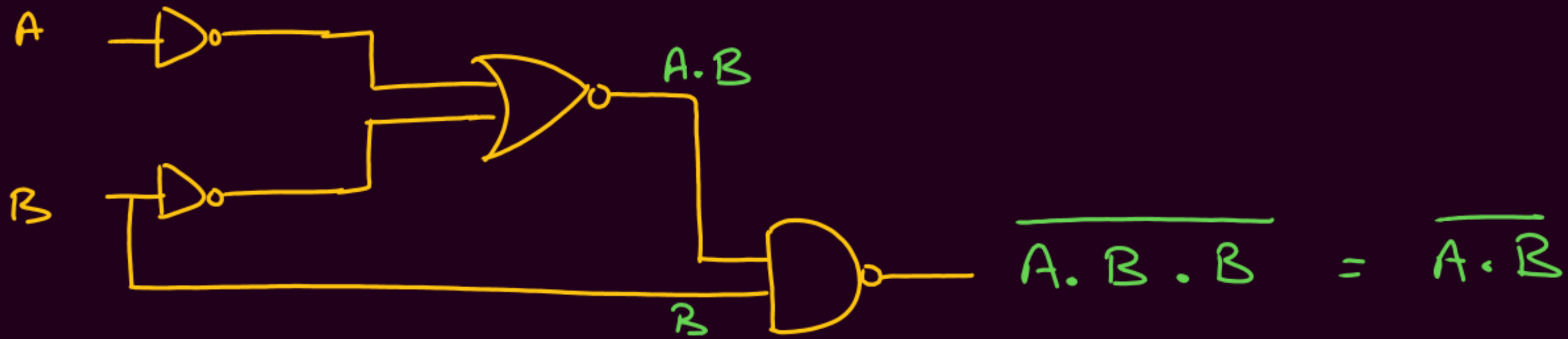

$$\begin{aligned}
 \overline{A.B.B} &= \overline{A.B} \\
 \overline{(A.B).B} &= \overline{A.B} + \overline{B} \\
 &= \overline{A} + \overline{B} + \overline{B} \\
 &= \overline{A} + \overline{B} \\
 &= \overline{A.B}
 \end{aligned}$$

Semiconductors


- low voltage
- Cheap
- Control (σ)

CB

VB



Band Theory

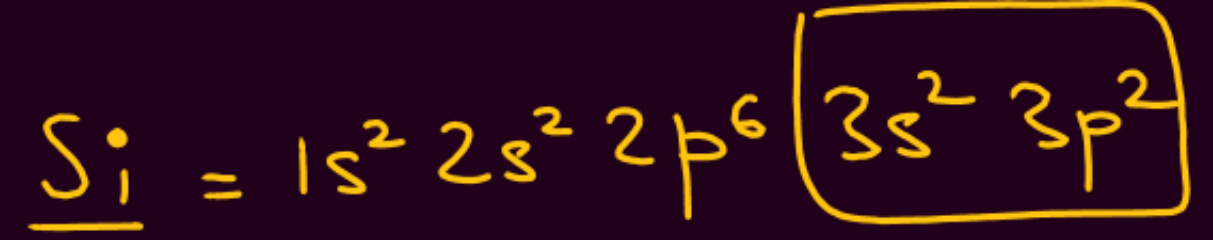

Ge

OK

4N Empty

6N 3p

2N 3s

4N filled


r_0

r

Discrete

Continuous

Bands

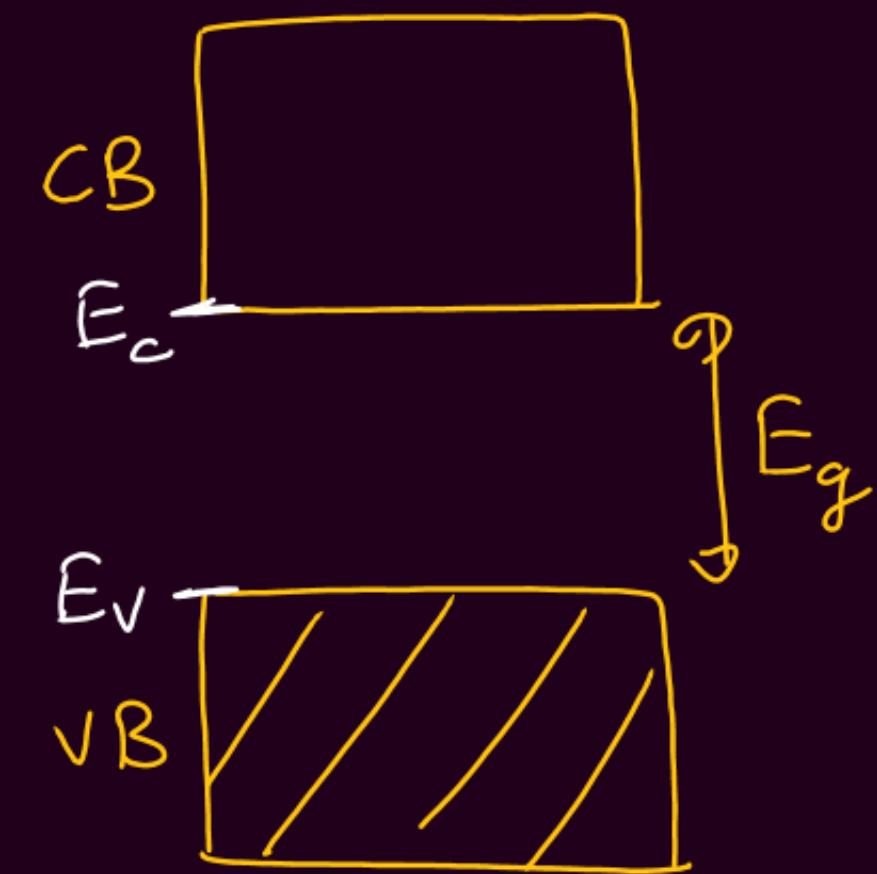

① VB $\rightarrow$ Highest fully occupied Energy Band

② CB $\rightarrow$ Lowest partially / completely Empty Energy Band

Band Gap (Forbidden) E_g

$$E_g = E_c - E_v$$

$E_g =$ Diff. of lowest energy level of CB
and highest — " — VB

Conductors


Na



Zn




Semiconductors

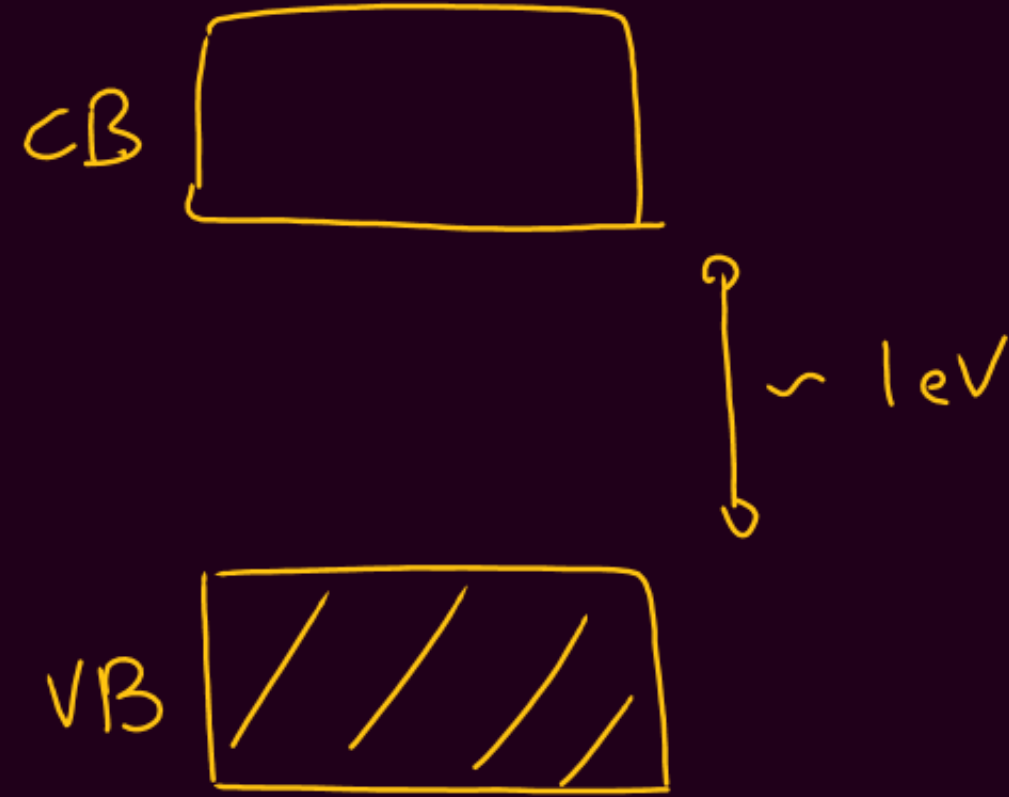

Room Temp. $kT \approx 0.026 \text{ eV}$



Insulators

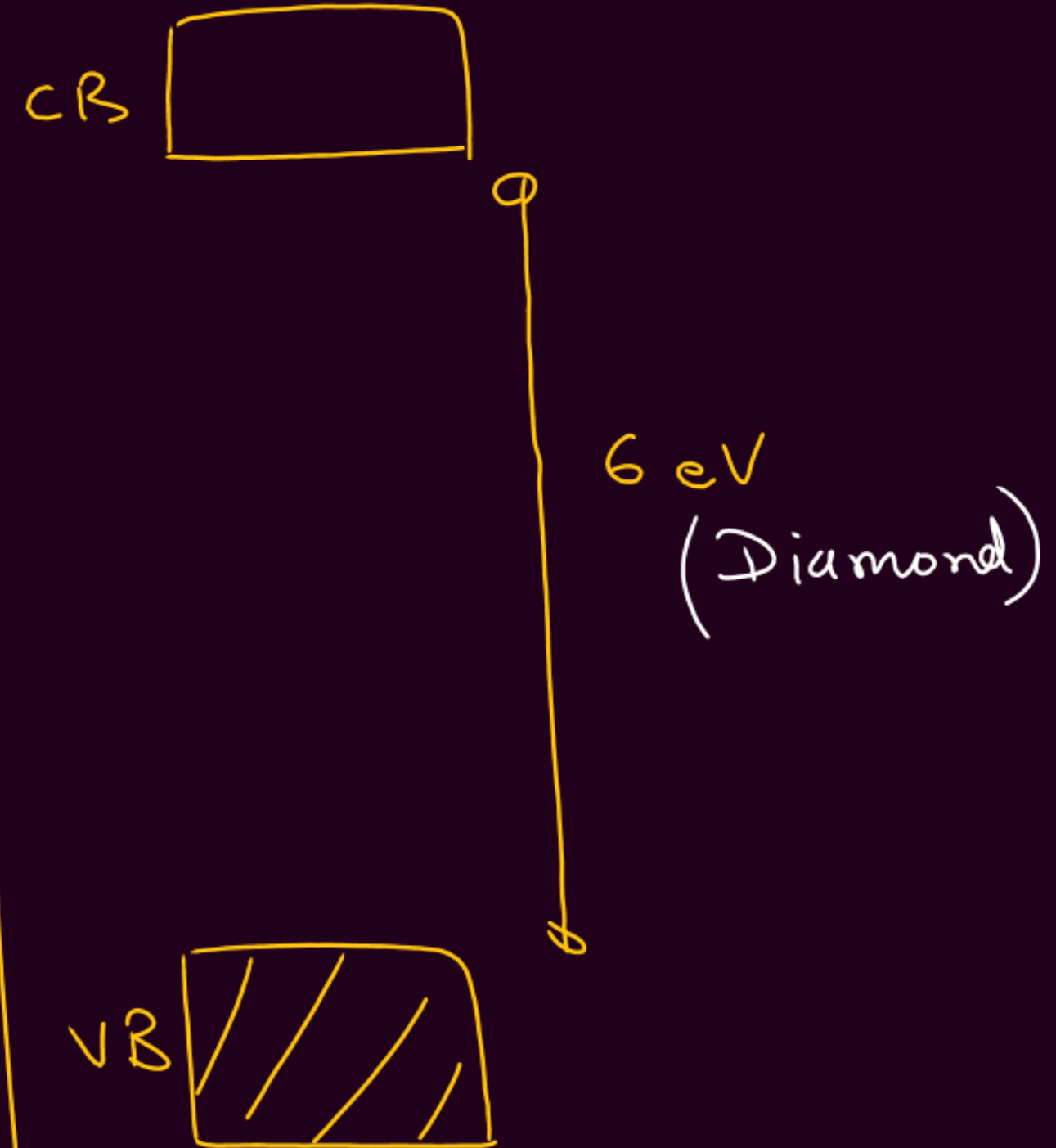

Intrinsic SC

(Pure)

Room Temp.

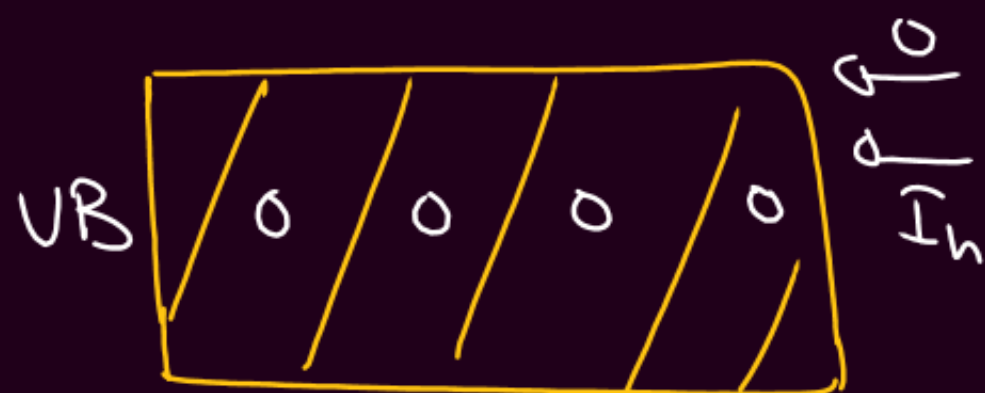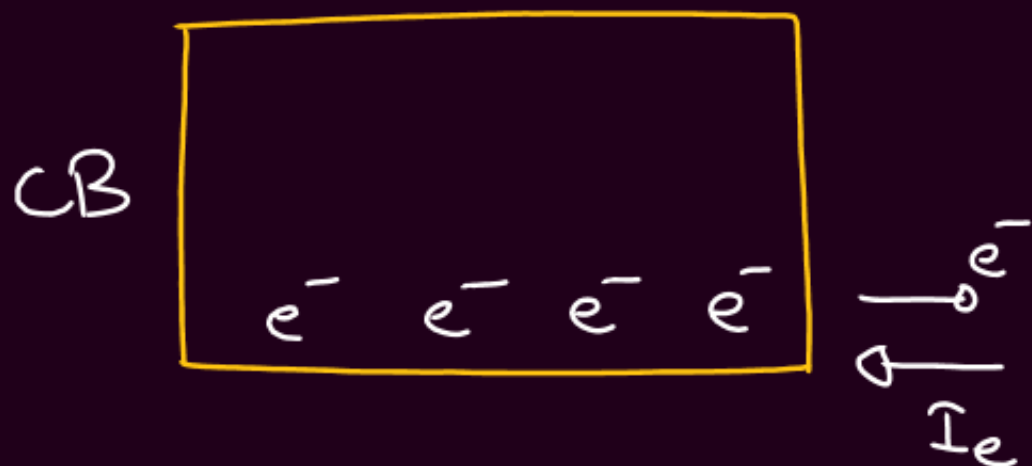

e^- → electrons in CB
holes → vacant sites in VB

Rate of gen. of e^- -h pair

Temp. (T ↑ → Rate ↑)
 $\boxed{\eta_i}$ Incident Radiation ($E_{ph} \geq E_g$)

$$n_e = n_h = n_i$$

$$\boxed{n_e n_h = n_i^2}$$
 ✓

→ Mobility $\mu_e > \mu_h$

→ Effective mass of holes $> e^-$

→ Conductivity $\sigma = \sigma_e + \sigma_h = n_e e \mu_e + n_h e \mu_h$

→ Resistivity

$$\rho = \frac{m}{n e^2 \tau}$$

Temp ↑ n ↑ ρ ↓



→ Recombination

→ Equilibrium

$$\left(\text{Rate of gen.} \right) = \left(\text{Rate of Recomb.} \right)$$

Extrinsic SC

Doping → To Add Impurity

P-type

Al
Ga

Si

Ge

Trivalent / Acceptor

$$n_e \ll n_h$$

$$I_e \ll I_h$$

holes → majority

e^- → minority



o o o o o E_A



$$n_i = 10^{15} / m^3$$

$$Si \Rightarrow 10^{28} / m^3$$

$$1 \text{ ppm} \sim 10^{22} / m^3$$

$$n_h \approx 10^{22} / m^3$$

$$n_e n_h = n_i^2$$

$$n_e \approx 10^8 / m^3$$

Neutral

N-type

Si
Ge

P
As

Pentavalent / Donor

$$n_e \gg n_h$$

$$I_e \gg I_h$$



e^- → majority

h → minority




$$n_e \approx 10^{22} / m^3$$

$$n_h \approx 10^8 / m^3$$

Neutral

P-N Junction Diode

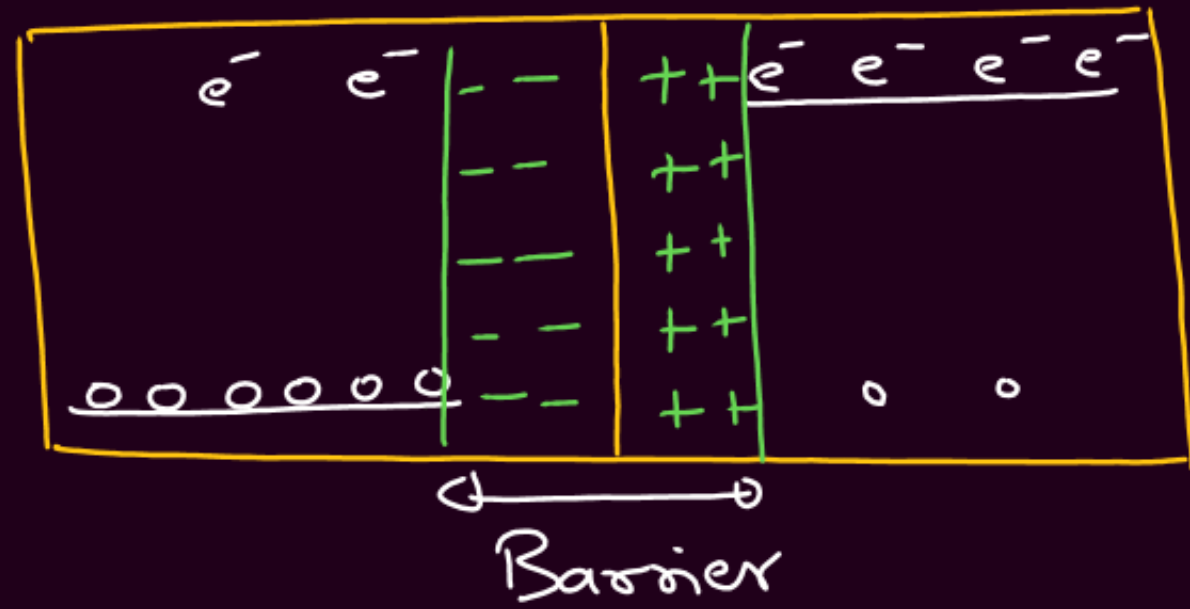

Equilibrium

$$I_{\text{Diff}} = I_{\text{Drift}}$$



→ Diffusion

→ Conc. Gradient → Doping level

→ Diffusion current P → N

→ Depletion Region ~ (non)

→ Depleted of charge carriers

→ Electric field [N → P]

$e^- \rightarrow N$
 $h \rightarrow P$

→ majority charge carriers

→ Minority charge carriers

→ Drift current (N → P)



↳ Rate of gen of e^-h pair ↳ Temp.
↳ Radiation

→ Barrier Potential

↳ Si (0.7V)

↳ Ge (0.3V)



Forward Bias

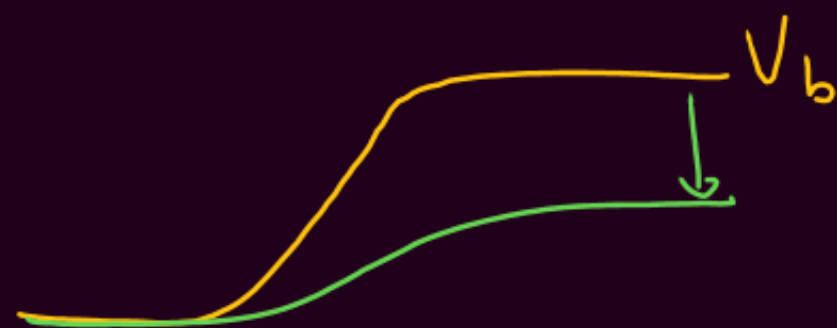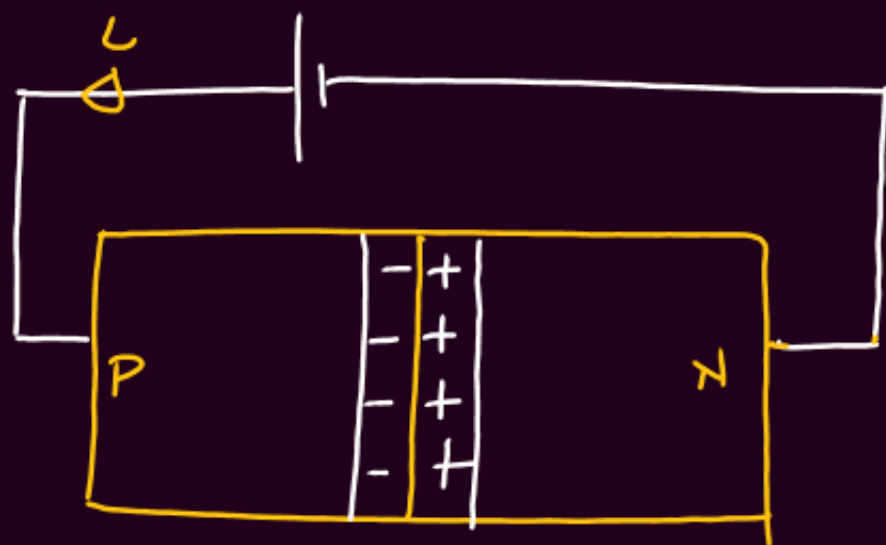


- width D.R. ↓
- $I_{\text{diffusion}}$ (mA)
- (majority) $P \rightarrow N$
- Barrier Potential ↓




Reverse Bias

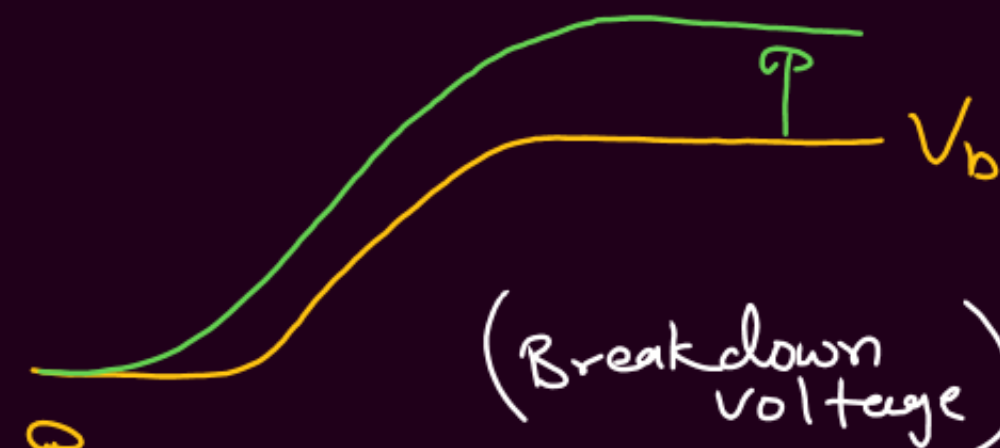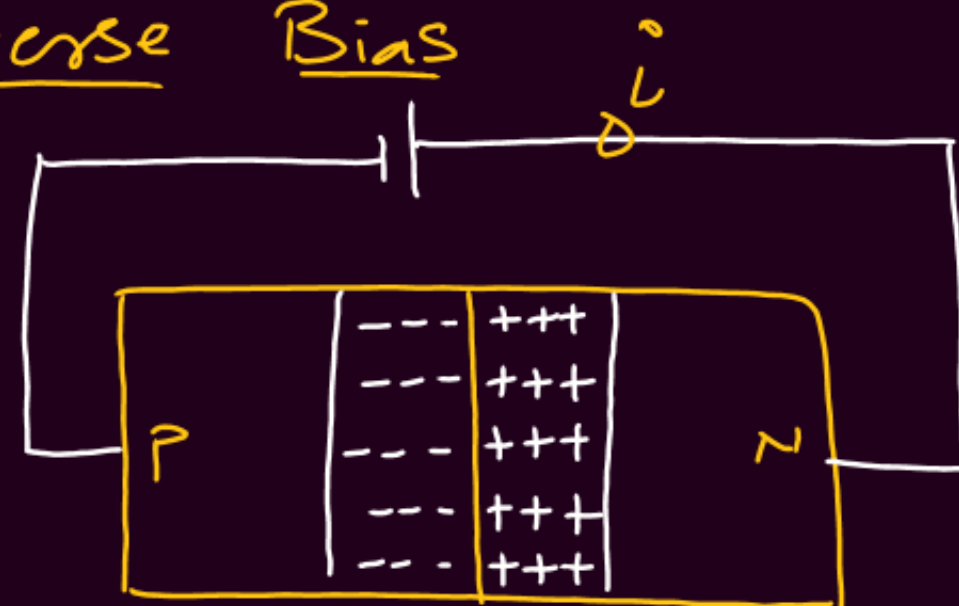

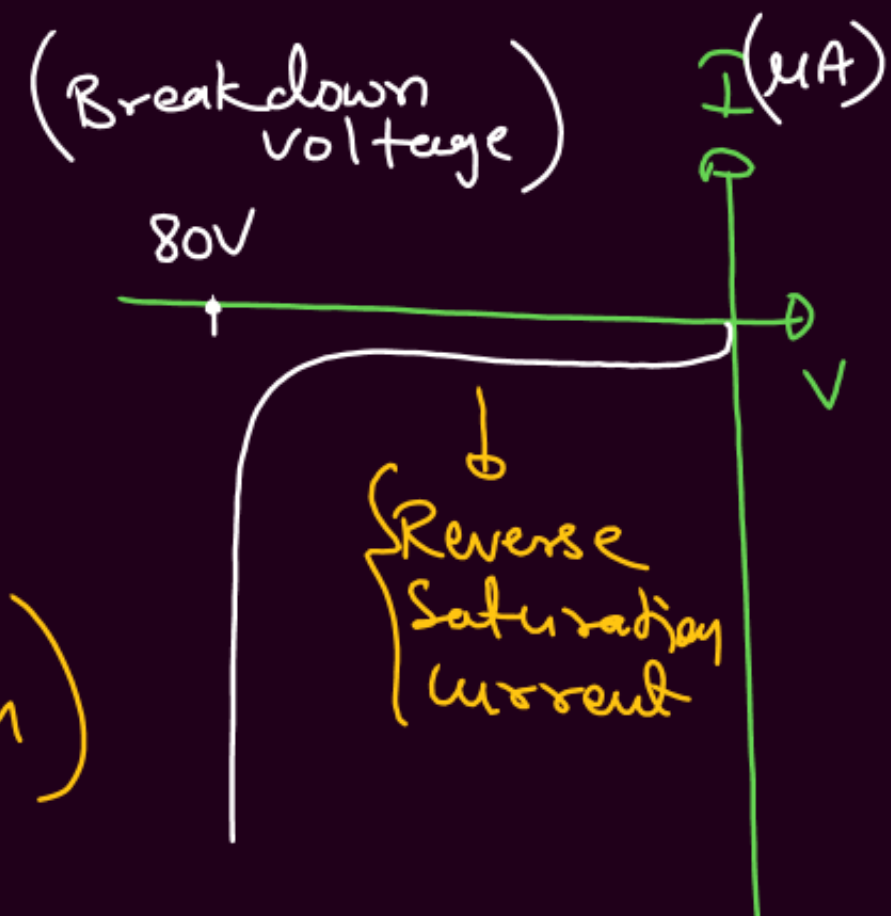- width D.R. ↑
- Barrier Potential ↑
- Drift current (μA)
- minority (Temp. Radiation) $N \rightarrow P$



I-V characteristic

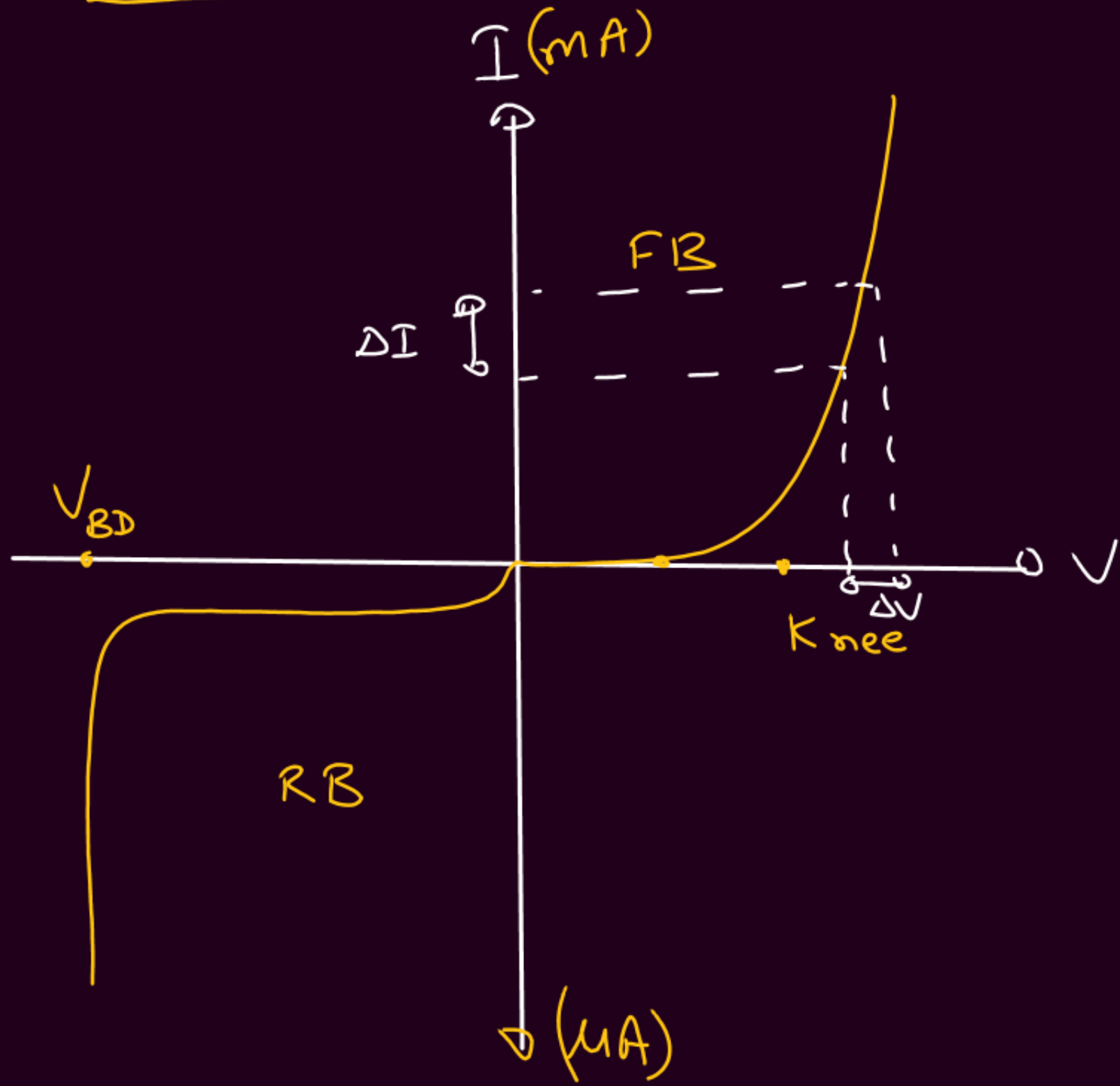

Dynamic Resistance

$$r_d = \frac{\Delta V}{\Delta I} \propto \frac{1}{(\text{Slope of } I \text{ vs } V)}$$

$$r_{FB} \sim k\Omega$$

$$r_{RB} \sim m\Omega$$

FB $\rightarrow$ SC

RB $\rightarrow$ OC

Q.



FB



RR



RR




RR



FB

Q.

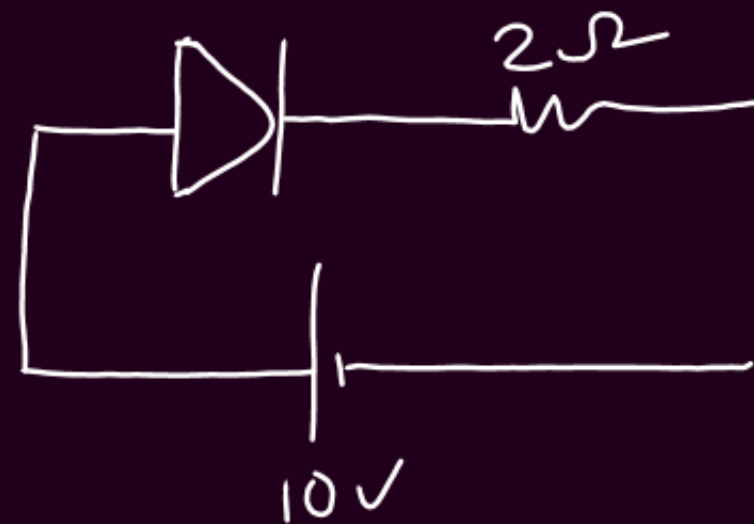


$$I^0 = \frac{10}{2} = 5A$$

$$V_D = 0$$

$$V_R = 10V$$


Q.

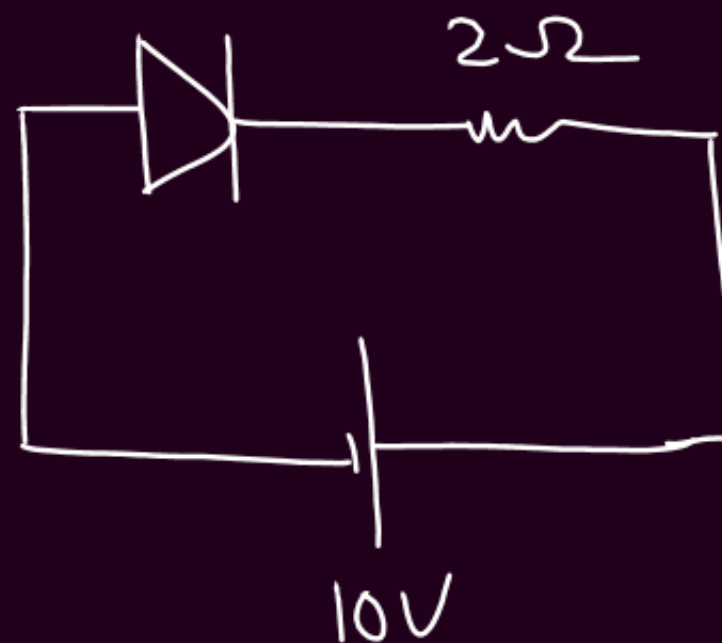

$$I^0 = 0$$

$$V_D = 10V$$


$$V_R = 0$$

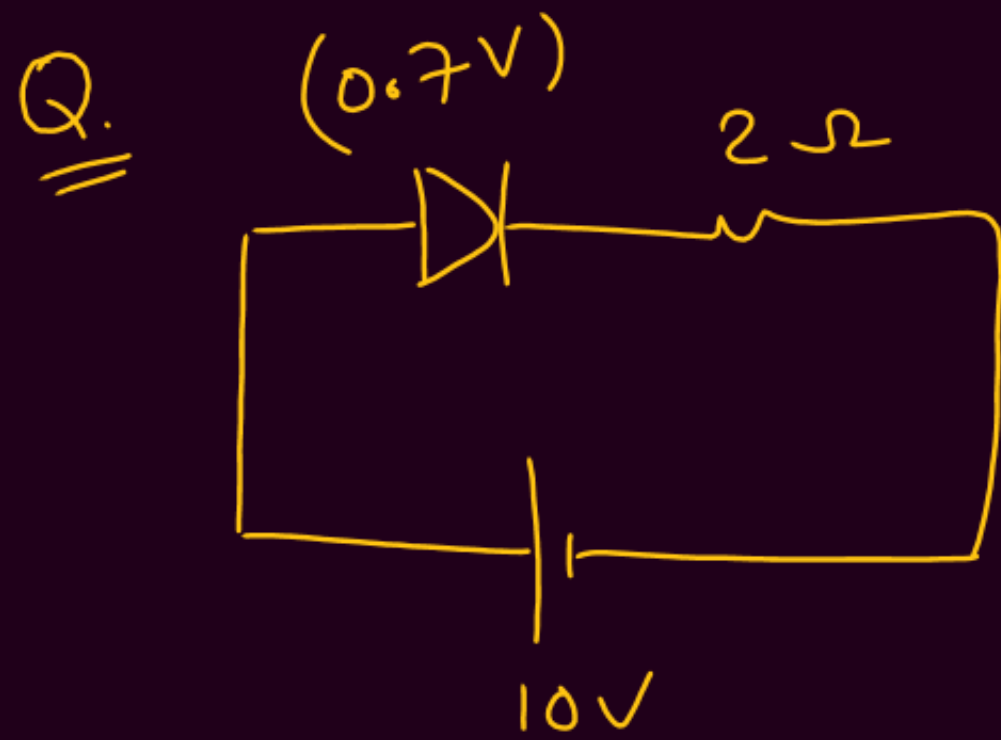


$$I = \frac{10 - 0.7}{2} = 4.65 \text{ A}$$

$$V_D = 0.7 \text{ V}$$

$$V_R = 9.3 \text{ V}$$

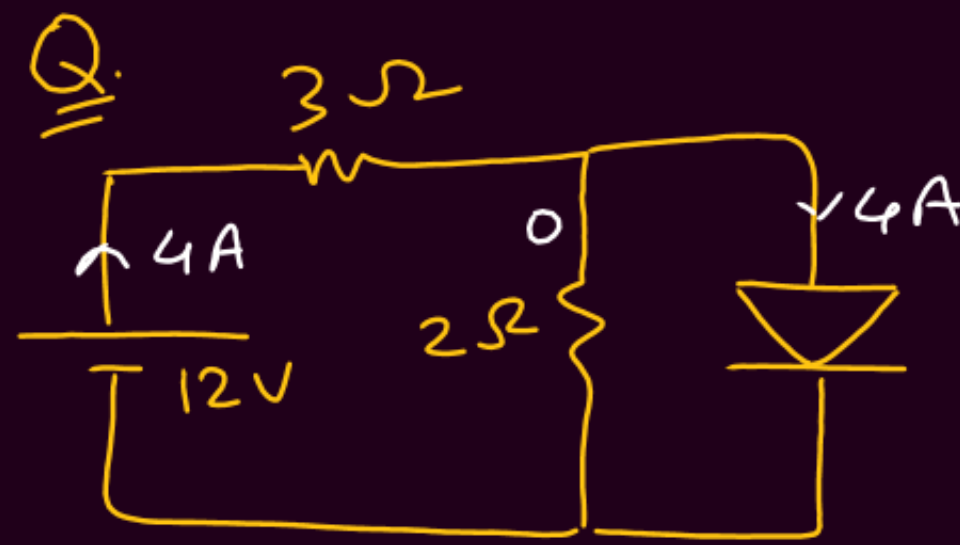



Current in Each Branch?

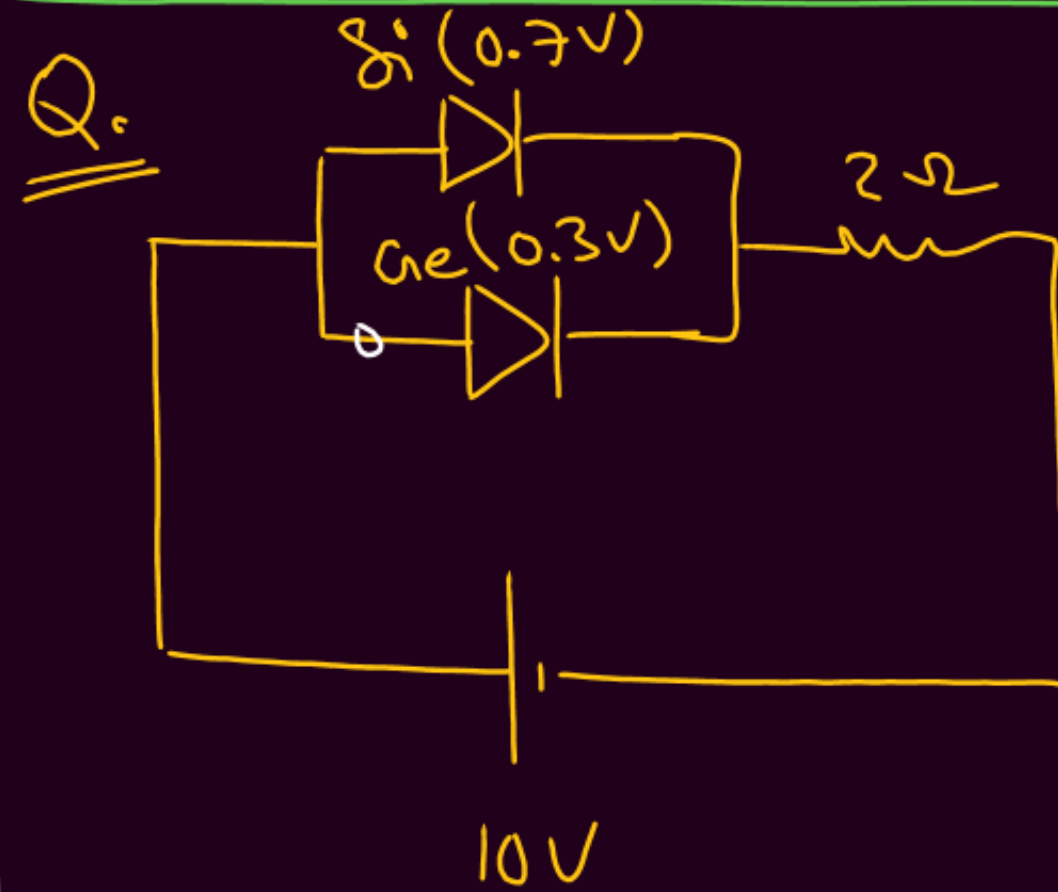

$$I = \frac{10 - 0.3}{2} = 4.85 \text{ A}$$



App 8

① Half Wave Rectifier

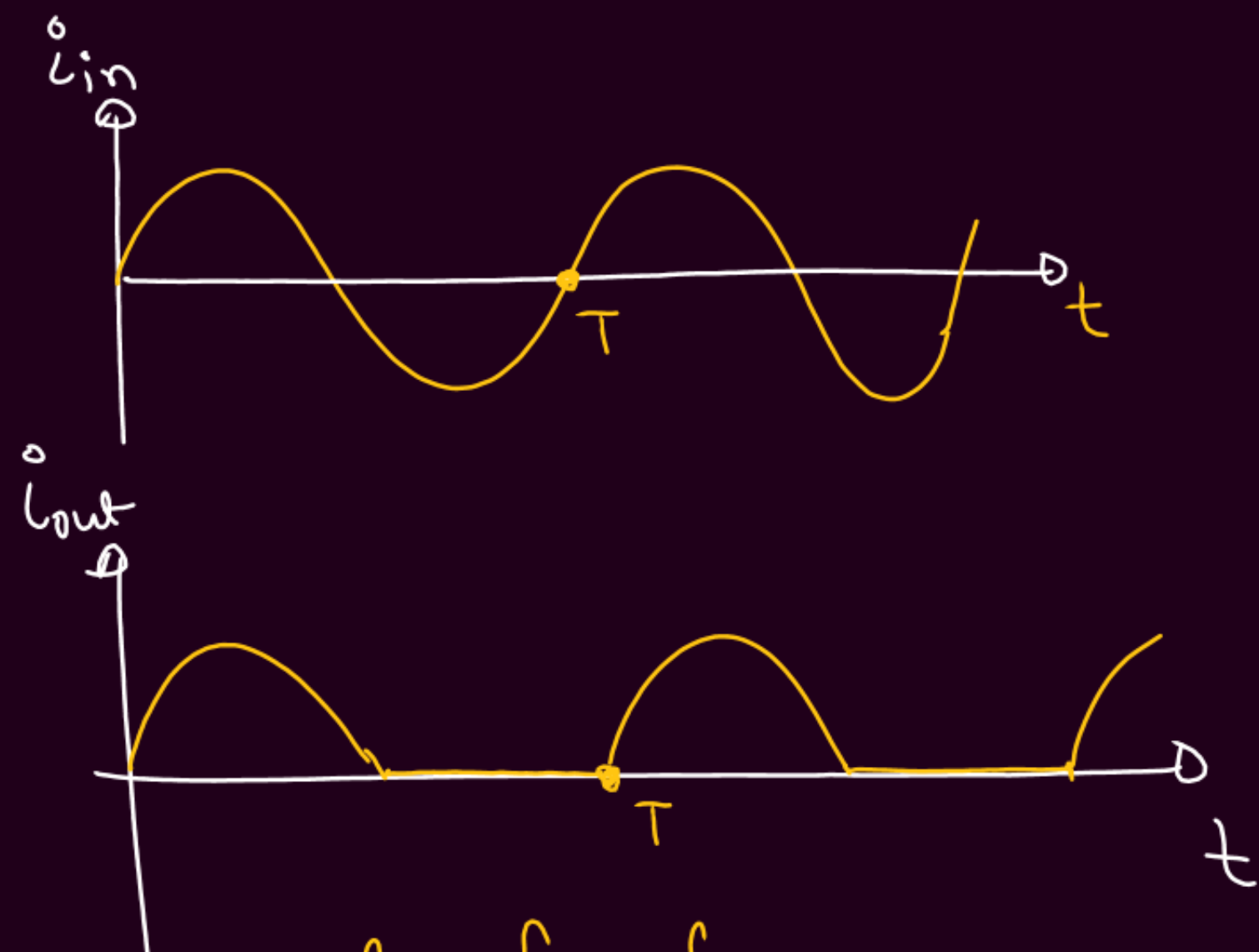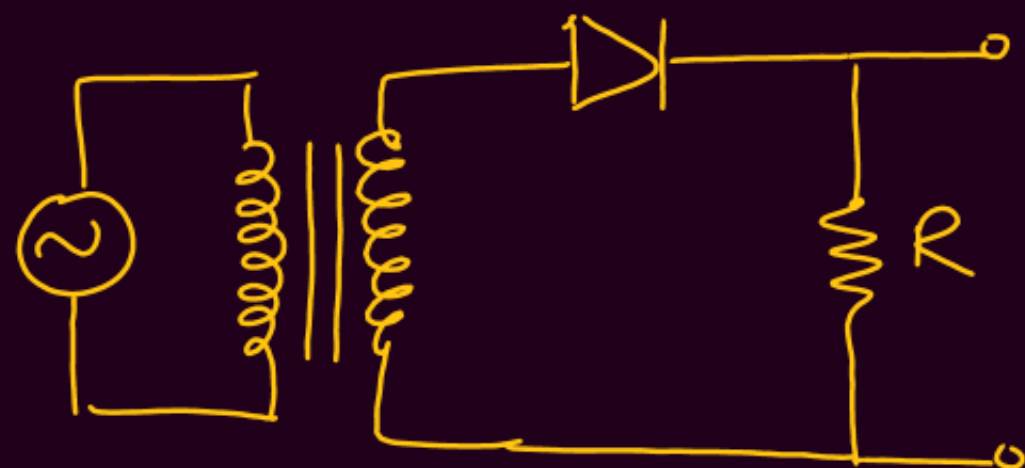


$$f_{in} = f_0 \quad f_{out} = f_0$$

② Full Wave Rectifier Center Tap

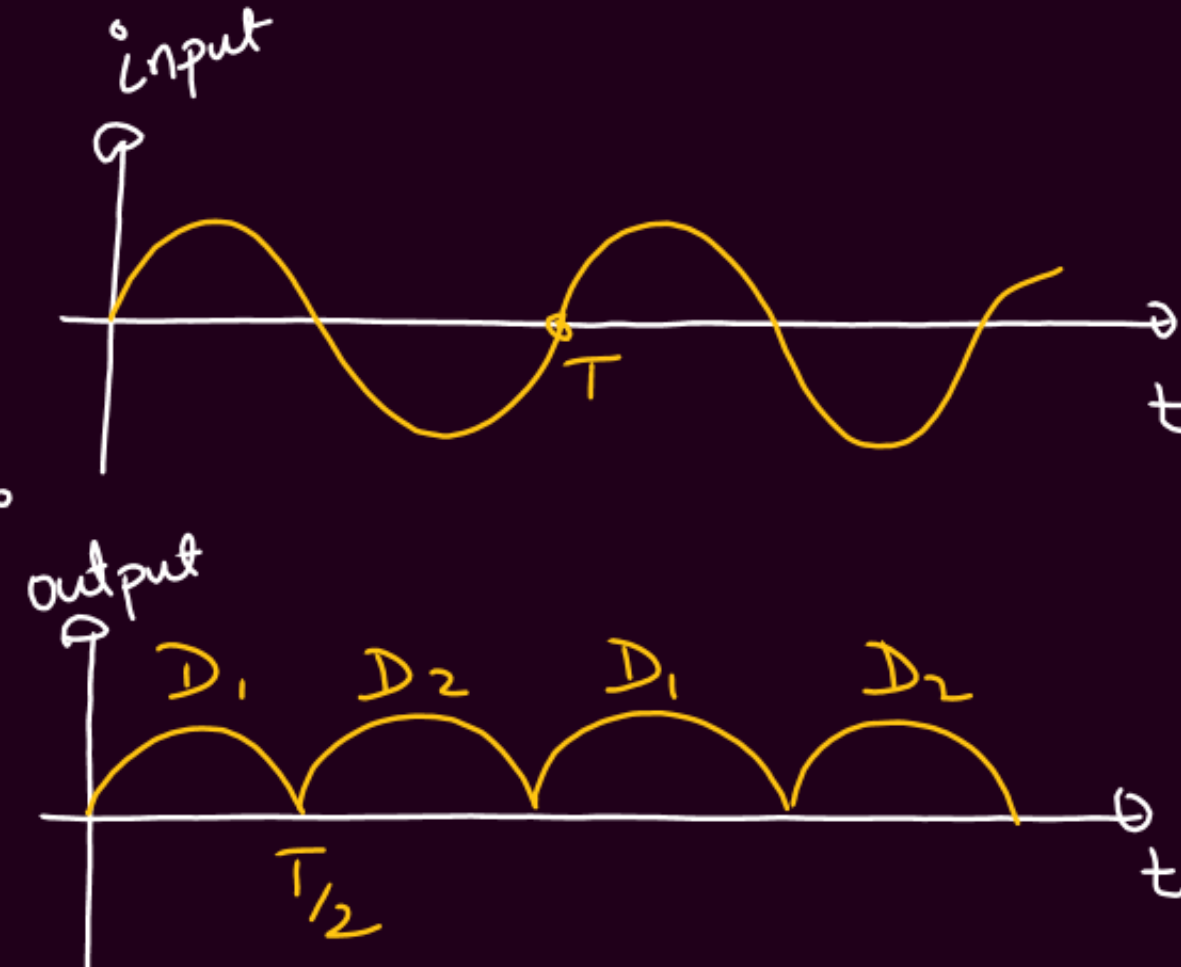
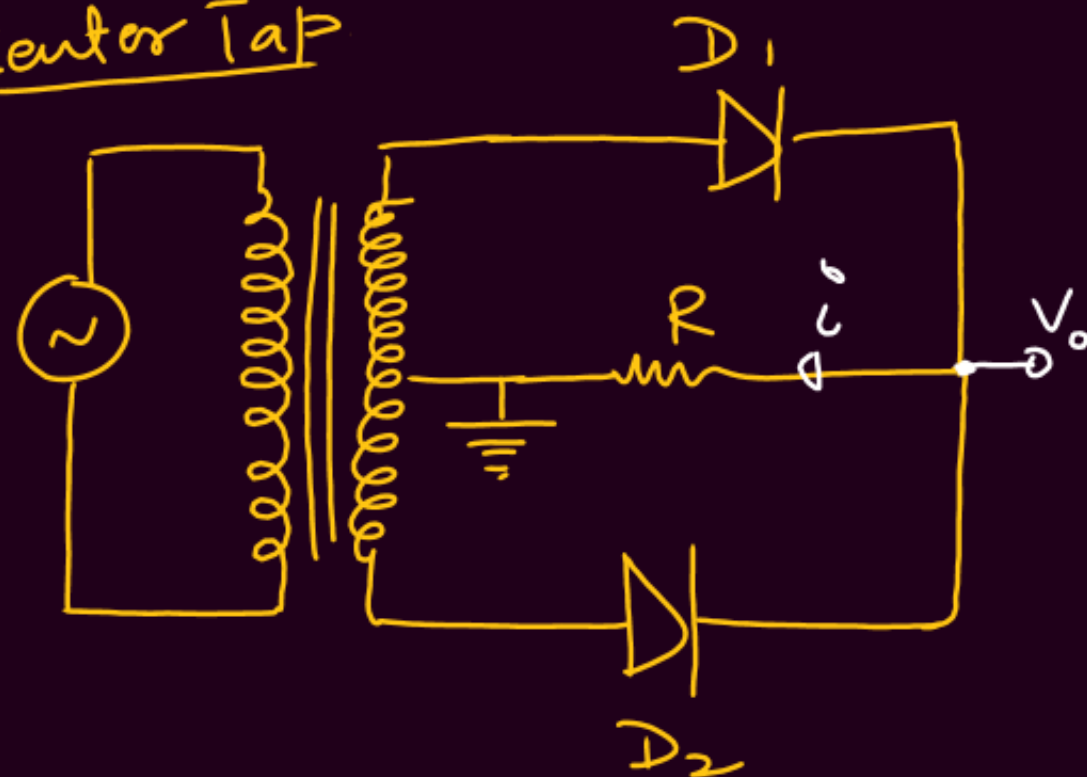


$$\begin{array}{lcl} \text{input} & \rightarrow & f \quad T \\ \text{output} & \rightarrow & 2f \quad T/2 \end{array}$$


Bridge

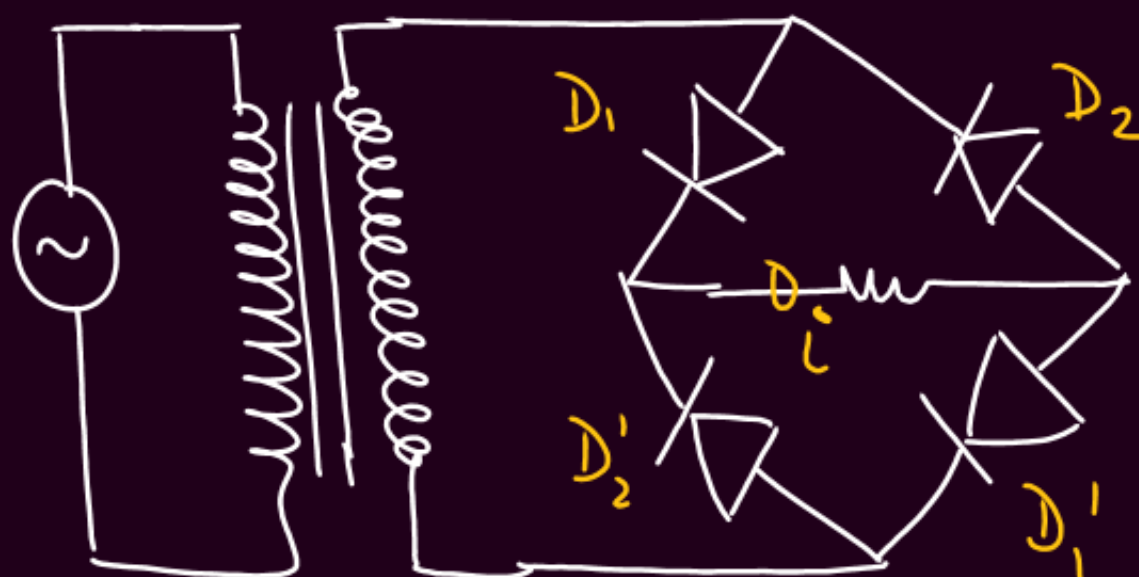


Filters → To remove ripples

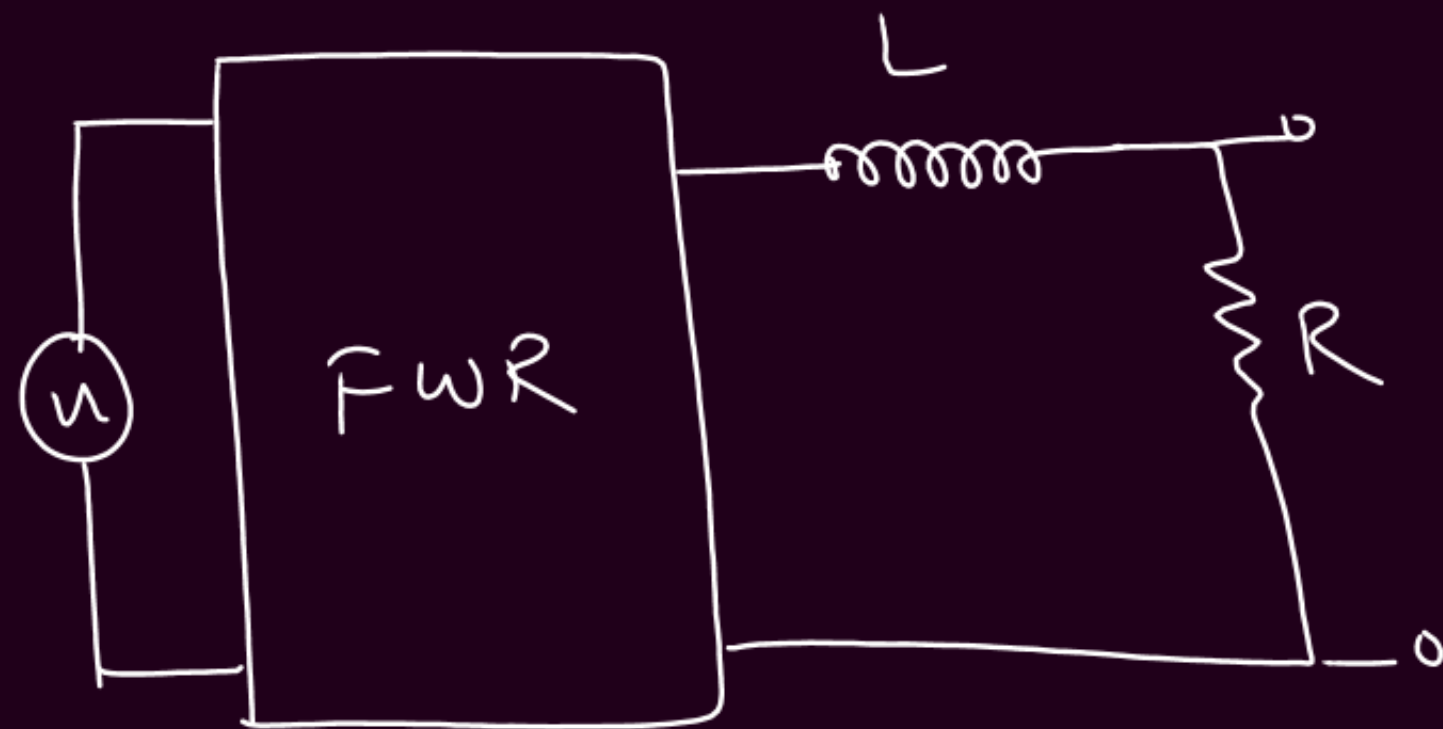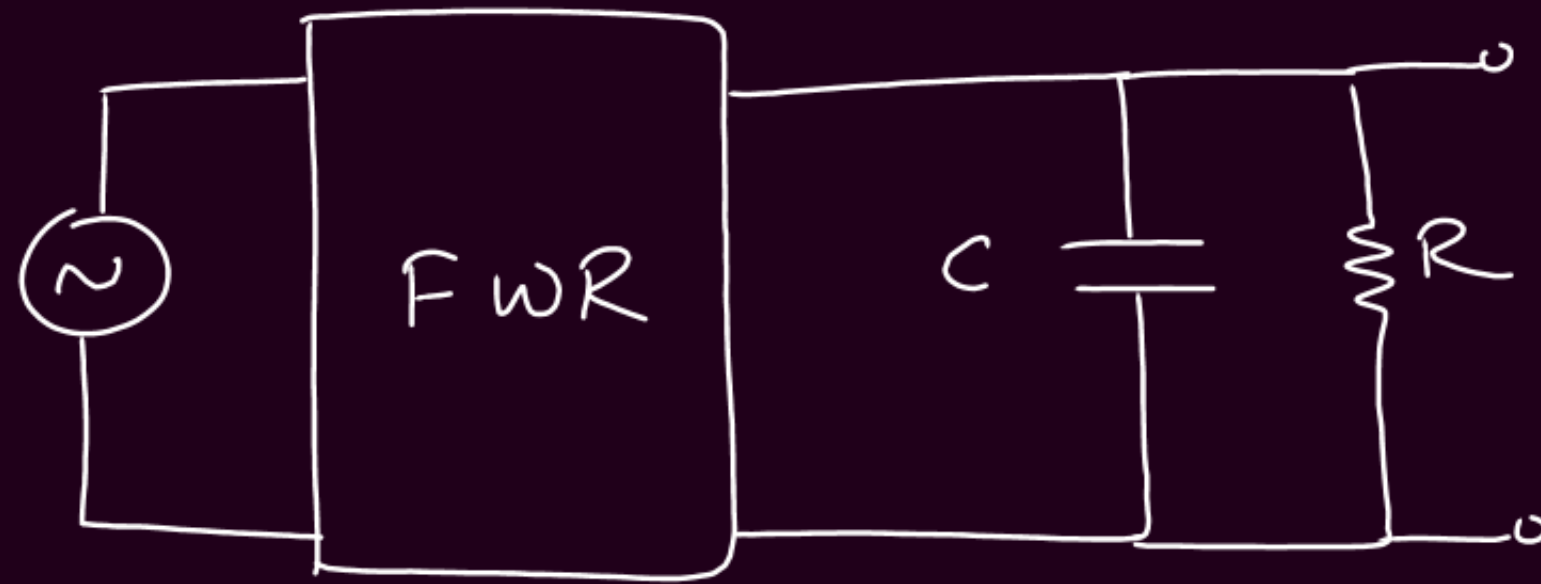

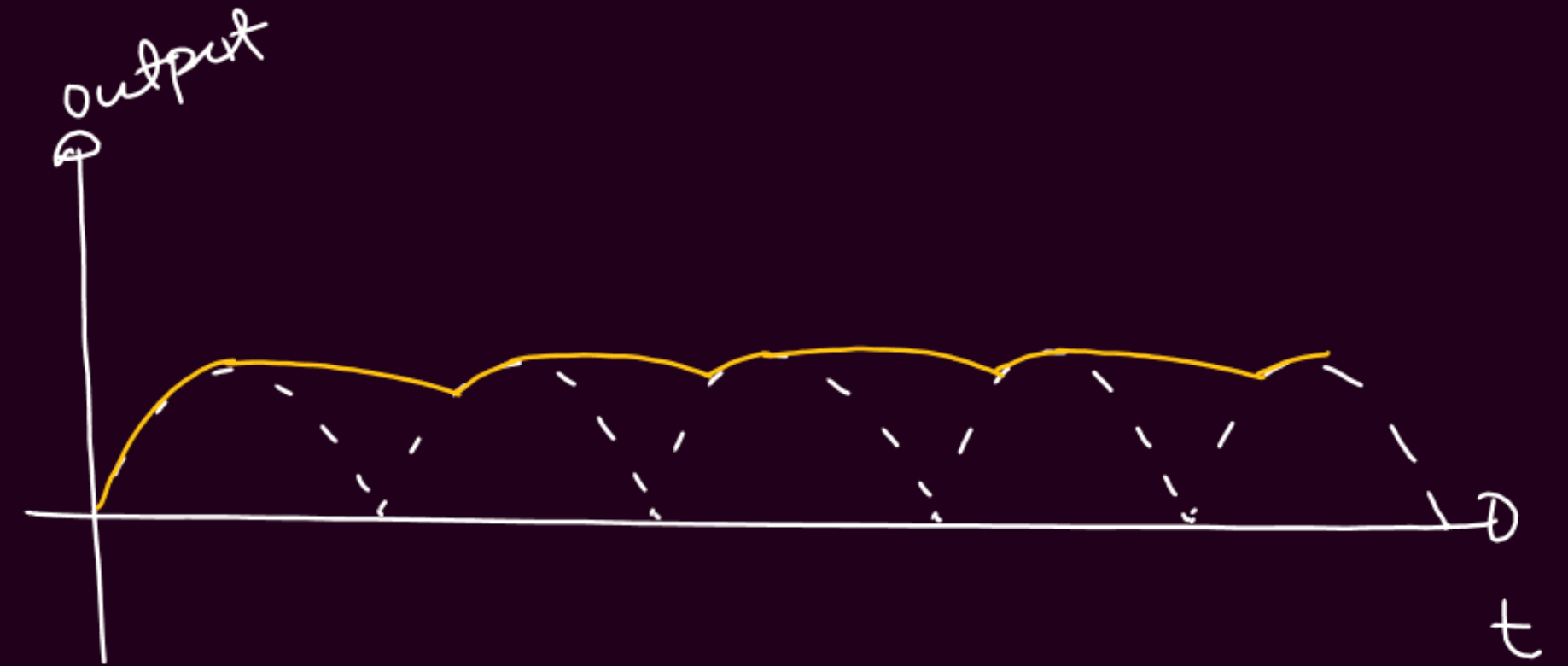
C in parallel } of large value
L in series }



	MWR	FWR
Ripple factor	1.21	0.48
Efficiency	40.6%	81.2%


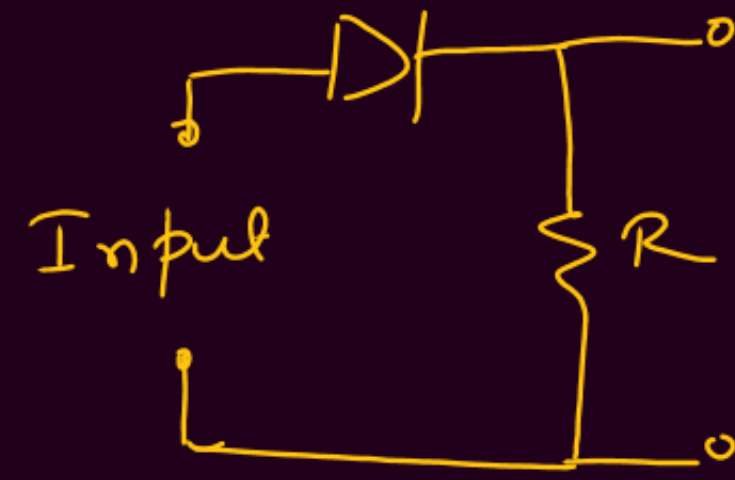


HWR

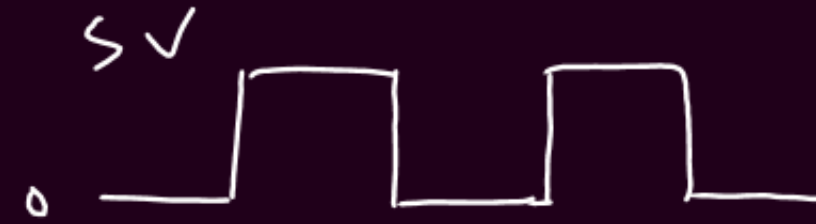

Zener Diode

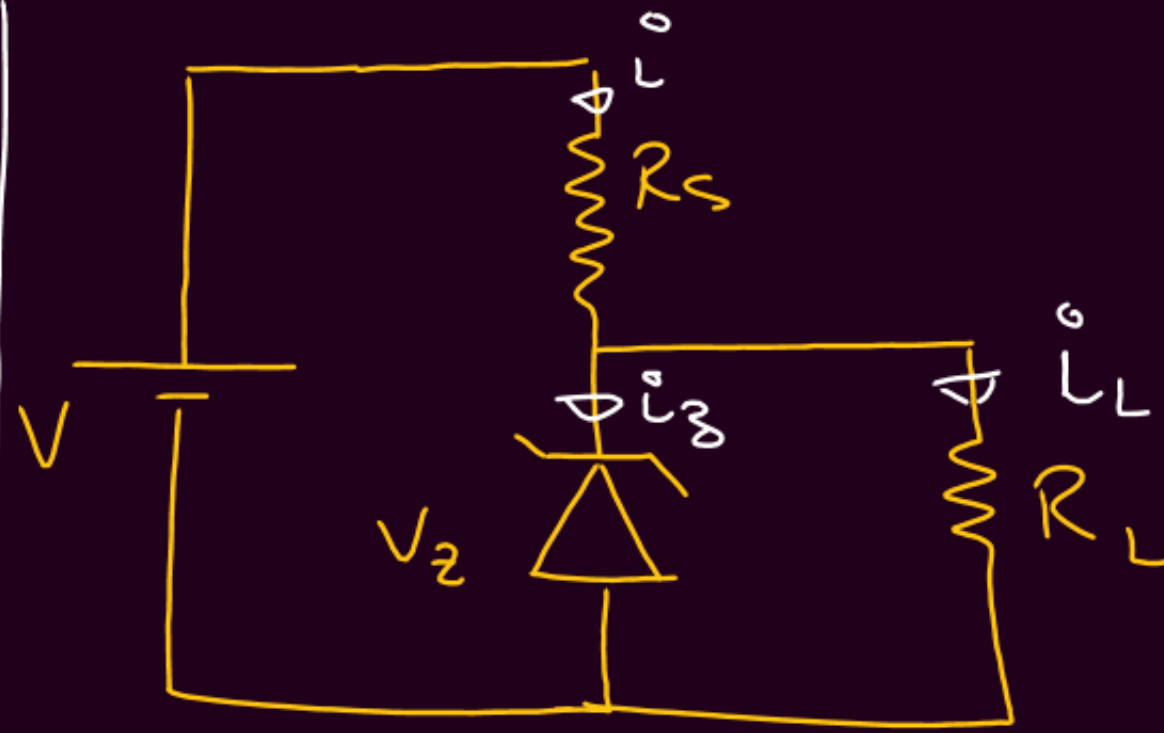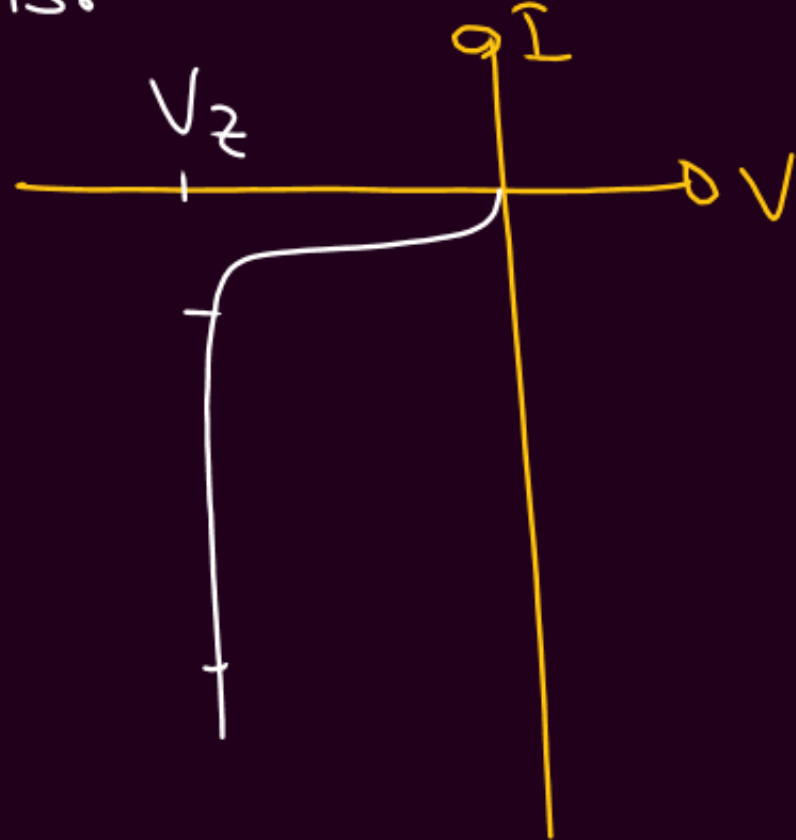- Voltage Regulator
- Both P & N
 - ↳ Heavily Doped
- Width of D.R. very small
- B.D. voltage (Rating V_z)
 - ↳ (5V)
- Used in R.B. under B.D.




KVL
① $V_z = i_L R_L$

KVL
② $V - V_z = i R_s$

KCL
③ $i_z = i - i_L$

Q.

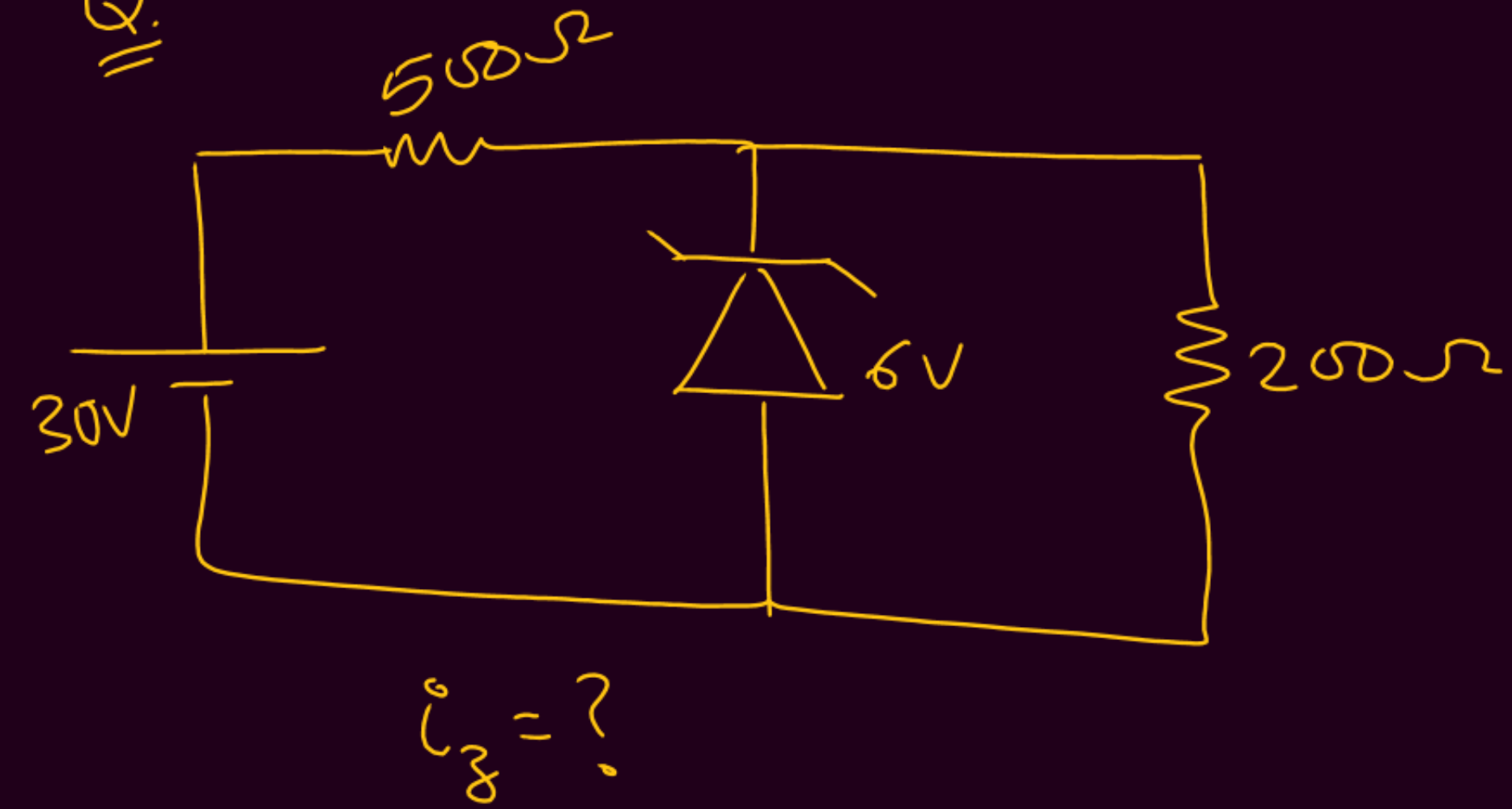

$$\textcircled{1} \quad 6 = i_L 200$$

$$i_L = 0.03 \text{ A}$$

$$\textcircled{2} \quad 30 - 6 = i(500)$$

$$i = 0.048 \text{ A}$$

$$\textcircled{3} \quad i_z = 0.018 \text{ A} = \underline{18 \text{ mA}}$$

Avalanche B.D.


- Low Doping (Low $\vec{E}$)
- Collision of e^-
- Low B.D. voltage
- Excessive Heat
- Damage
- Temp. $\uparrow$ B.D. voltage $\uparrow$

Zener B.D.

- Heavy Doping (Large $\vec{E}$)
- Quantum Tunneling
- High B.D. voltage
- Reversible
- Temp. $\uparrow$ B.D. voltage $\downarrow$

Optoelectronic Devices

① Photodiode

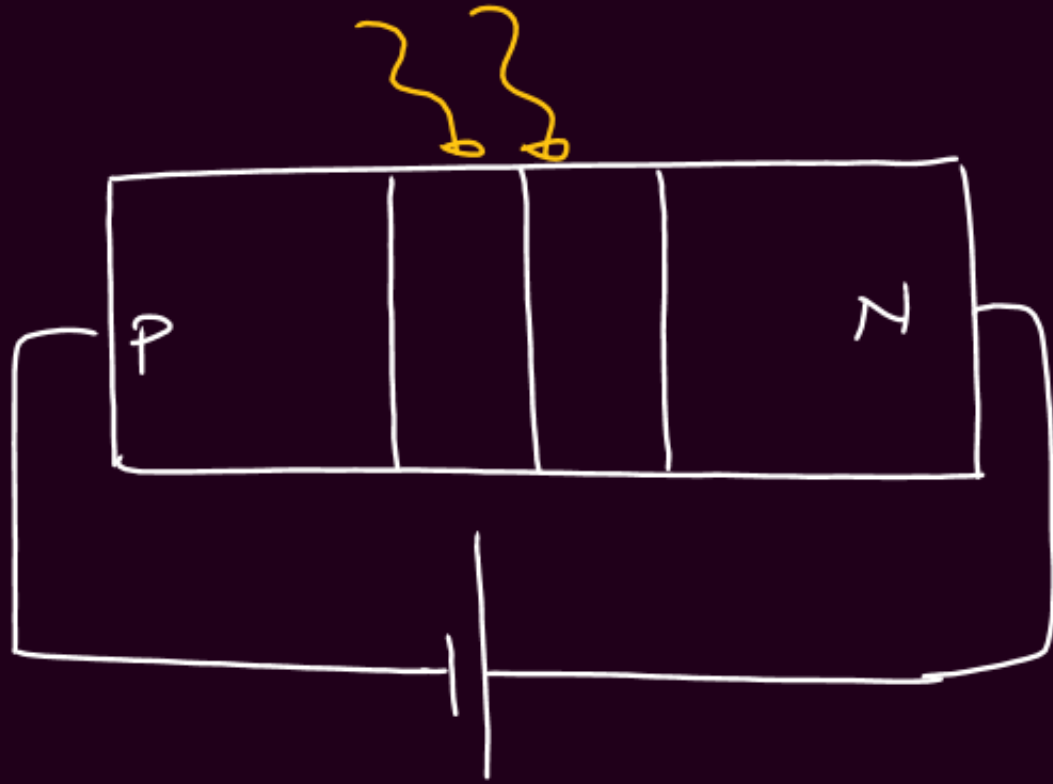

→ Radiation ($E_{ph} \geq E_g$)


↳ the Rate of gen. of e^-h pair

→ Drift

→ Used in R.B.

→ (Reverse i_s) $\propto$ (Intensity)

→ To detect optical signals

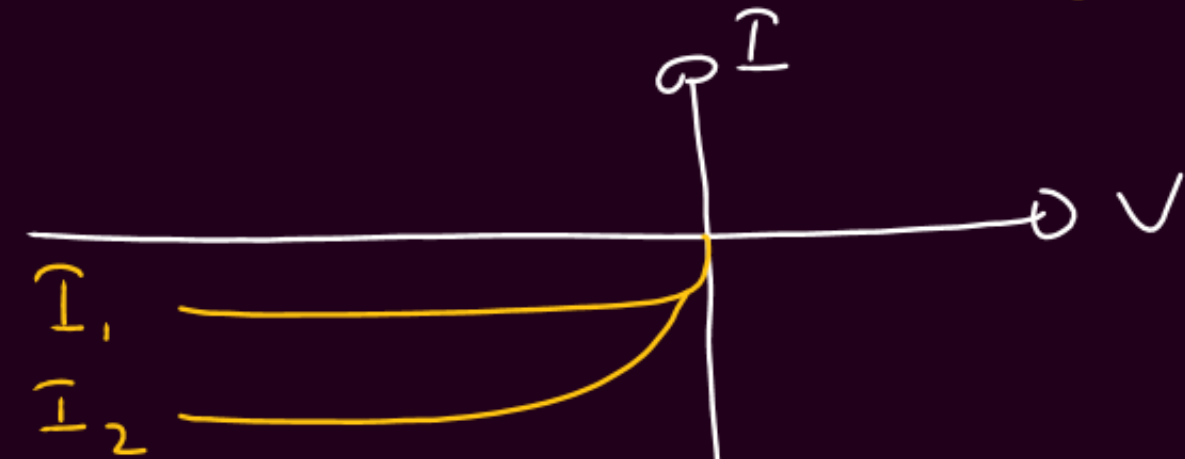

Intensity

$$I_1 < I_2$$

② LED — 

→ Recombination

↳ Photon

↳ Visible

E_g (1.8 eV to 3 eV)

→ Forward Bias

→ Heavily Doped

→ Remote Control
Burglar Alarm

→ E_{ph} is equal to or slightly less than E_g

→ Forward current

Small

increase

Intensity

Small

→ I then max.

then it 

(Recombination → Heat)

→ GaAs (2R)


→ $GaAs_{0.6}P_{0.4}$ (Red)

LED vs Incandescent Lamp


- ↳ Low voltage
- ↳ Fast action
- ↳ Fast on & off
- ↳ Long life

→ Nearly monochromatic



③ Solar Cell

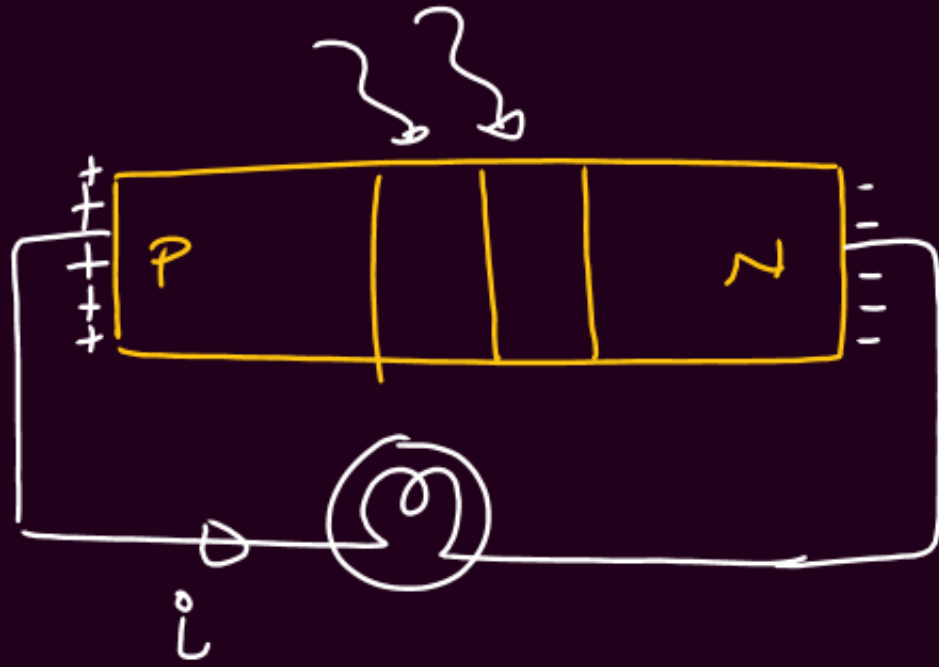

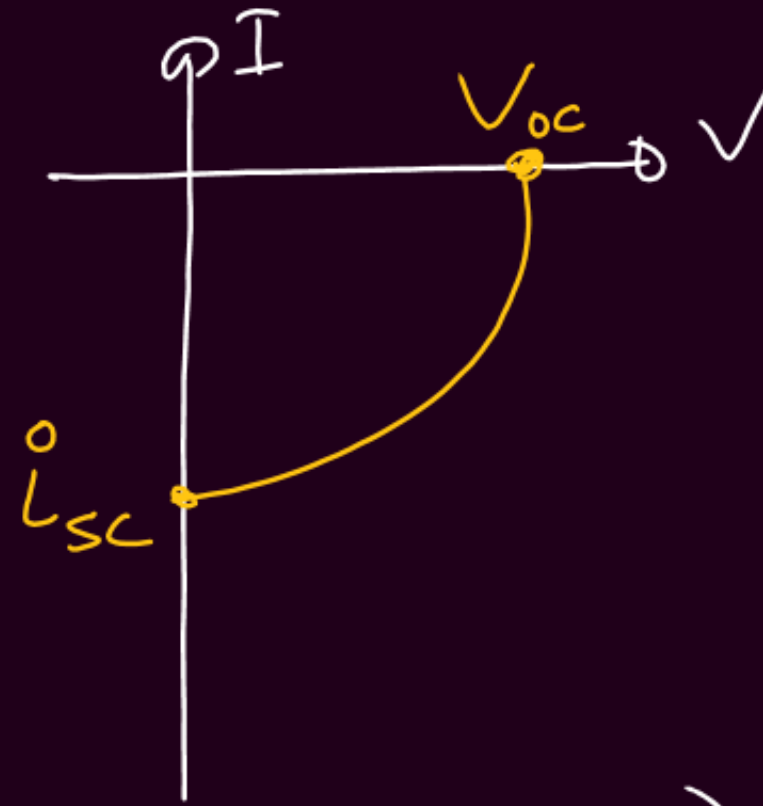- generation (e^-h pair)
- separation ($\vec{E} \rightarrow \text{Drift}$)
- collection




I (Solar Radiation)

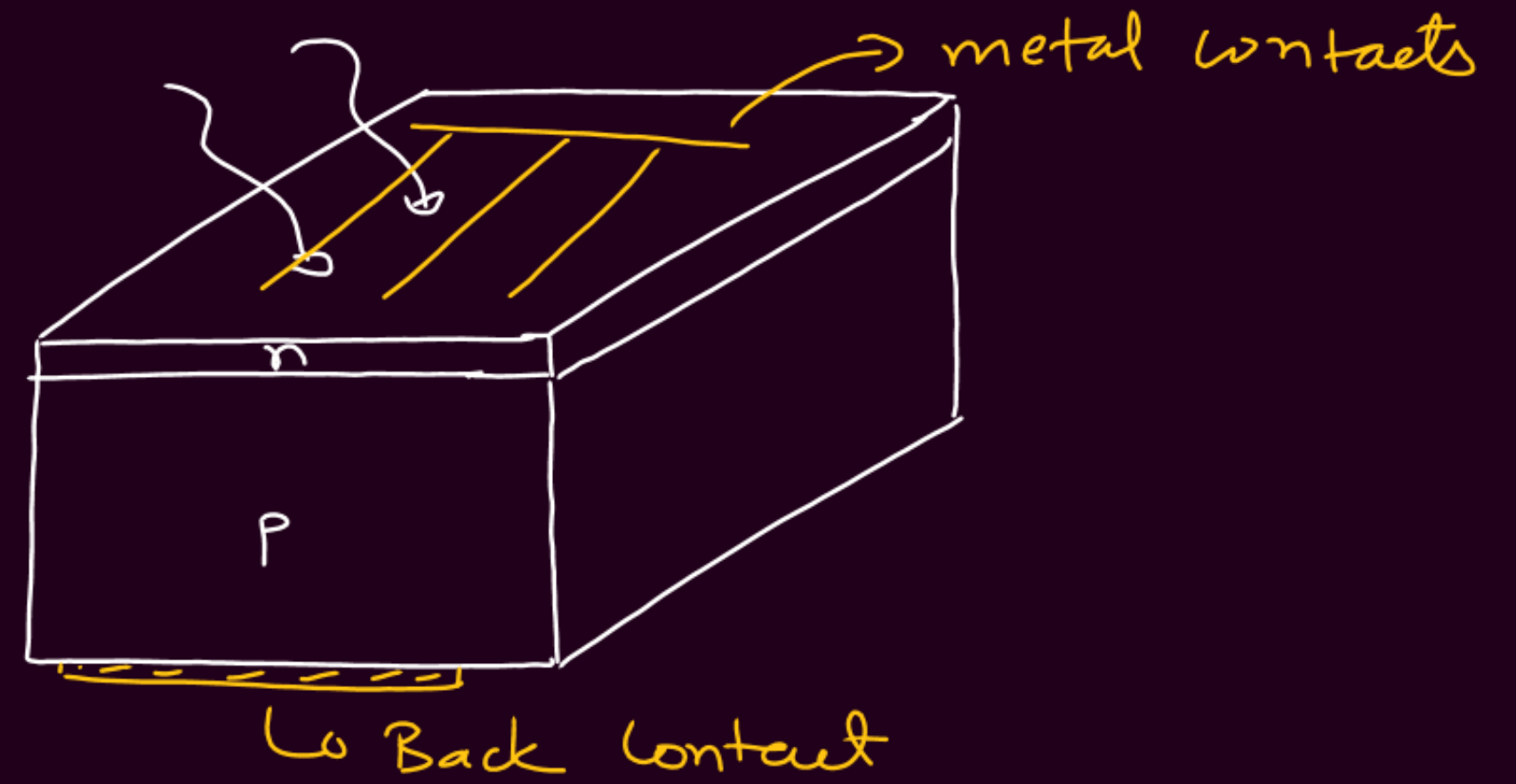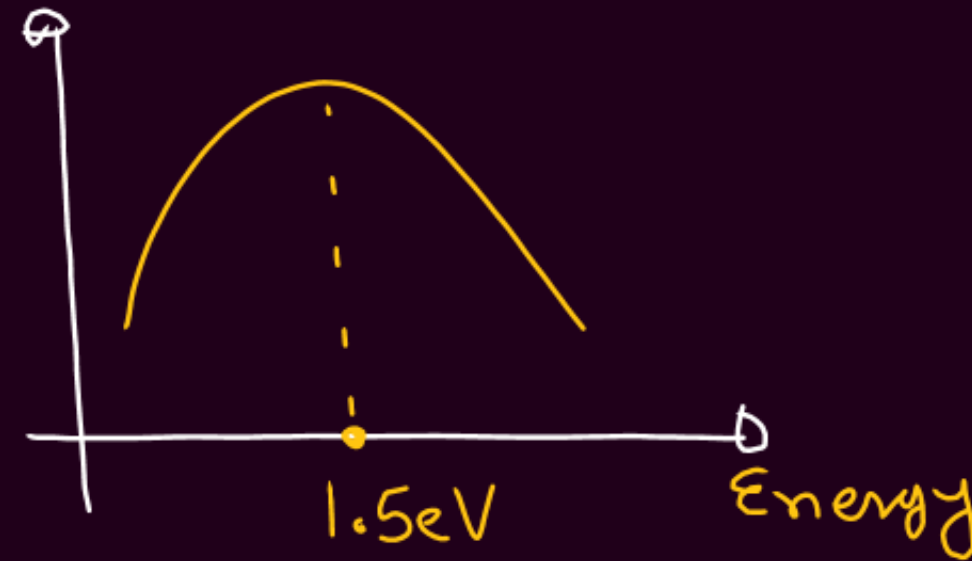



- Solar cell → material
- E_g (1 to 1.8 eV)
- High optical Absorption
- Availability & cost

Realisation of Gates


① OR Gate

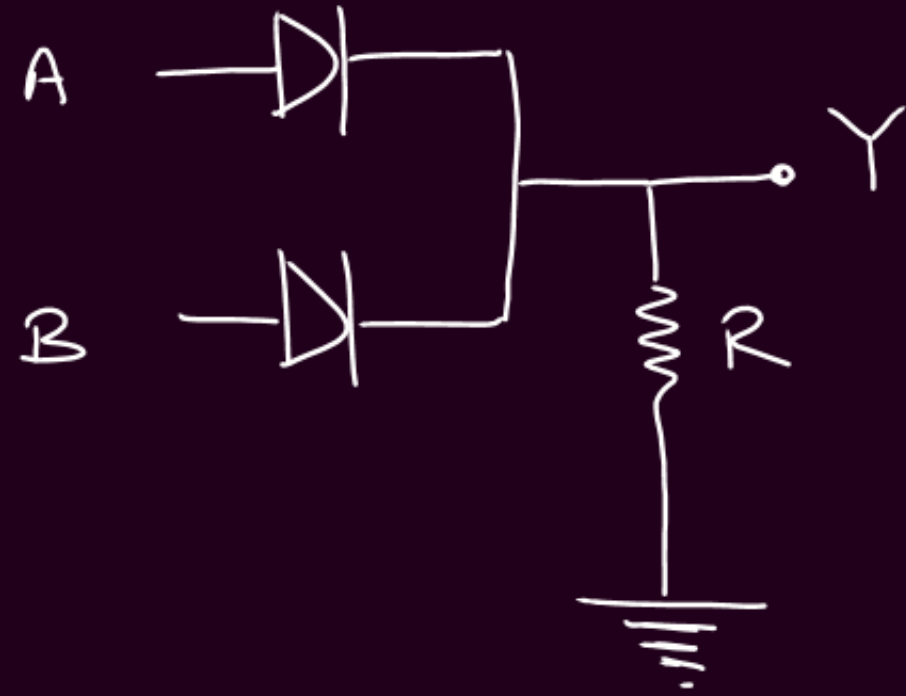


② AND Gate

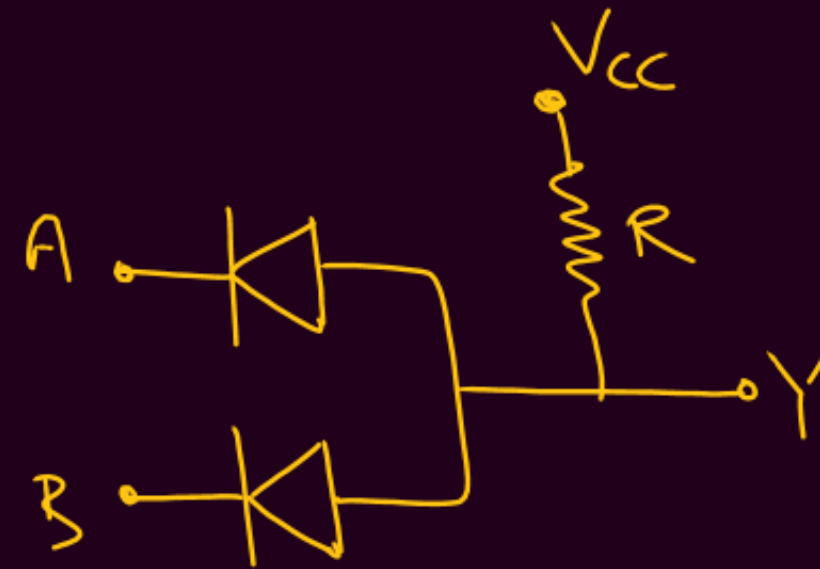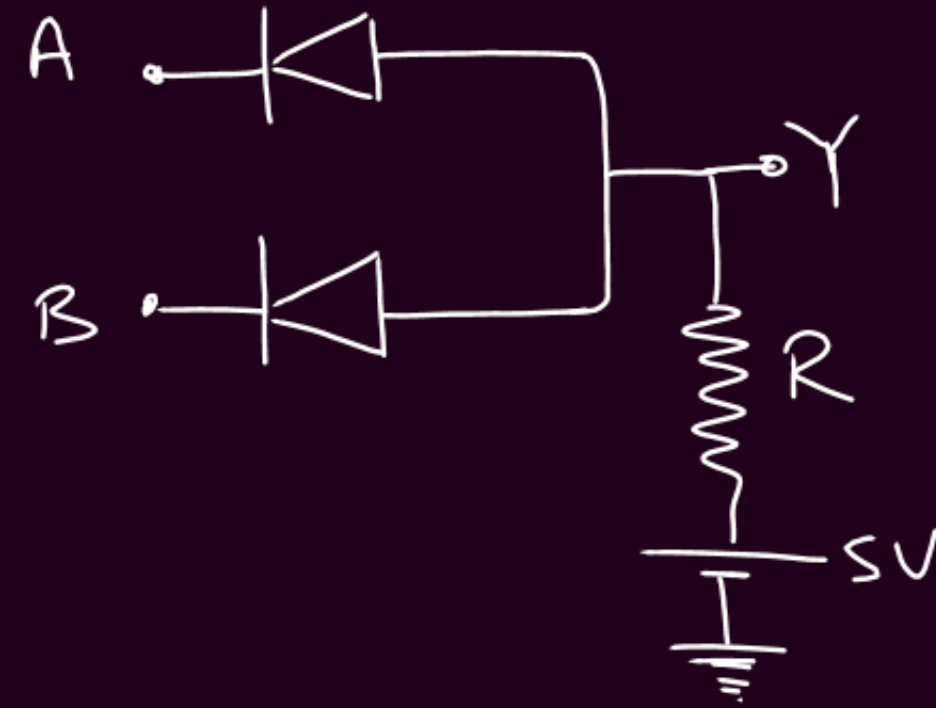

③ NOT Gate

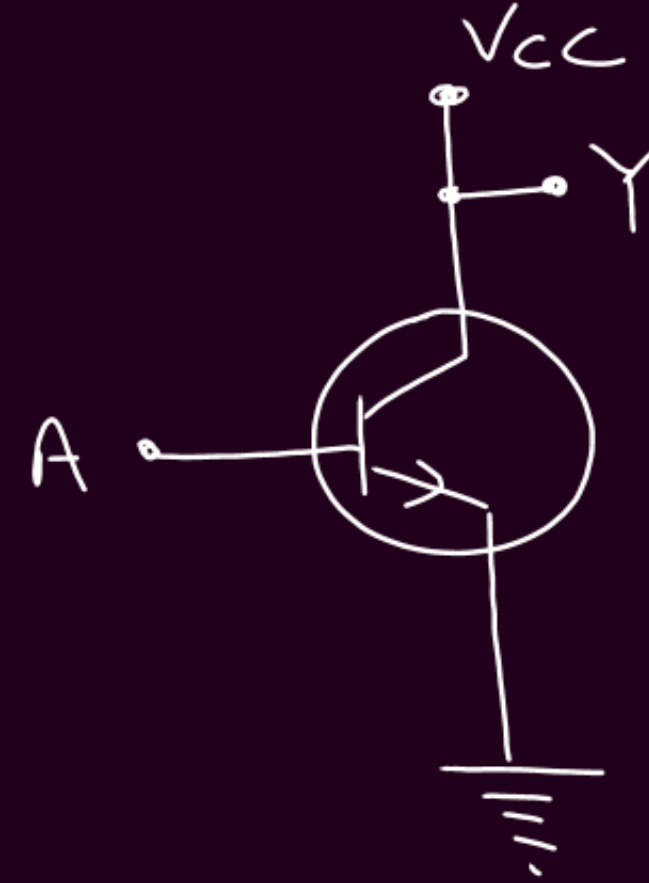

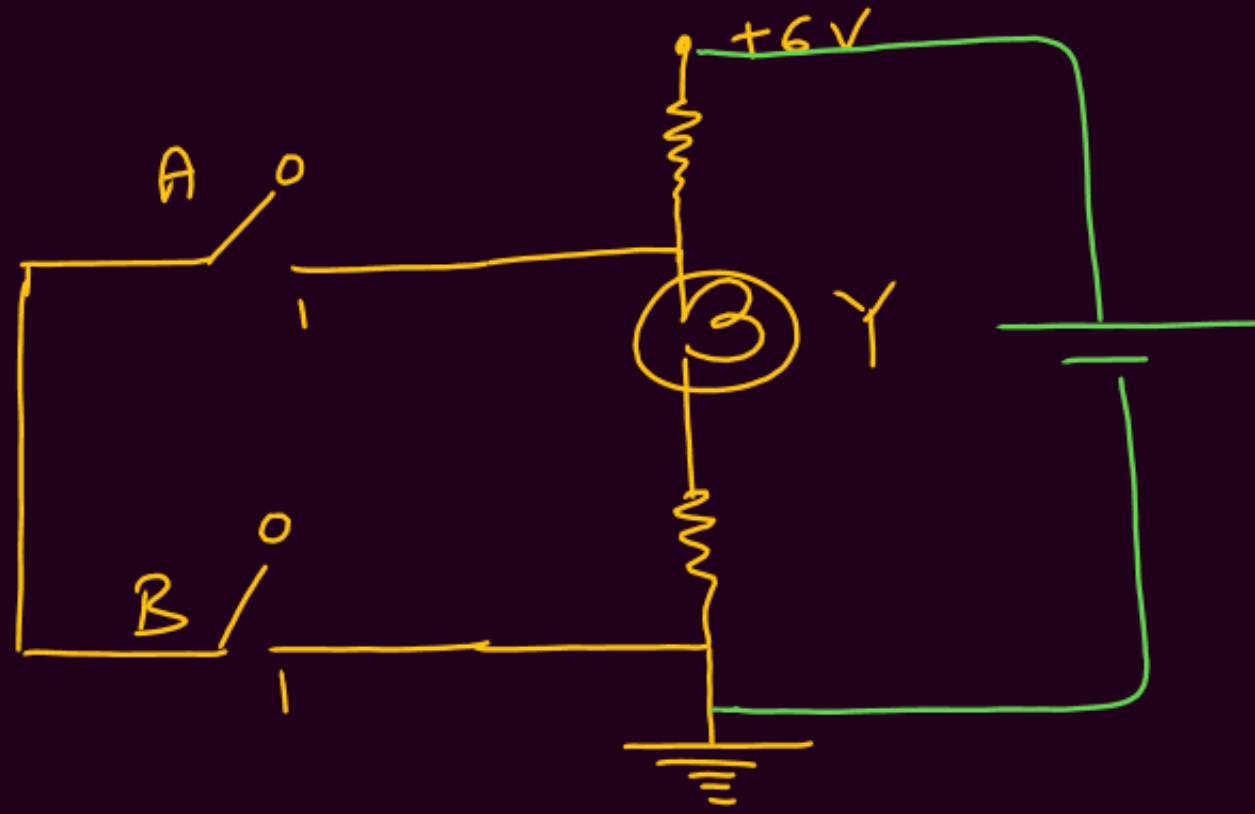

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

NAND

short