


Current Electricity

Current

$$i_{av} = \frac{\Delta q}{\Delta t}$$


$$i_{inst} = \frac{dq}{dt}$$

$$1A = 1C/s$$

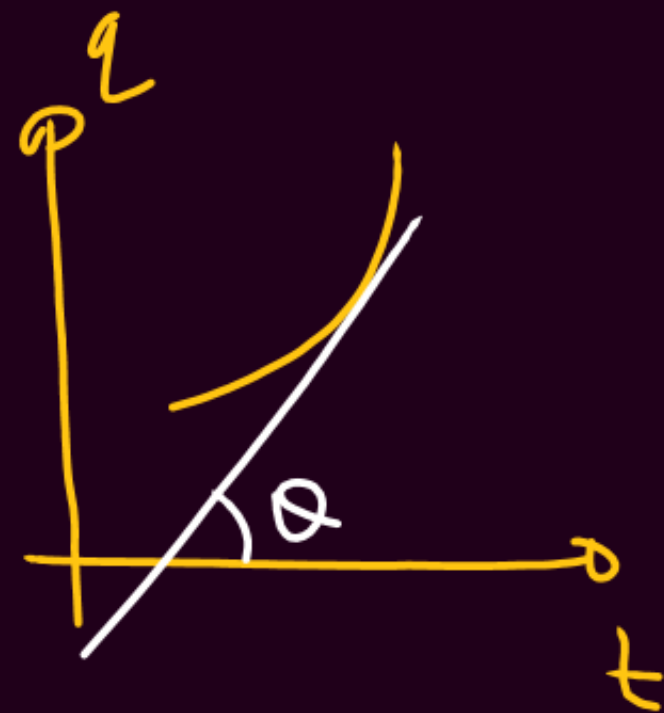

$$i = \frac{dq}{dt} = \tan \theta$$

$$\Delta q = \int i dt$$

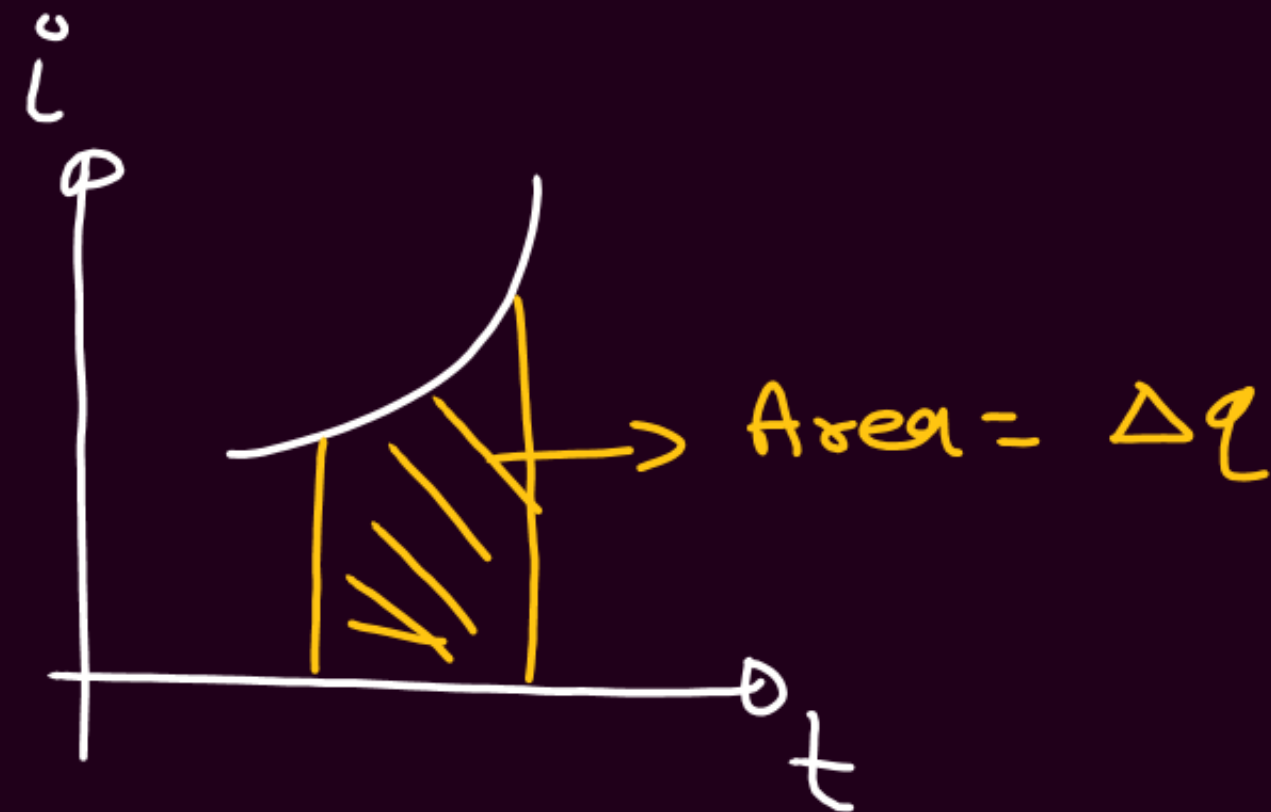


$$e = 1.6 \times 10^{-19} \text{ C}$$

$$m_e = 9.1 \times 10^{-31} \text{ kg}$$

$$\alpha\text{-particle} = \text{He}^{2+} \quad \begin{pmatrix} p & n \\ n & p \end{pmatrix}$$

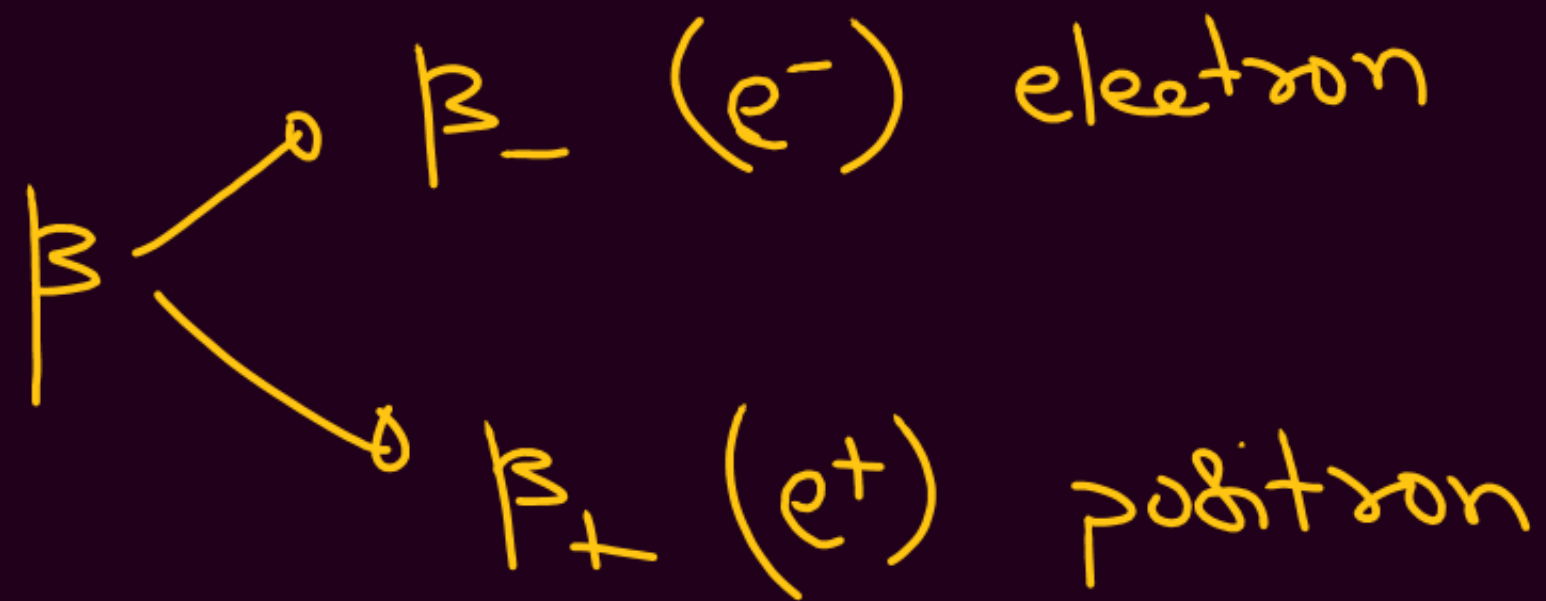Deuteron $\begin{pmatrix} p & n \end{pmatrix}$




Q $10^6 e^-$
 10 cm^2
per min

$$i = \frac{10^6 \times (1.6 \times 10^{-19})}{60}$$

$$i = \frac{8}{3} \times 10^{-15} \text{ A}$$

Q

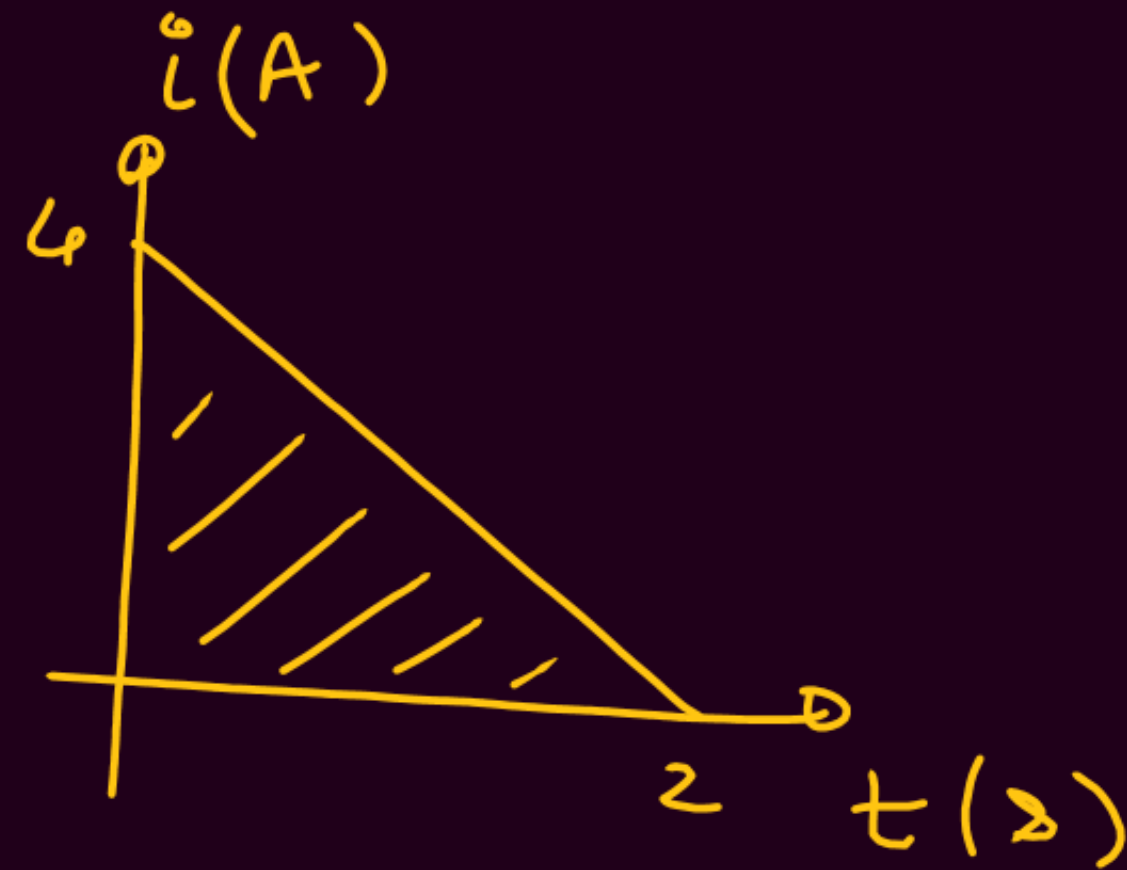

$$\Delta q = \text{Area} = \frac{1}{2} (2)(4) = \underline{\underline{4 \text{ C}}}$$

Q. $q = (t^2 - 4t + 2) \text{ C}$

Find 't' when $i = 0$

$$i = \frac{dq}{dt} = 2t - 4 = 0$$

t = 2s

Q. $q = (t^2 - 2t + 5)$

① i_{av} in 2s

$$t = 2s \quad q = 2^2 - 2(2) + 5 = 5$$


$$t = 0 \quad q = 0 - 0 + 5 = 5$$

$$i_{av} = \frac{\Delta q}{\Delta t} = \frac{5 - 5}{2} = 0$$

② i at 3s

$$i = \frac{dq}{dt} = 2t - 2$$

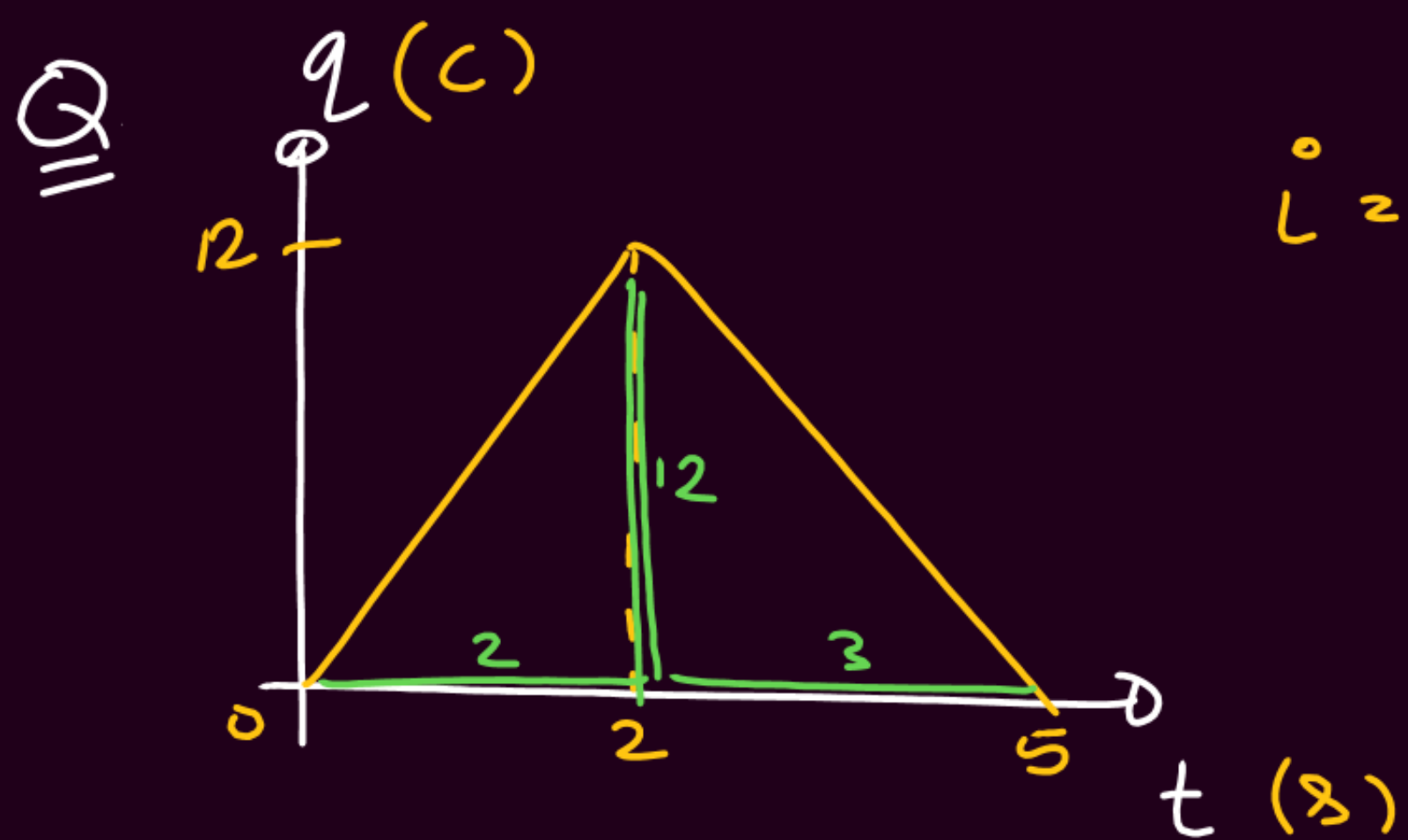
$$\underline{t = 3s} \quad i = (2 \times 3) - 2 = \underline{4A}$$



$t = 1s$ $i = \frac{12}{2} = 6A$

$t = 3s$ $i = -\frac{12}{3} = -4A$

$i = \frac{dq}{dt} = \text{slope}$

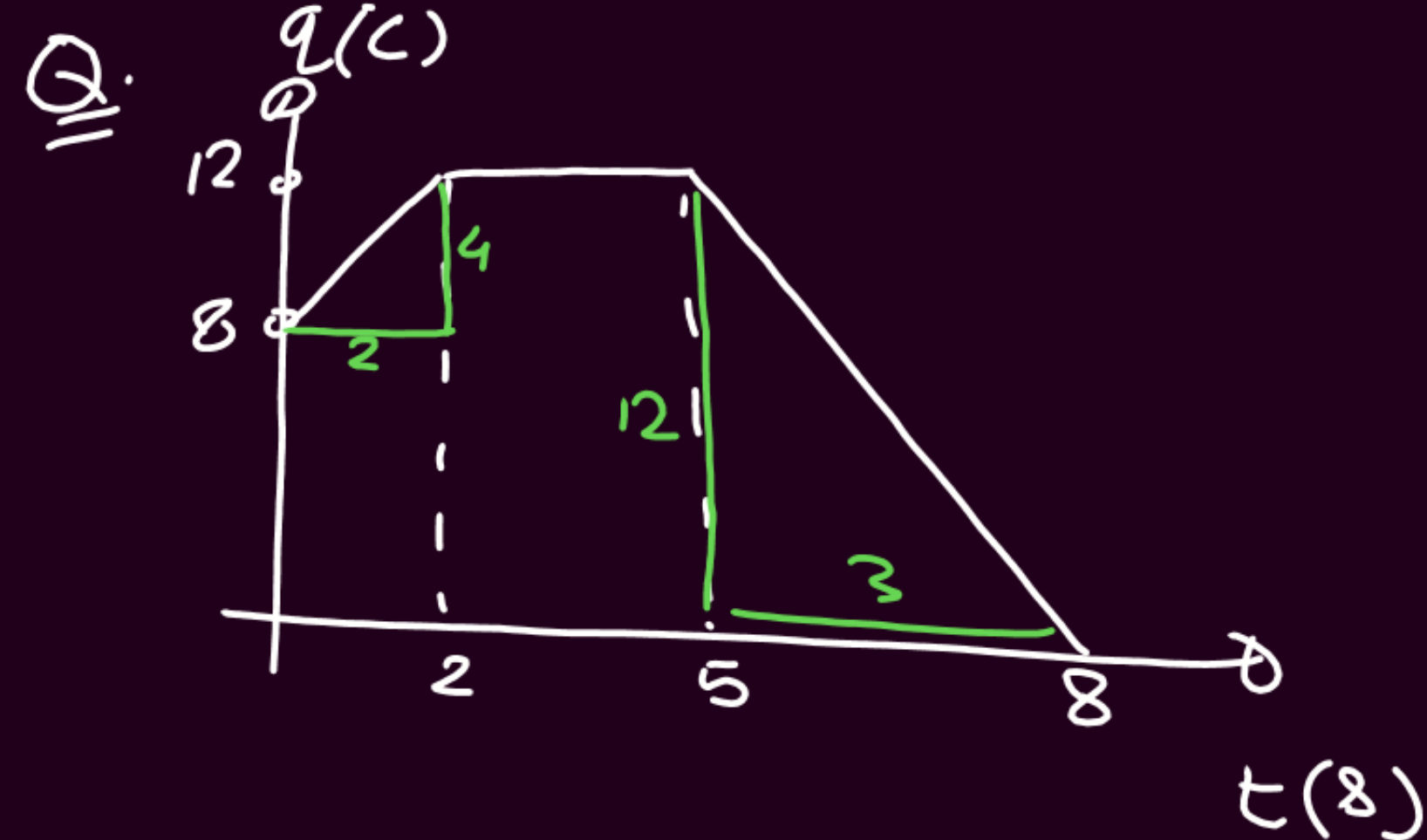

$t = 1s$ $i = \frac{12}{2} = 6A$

$t = 3s$ $i = 0$

$t = 7s$ $i = -\frac{12}{3} = -4A$


Sign convention

$$\oplus \quad \vec{v} \quad \vec{i}$$

$$\ominus \quad \vec{v} \quad \vec{i}$$

Point charge in UCM

UCM with uniform Speed

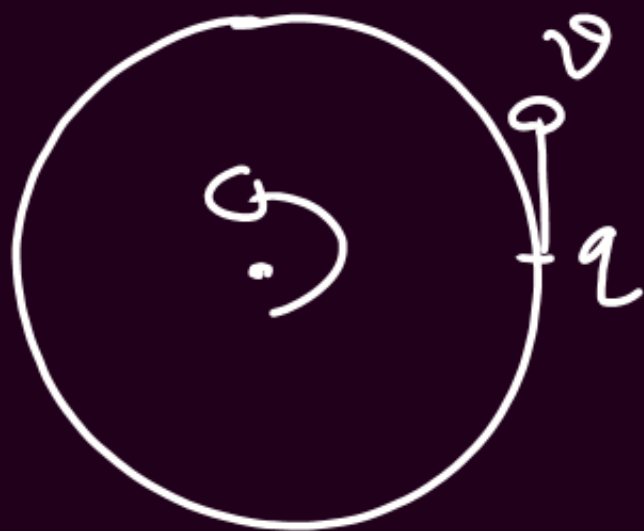

$$i = qf = \frac{q}{T} = \frac{qv}{2\pi r}$$

Q. e^- or state of H-atom

$$i^0 = \frac{qv}{2\pi r} = \frac{(1.6 \times 10^{-19})(2.18 \times 10^6)}{2(3.14)(0.53 \times 10^{-10})}$$

$$i^0 = \frac{\cancel{1.6} \times \cancel{2.18}}{\cancel{2(3.14)}(\cancel{0.53})} (10^{-3}) = \underline{10^{-3} \text{ A}}$$

Current Density ($\vec{j}$)

$$\vec{j} = \frac{i}{A}$$

$$i = \vec{j} \cdot \vec{A}$$


Microscopic View



Conductor $\rightarrow$ free e^-
[in Abundance]

$\rightarrow$ Random motion

$\rightarrow$ $\vec{v}_{av} = 0$

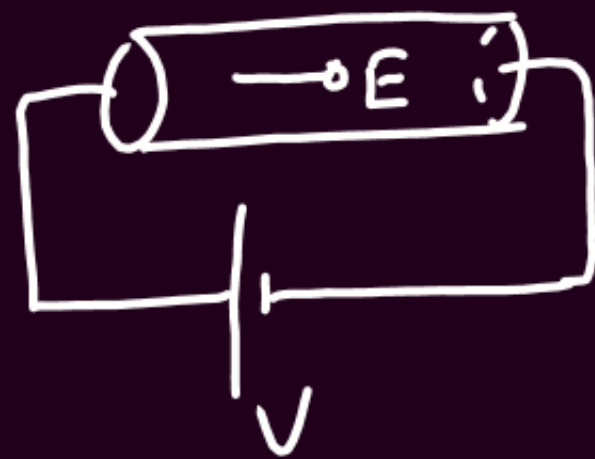

$V = \text{Voltage} = \text{Potential difference (P.D.)}$

$$E = \frac{V}{l}$$

$\rightarrow$ Thermal Speed $\sim 10^5 \text{ m/s}$

$\rightarrow$ Drift speed $\sim 10^{-4} \text{ m/s}$ (v_d)

$\rightarrow$ Relaxation time $\tau \sim 10^{-14} \text{ s}$

$\rightarrow$ Mean free path $\lambda \sim 10 \text{ \AA}$

$$\textcircled{1} \quad v_d = \frac{eE}{m} \tau$$

$$\textcircled{2} \quad i = neA v_d$$

n = no. of free e^- per unit volume

nA = _____ " _____ length

$$\textcircled{3} \quad \frac{i}{A} = ne \left(\frac{eE\tau}{m} \right)$$

$$\vec{j} = \sigma \vec{E}$$

Microscopic form of Ohm's law

$$\textcircled{5} \quad \frac{i}{A} = \frac{1}{R} \left(\frac{V}{l} \right)$$

$$i = \left(\frac{A}{Rl} \right) V$$

$$i = \frac{1}{R} V$$

ohm's law

$$i \propto V$$

$$\textcircled{4} \quad \sigma = \frac{ne^2 \tau}{m} = \text{Electrical Conductivity}$$

$$\rho = \frac{m}{ne^2 \tau}$$

$$\rho = \frac{1}{\sigma}$$

= Resistivity
(Specific Resistance)


⑥ Mobility (μ)

$$\boxed{\mu = \frac{v_d}{E}} = \frac{e\tau}{m} = \frac{\sigma}{ne}$$

$$\boxed{\sigma = ne\mu}$$

Resistivity

Metals

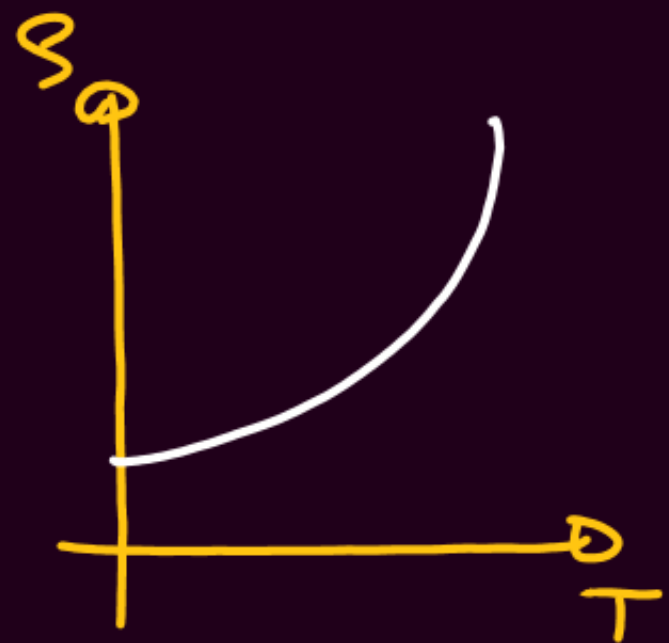


Cu

As Temp ↑

Collision → frequent

$\tau \downarrow$

$$\rho = \frac{m}{ne^2\tau}$$

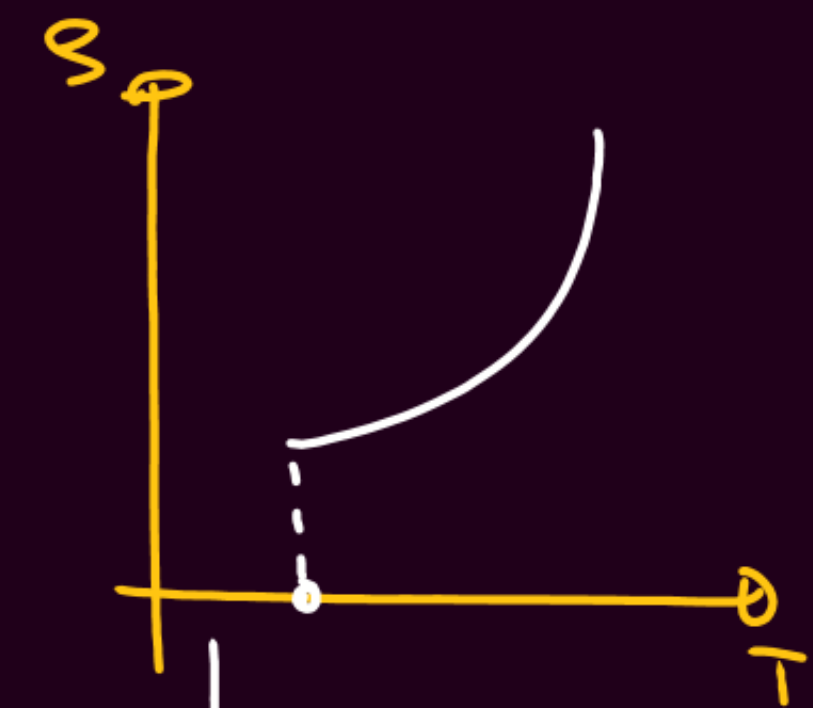

Superconductivity

ρ ↑

α = ⊕

ρ



Alloy → nichrome


$$\rho = \rho_0(1 + \alpha \Delta\theta)$$

$$\boxed{R = R_0(1 + \alpha \Delta\theta)}$$

α = Temp. Coeff of Resistance

SC / Insulator / Dielectric

Si / Ge

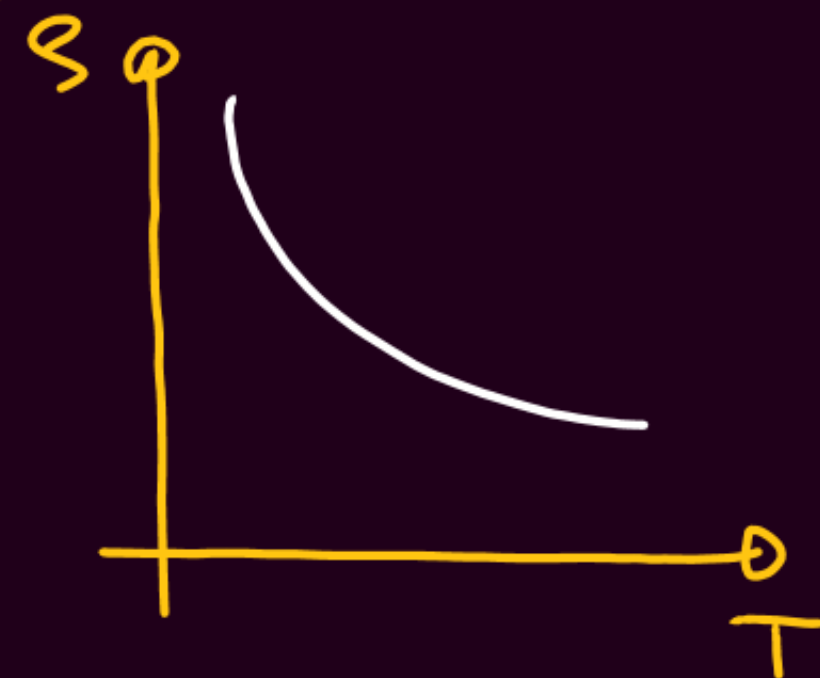


As Temp ↑

n ↑ [no. of charge carrier]

$$\rho = \frac{m}{ne^2\tau}$$

ρ ↓

α = ⊖

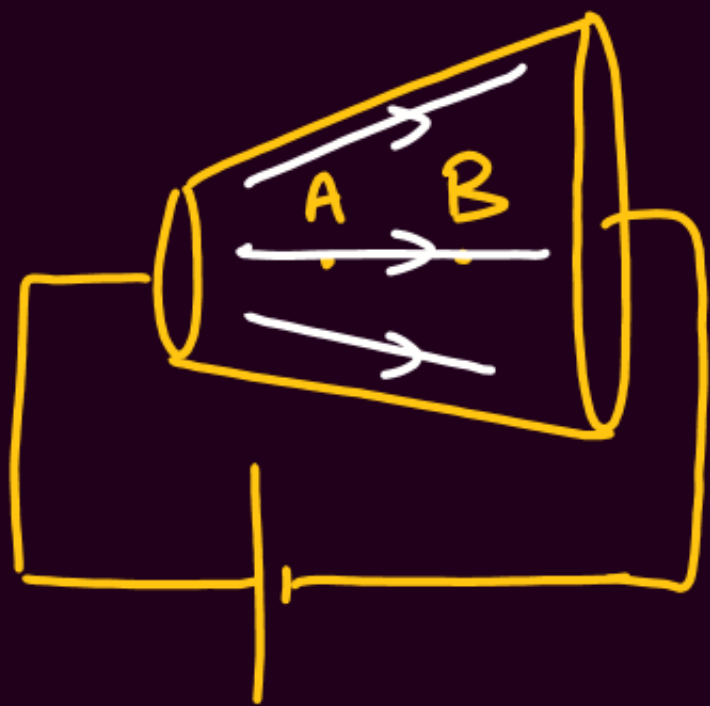

$$i_A = i_B \quad [\text{Series}]$$


$$j_A > j_B \quad \left[j = \frac{i}{A} \right]$$

$$E_A > E_B \quad [j = \sigma E]$$

$$V_A > V_B$$

$$V_{dA} > V_{dB} \quad [i = neAv_d]$$

Potential →

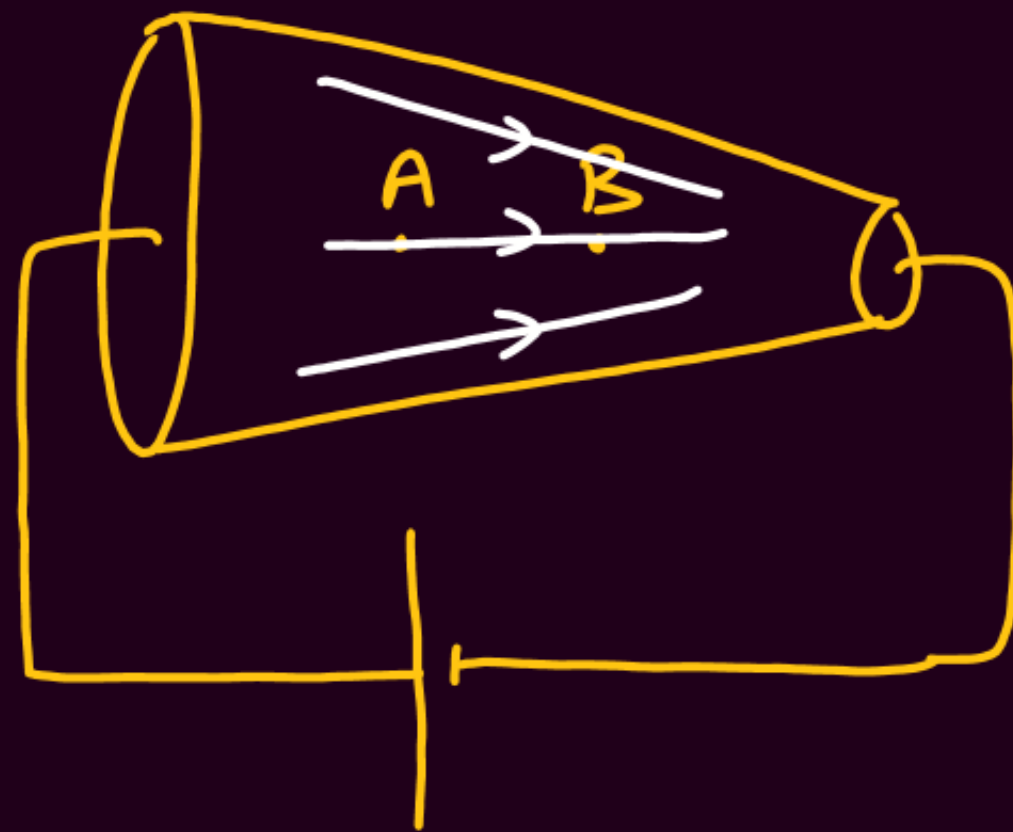

$$i_A = i_B$$

$$j_A < j_B$$

$$E_A < E_B$$

$$V_A > V_B$$


$$V_{dA} < V_{dB}$$

Conductor

- Electrostatic
- Current

$$E_{in} = 0$$

$$E_{in} \neq 0$$

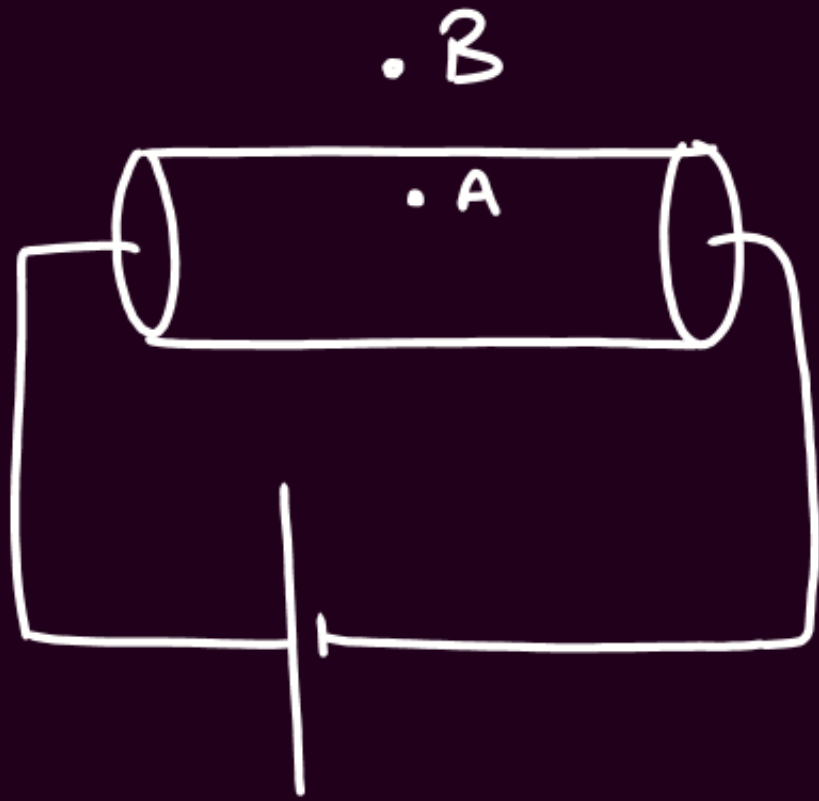

1) $E = 0$

$$B = 0$$

2) $E \neq 0$

$$B \neq 0$$

(A)

3) $E = 0$

$$B \neq 0$$

(B)

4) $E \neq 0$

$$B = 0$$

Q. 2 A
4 cm²
10²² / cm³

$$i = neA v_d$$

$$2 = (10^{22} \times 10^6) (1.6 \times 10^{-19}) (4 \times 10^{-4}) v_d$$

$$v_d = \frac{2}{1.6 \times 4 \times 10^5} = 0.3 \times 10^{-5} \text{ m/s}$$

$$= 3 \times 10^{-6} \text{ m/s}$$

$$1 \text{ cm} = 10^{-2} \text{ m}$$

$$1 \text{ cm}^2 = 10^{-4} \text{ m}^2$$

$$1 \text{ cm}^3 = 10^{-6} \text{ m}^3$$

$$[4 \text{ cm}^2 = 4 \times 10^{-4} \text{ m}^2]$$

$$\left[\frac{10^{22}}{\text{cm}^3} = \frac{10^{22}}{10^{-6} \text{ m}^3} \right]$$

Physics

Page-98

1 to 10

Page-102

2, 4, 9

Page-124

1, 2, 6 to 12

14, 15,

Page-130

13, 14, 26,

30,

Q. $i = neAv_d$

$$4 = (nA) (1.6 \times 10^{-19}) 10^{-4}$$

$$(nA) = \frac{4}{1.6} \times 10^{23} = 2.5 \times 10^{23} / \text{m}$$

① $\boxed{10\Omega}$ $\rightarrow$ $\boxed{12\Omega}$ R
 R_0 200°C $\theta = ?$

$$R = R_0(1 + \alpha \Delta\theta)$$

② $\boxed{10\Omega}$ $\rightarrow$ $\boxed{30\Omega}$ R_2
 R_1 200°C $\theta = ?$

$$R = R_0(1 + \alpha \theta)$$

$\hookrightarrow$ Resistance at 0°C

$$\boxed{\frac{R_2}{R_1} = \frac{1 + \alpha \theta_2}{1 + \alpha \theta_1}} \quad \boxed{\theta_1 / \theta_2 \quad ^\circ\text{C}}$$

① $\alpha = 10^{-3}/^\circ\text{C}$ $12 = 10(1 + 10^{-3} \Delta\theta)$
 $1.2 = 1 + 10^{-3} \Delta\theta$
 $0.2 = 10^{-3} \Delta\theta$

$$\Delta\theta = 200^\circ\text{C}$$

$$\boxed{\theta_f = 400^\circ\text{C}}$$

② $\alpha = 10^{-3}/^\circ\text{C}$

$$\frac{30}{10} = \frac{1 + 10^{-3} \theta_2}{1 + 10^{-3}(200)}$$


$$3.6 = 1 + 10^{-3} \theta_2$$

$$2.6 = 10^{-3} \theta_2$$

$$\boxed{2600^\circ\text{C} = \theta_2}$$


Ohm's law

$$i = \frac{1}{R} (V)$$
$$y = mx$$

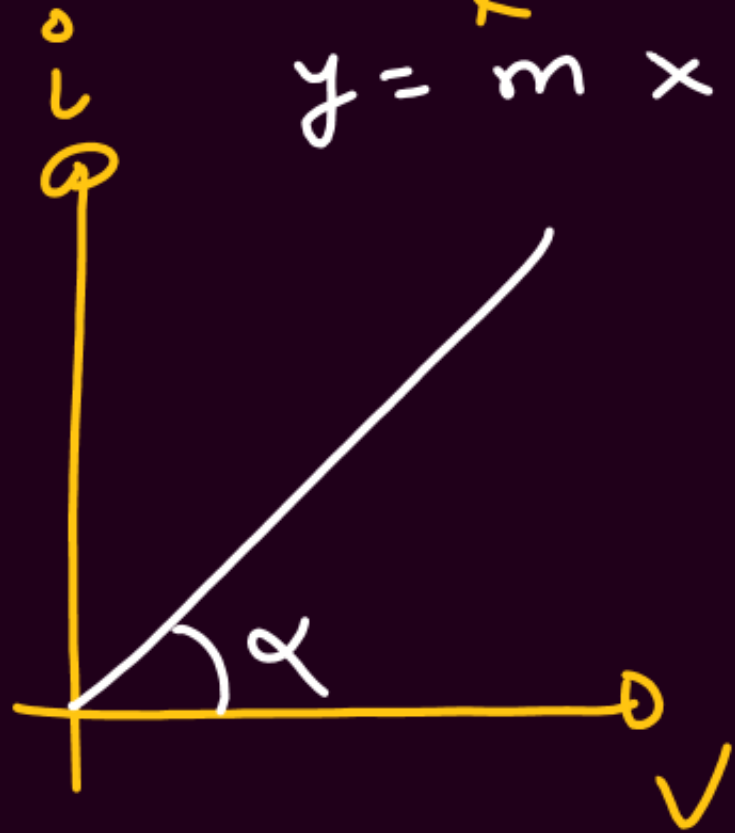


$$\text{slope} = \tan \alpha = \left(\frac{1}{R}\right)$$

$$V = (R)i$$
$$y = mx$$

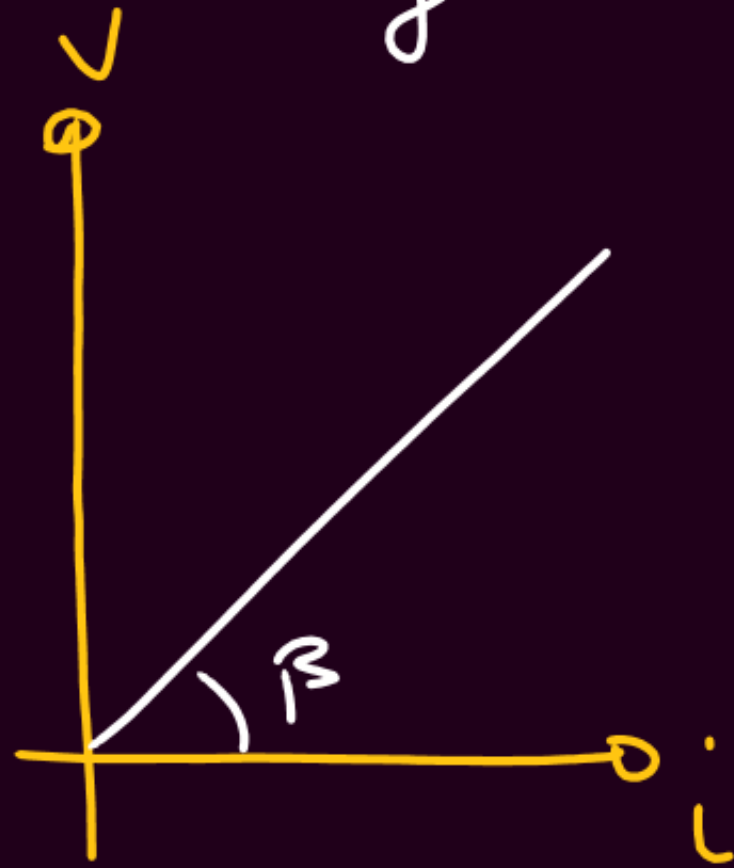


$$\text{slope} = \tan \beta = R$$

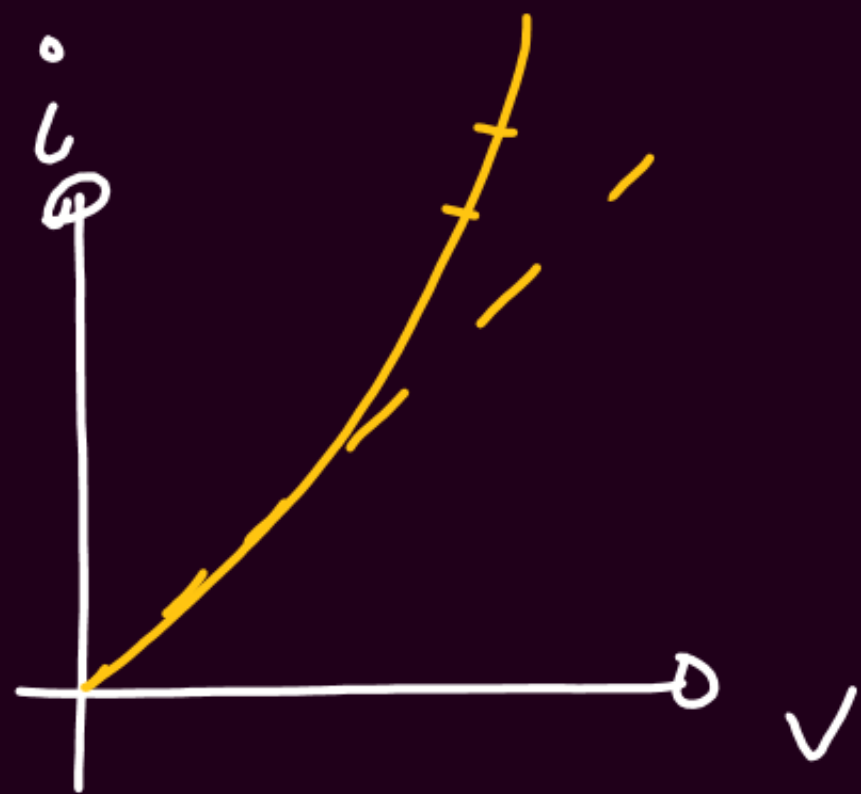



ohm's law $\rightarrow$ "ohmic"

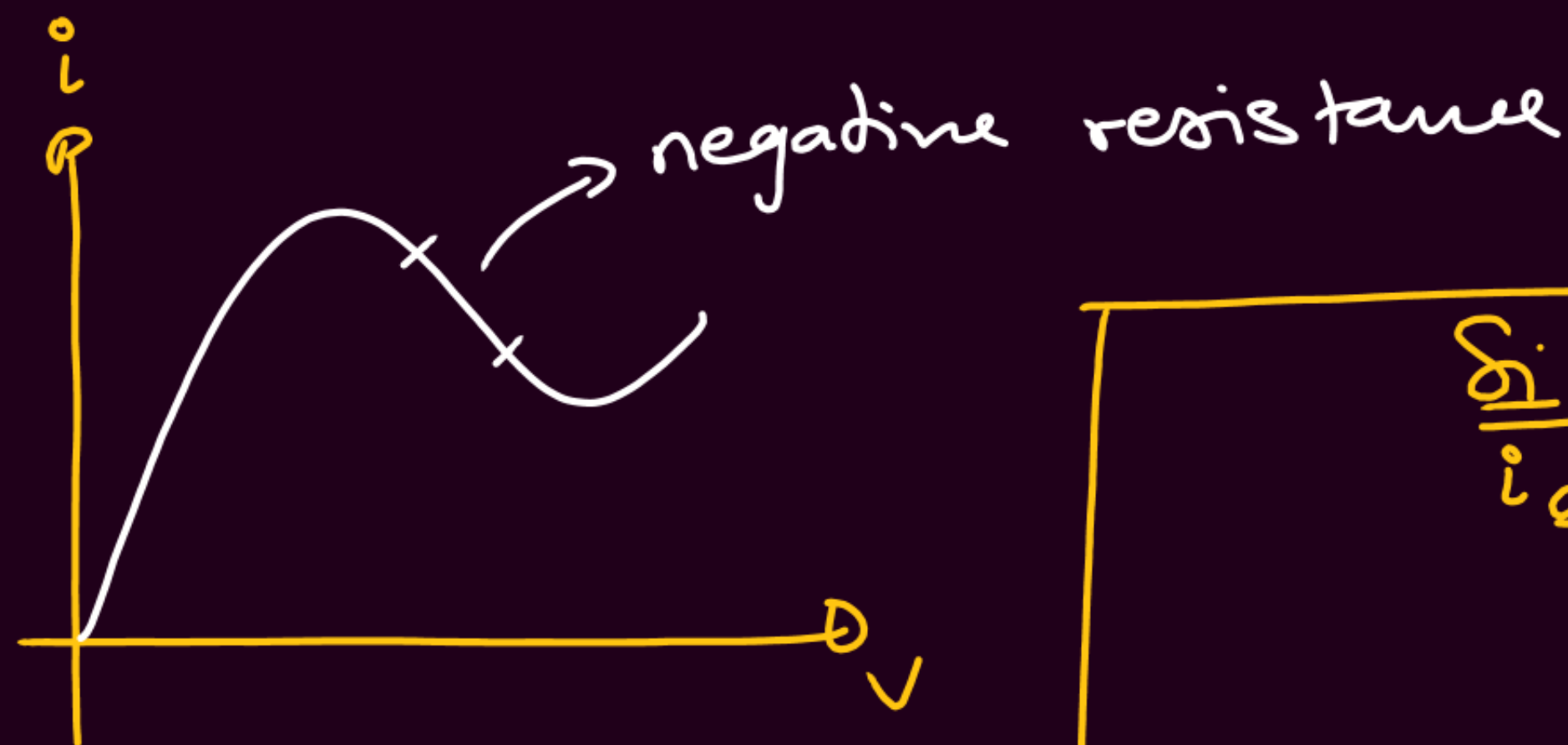Dynamic Resistance $r_d = \frac{\Delta V}{\Delta i}$




GaAs

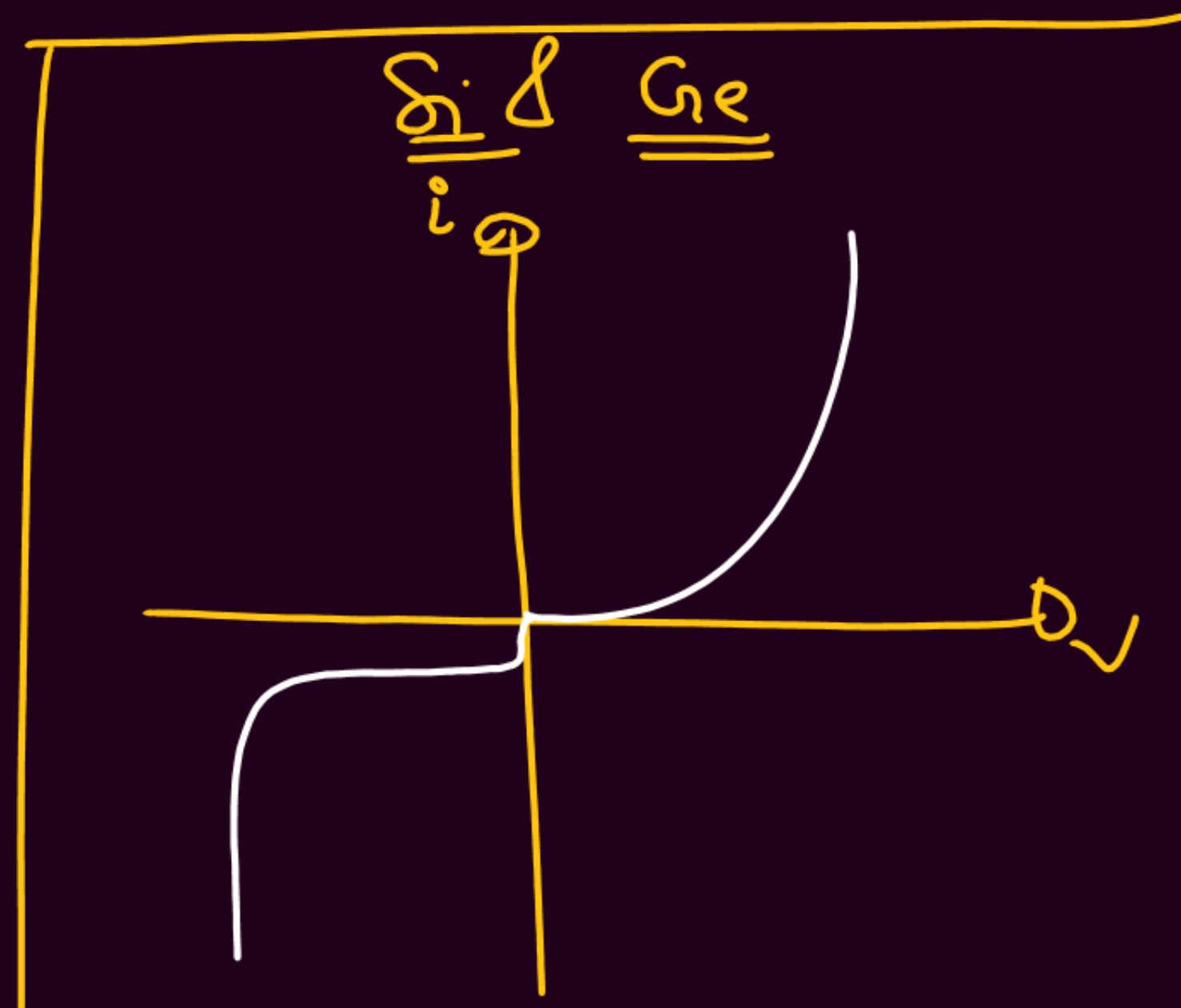

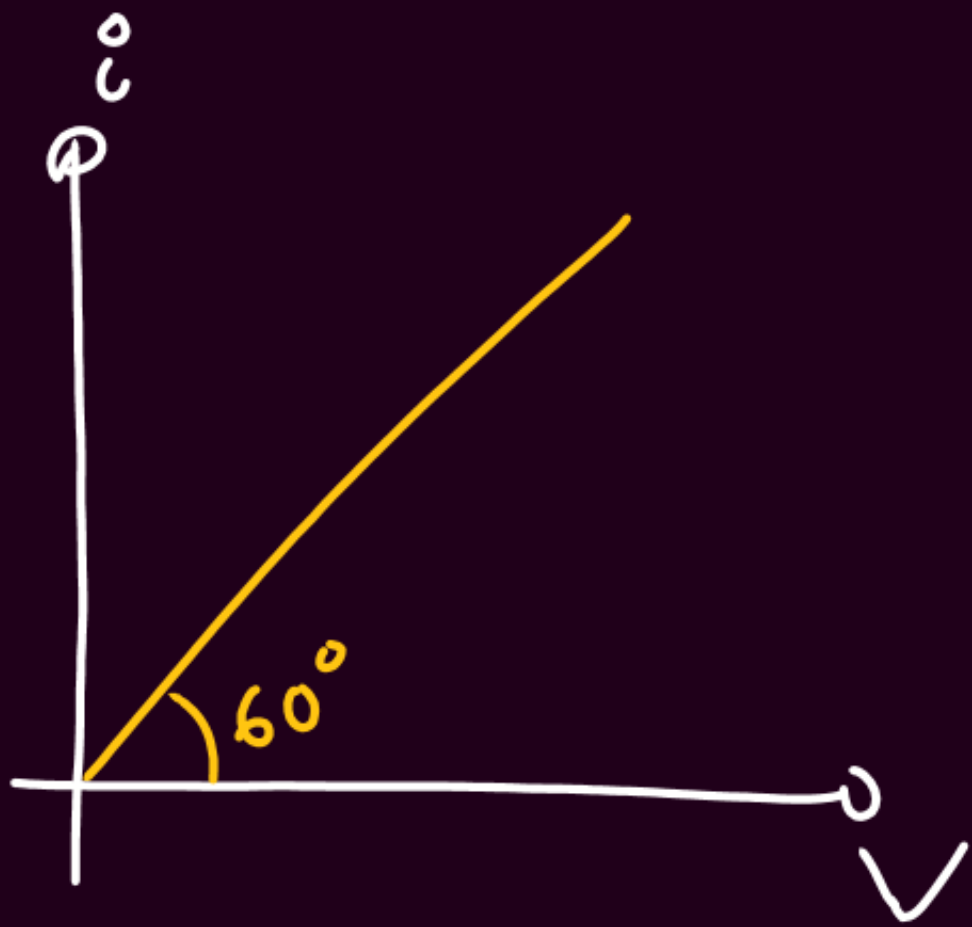
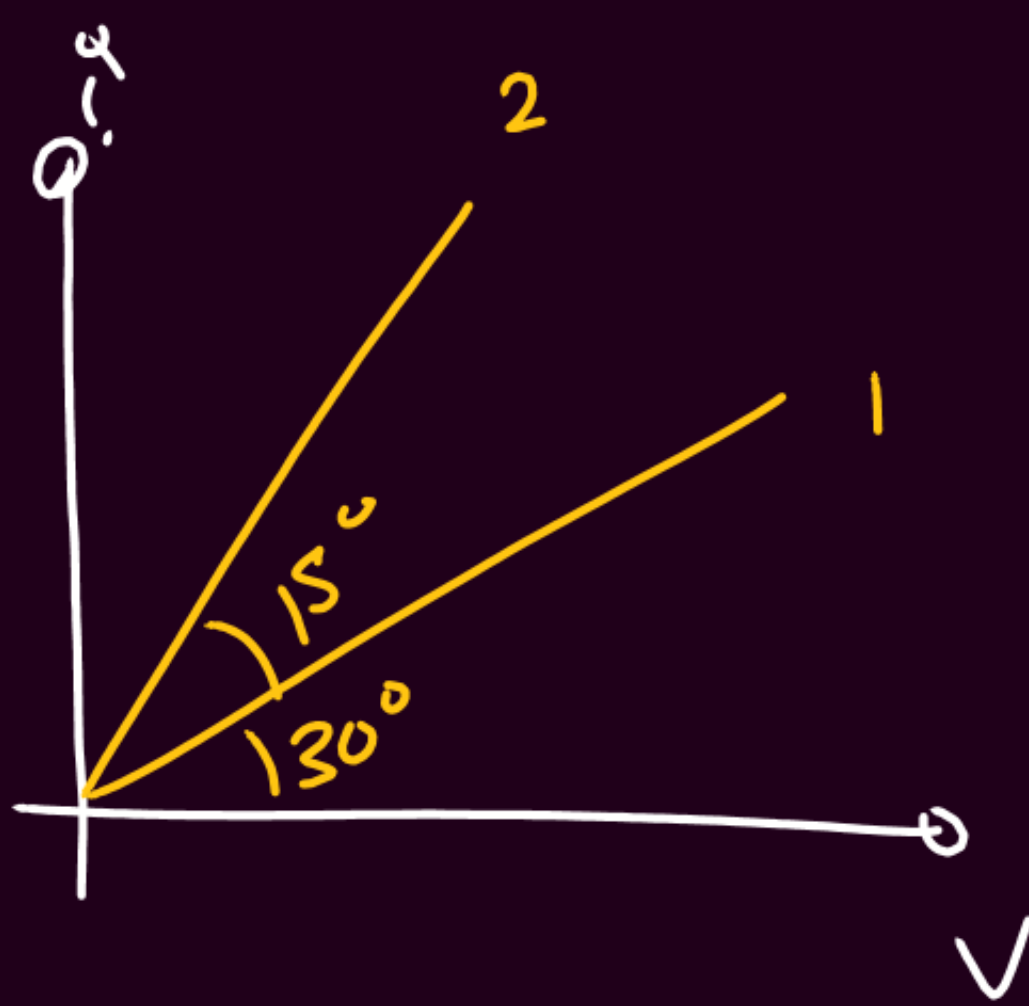
$$R = \frac{1}{\tan 60^\circ} = \frac{1}{\sqrt{3}}$$



$$R_1 = \frac{1}{\tan 30^\circ} = \frac{\sqrt{3}}{1}$$

$$R_2 = \frac{1}{\tan 45^\circ} = 1$$


$$\frac{R_2}{R_1} = \frac{1}{\sqrt{3}}$$

$$R = \frac{\rho l}{A}$$


- length
- Area
- material
- Temp.




$$R = \frac{\rho l}{\pi r^2}$$

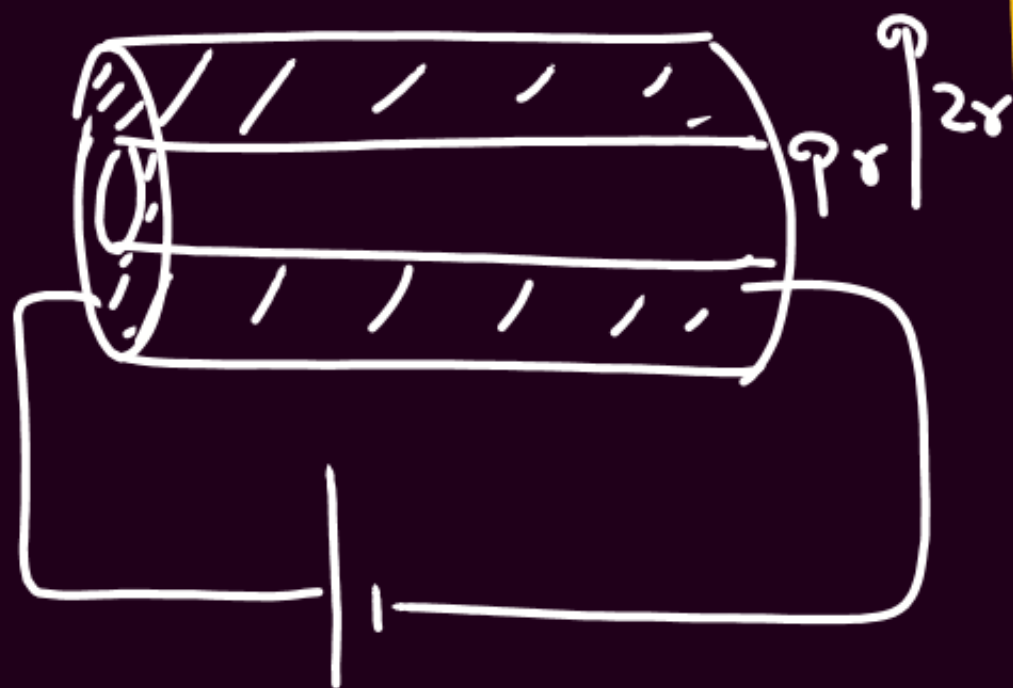
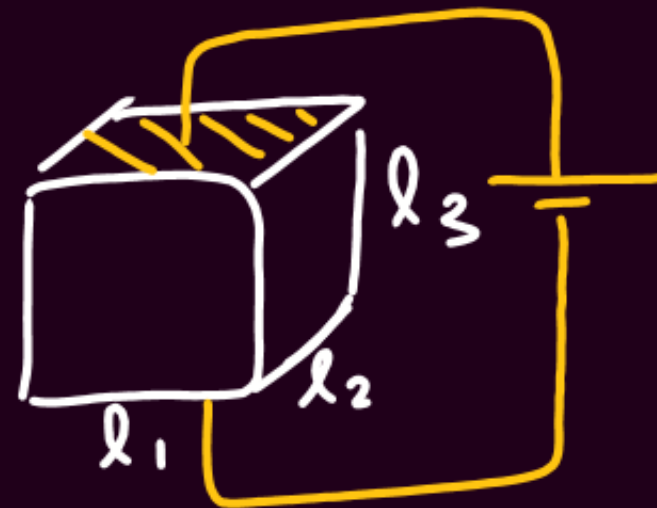
$$R = \frac{\rho l}{\pi((2r)^2 - r^2)} = \frac{\rho l}{3\pi r^2}$$




$$R = \frac{\rho l_3}{l_1 l_2}$$

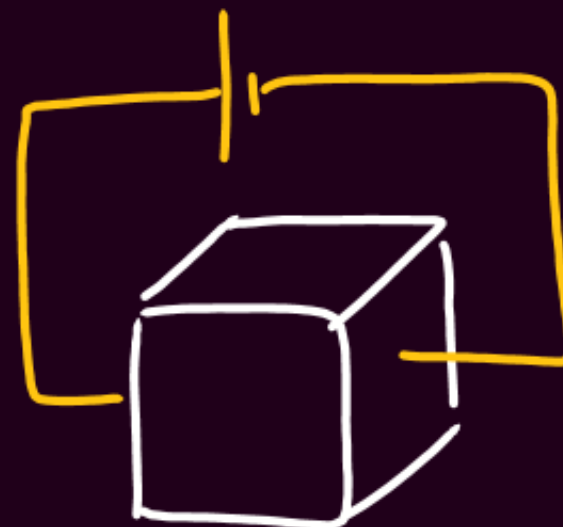

$$R = \frac{\rho l_1}{l_2 l_3}$$



$$R = \frac{\rho l_2}{l_1 l_3}$$

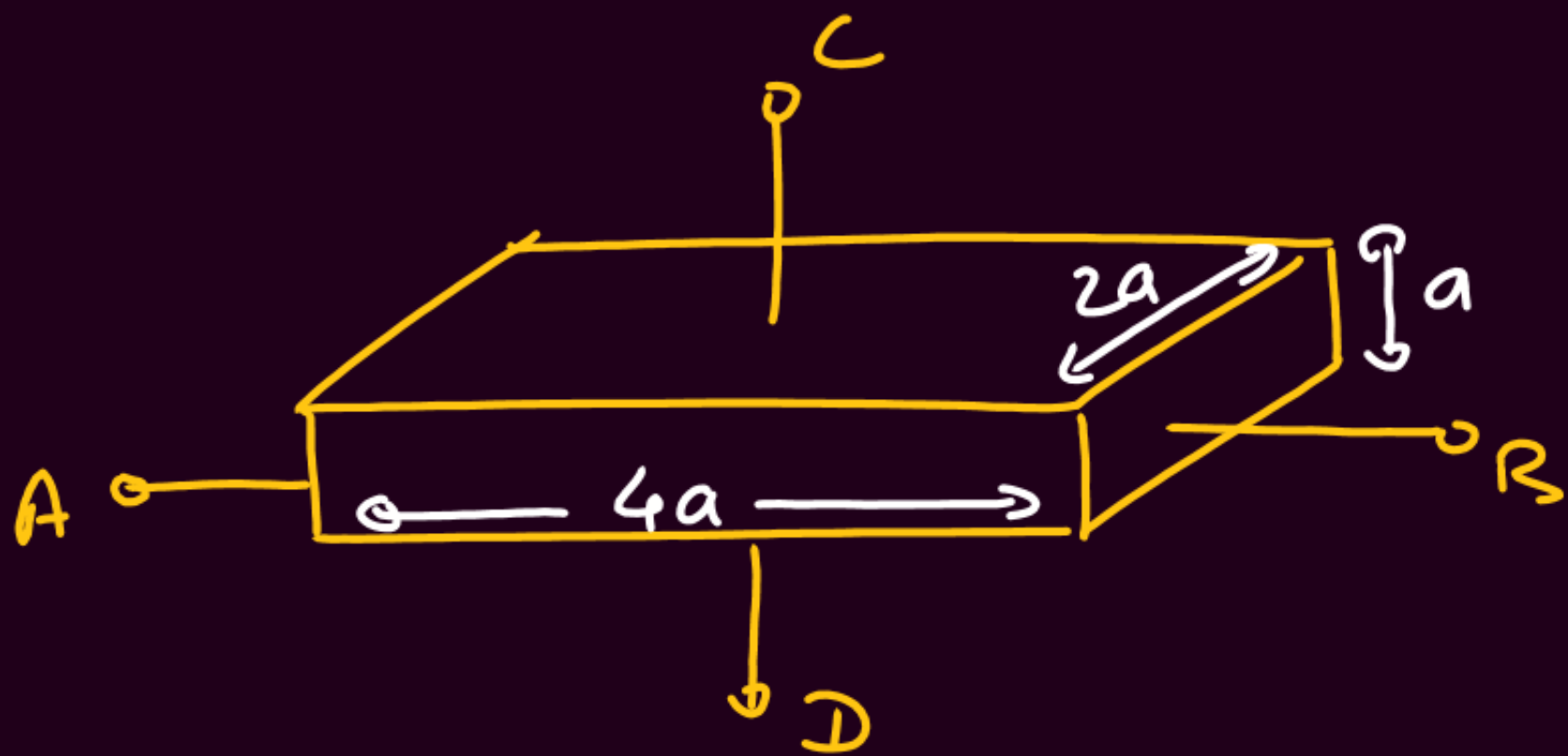

$$\frac{R_{AB}}{R_{CD}} = \frac{2}{1/8} = \frac{16}{1}$$

$$R_{AB} = \frac{S(4a)}{a(2a)} = \frac{2S}{a}$$

$$R_{CD} = \frac{S(a)}{(2a)(4a)} = \frac{S}{8a}$$

wire $(l, r) \rightarrow R_0 = \frac{3l}{\pi r^2}$

(Double, Half)

$$R = \frac{3(2l)}{\pi \left(\frac{r}{2}\right)^2} = \underline{\underline{8R_0}}$$

Wire

↳ Volume Const

↳ Stretched

↳ melt & recast

↳ Drawn into

$$R = \frac{\rho l}{A}$$

$$R = \frac{\rho l^2}{V} = \frac{\rho V}{A^2} = \frac{\rho V}{\pi^2 r^4}$$

$$\frac{\Delta R}{R} = 2\left(\frac{\Delta l}{l}\right) = -2\left(\frac{\Delta A}{A}\right) = -4\left(\frac{\Delta r}{r}\right)$$

① if $l \rightarrow 2l$ then $R \rightarrow 4R$

② if $A \rightarrow 2A$ then $R \rightarrow \frac{R}{4}$

③ if $r \rightarrow 2r$ then $R \rightarrow \frac{R}{16}$

④ if $l \uparrow$ by 2% then $R \uparrow$ by 4%

⑤ if $A \uparrow$ by 2% then $R \downarrow$ by 4%

⑥ if $r \uparrow$ by 2% then $R \downarrow$ by 8%

Equivalent σ / σ

① Series 

[Assume - Area]

$$R_{eq} = R_1 + R_2$$

$$\frac{R_{eq}(l_1 + l_2)}{A} = \frac{R_1 l_1}{A} + \frac{R_2 l_2}{A}$$

$$R_{eq} = \frac{R_1 l_1 + R_2 l_2}{l_1 + l_2}$$

$$\frac{(l_1 + l_2)}{\sigma_{eq} A} = \frac{l_1}{\sigma_1 A} + \frac{l_2}{\sigma_2 A}$$

$$\sigma_{eq} = \frac{l_1 + l_2}{\frac{l_1}{\sigma_1} + \frac{l_2}{\sigma_2}}$$

② Parallel



[Assume - length]

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$\frac{A_1 + A_2}{\sigma_{eq} l} = \frac{A_1}{\sigma_1 l} + \frac{A_2}{\sigma_2 l}$$

$$\sigma_{eq} = \frac{A_1 + A_2}{\frac{A_1}{\sigma_1} + \frac{A_2}{\sigma_2}}$$

$$\frac{\sigma_{eq}(A_1 + A_2)}{l} = \frac{\sigma_1 A_1}{l} + \frac{\sigma_2 A_2}{l}$$


$$\sigma_{eq} = \frac{\sigma_1 A_1 + \sigma_2 A_2}{A_1 + A_2}$$

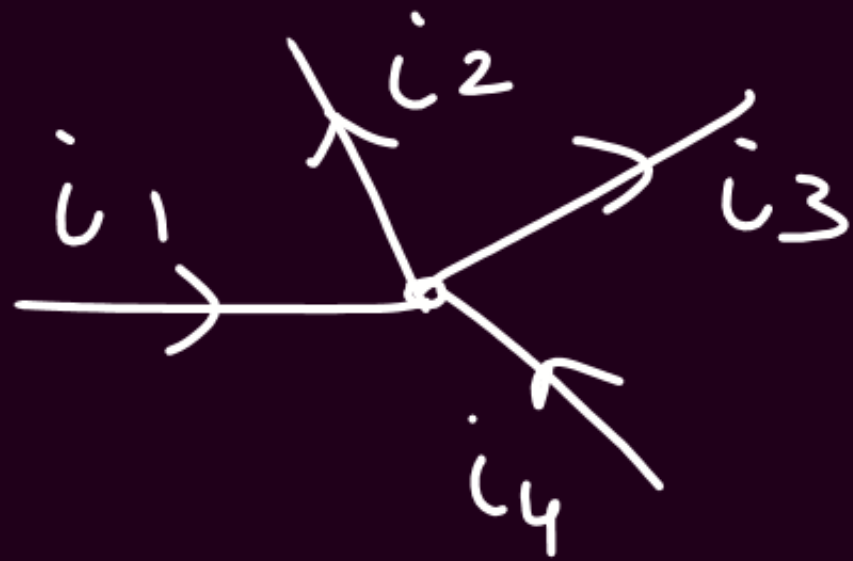Kirchoff's current law (KCL) [Junction law]
→ law of conservation of q




Total incoming = Total outgoing

$$i_1 + i_4 = i_2 + i_3$$

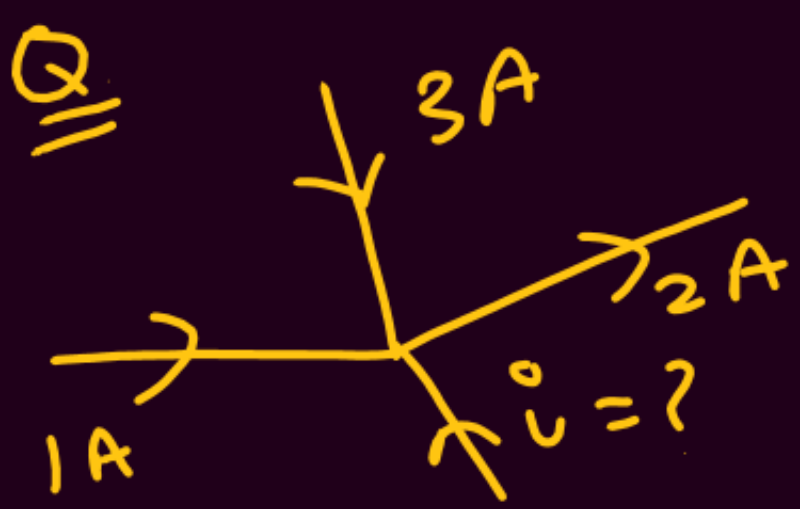

$$1 + 3 + i = 2$$

$$\boxed{i = -2A}$$

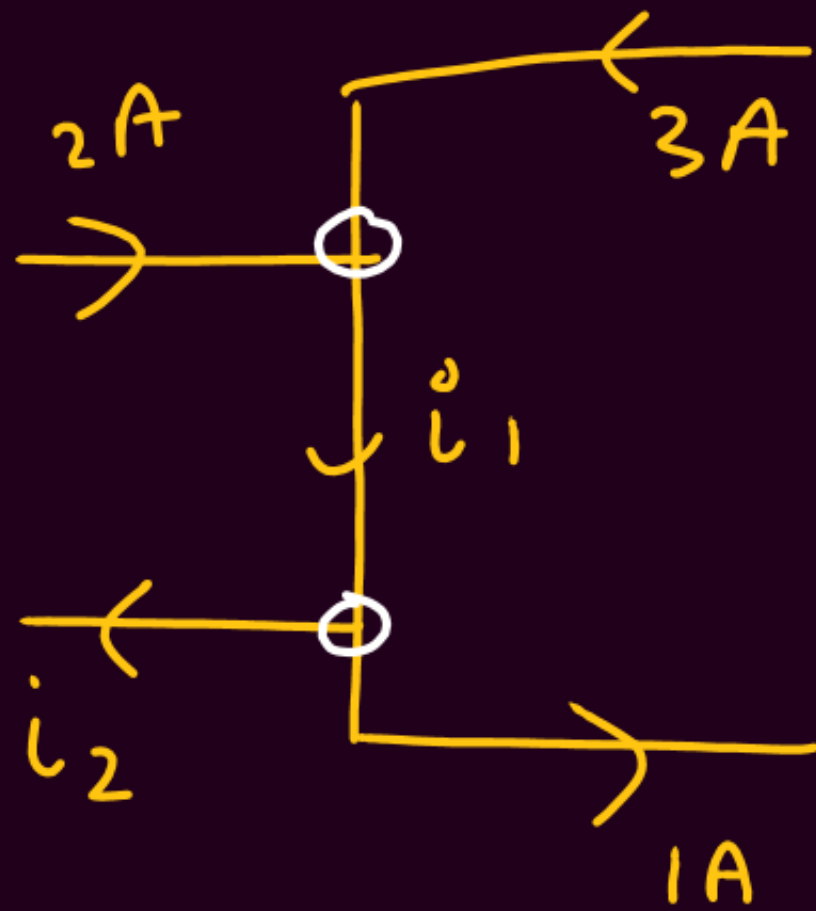


$$2 + 3 = i_1$$

$$\boxed{i_1 = 5A}$$

$$i_1 = i_2 + 1$$


$$5 = i_2 + 1$$

$$\boxed{i_2 = 4A}$$

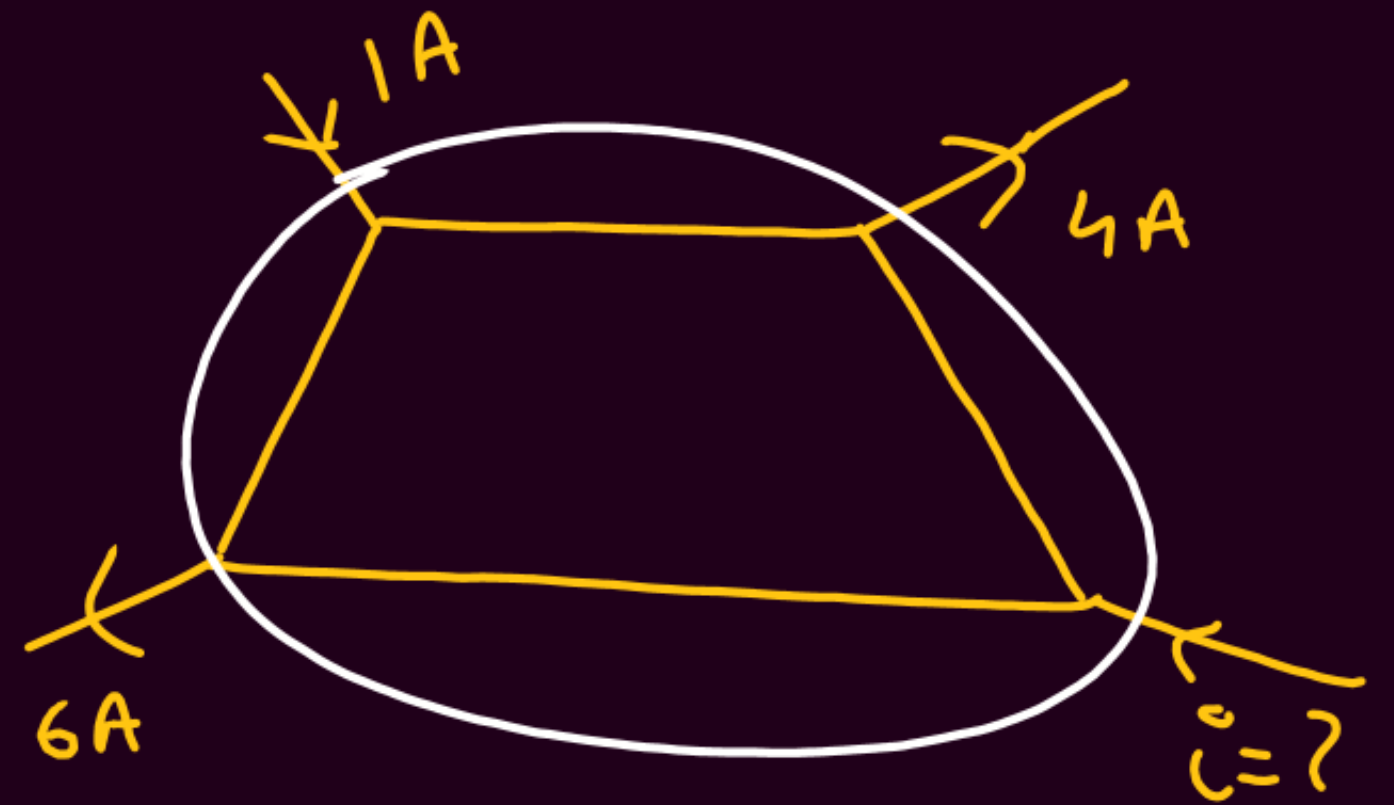

$$1 + i = 6 + 4$$

$$\underline{i = 9A}$$

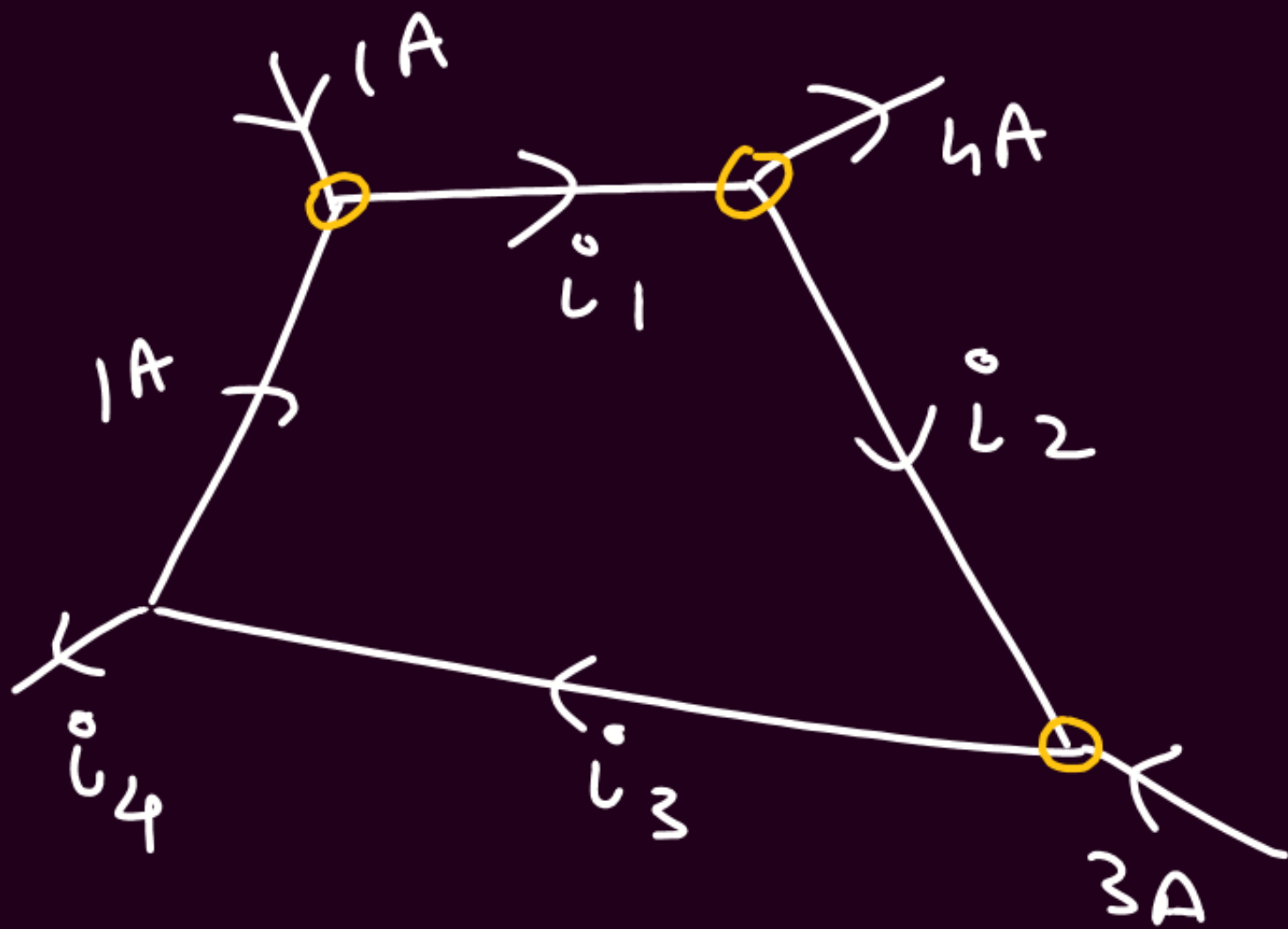

$$1 + 1 = i_1$$

$$i_1 = 2A$$

$$i_1 = 4 + i_2$$

$$i_2 = -2A$$

$$\begin{cases} i_2 + 3 = i_3 \\ -2 + 3 = i_3 \end{cases}$$

$$i_3 = 1A$$

$$i_3 = i_4 + 1$$


$$1 = i_4 + 1$$

$$i_4 = 0$$


Sign convention

→ P.D betⁿ A & B } [B to A]
→ Potential of A wrt B }

$$V_{AB} = V_A - V_B$$

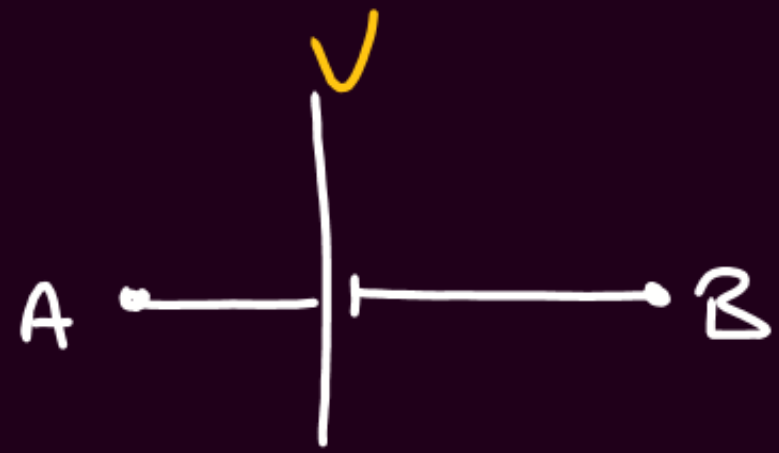

$$V_{AB} = V$$

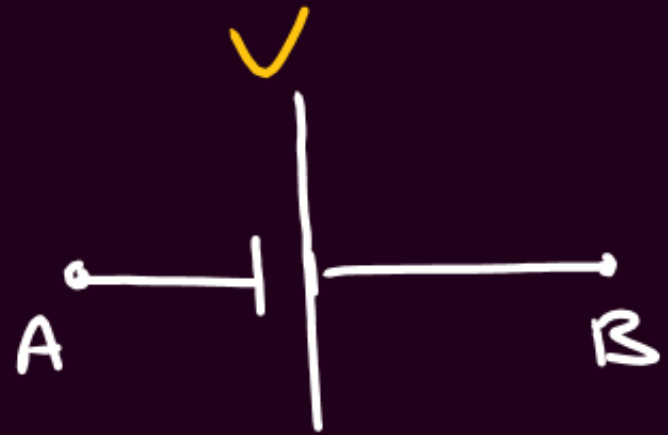

$$V_{AB} = -V$$



$$V_{AB} = iR$$



$$V_{AB} = -iR$$




$$V = 2 + 10$$



$$V = -10 - 4$$


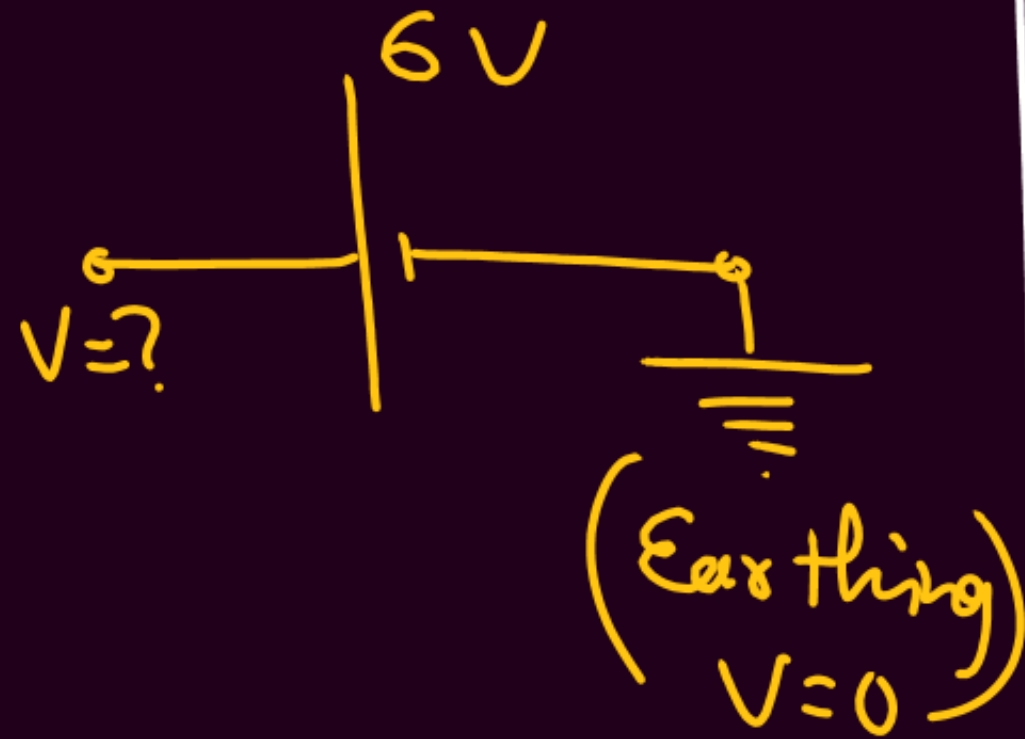
$$V = 1 + (2)(3) = \underline{\underline{7V}}$$



$$V = 0 + 6$$




$$V = 3 - 6 + 10 = 7V$$



$$V = -4 + 6 + (5)(3)$$

$$\underline{\underline{V = 17V}}$$

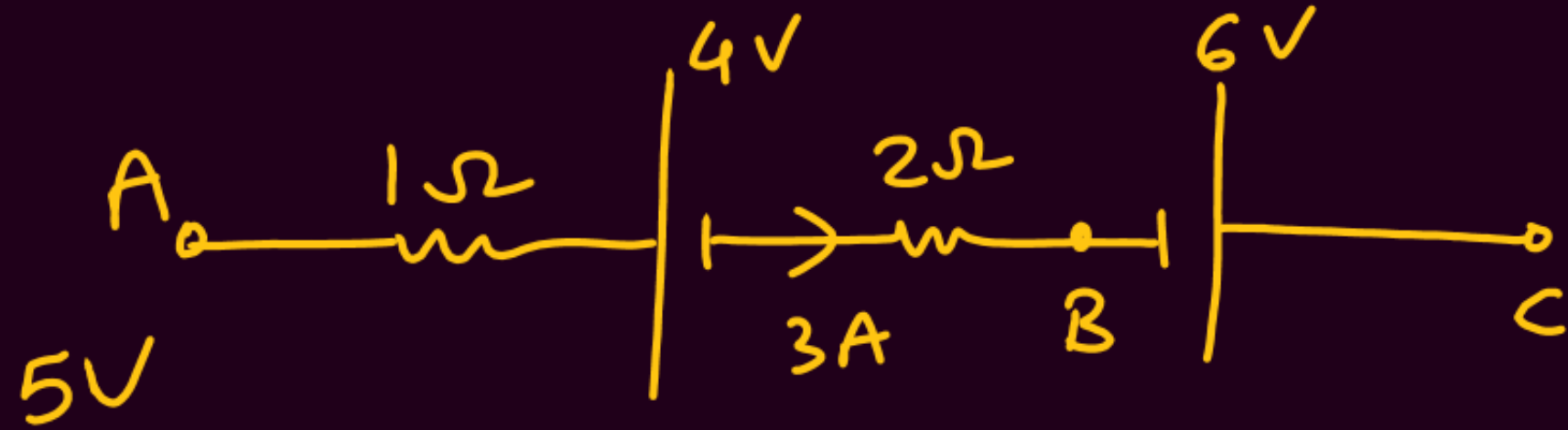


given $V_A = 5V$

$$V_B = 5 - (3)(1) - 4 - (3)(2) = -8V$$

(A) $V_C = \underbrace{5 - (3)(1) - 4 - (3)(2)} + 6$


(B) $V_C = -8 + 6$

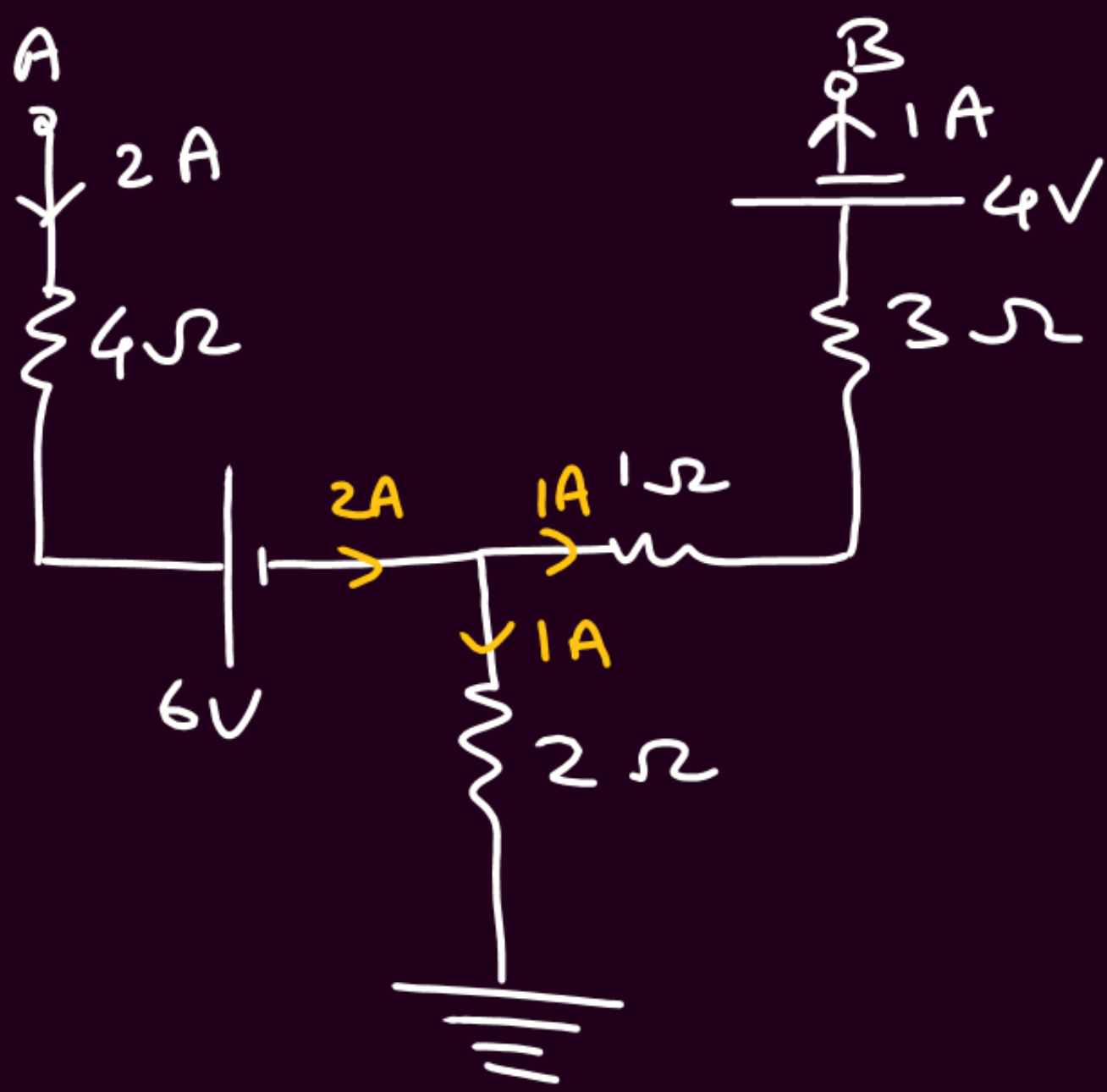


$$V_A = 0 + (1)(2) + 6 + (2)(4) = 16V$$

$$V_B = 0 + (1)(2) - (1)(2) - (1)(3) - 4 = \underline{-6V}$$

Junction Potential

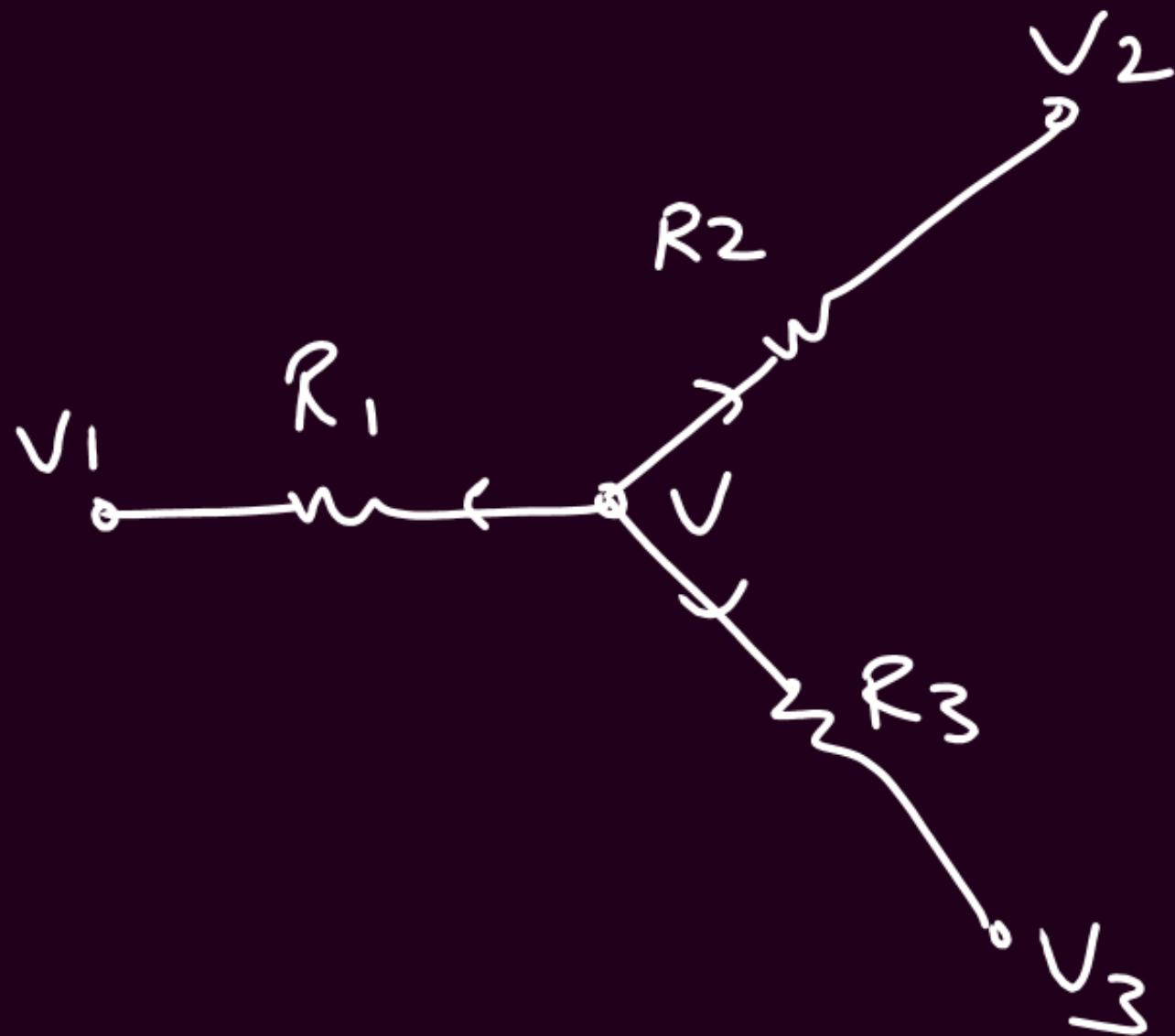
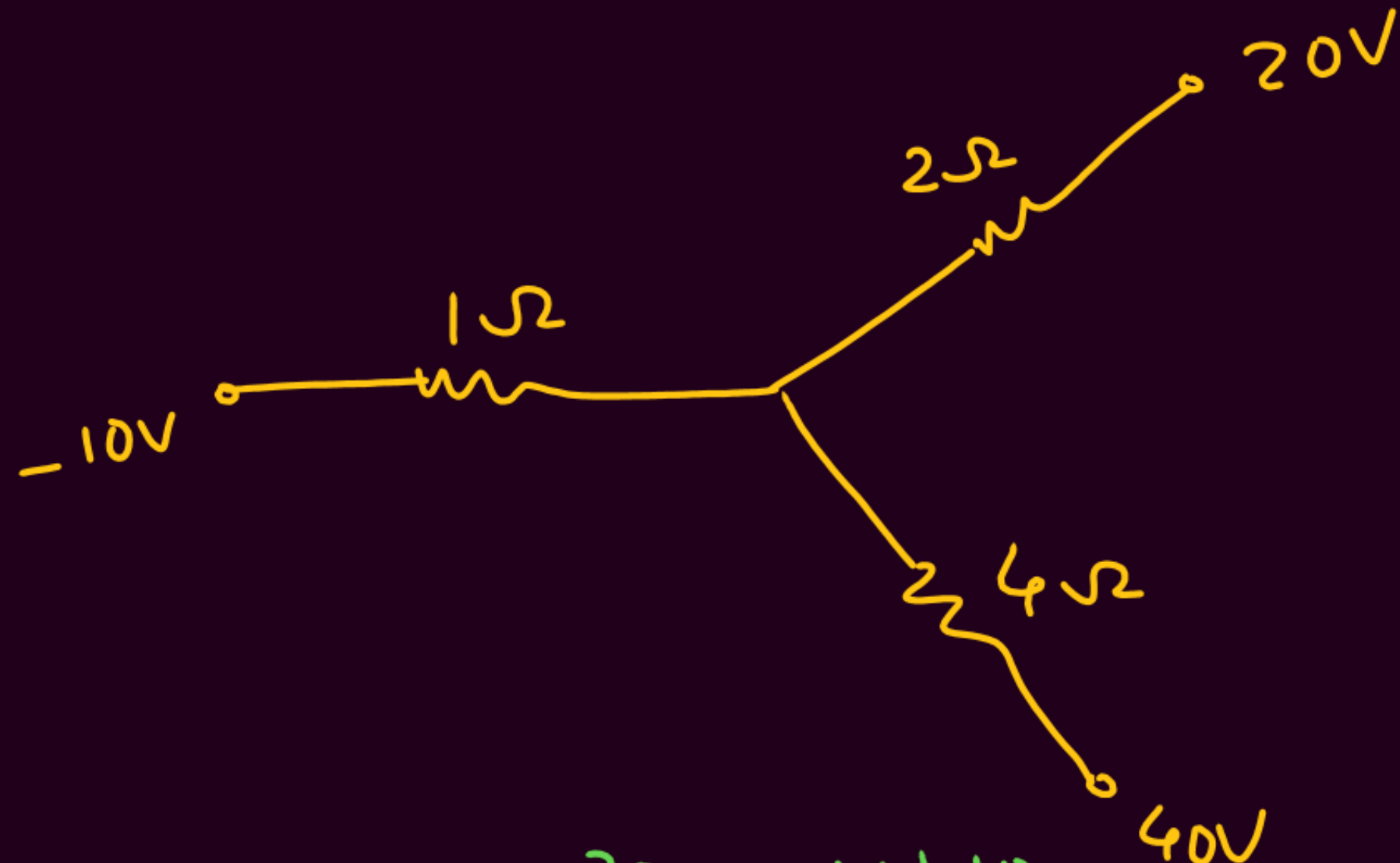
$$\frac{V-V_1}{R_1} + \frac{V-V_2}{R_2} + \frac{V-V_3}{R_3} = 0$$



$$\frac{V-40}{4} + \frac{V-20}{2} + \frac{V+10}{1} = 0$$


$$(V-40) + 2(V-20) + 4(V+10) = 0$$

$$7V = 40$$

$$\left[i_{4\Omega} = \frac{V-40}{4} = \frac{40/7 - 40}{4} = -\frac{60}{7} \text{ A} \right]$$


$$\boxed{V = \frac{40}{7} \text{ V}}$$

Kirchoff's Voltage Law (KVL) [Loop Law]

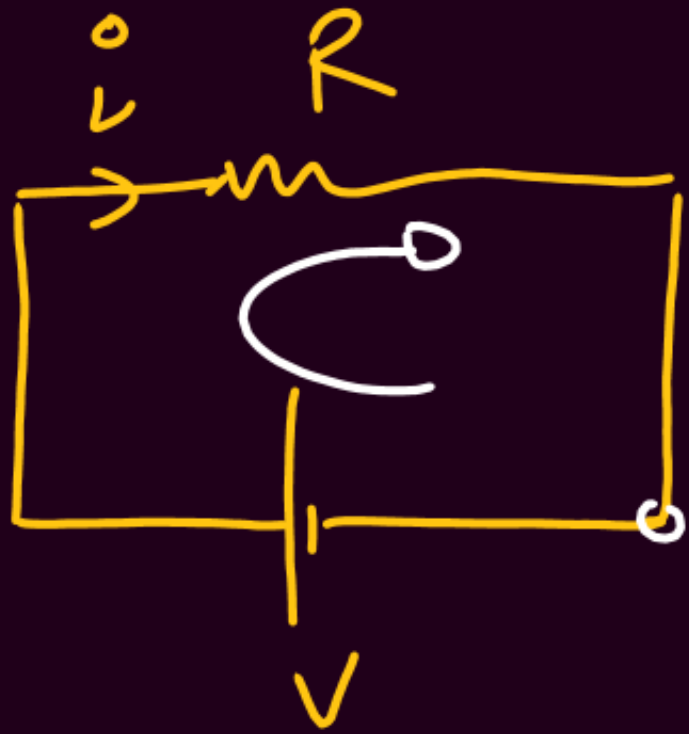

$$V - iR = 0$$

$$V = iR$$


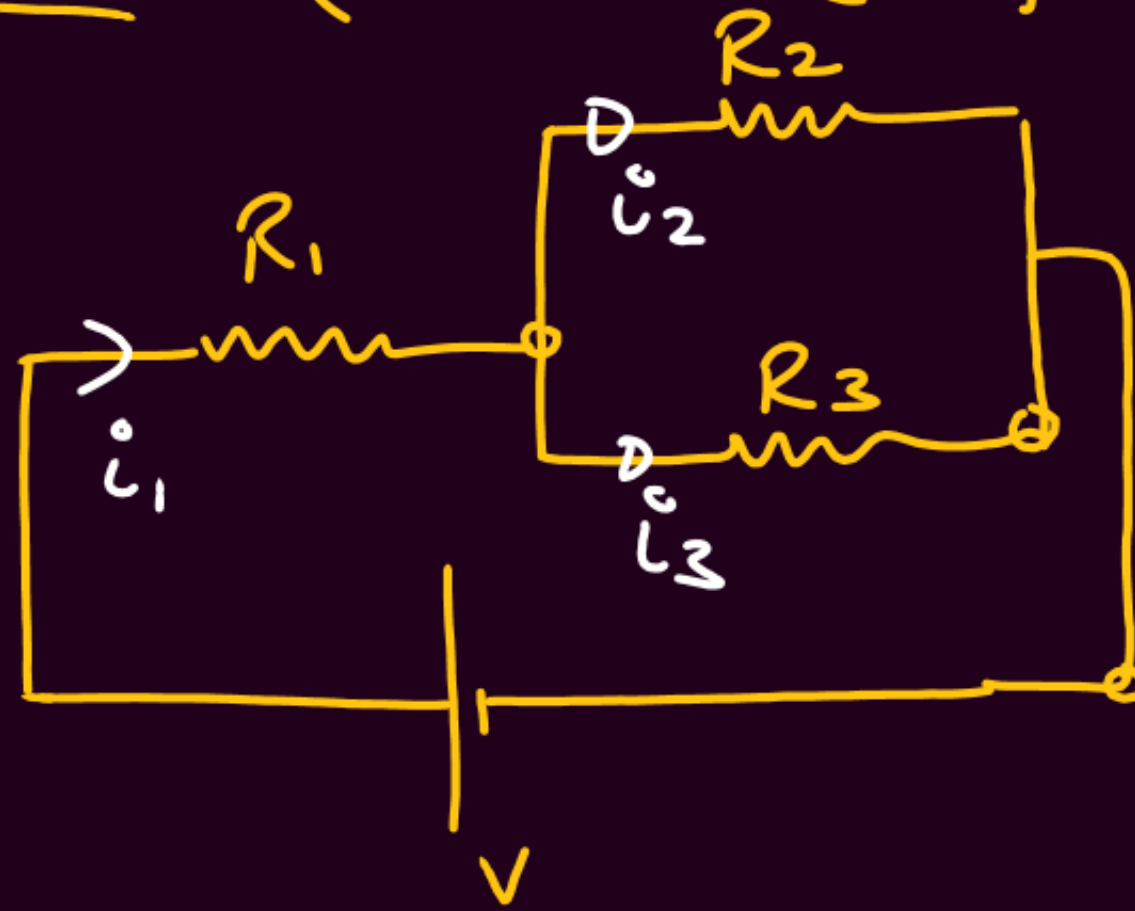


$$\text{KVL } \textcircled{1} \quad V - i_1 R_1 - i_2 R_2 = 0$$

$$\text{KVL } \textcircled{2} \quad i_3 R_3 - i_2 R_2 = 0$$

$$\text{KCL } \textcircled{3} \quad i_1 = i_2 + i_3$$

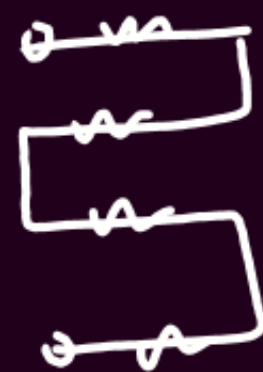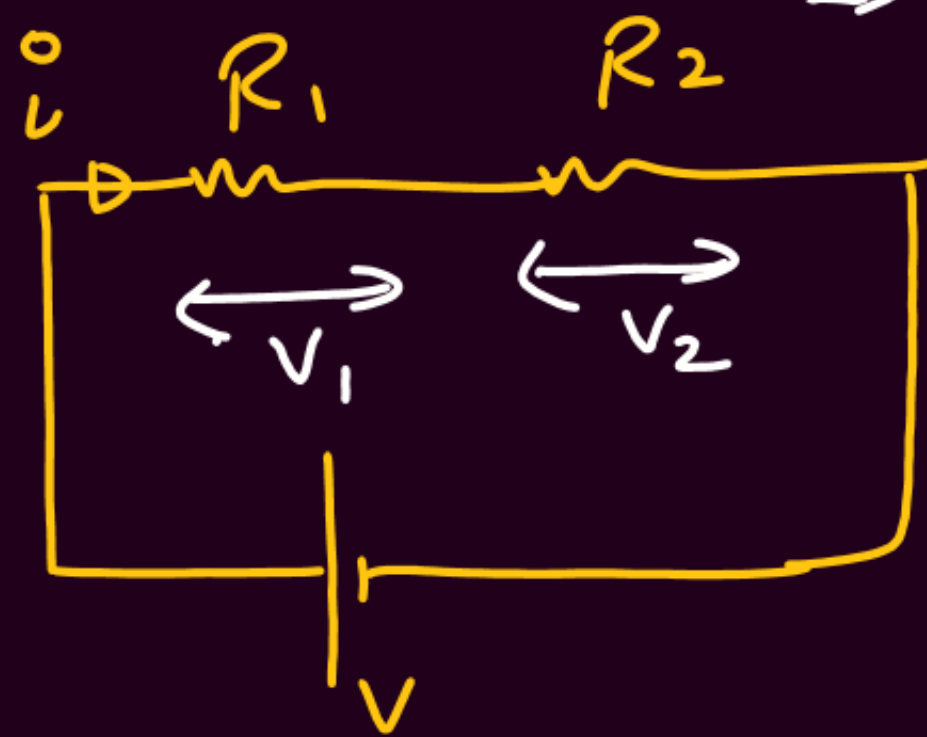Series Combination → Same Current
→ No Branching



$$R_{eq} > R_1$$

$$R_{eq} > R_2$$

$$\textcircled{1} R_{eq} = R_1 + R_2$$

$$\textcircled{2} n\text{-identical in series } \boxed{R_{eq} = nR}$$


$$\textcircled{3} V_1 = iR_1$$

$$V_1 = \frac{VR_1}{(R_1 + R_2)}$$

$$V_2 = \frac{VR_2}{R_1 + R_2}$$

Parallel Combination → Same P.D.

→ Betⁿ Same points

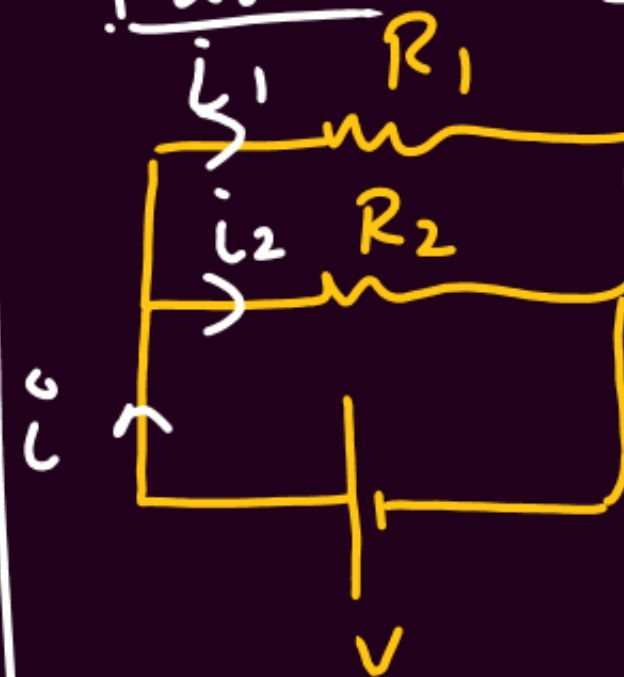

$$\textcircled{1} \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\boxed{R_{eq} = \frac{R_1 R_2}{R_1 + R_2}}$$

$$R_{eq} < R_1$$

$$R_{eq} < R_2$$

$\textcircled{2}$ n-identical in parallel


$$R_{eq} = \frac{R}{n}$$

$$\textcircled{3} i_1 R_1 = i_2 R_2$$


$$\boxed{i_1 = \frac{i R_2}{R_1 + R_2}}$$

$$i_2 = \frac{i R_1}{R_1 + R_2}$$


⑧

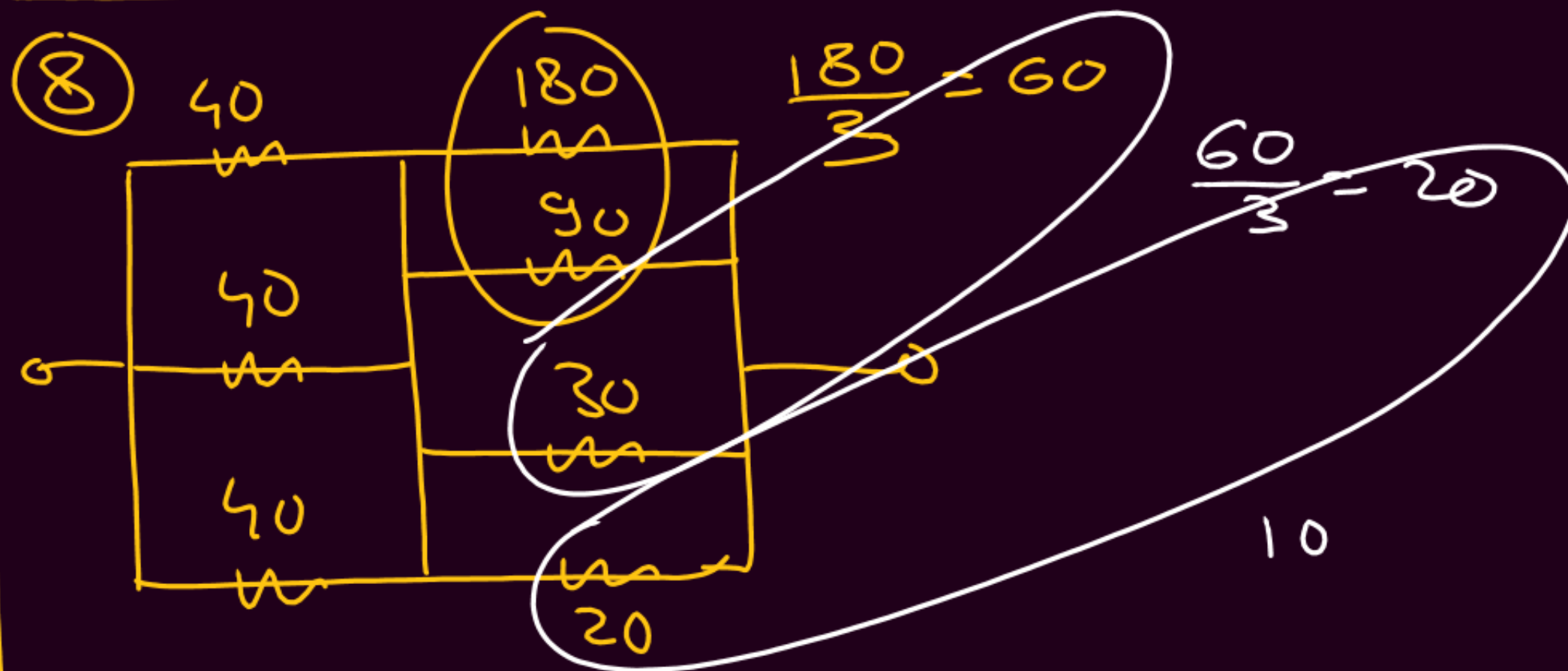
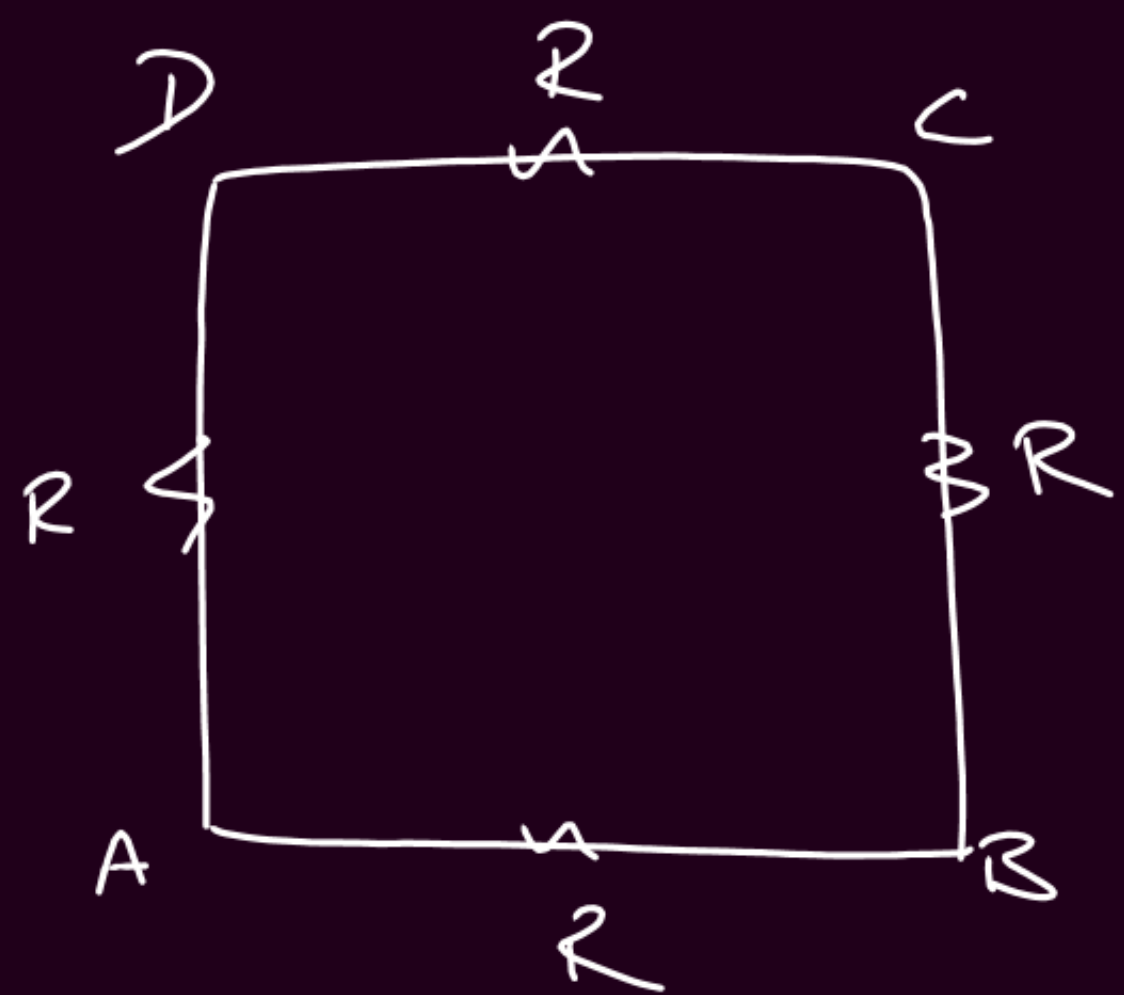
$$\frac{40}{3} + 10 = \frac{70}{3} \Omega$$



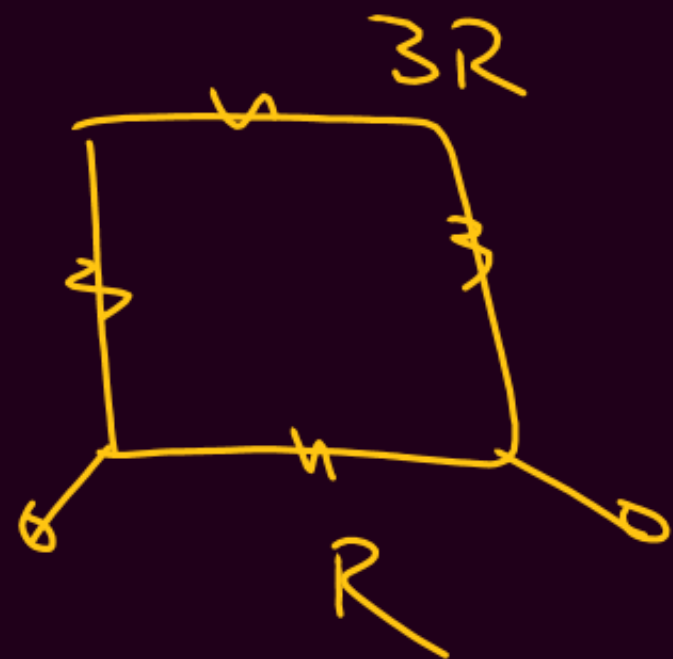
$$\frac{R_{AB}}{R_{AC}} = ? \quad \left(\frac{3}{4} \right)$$





$$R_{AB} = \frac{3R}{4}$$



$$R_{AC} = R$$

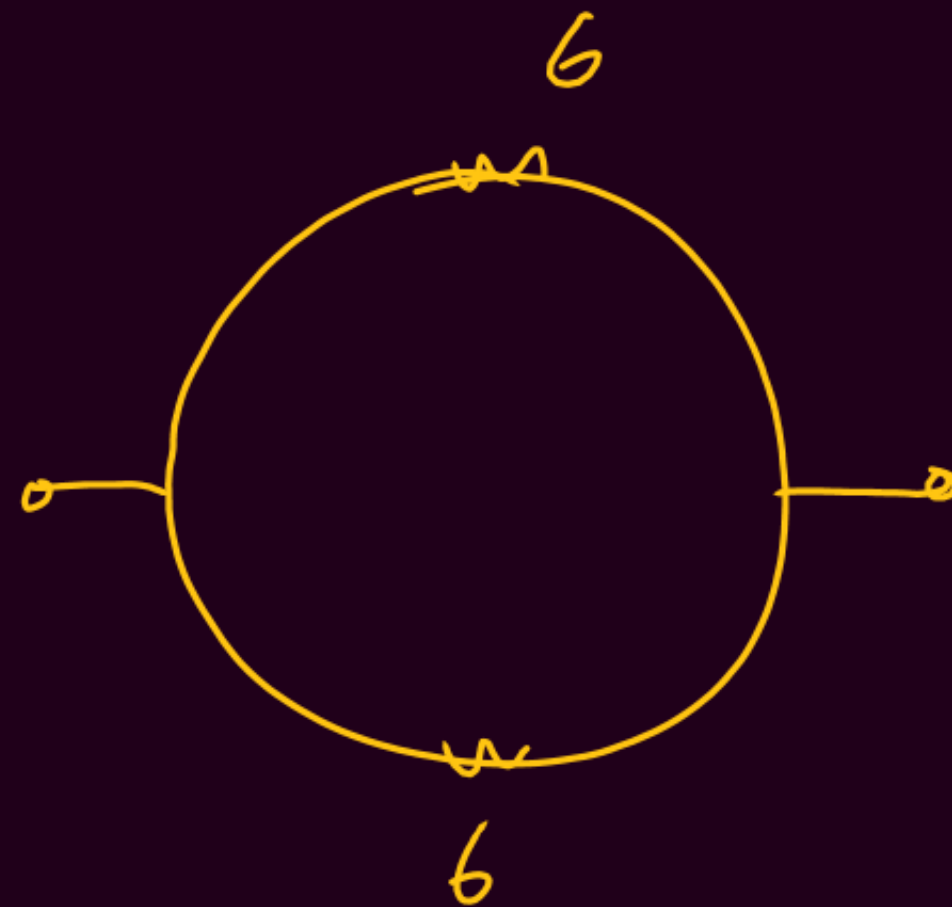

$$R_{eq} = 3\Omega$$

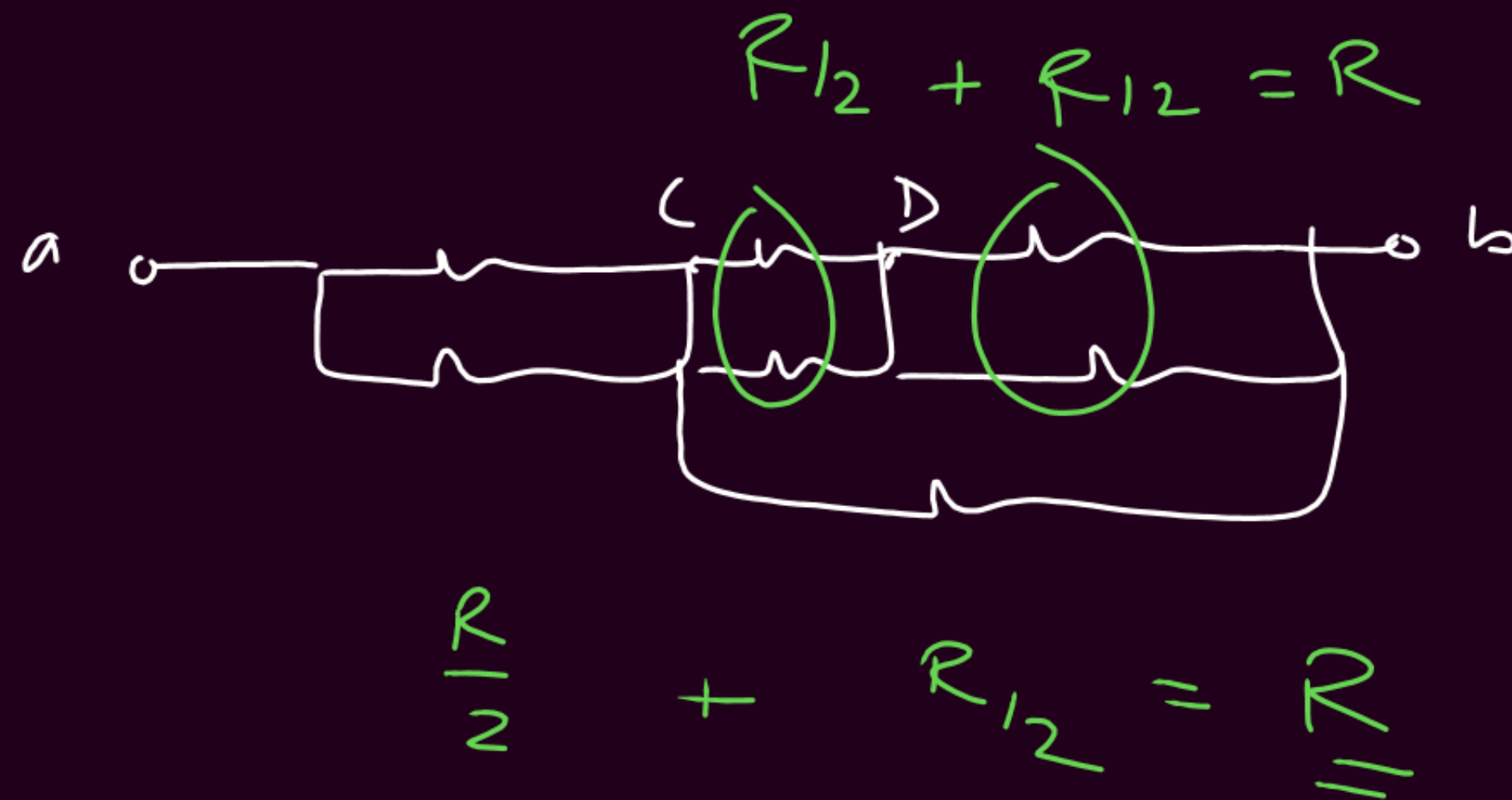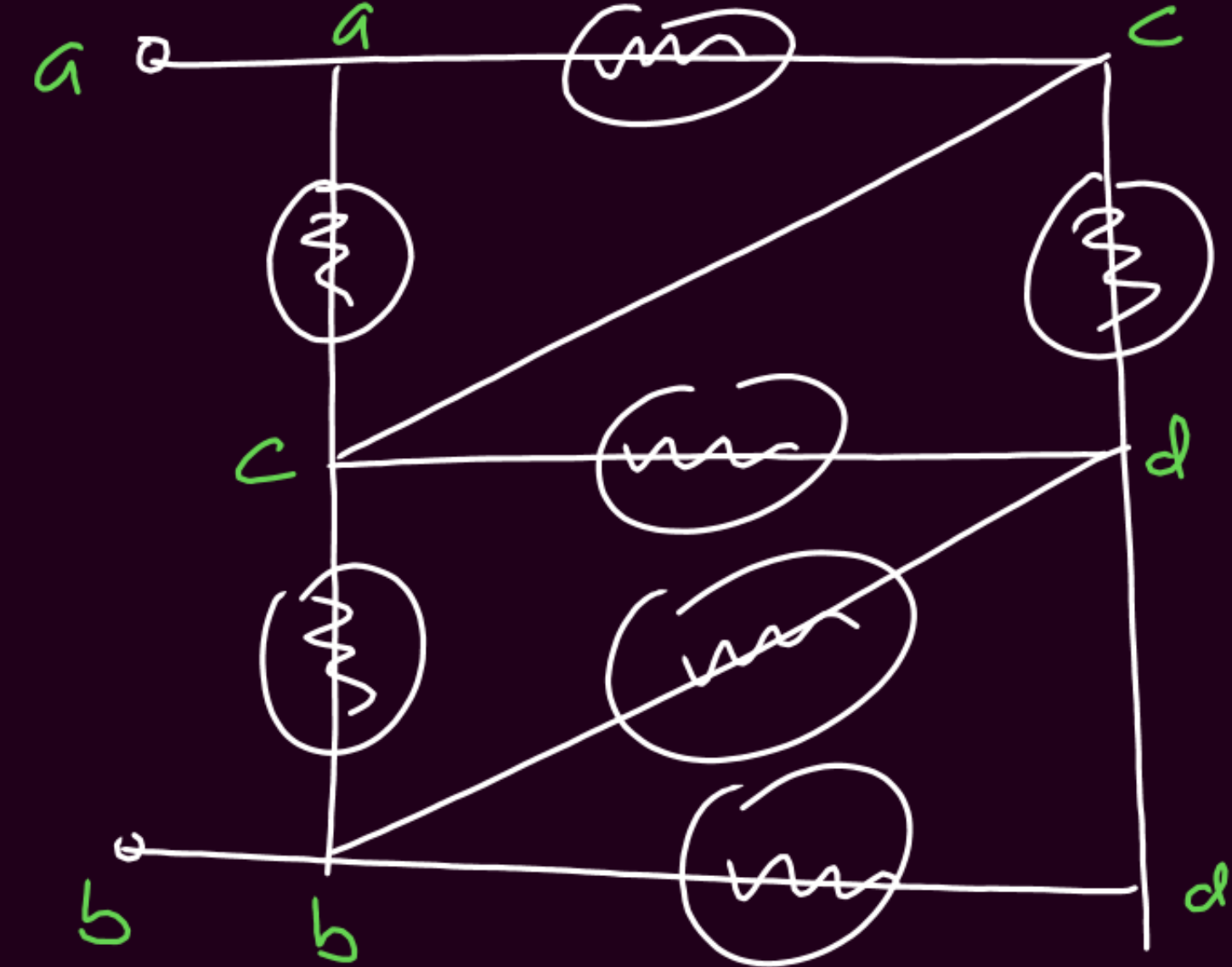

Wheatstone Bridge




Balance WSB if $i_g = 0$



$$\text{then } \frac{R_1}{R_2} = \frac{R_3}{R_4}$$



and vice versa

$$V_p = V_q$$


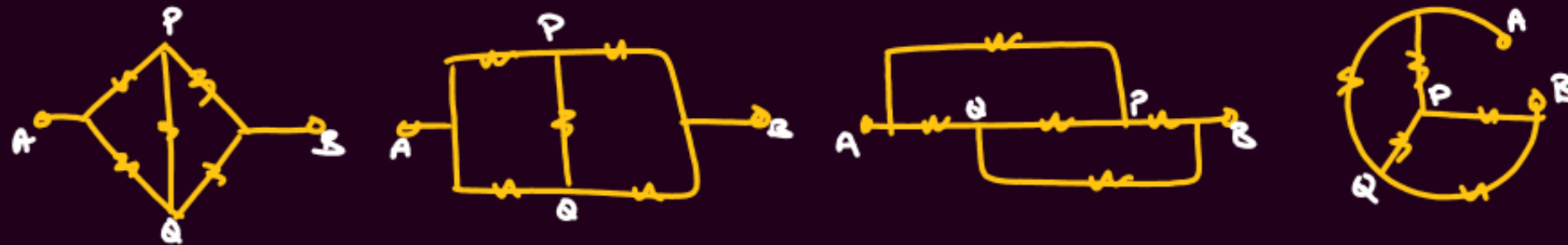


Extended WSB

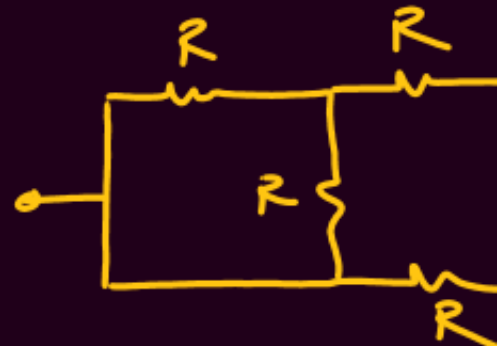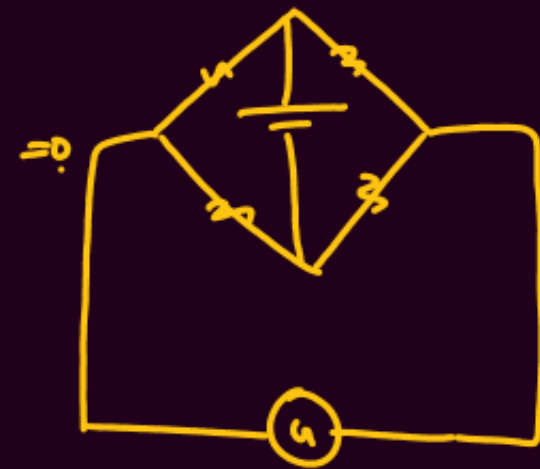

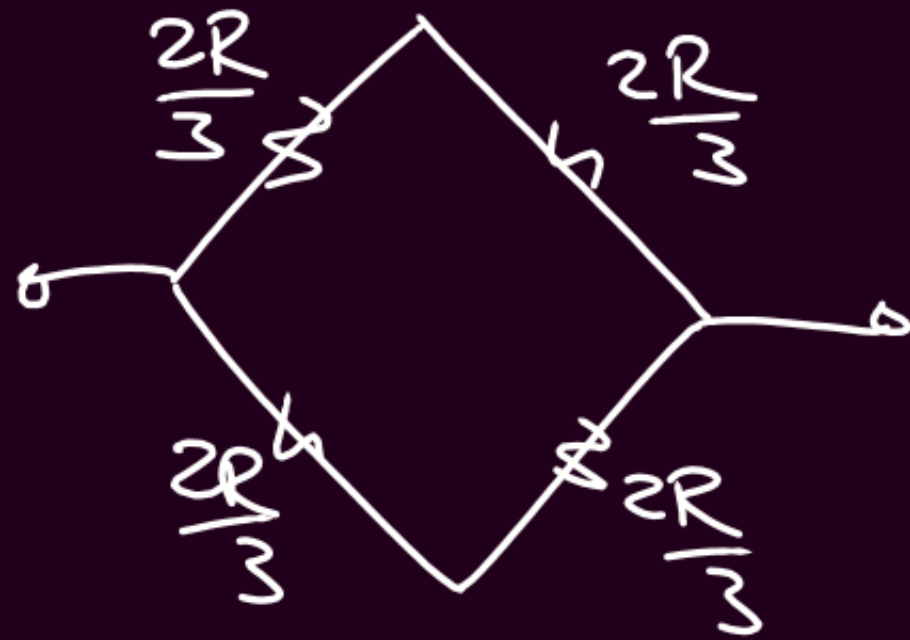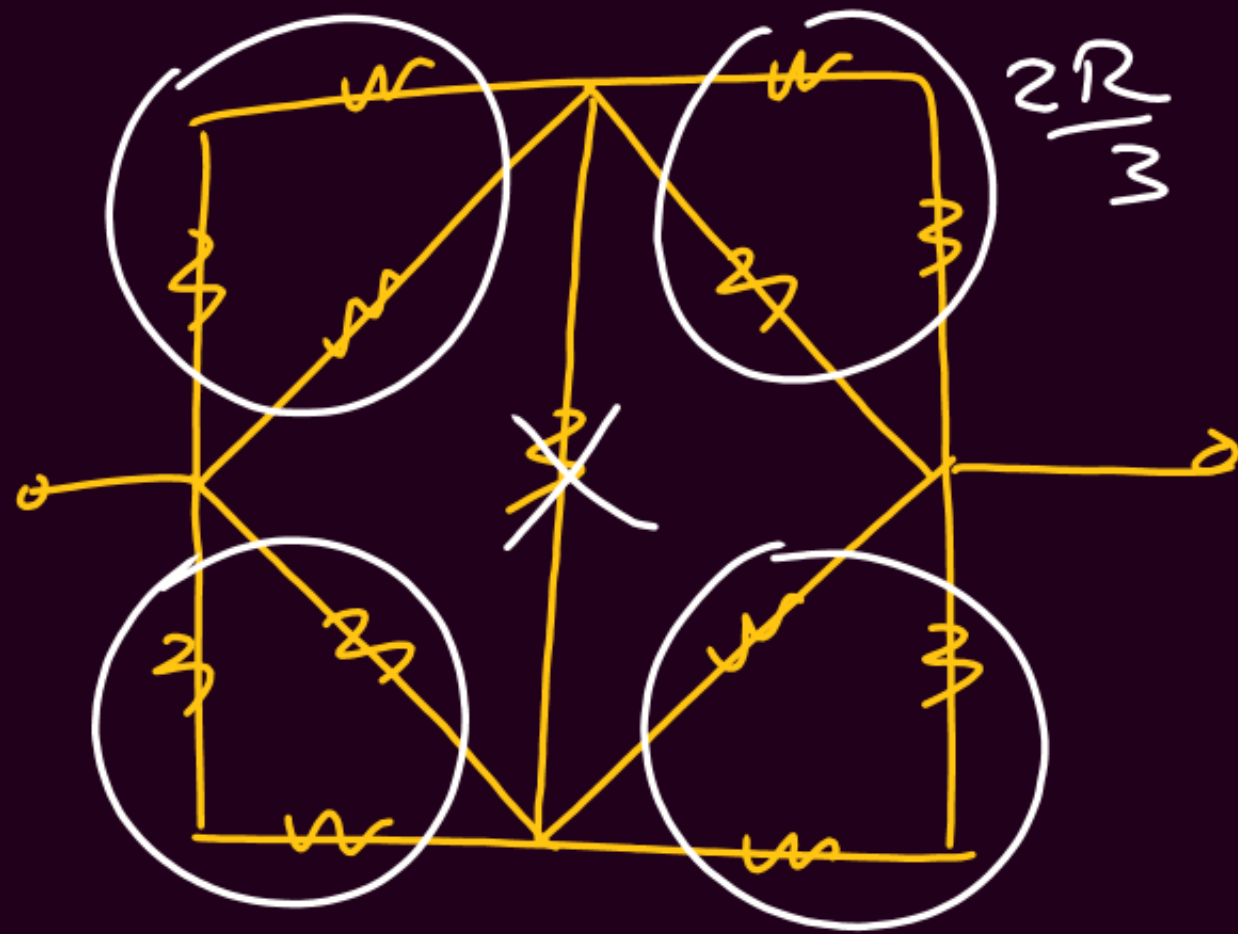

$$R_{eq} = \frac{2R}{3}$$

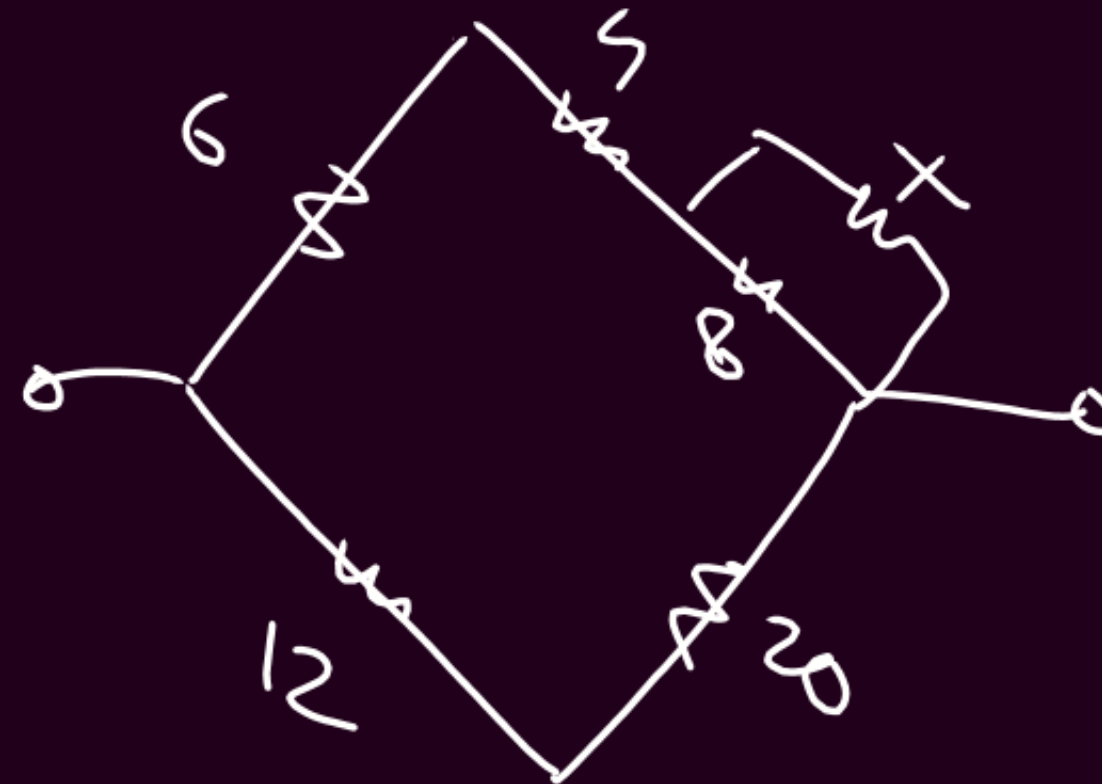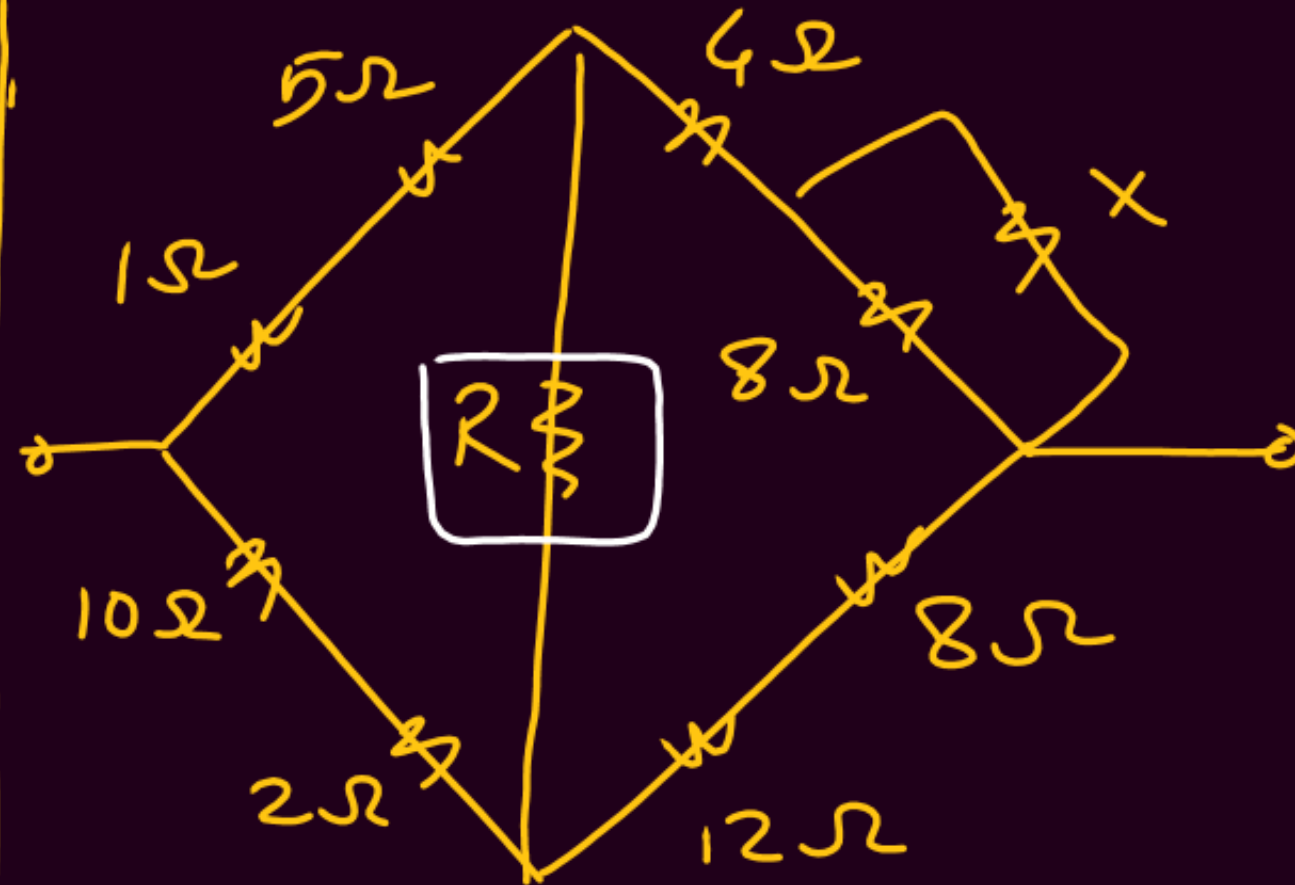





if current through R is '0' then find x ?

$$\frac{6}{12} = \frac{4 + \frac{8x}{8+x}}{20}$$

$$10 = 4 + \frac{8x}{8+x}$$

$$6 = \frac{8x}{8+x}$$

$$\boxed{x = 24 \Omega}$$

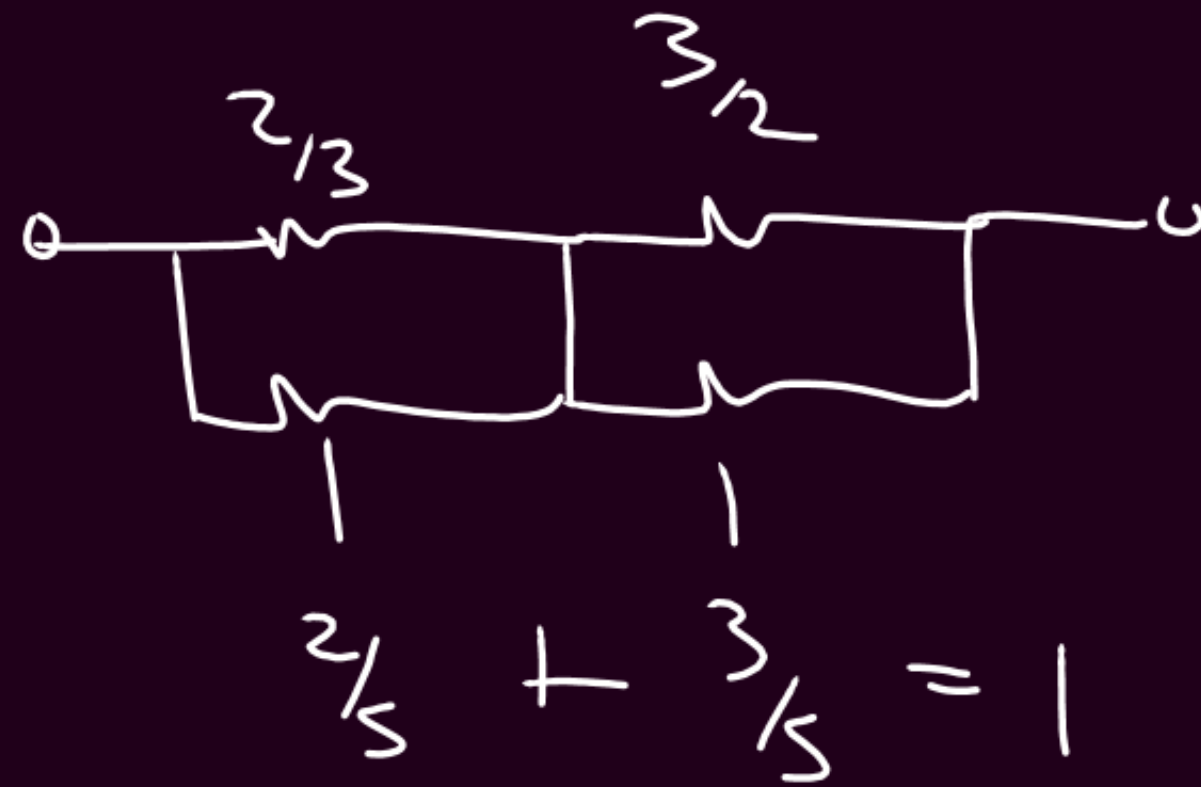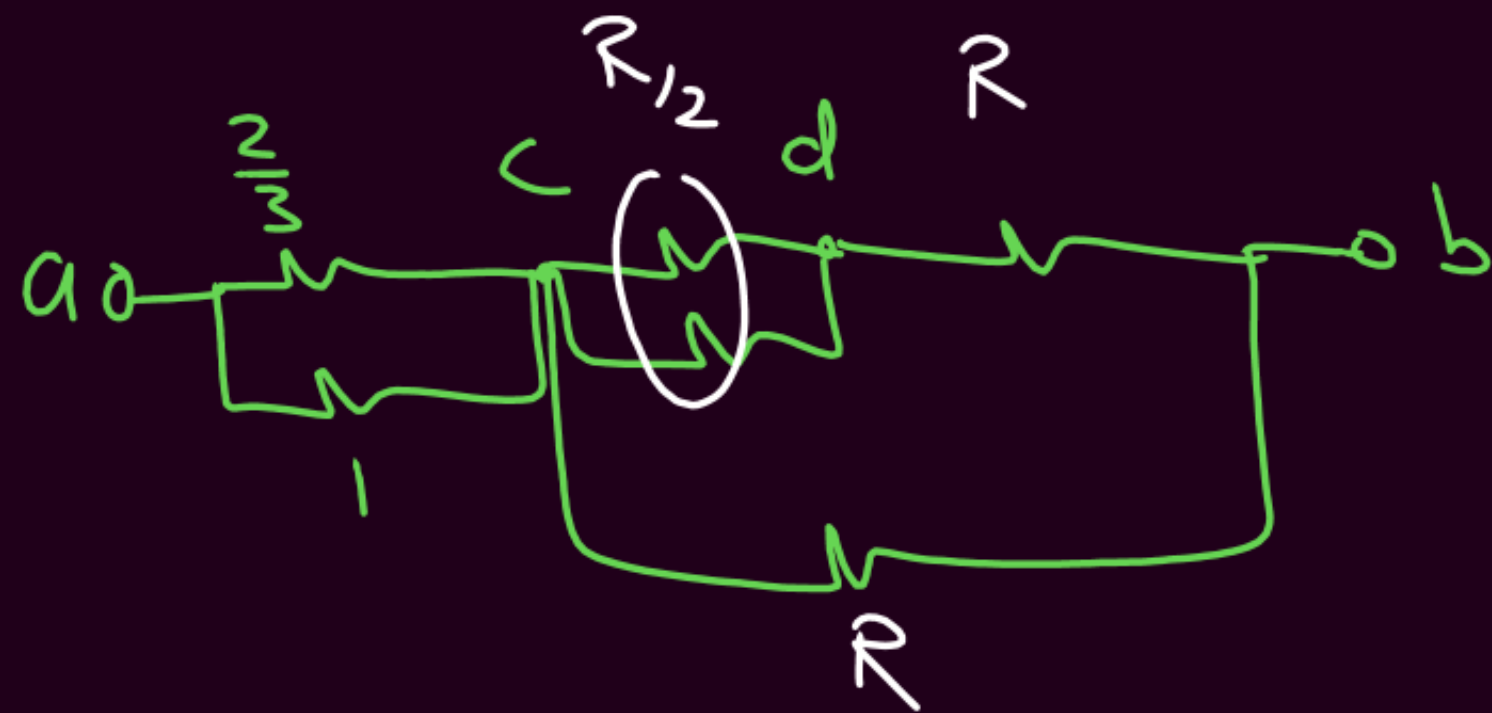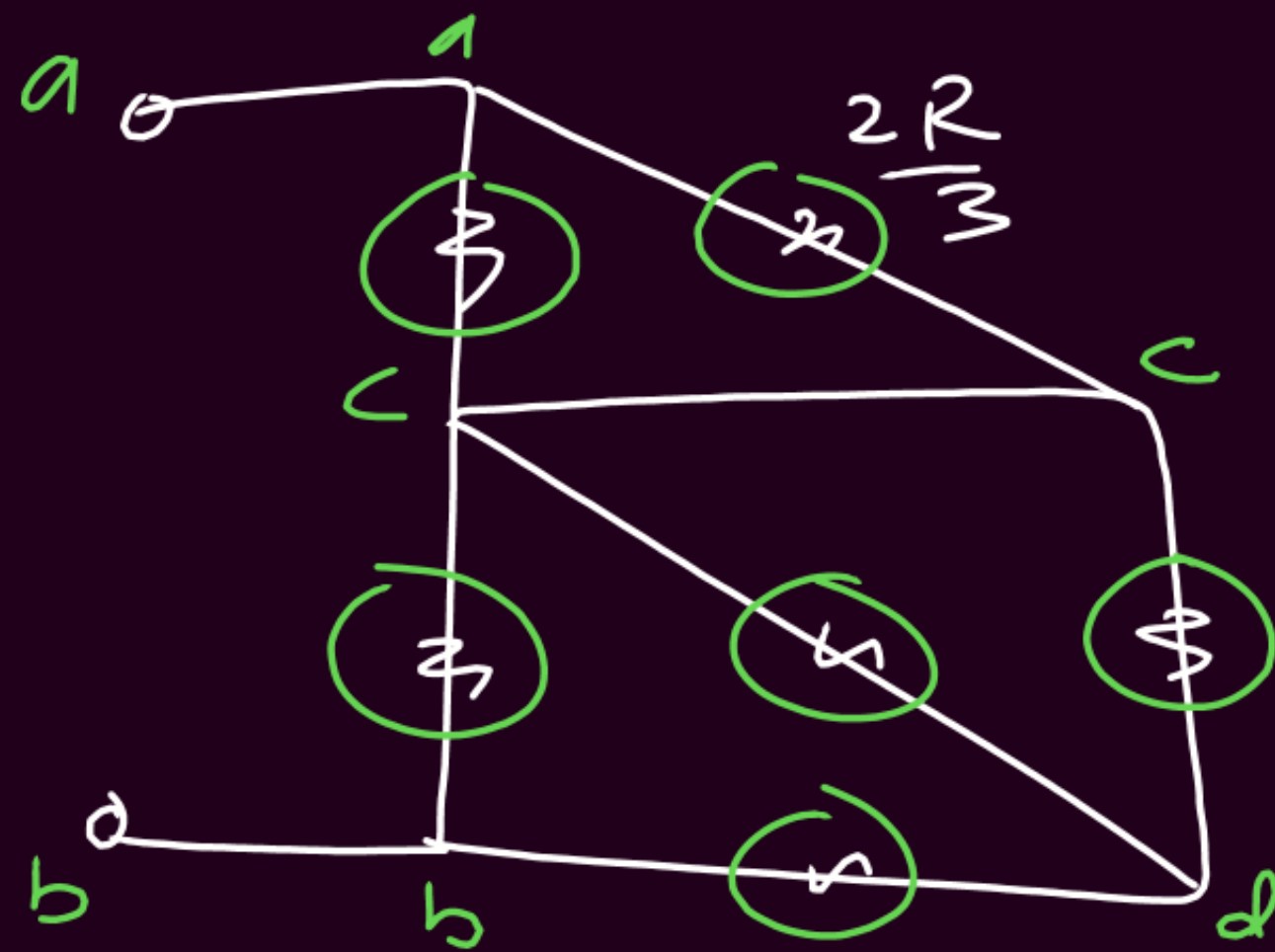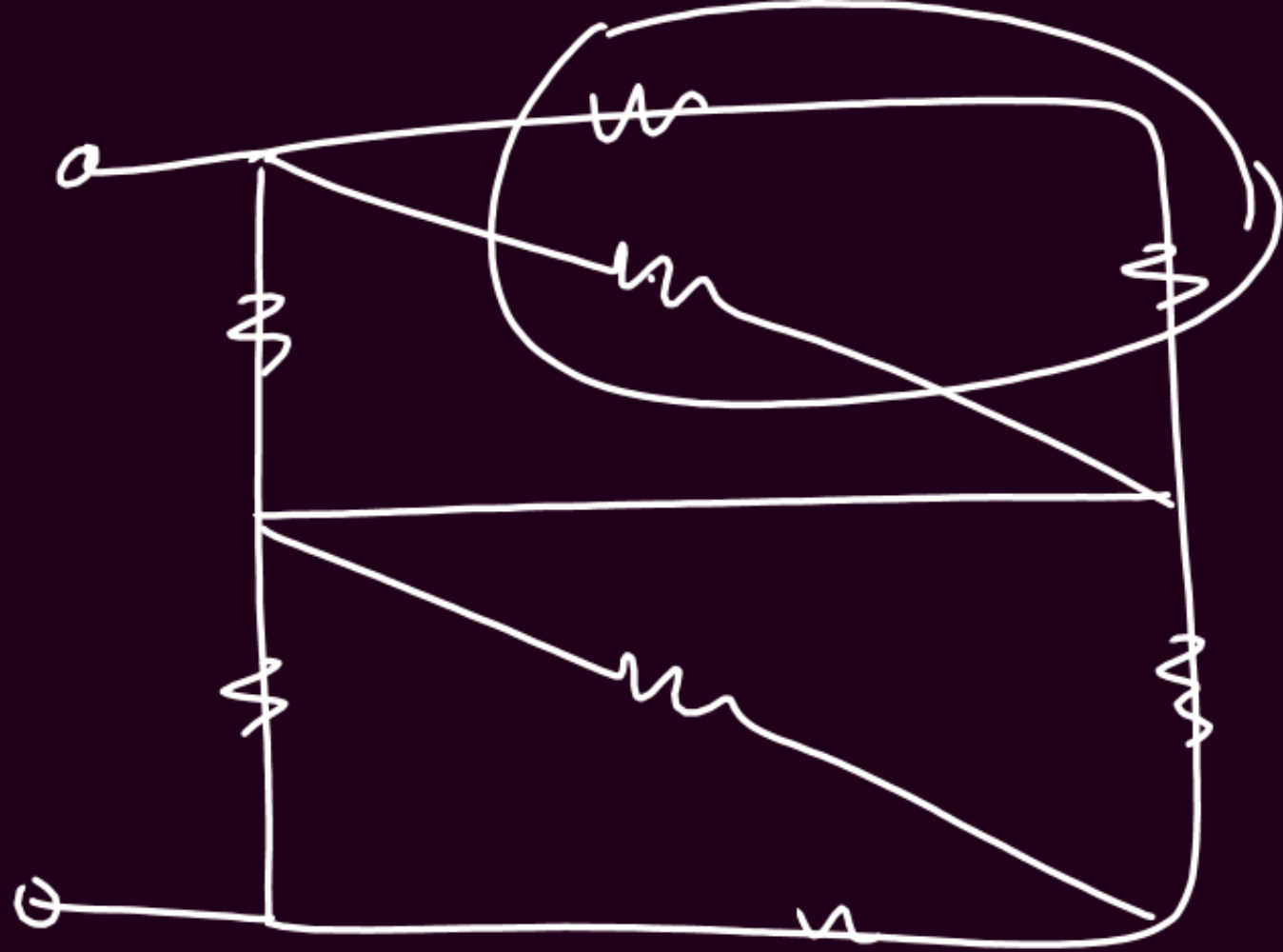

$$\frac{2}{5} + \frac{3}{5} = 1$$

Q. Left gap = 20 Ω
Balancing $\Rightarrow$ 40cm

$$\underline{\underline{x = ?}}$$

$$\frac{20}{40} = \frac{x}{60}$$

$$\boxed{x = 30\Omega}$$

Q $\frac{x}{20} = \frac{R}{80}$

$$\frac{x+10}{30} = \frac{R}{70}$$

$$\frac{x}{\cancel{20}} \cdot \frac{\cancel{30}}{x+10} = \frac{\cancel{R}}{\cancel{80} \cdot \frac{70}{\cancel{R}}}$$

$$\frac{3x}{x+10} = \frac{7}{4}$$

$$12x = 7x + 70$$

$$5x = 70$$

$$\boxed{x = 14\Omega}$$

extra



$$2 < R_{eq} < 3$$



$$\frac{X(1)}{X+1} + 2 = X$$

$$X = (X-2)(X+1)$$

$$X = X^2 + X - 2X - 2$$

$$X^2 - 2X - 2 = 0$$

$$ax^2 + bx + c = 0$$

$$X = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$


$$X = \frac{-(-2) \pm \sqrt{4 - 4(1)(-2)}}{2(1)}$$

$$X = \frac{2 \pm \sqrt{12}}{2} = \frac{2 \pm 2\sqrt{3}}{2}$$


$$X = (1 \pm \sqrt{3})$$

$$R_{eq} = (1 + \sqrt{3})$$


$$R_1 + R_2 = X$$

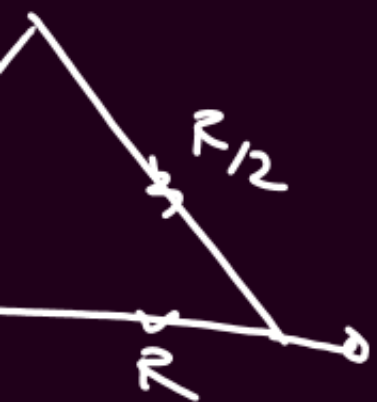

VPS $\rightarrow$ Current Division

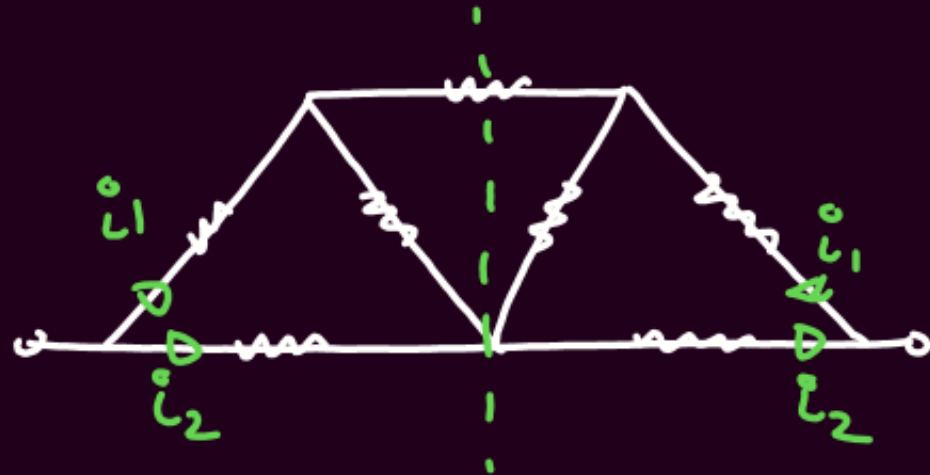



Cube

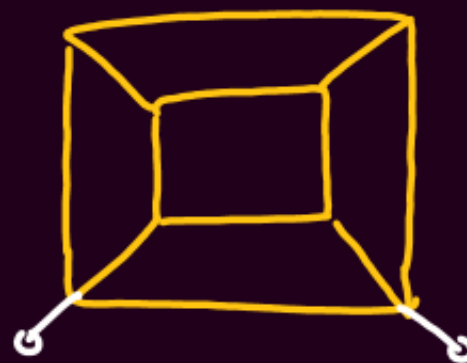

Edge

$$\frac{7R}{12}$$

$$\frac{12C}{7}$$

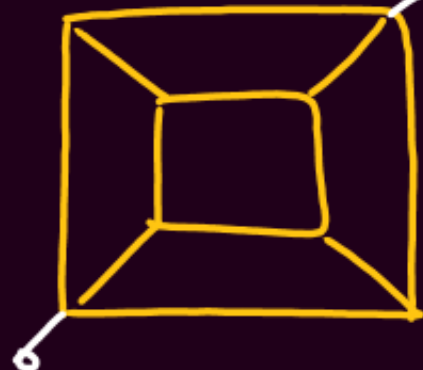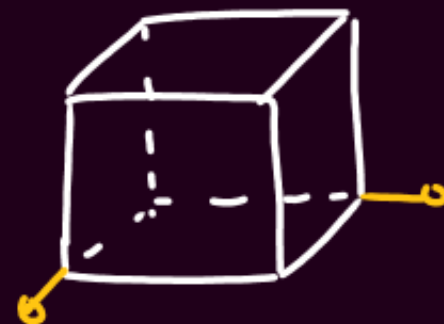

Face diagonal

$$\frac{3R}{4}$$


$$\frac{4C}{3}$$



Body diagonal


$$\frac{5R}{6}$$

$$\frac{6C}{5}$$

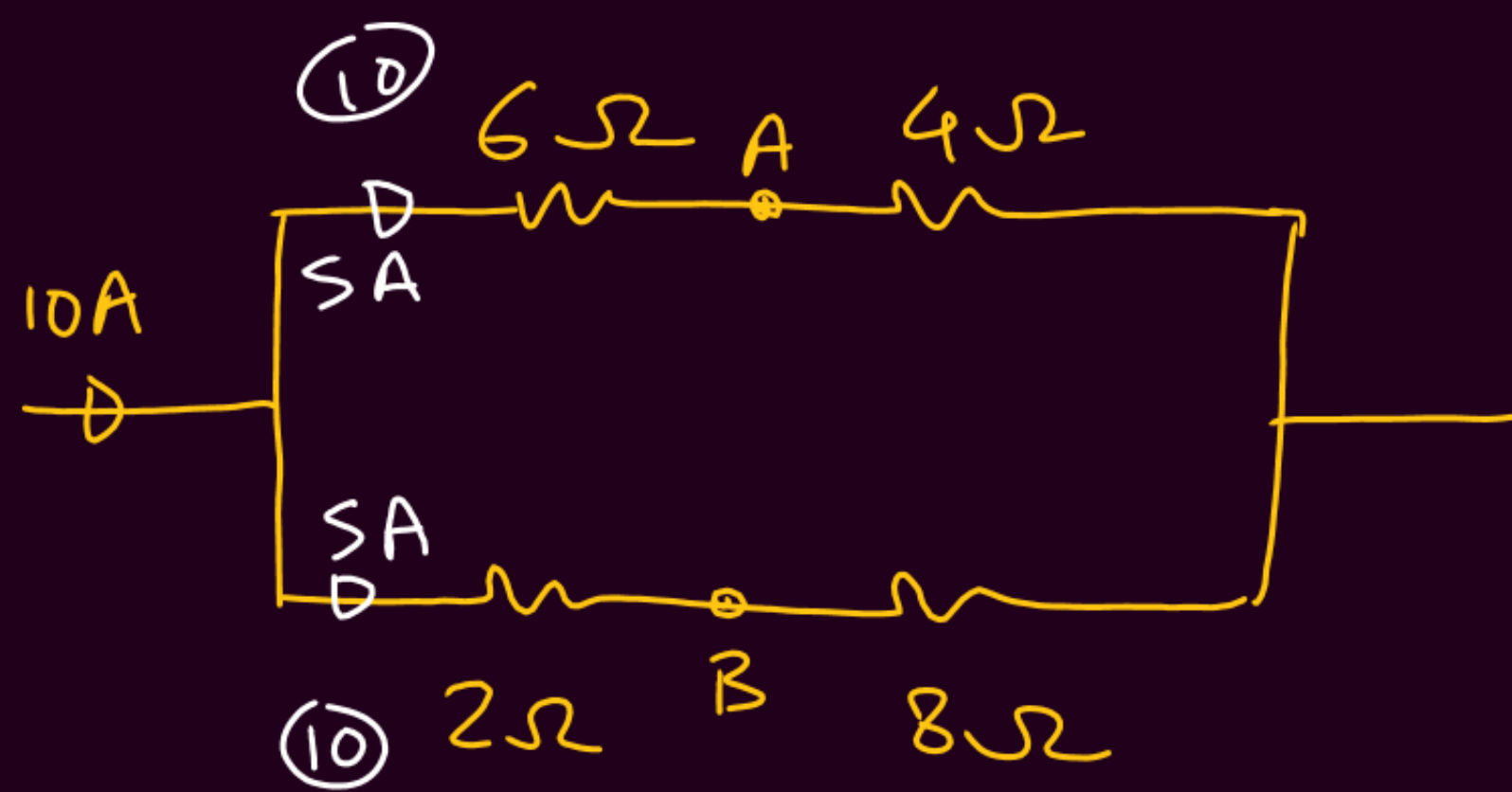


$$V_{AB} = + (5)(2) - (5)(6)$$

$$= -20V$$

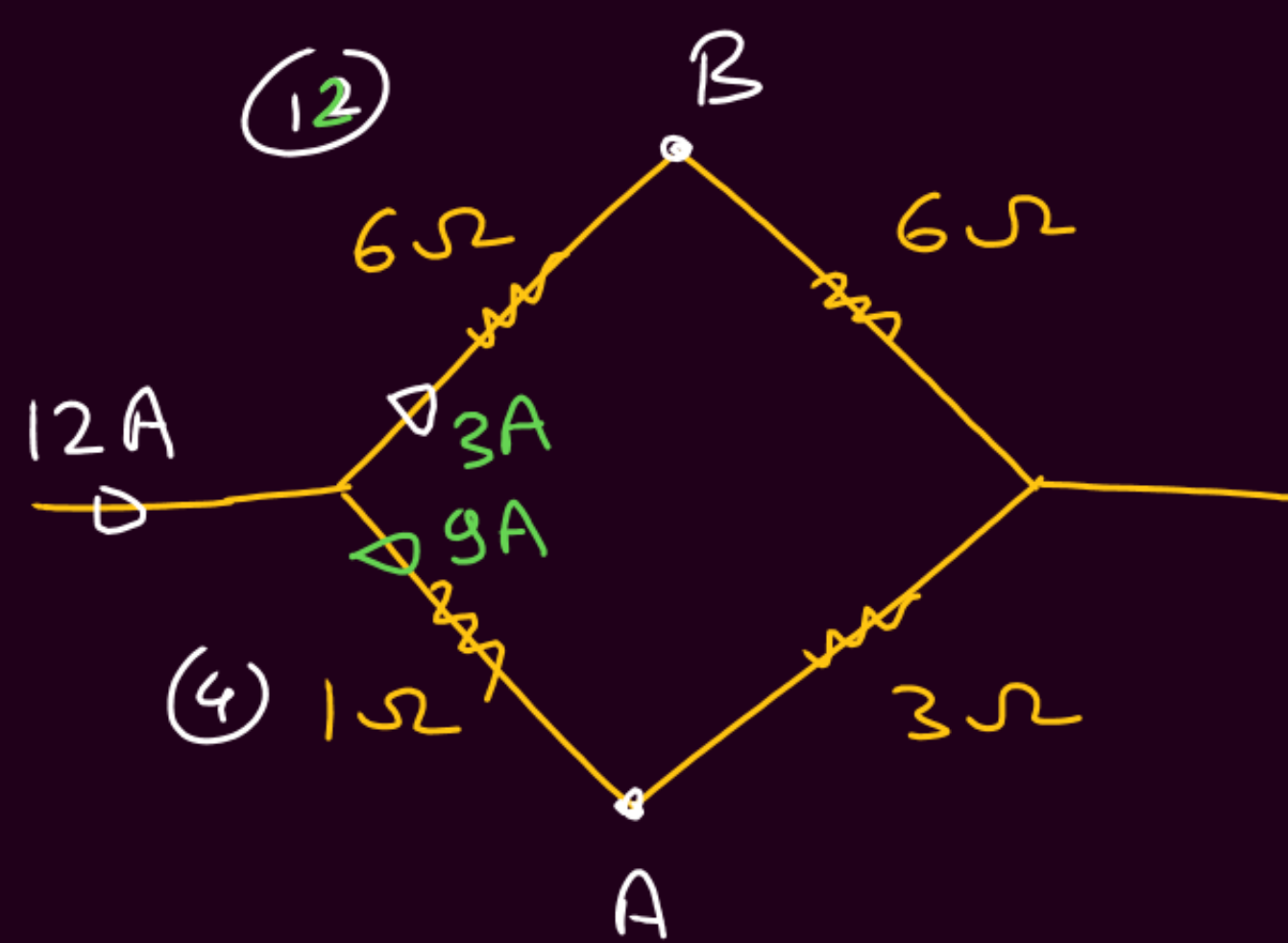

$$\frac{(12) \times 4}{12 + 4} = 3A$$
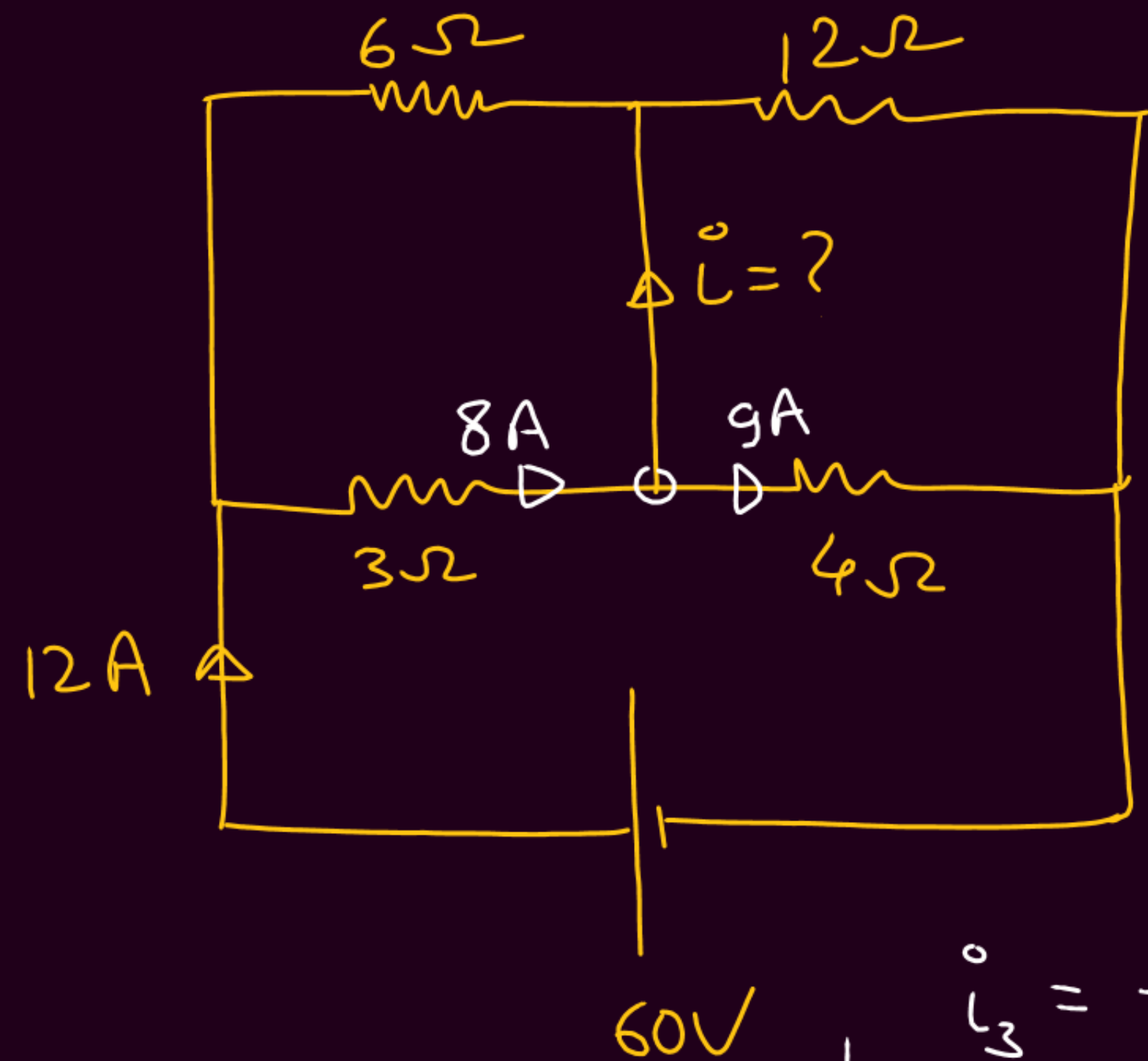
$$V_{AB} = (3)(6) - (9)(1) = \underline{\underline{9V}}$$



$$8 = 9 + i^\circ$$


$$i^\circ = -1A$$

$$R_{eq} = 5\Omega$$

$$i^\circ = \frac{60}{5} = 12A$$


$$i_3^\circ = \frac{12 \times 6}{3 + 6} = 8A$$
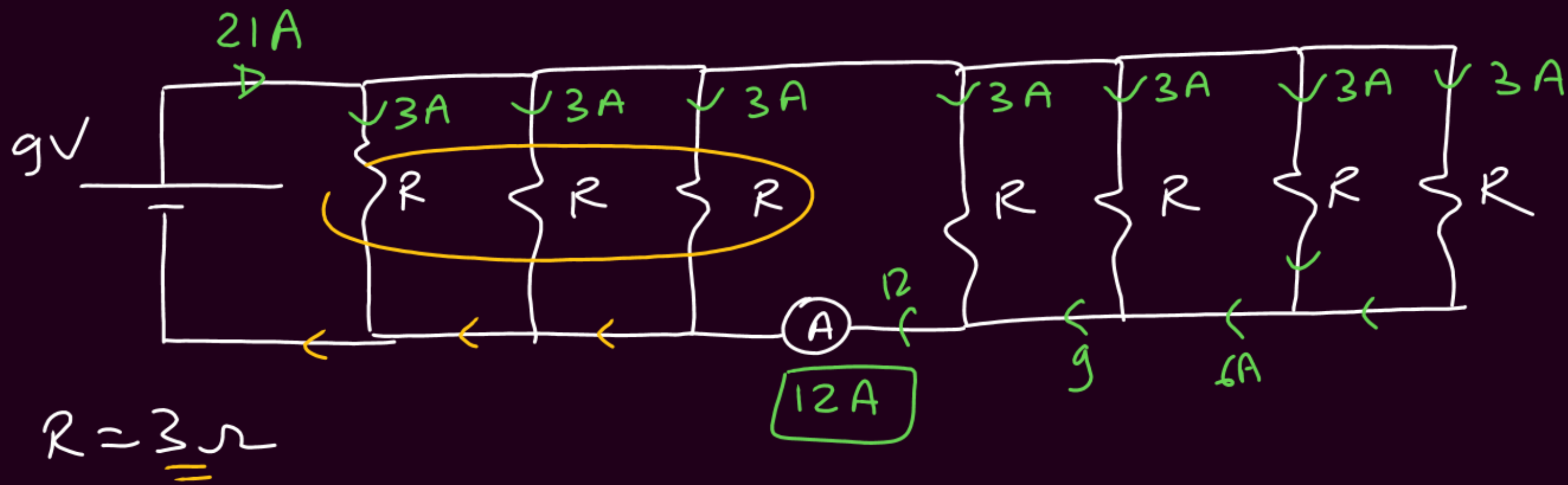
$$i_4^\circ = \frac{12 \times 12}{4 + 12} = 9A$$



Graphs

①

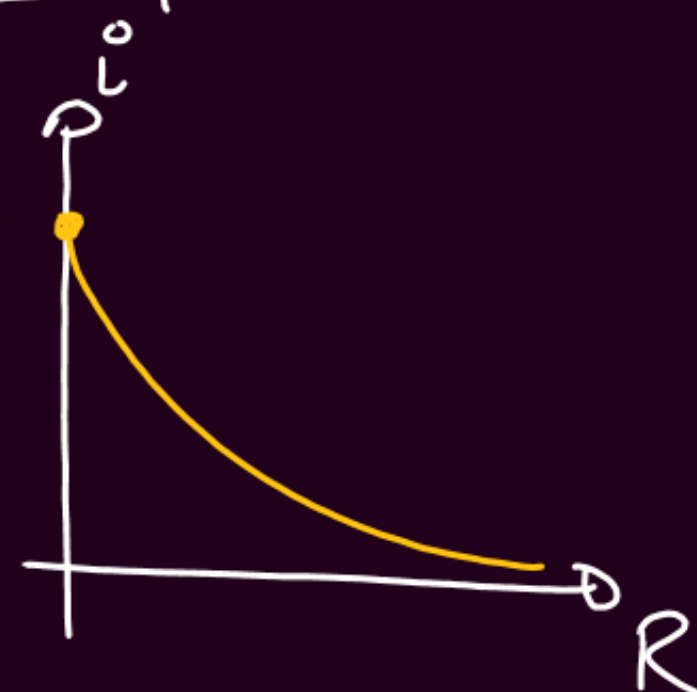


$$R=0 \quad i = \frac{E}{r}$$

$$R \rightarrow \infty \quad i \rightarrow 0$$

$$i = \frac{E}{R+r}$$

②

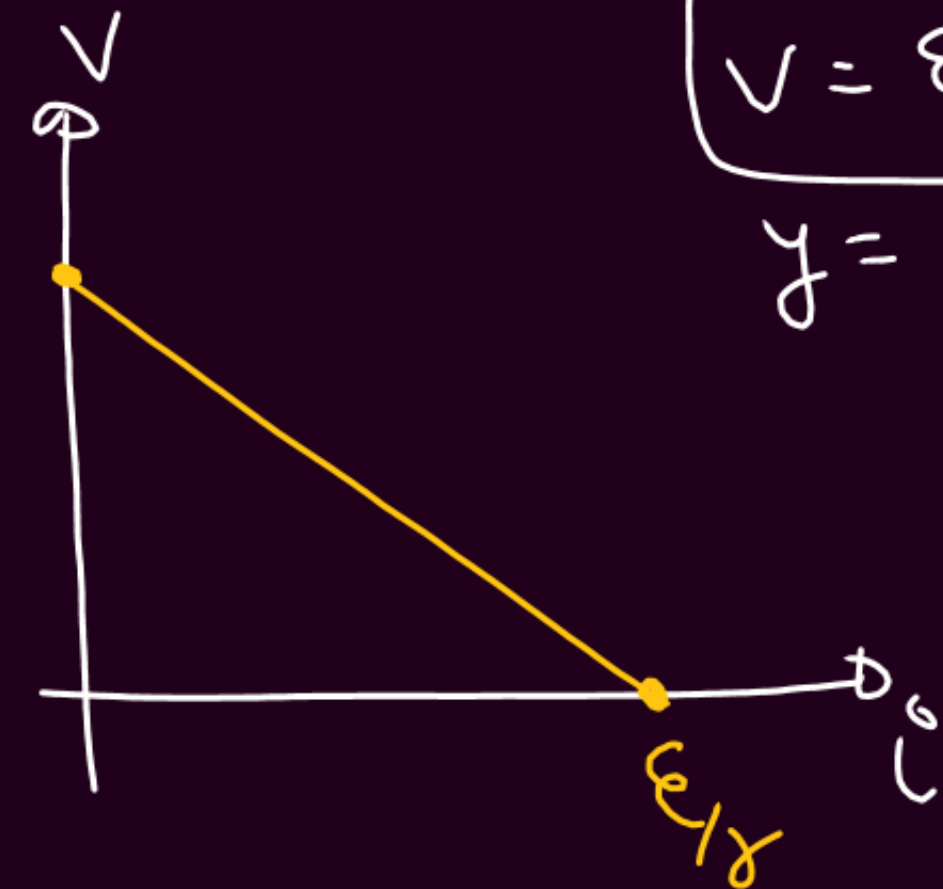


$$V = E - ir$$

$$y = c + xm$$

$$i=0 \quad V=E$$

$$i = \frac{E}{r} \quad V=0$$

$$\text{slope} = -r$$

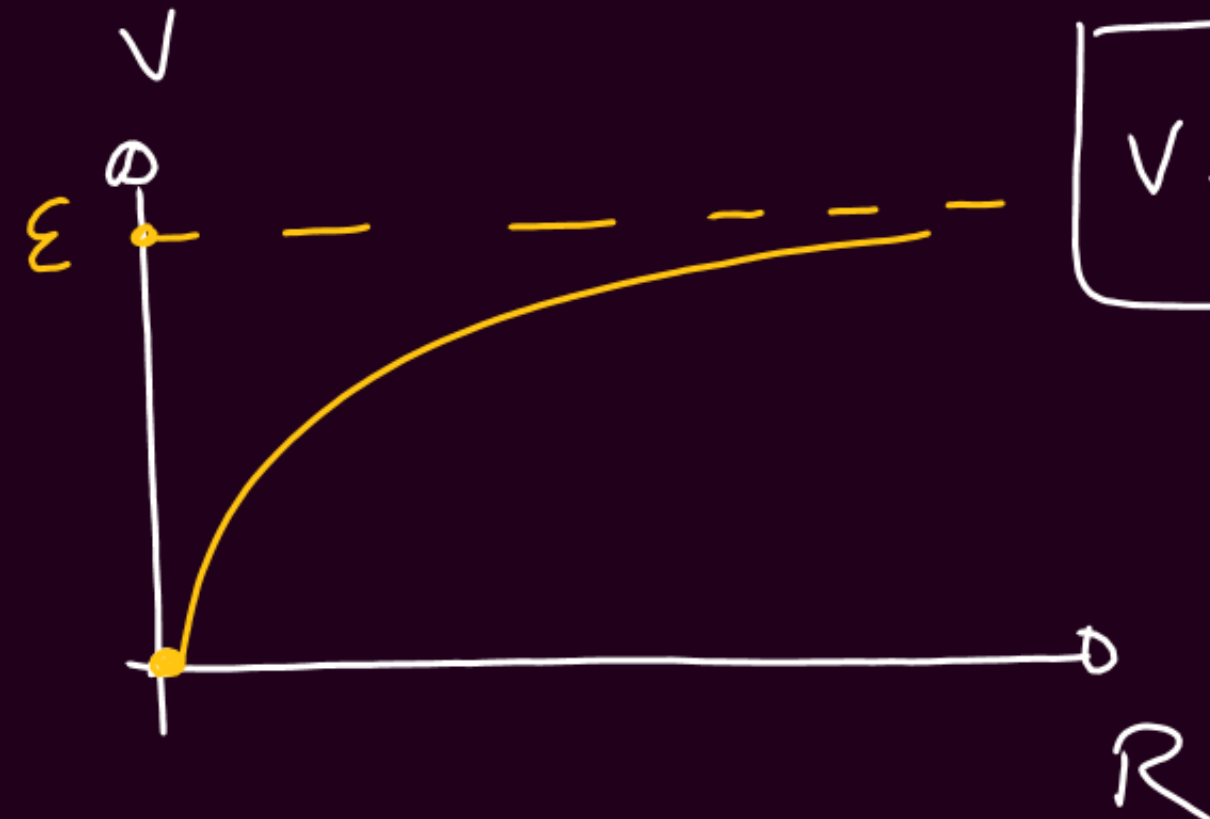

$$V = \frac{ER}{R+r}$$

$$R=0, \quad V=0$$

$$R \rightarrow \infty, \quad V=E$$

Q. $(10V, 2\Omega)$

$R = 3\Omega$

① $i = \frac{\mathcal{E}}{R+r} = \frac{10}{3+2} = 2A$

② $V_{\text{cell}} = \mathcal{E} - ir = 10 - 2 \times 2 = \underline{6V}$
 $= iR = 2 \times 3 = \underline{6V}$

Q. $1\Omega \rightarrow 3A$

$3\Omega \Rightarrow 2A$

$5\Omega \Rightarrow i = ?$

$i = \frac{\mathcal{E}}{R+r}$

$3 = \frac{\mathcal{E}}{1+r} \quad \left\{ \begin{array}{l} \mathcal{E} = 3 + 3r = 6 + 2r \\ \boxed{r = 3\Omega} \end{array} \right.$


$2 = \frac{\mathcal{E}}{3+r} \quad \left\{ \begin{array}{l} \mathcal{E} = 3 + 3(3) = \underline{12V} \end{array} \right.$

$i = \frac{\mathcal{E}}{5+r} = \frac{12}{5+3} = \frac{12}{8} = \underline{1.5A}$

Q.




O.C. $V = \mathcal{E} = 10V$

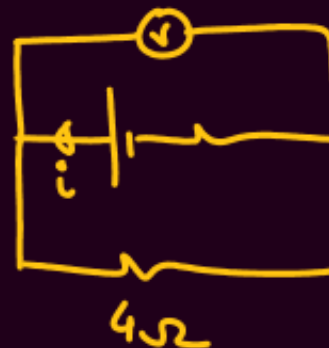

$V = \mathcal{E} - ir = 8V$

$\boxed{r = R \left(\frac{\mathcal{E}}{V} - 1 \right)} = 4 \left(\frac{10}{8} - 1 \right) = 1\Omega$

$$(2) + 4 - 10 + i(1) = 0$$

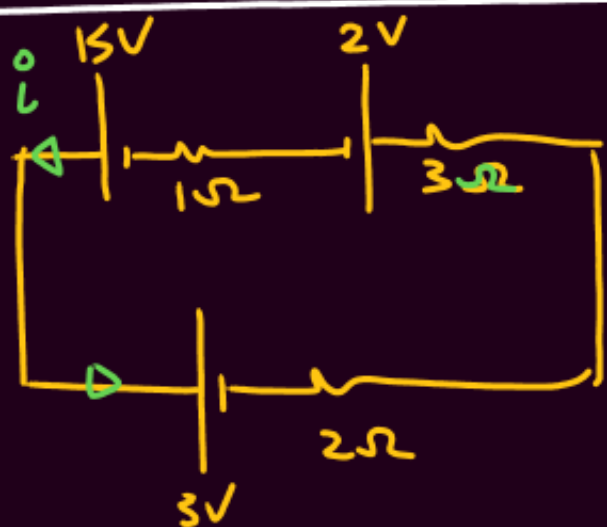

$$= \frac{15 - 2 - 3}{1 + 3 + 2} = \frac{10}{6} = \frac{5}{3} \text{ A}$$

Parallel Combination (Extra)



$$\mathcal{E}_q = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2}$$

$$r_q = \frac{r_1 r_2}{r_1 + r_2}$$



n -identical cells
in parallel

$$\textcircled{1} \mathcal{E}_q = \mathcal{E}$$

$$\textcircled{2} r_q = \frac{r}{n}$$

Series

$$\mathcal{E}_q = n\mathcal{E}$$

$$r_q = nr$$

Mixed Grouping

Extra


$$\textcircled{1} N = mn$$

$\textcircled{2}$ m cells in a row
 n such rows

$$\textcircled{3} \mathcal{E}_q = m\mathcal{E}$$

$$\textcircled{4} r_q = \frac{mr}{n}$$
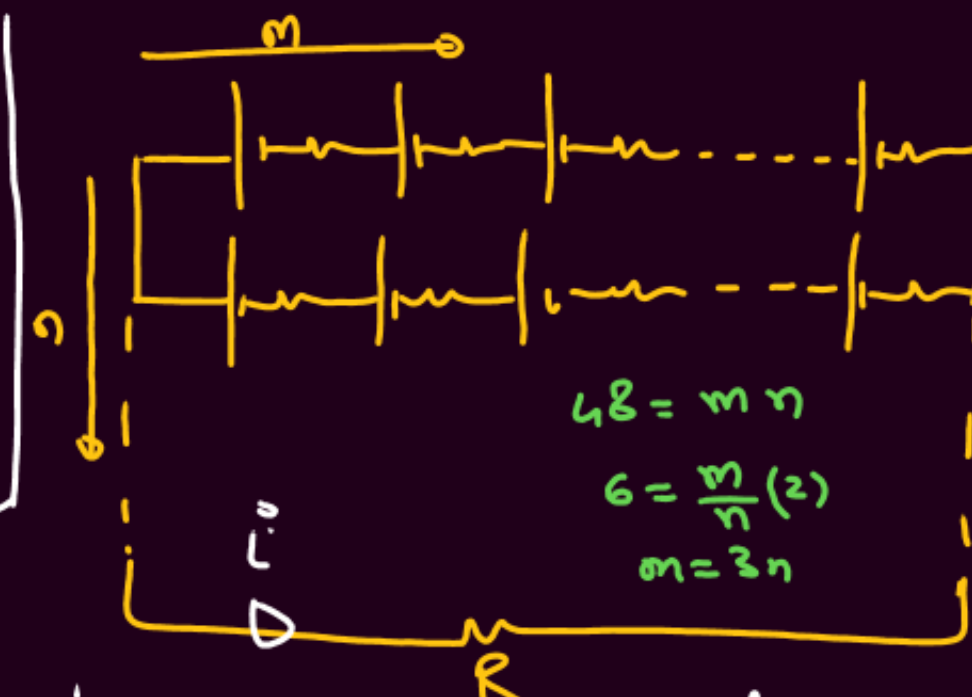
$$\textcircled{5} i = \frac{m\mathcal{E}}{R + \frac{mr}{n}}$$



$$48 = mn$$


$$6 = \frac{m}{n}(2)$$

$$m = 3n$$

For max i through R

when $\textcircled{2}$

$$R = \frac{mr}{n}$$

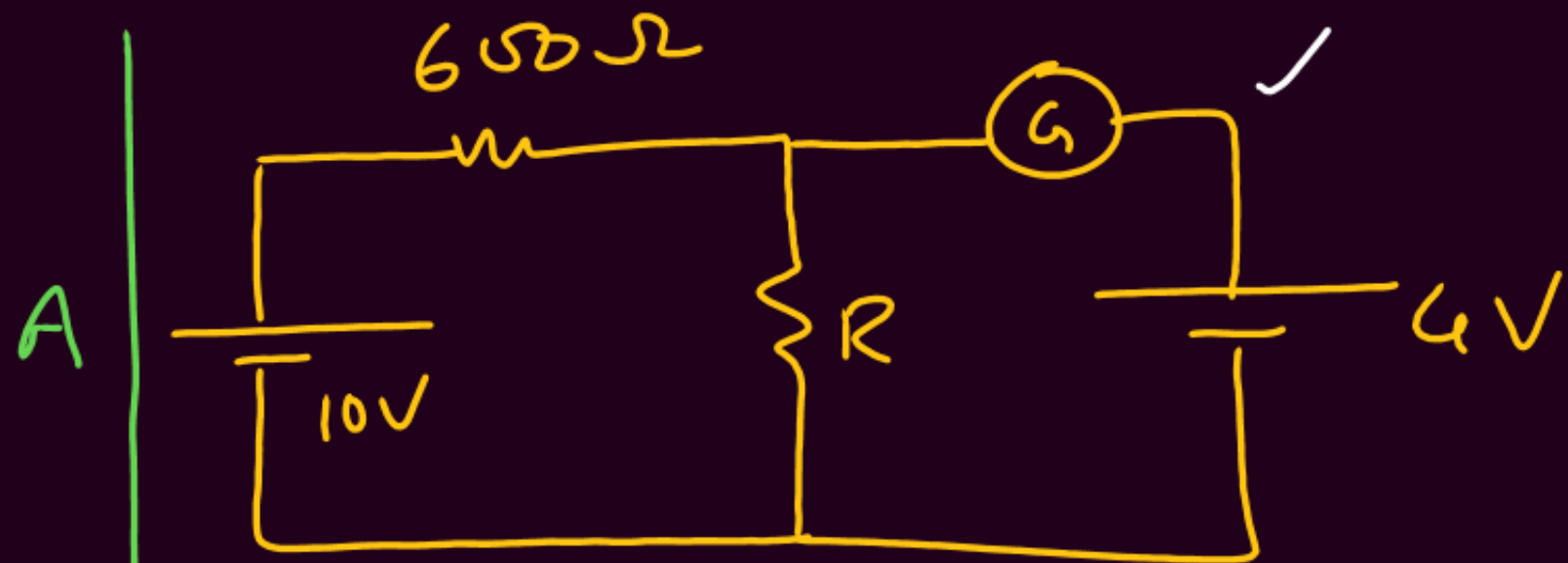

If $i_g = 0$
then find R

P4Q



↓

$$\epsilon_{ay} = 4$$

$$\frac{10R + 0}{R + 600} = 4$$

$$10R = 4R + 2400$$

$$6R = 2400$$

$$R = 400\Omega$$

Power

$$\frac{dw}{dt} = V \left(\frac{dq}{dt} \right)$$


$$P = V i = \frac{V^2}{R} = i^2 R$$

Power $\rightarrow$ W (watt)

$$1 \text{ kWhr} = 10^3 (3600) = \underline{3.6 \times 10^6 \text{ J}}$$

[Commercial unit
of energy]


$$\underline{\text{Heat}} = i^2 R t$$

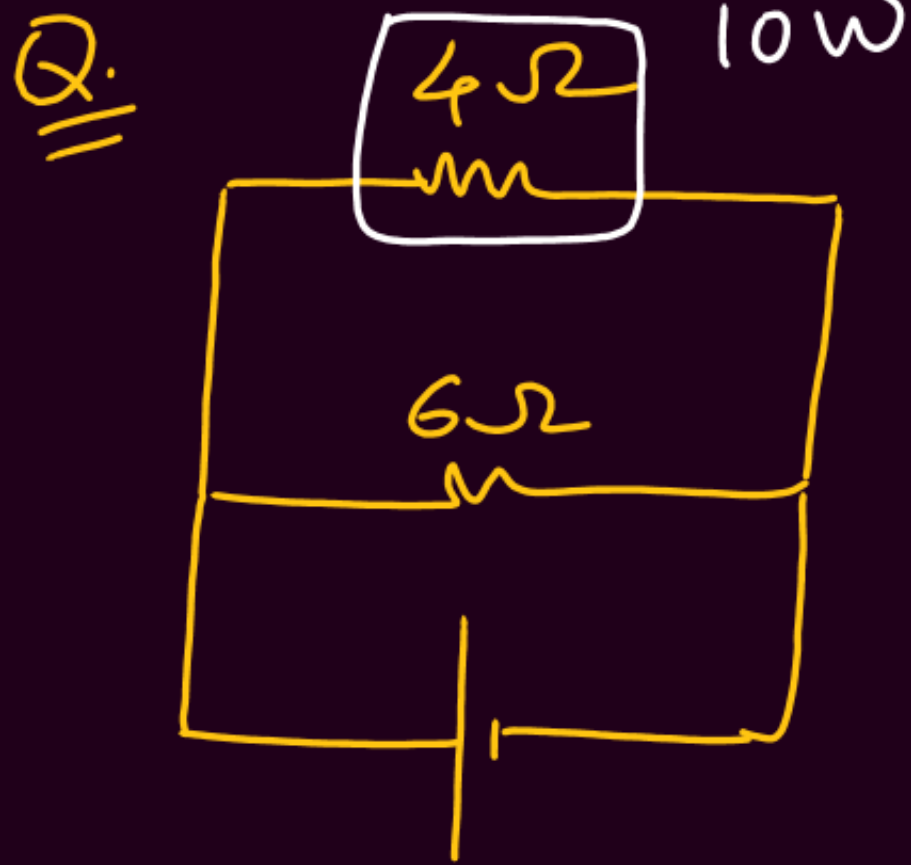

$$P = \frac{V^2}{R}$$

$$\frac{P}{10} = \frac{4}{6}$$

$$P = \frac{40}{6} = \frac{20}{3} W$$

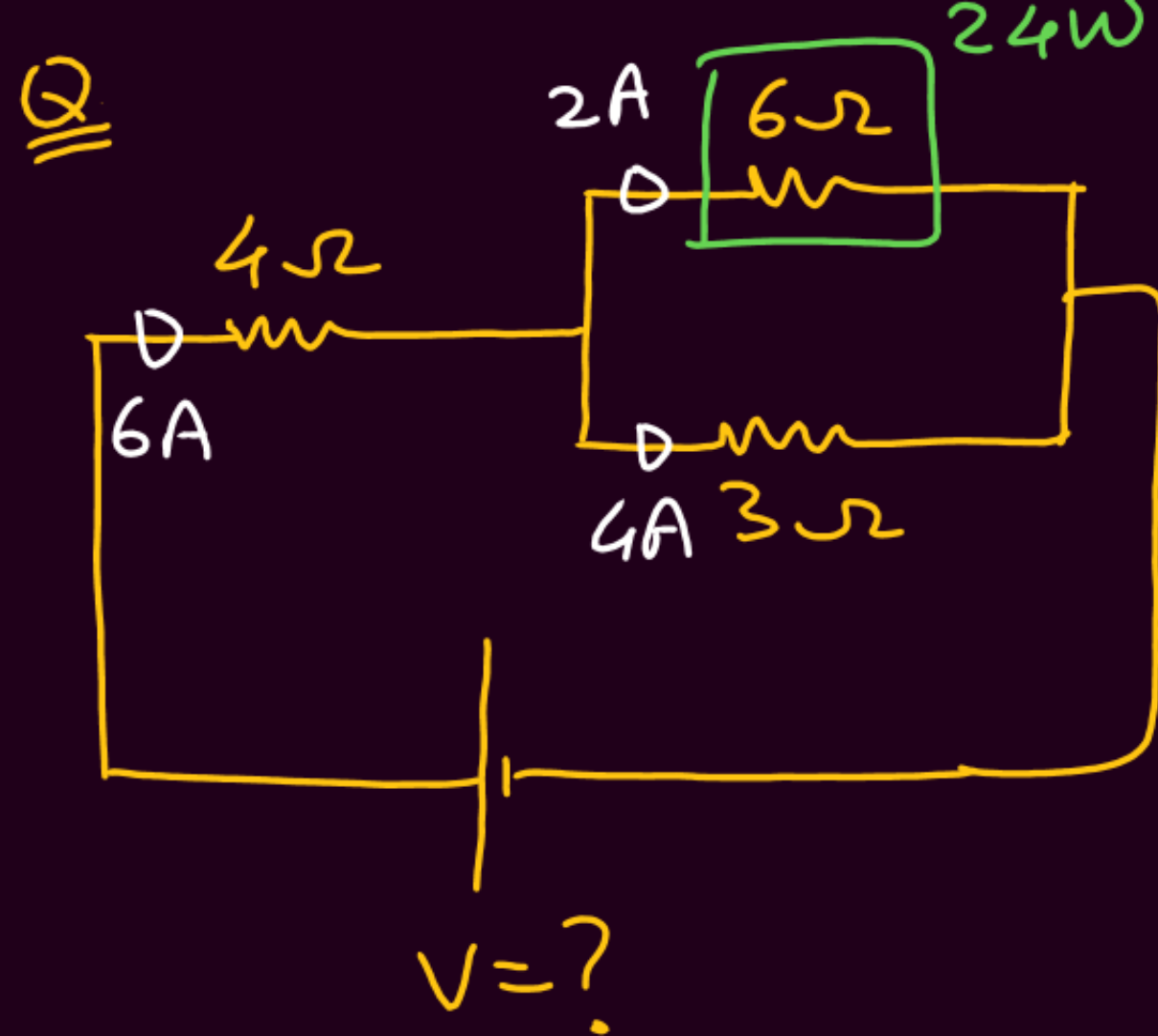

$$\textcircled{1} \quad 24 = I^2 (6)$$

$$I = 2A$$

$$\textcircled{2} \quad 2(6) = I(3)$$


$$I = 4A$$

$$V = 6 R_{eq}$$

$$= 6(6)$$

$$= 36V$$

[100W, 50V]

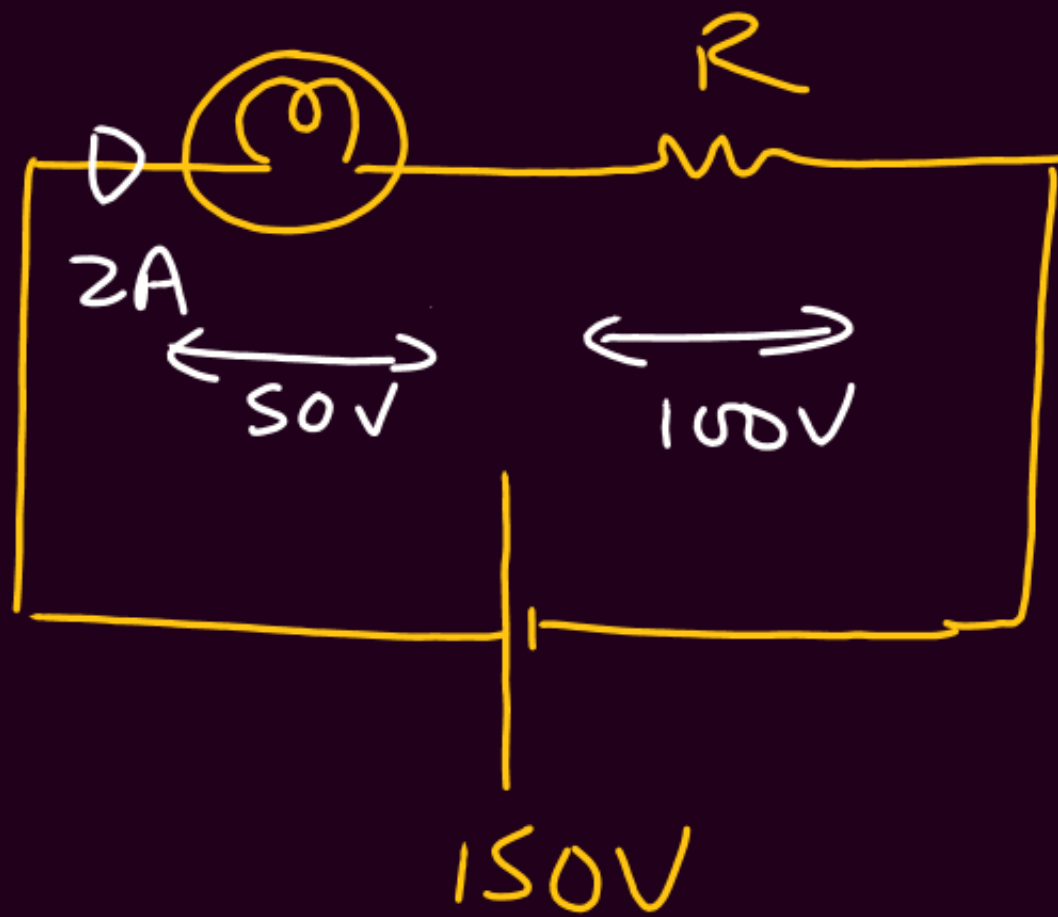

$R = ?$


$$100 = i^2 (50)$$

$$i = 2 \text{ A}$$

$$\textcircled{1} \quad 100 = 2R$$

$$R = 50 \Omega$$
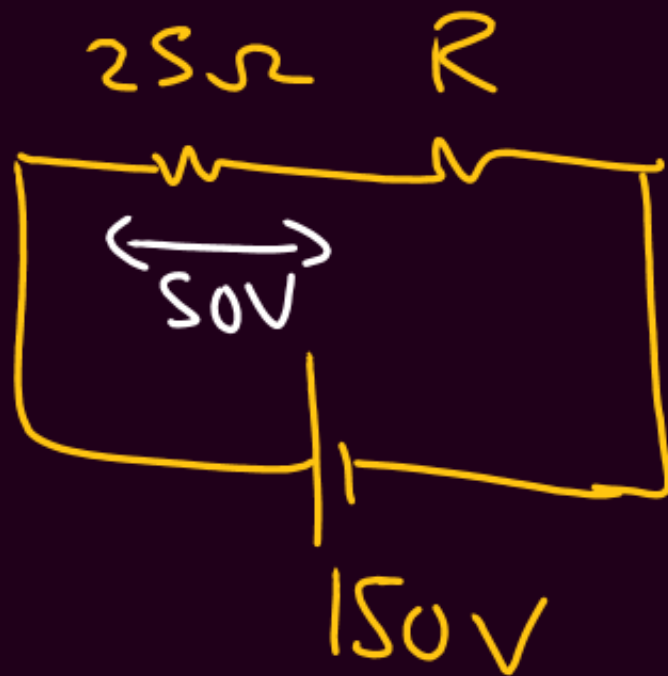
$$\textcircled{2} \quad R = \frac{(50)^2}{100} = 25 \Omega$$



$$\textcircled{I} \quad i = 2 \text{ A} = \frac{150}{25 + R}$$

$$\textcircled{II} \quad 50 = i^2 (25)$$
$$i = 2 = \frac{150}{25 + R}$$


Q: → Bulbs have same rated voltage
→ Combination → Rated Supply

Parallel



$$P_{\text{Total}} = P_1 + P_2$$

(2) Series

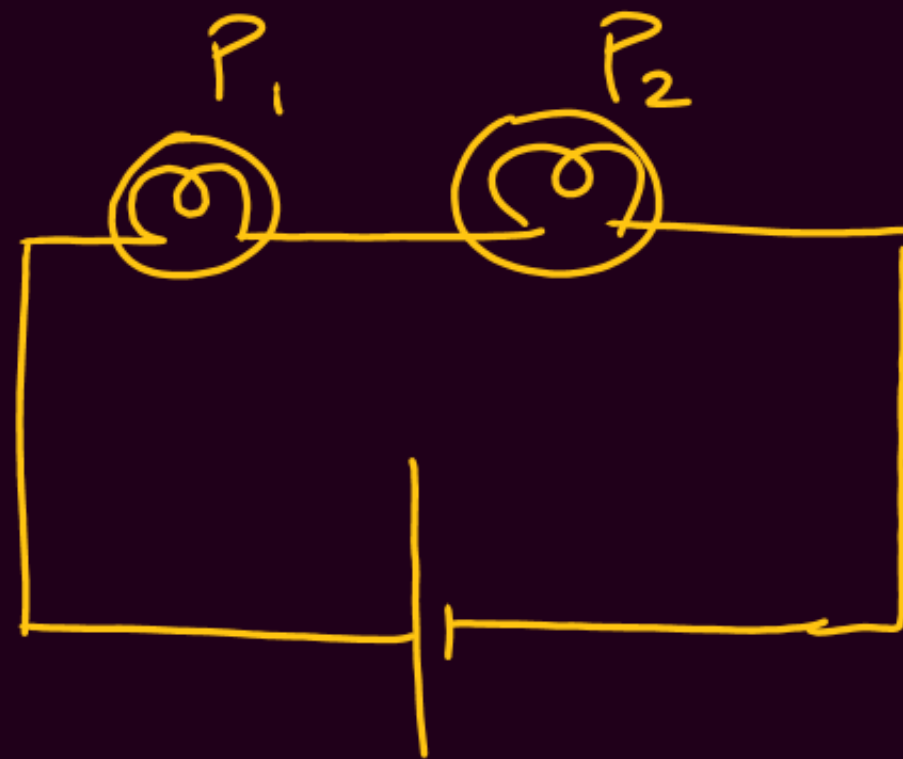

$$P_{\text{Total}} = \frac{P_1 P_2}{P_1 + P_2}$$


Q: 100 W 300 W


(1) Parallel $P = 100 + 300$
 $= 400 \text{ W}$

(2) Series $P = \frac{300}{4} = 75 \text{ W}$


100 W
50 V

200 W
200 V ✓

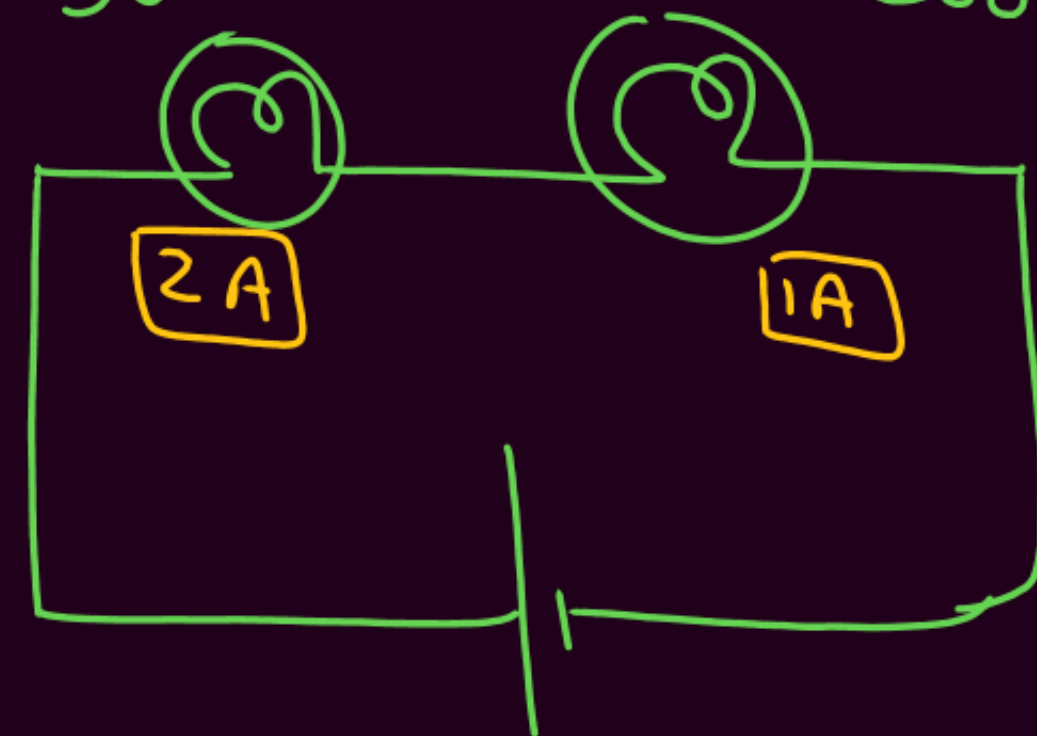

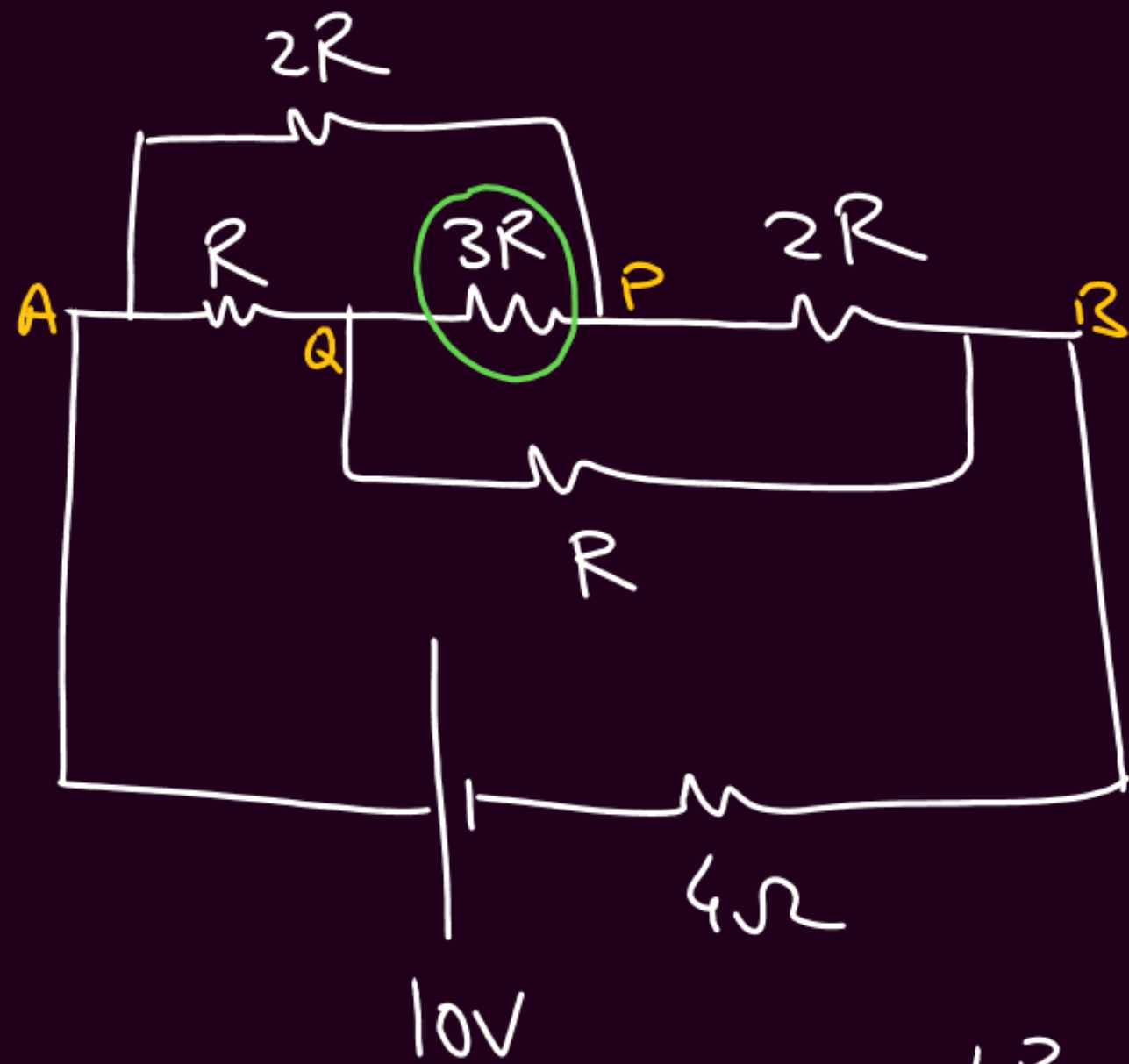

Find $R = ?$

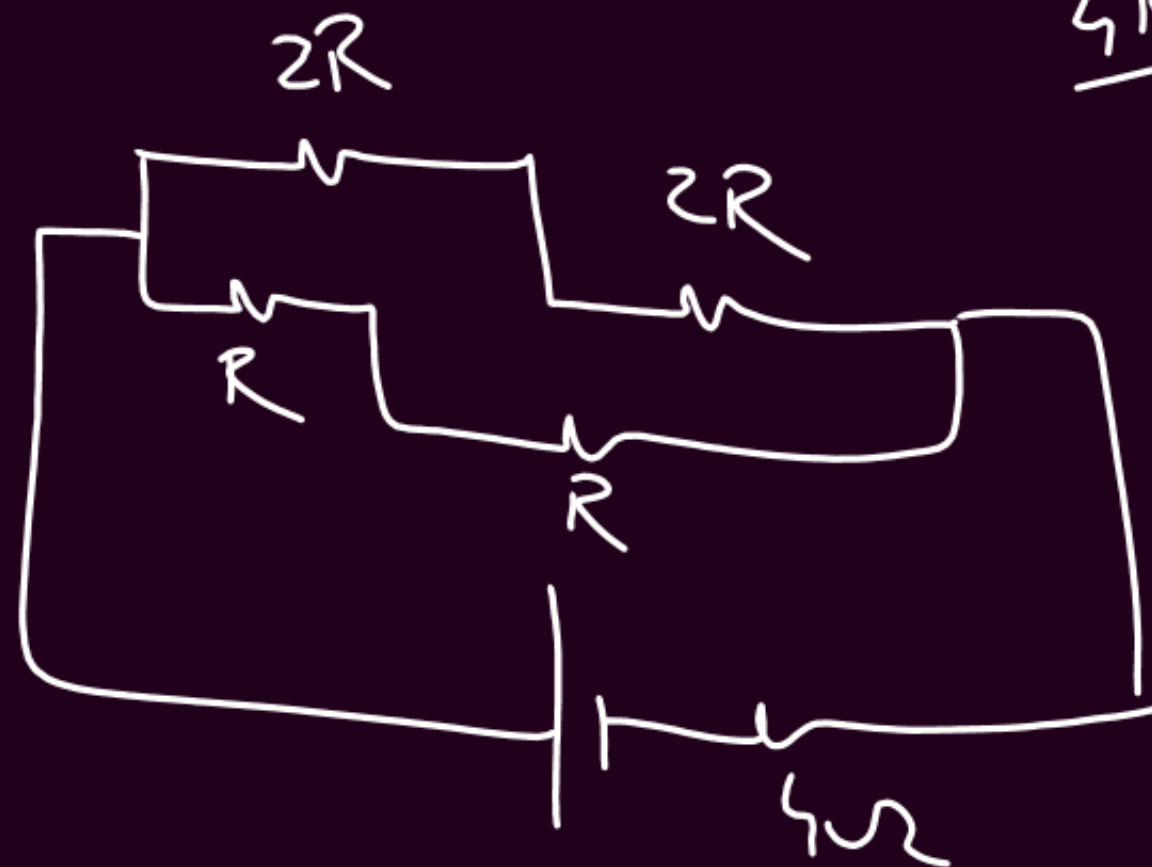

$$\frac{4R}{3} = 4$$

$$R = 3\Omega$$

2) 15W

4) 25W (X)






$$R = ?$$

To draw max
Power through
cell/R

$$R = 4\Omega$$

$$P = i^2 R$$

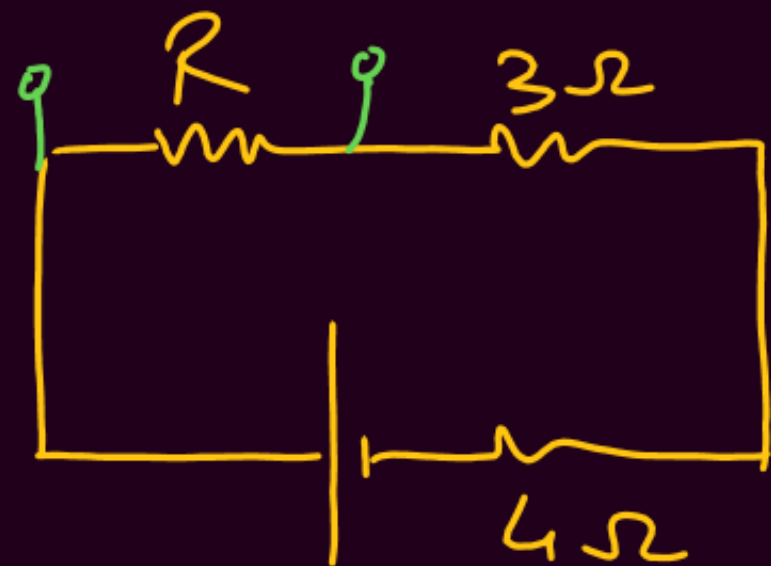

$$R = ?$$

To draw max
Power through R

$$R = 4 + 3 = 7\Omega$$

$$P = i^2 R$$




$$R = ?$$

To draw max Power
through cell

$$R + 3 = 4$$

$$R = 1\Omega$$

$$P = i^2 (R + 3)$$

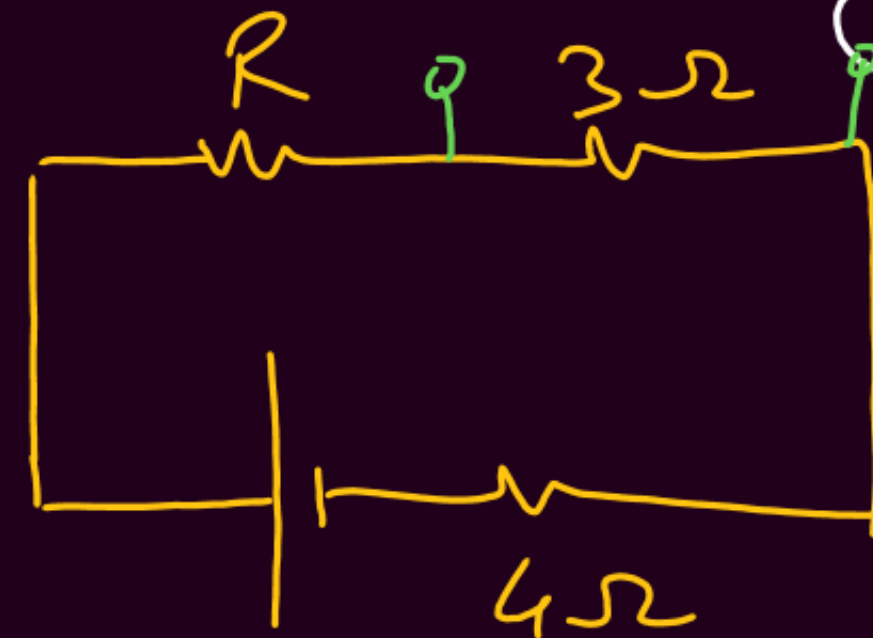

$$R = ?$$

To draw max Power
through '3Ω'

$$R = 0$$

$$P = i^2 (3)$$


Measuring Devices

① Ammeter

→ it should be connected in Series

→ $i_{\text{measured}} < i_{\text{true}}$


→ ideal $R_A = 0$

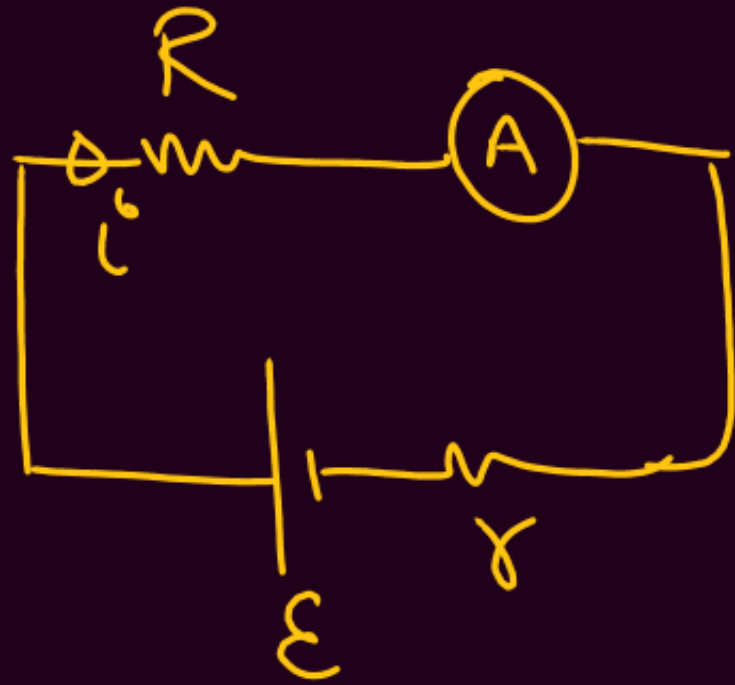

② Voltmeter

→ it should be conn. in parallel

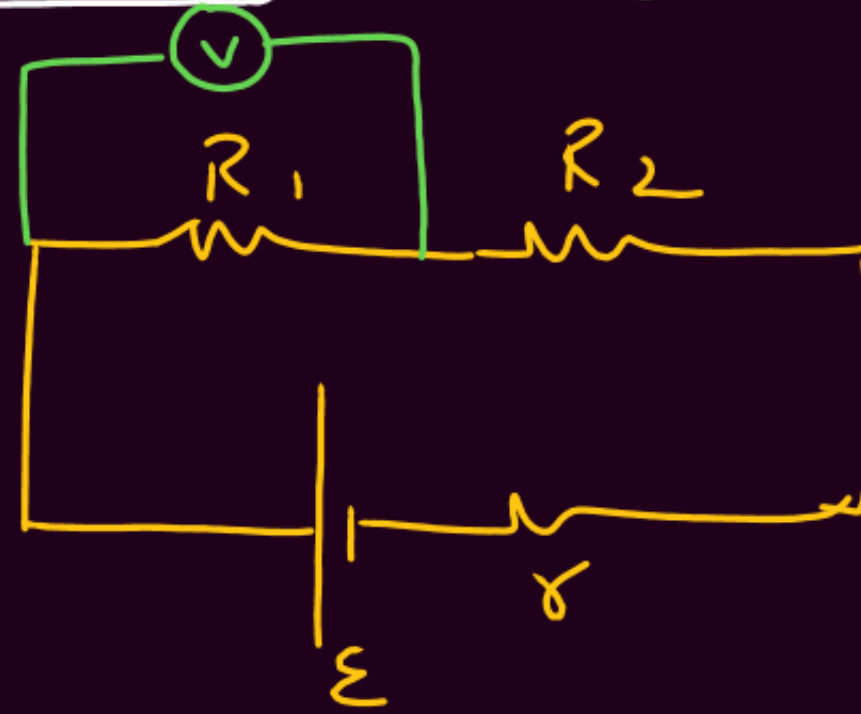
→ $V_{\text{measured}} < V_{\text{true}}$



→ ideal

$R_V \rightarrow \infty$


↳ "Potentiometer"

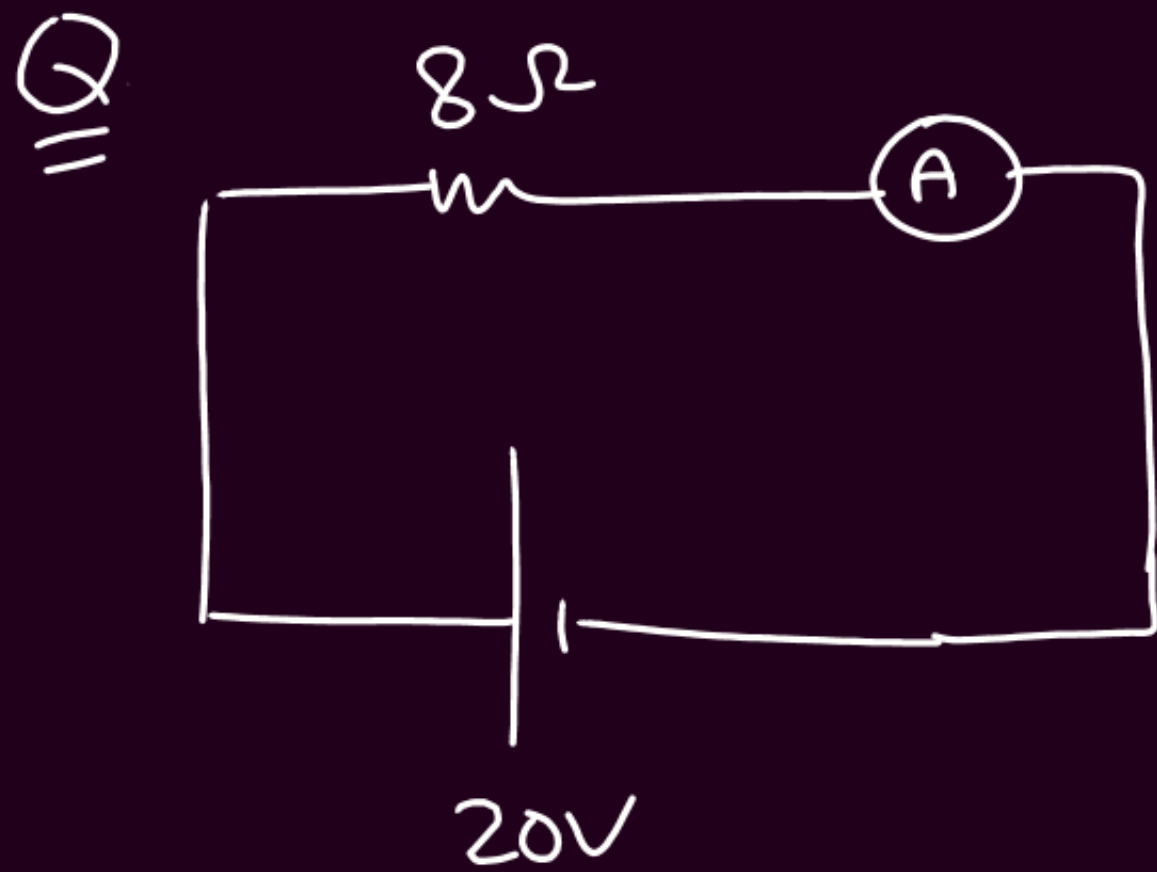

$$A = ?$$

Assume $\rightarrow$ ideal

$$A = \frac{20}{8} = 2.5 \text{ A}$$

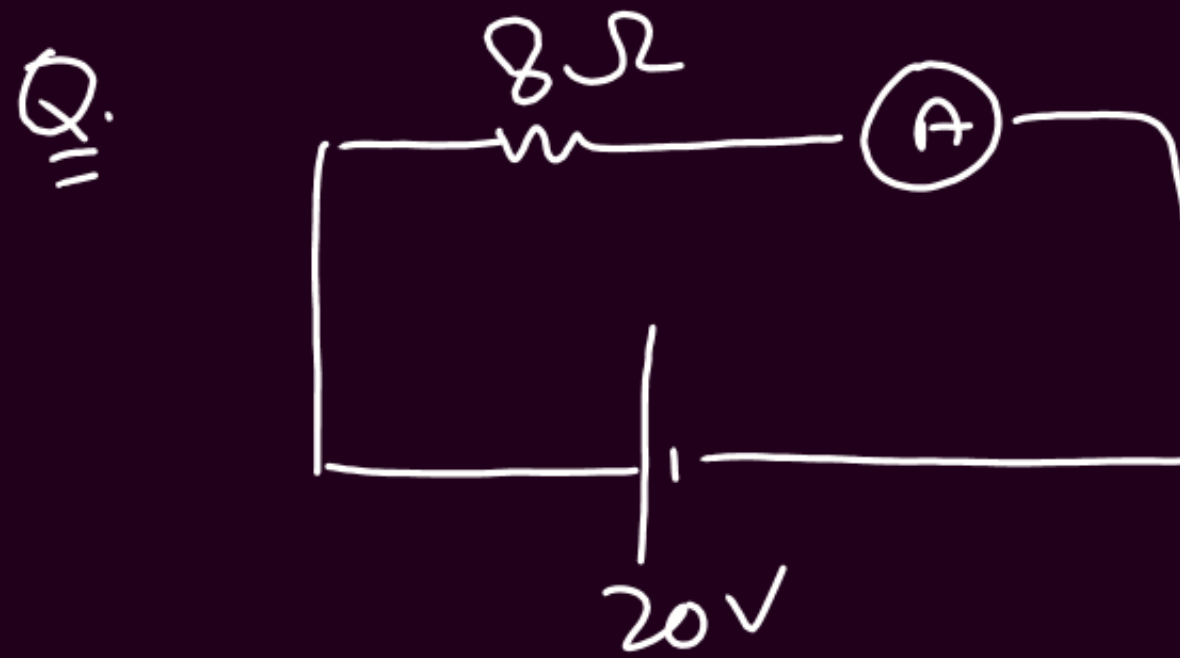


$$\text{if } A = 1 \text{ A} = \frac{20}{8 + R_A}$$

$$\text{then } R_A = ?$$


$$R_A = 12 \Omega$$

Q.11

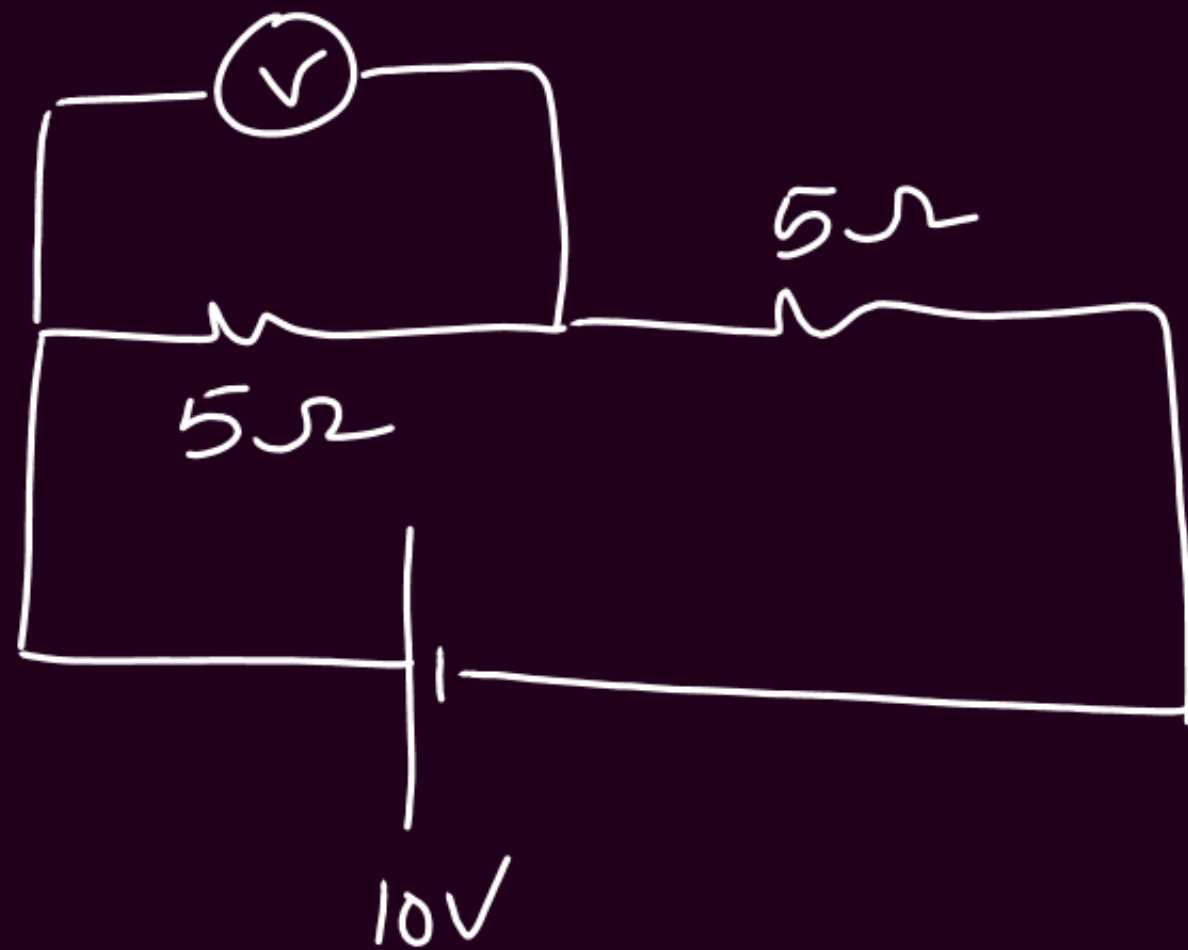

$V = ?$


Assume - ideal

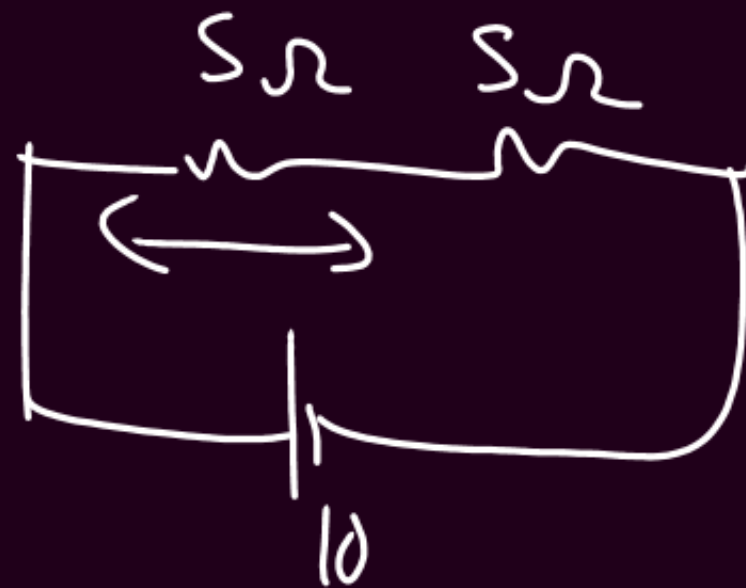

$$i = 1A$$

$$V = (1)(5) = 5V$$

Q.11

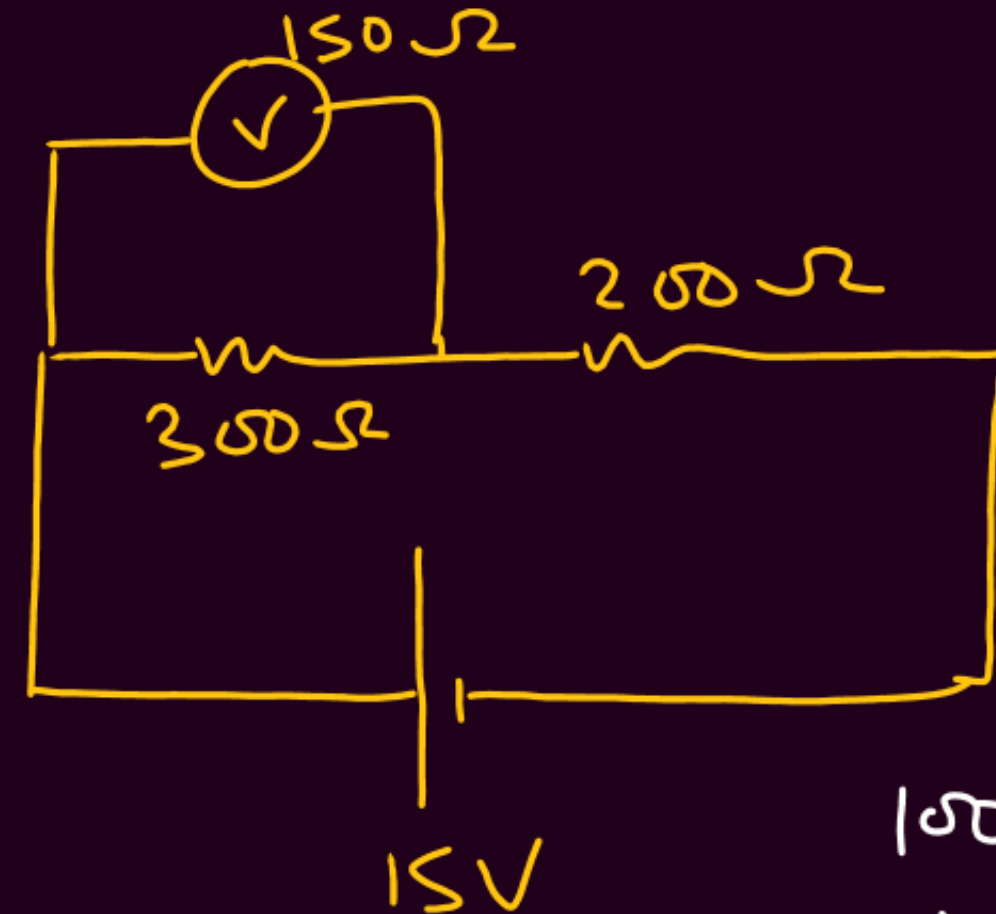


$$R_{eq} = 300\Omega$$

$$i = \frac{15}{300} A$$


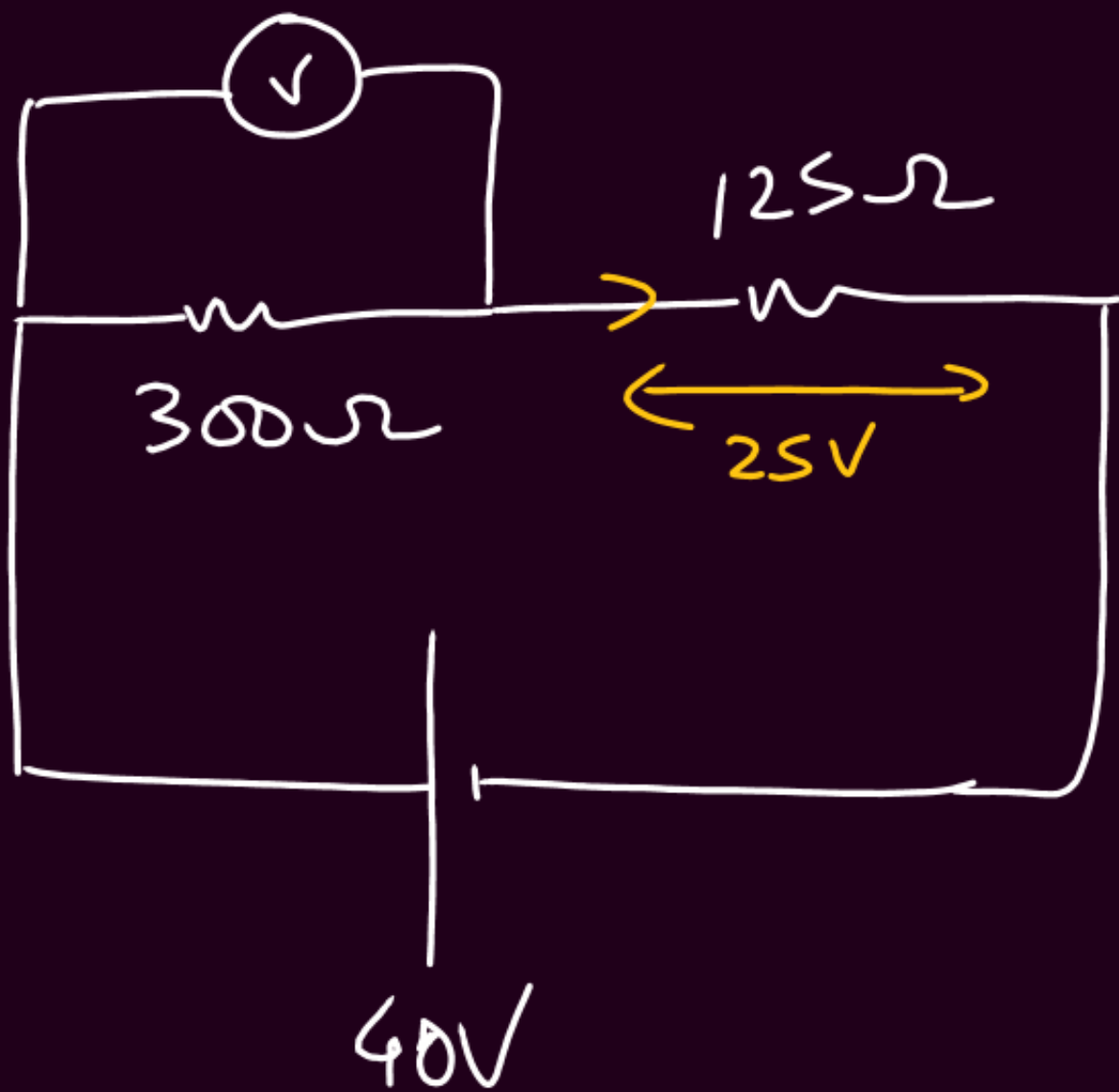
$$V = \left(\frac{15}{300} \right) 100 = \underline{\underline{5V}}$$



if $\textcircled{V} = 15V$

$R_v = ?$

$$i = \frac{25}{125} \text{ A} = \frac{40}{R_{eq}}$$

$$R_{eq} = 200 \Omega$$



$$200 = 125 + \frac{300R}{300+R}$$

$$75 = \frac{300R}{300+R}$$

$$300+R = 4R$$

$$300 = 3R$$



$$R = 100 \Omega$$

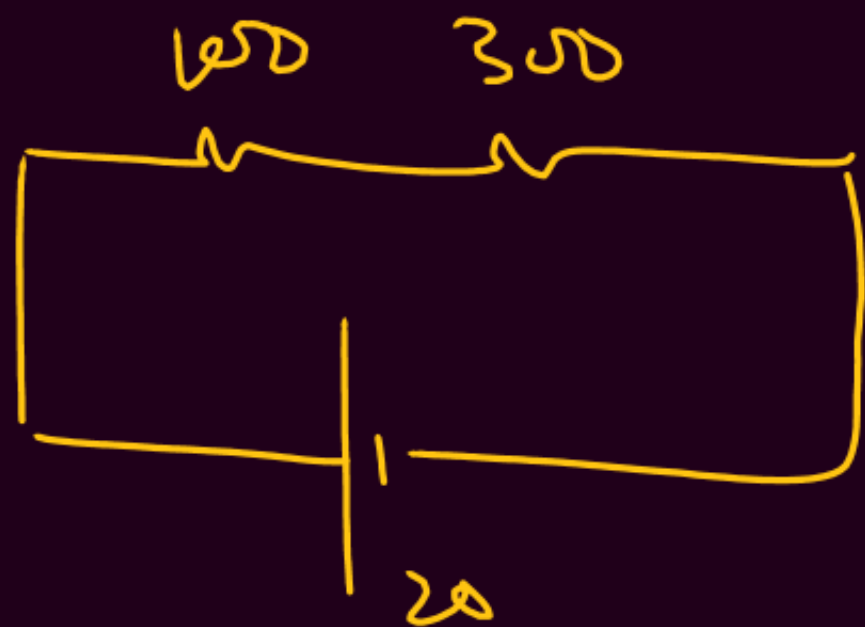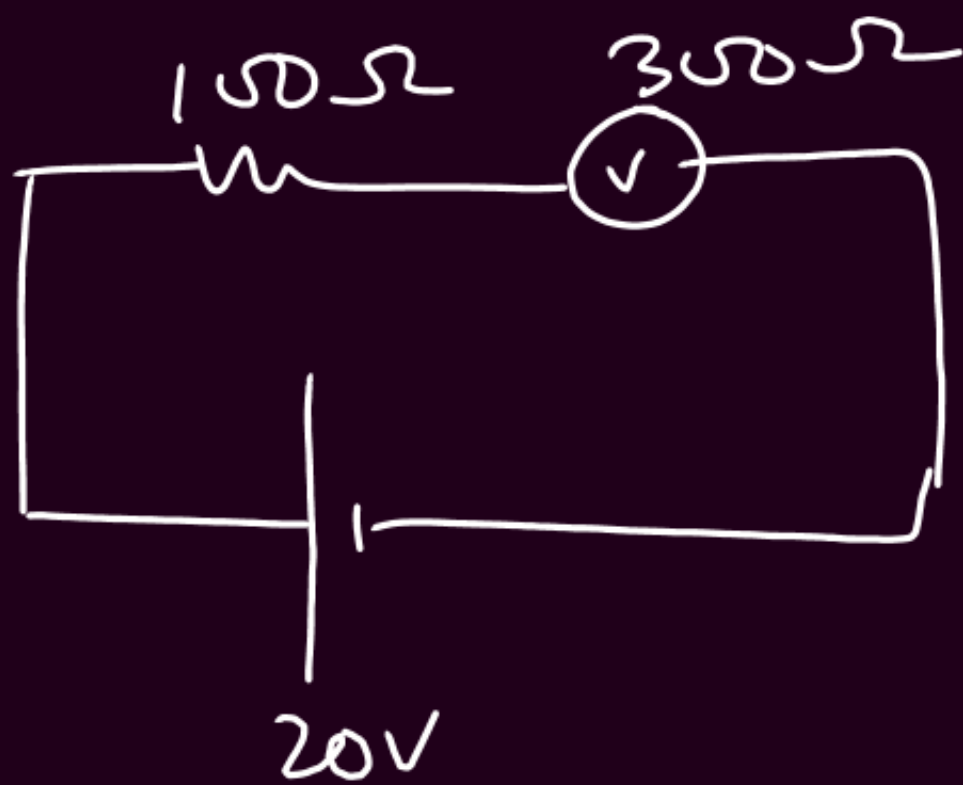

$$i = \frac{20}{400}$$

$$V = \frac{20}{400} \times 300 = 15V$$

PyQ

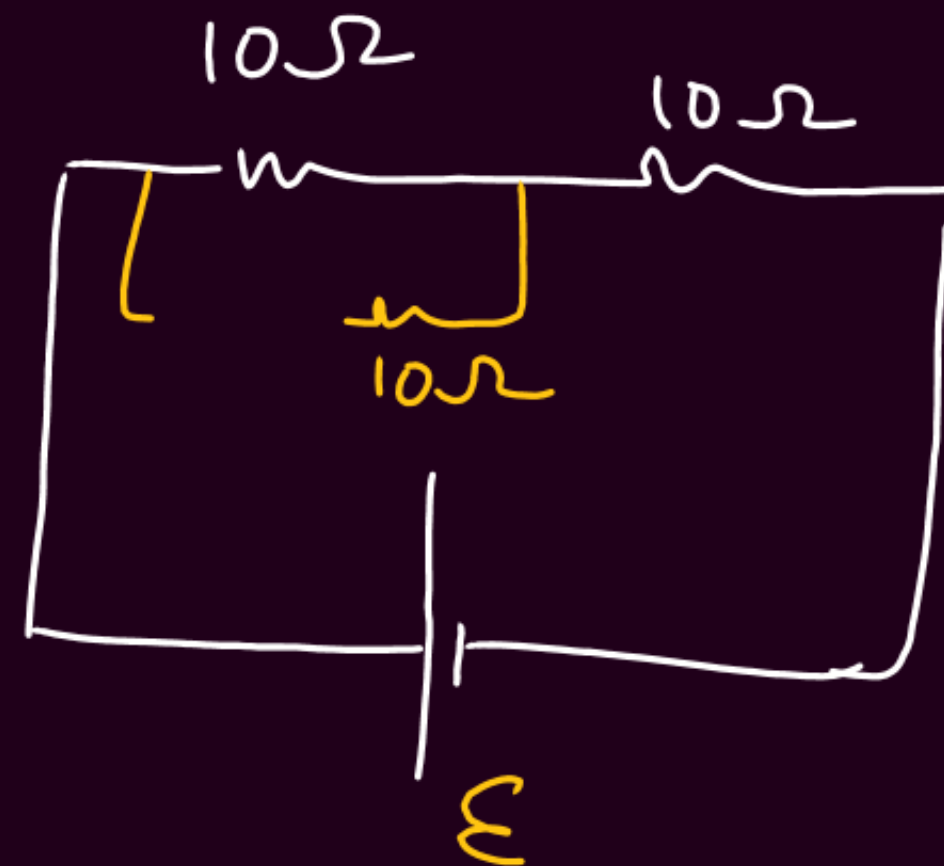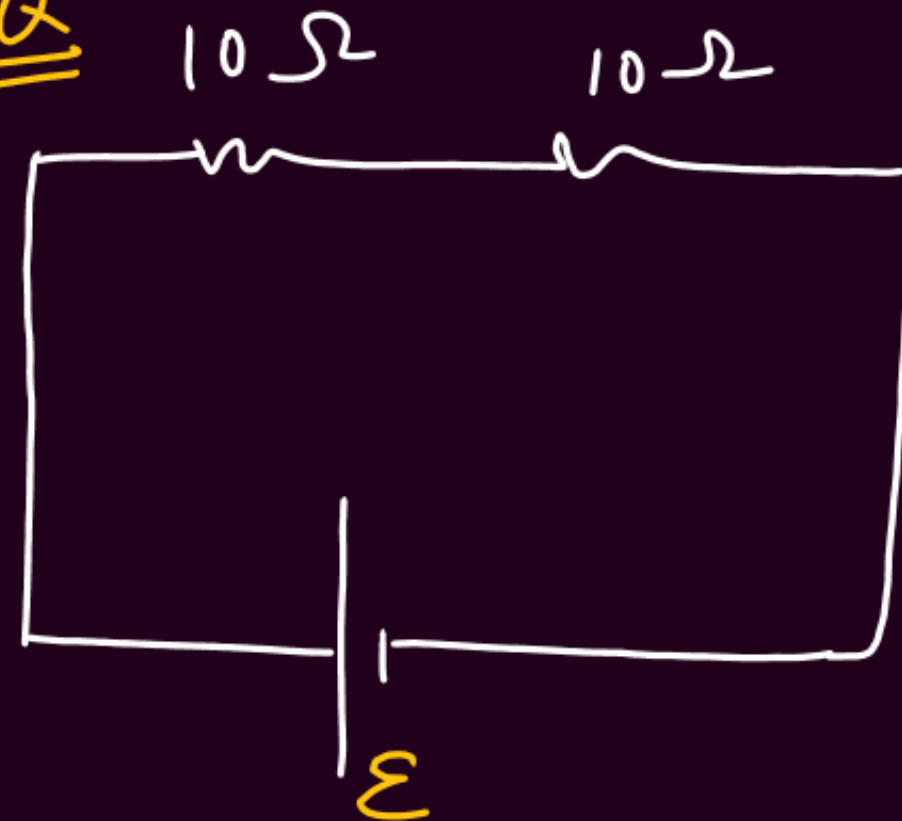


1) $V_1 = V_2$

2) $V_1 < V_2$


3) $V_1 > V_2$

[given V_1/V_2 are ideal]



11Q.

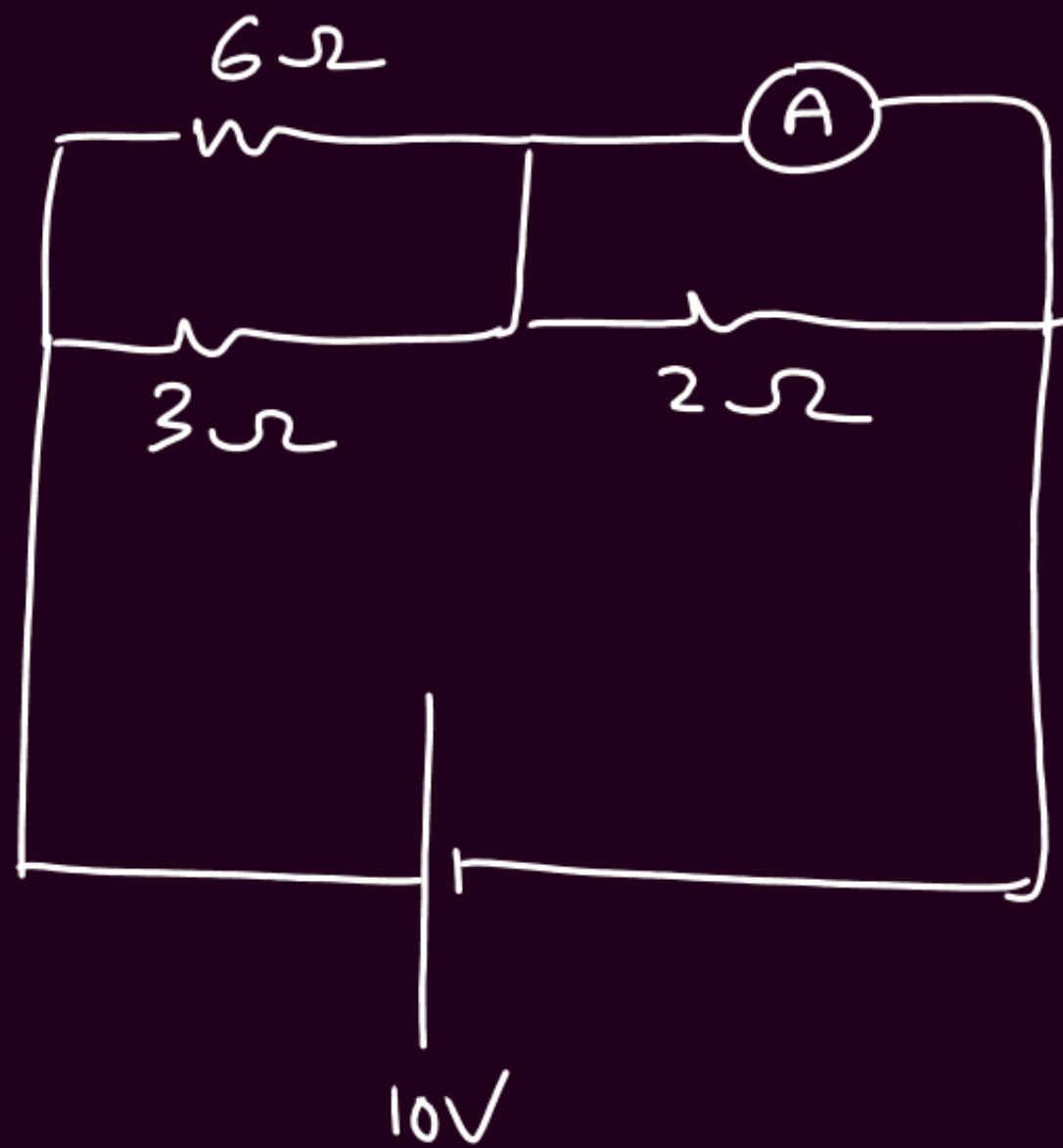


(A) = ?

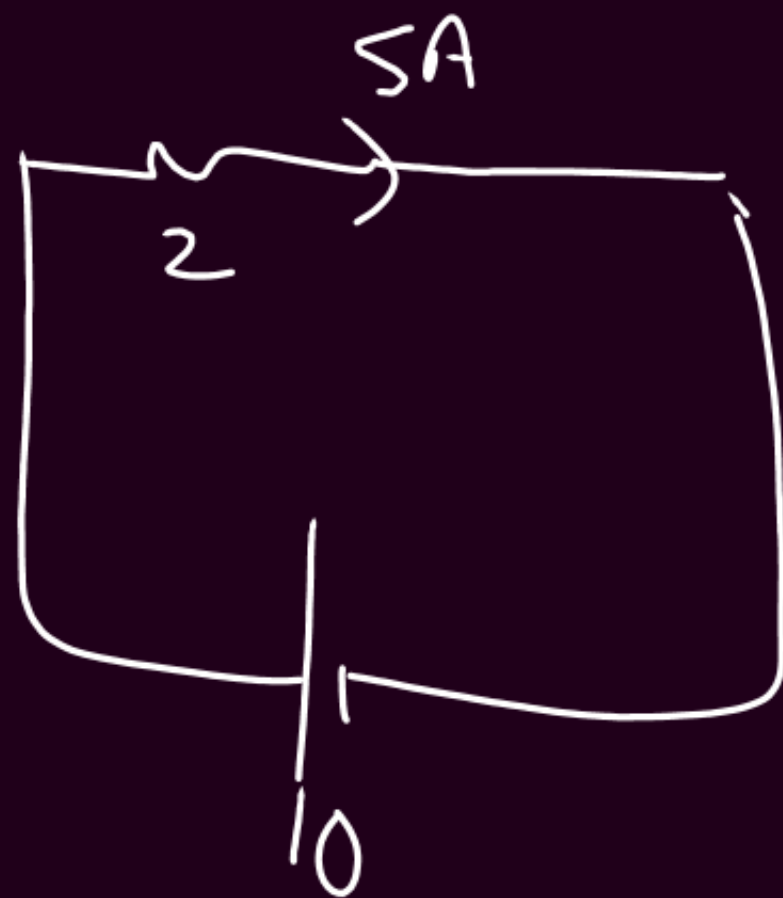


12Q.

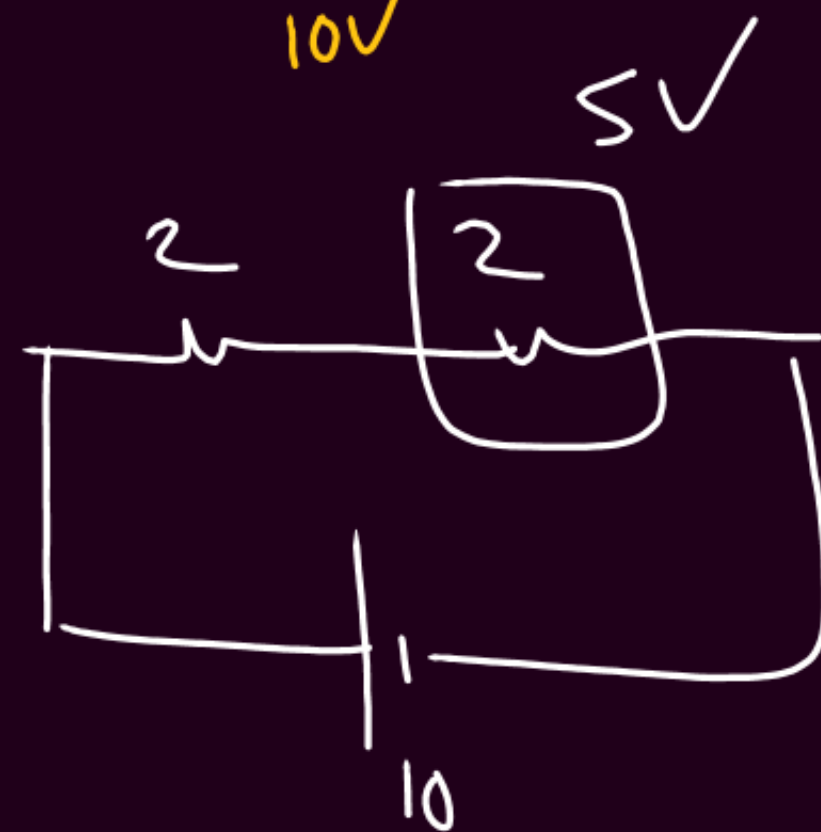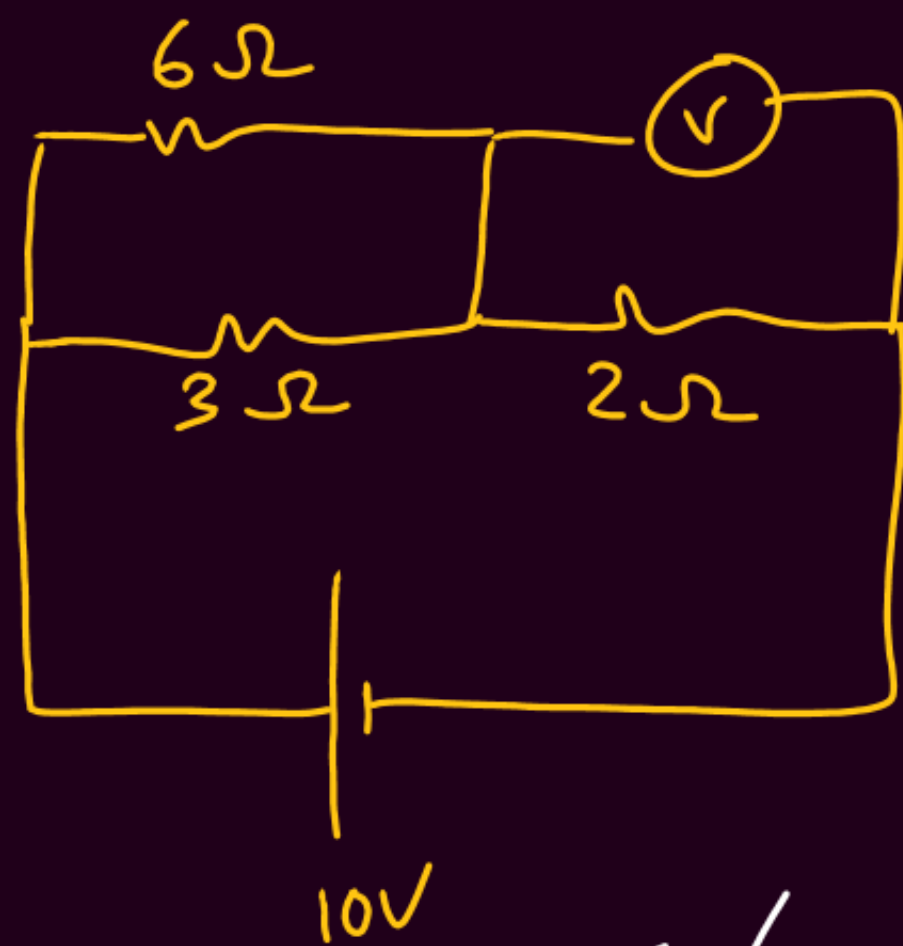

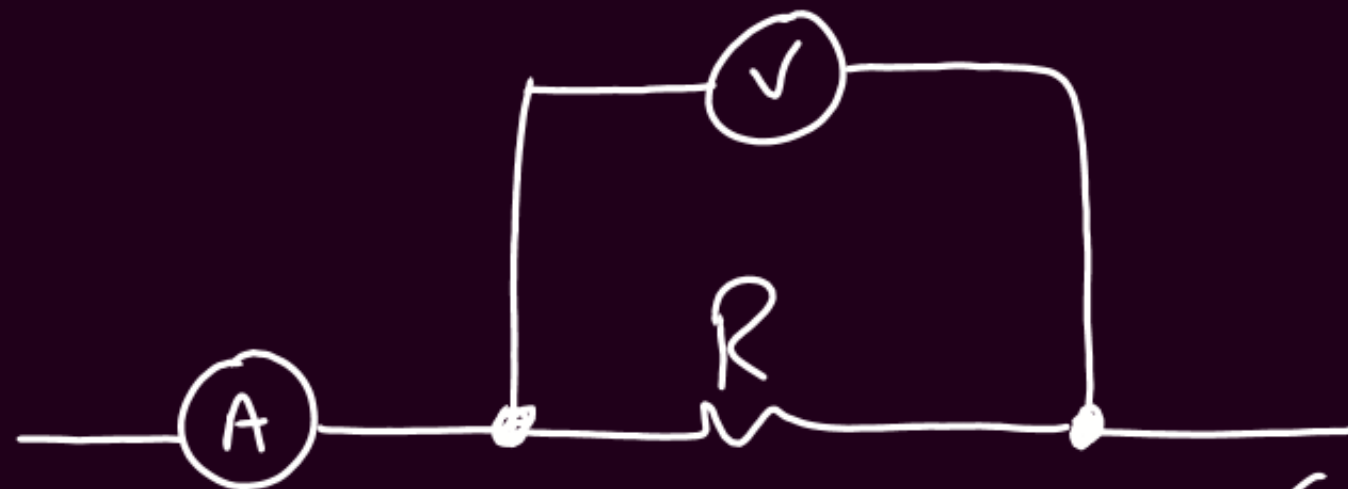

if $\textcircled{V} = 20\text{V}$

$\textcircled{A} = 4\text{A}$

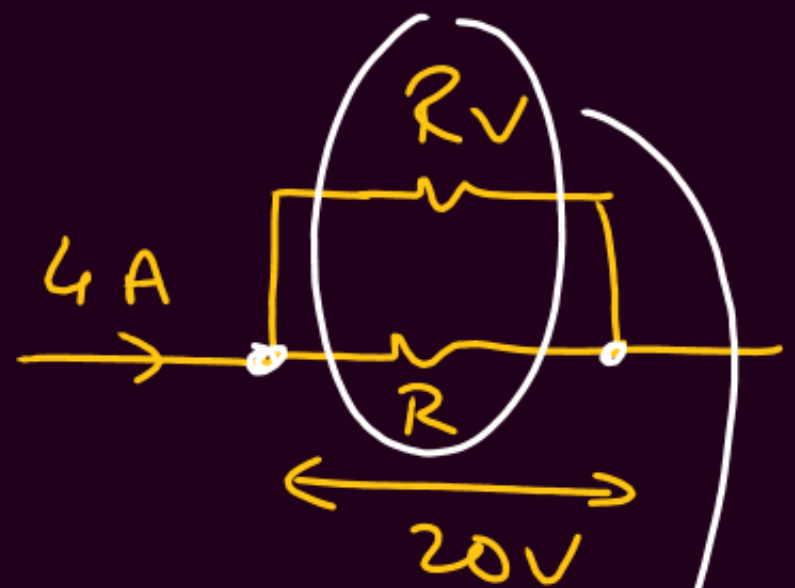


$$R_{eq} = \frac{20}{4} = 5\Omega$$

Then

1) $R = 5\Omega$

☒ 2) $R > 5\Omega$

3) $R < 5\Omega$

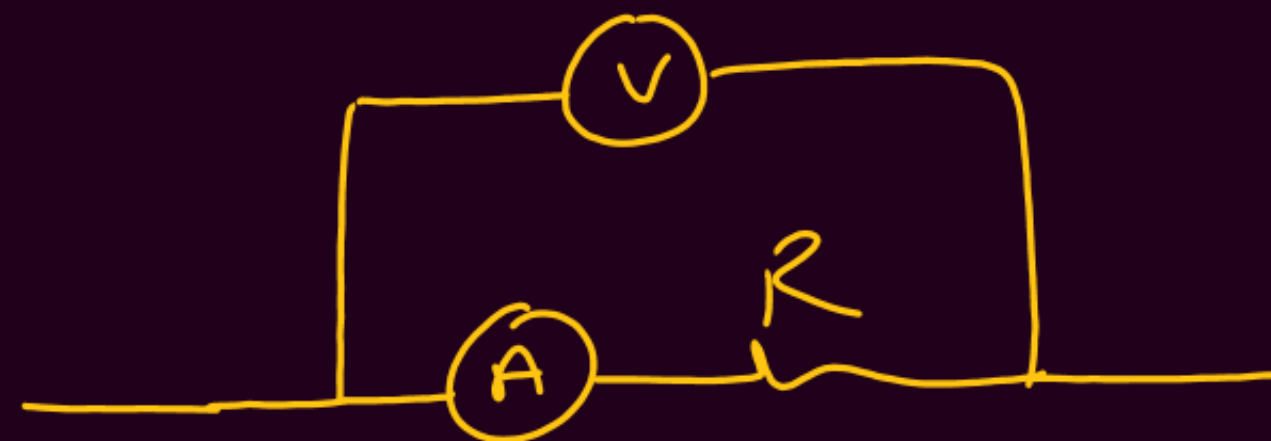

if $\textcircled{V} = 20\text{V}$


$\textcircled{A} = 4\text{A}$

Then

1) $R = 5\Omega$

2) $R > 5\Omega$


☒ 3) $R < 5\Omega$

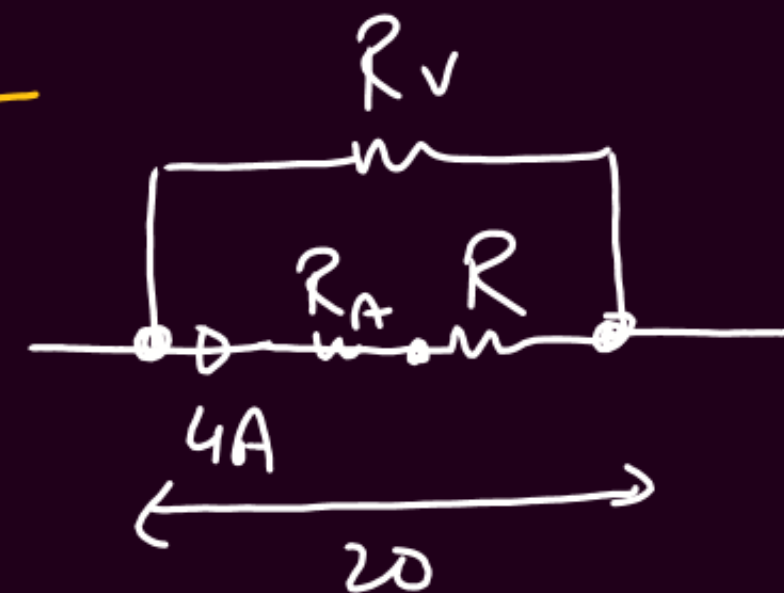

$$\frac{20}{4} = 5 = R_A + R$$



Conversion of (G) to (A)

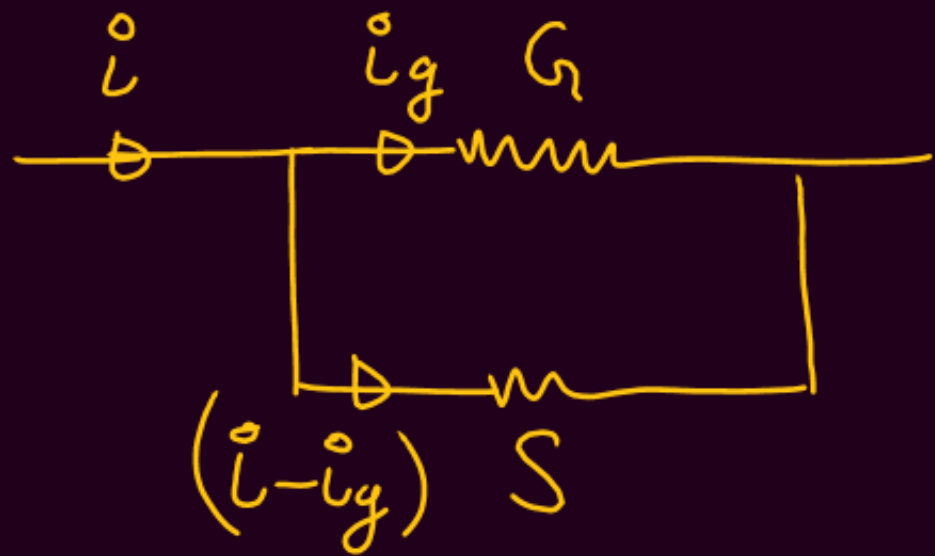

Shunt = Resis in parallel

① Concept $i_g G = (i - i_g) S$

✓ ② $n = \frac{\text{new rating}}{\text{old rating}} = \frac{i}{i_g}$

✓ ③ $S = \frac{G}{n - 1}$

④ $R_A = \frac{GS}{G + S}$ $\approx S$

Conversion of (G) into (V)



① Concept $V_{\text{new}} = i_g (R_L + R_s)$

② $n = \frac{\text{new rating}}{\text{old rating}} = \frac{V_{\text{new}}}{i_g R_L}$

③ $R_s = (n-1) R_L$

Q. (G) ($10\mu A$, 200Ω)

(A) $1mA$

$S = ?$

$$n = \frac{1 \times 10^{-3}}{10 \times 10^{-6}} = 100$$

$$S = \frac{G}{n-1} = \frac{200}{100-1}$$

$$S = \frac{200}{99} \Omega \approx 2\Omega$$

Q. (G) (1000Ω , $10mA$)


(A) $0.5A$

$$S = \frac{1000}{49} \approx 20\Omega$$

$$n = \frac{0.5}{10 \times 10^{-3}} = 50$$


⑥ (200 Ω , 10 mA)

① 50 mA

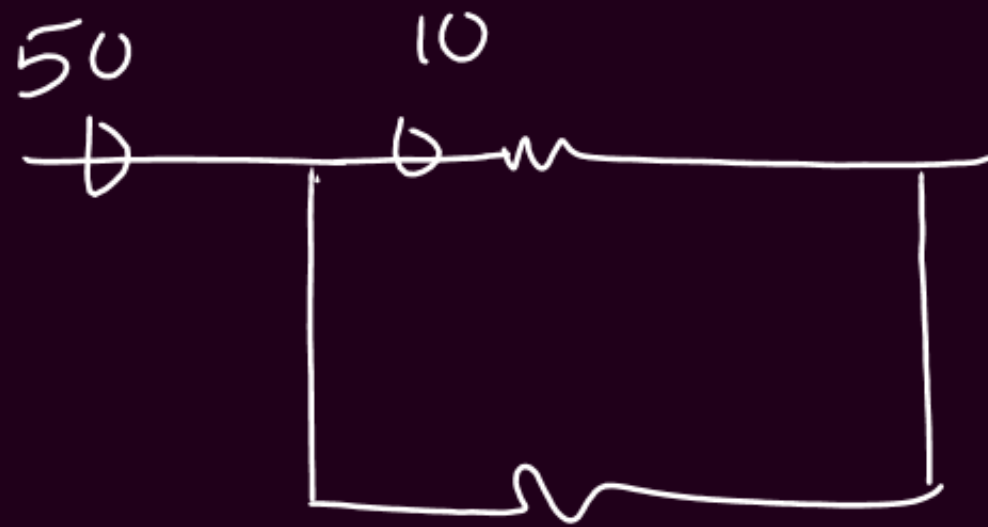

$$\eta = \frac{50}{10} = \frac{20}{i}$$

$$\boxed{i = 4 \text{ mA}}$$

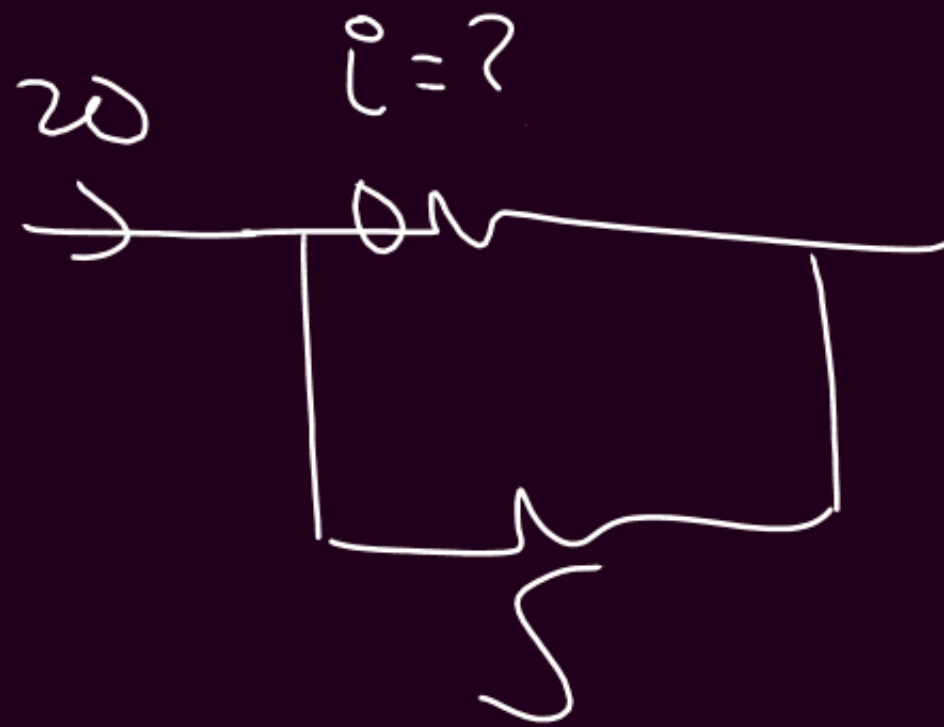

$$i_s = 20 - 4 = \underline{16 \text{ mA}}$$

$$\textcircled{G} (200 \Omega, 10 \text{ div/mA})$$

$$\textcircled{A} (2 \text{ div/mA})$$

$$n = \frac{\left(\frac{1}{2}\right)}{\left(\frac{1}{10}\right)} = \frac{10}{2} = 5$$

$$S = \frac{200}{5-1} = 50 \Omega$$

per div

$$\frac{1}{10} \text{ mA/div}$$

$$\frac{1}{2} \text{ mA/div}$$



$$\textcircled{G} (200 \Omega, 1 \text{ mA})$$

$$\textcircled{V} 2 \text{ V}$$

$$n = \frac{2}{(10^{-3})(200)} = 10$$

$$\begin{aligned} R_s &= (n-1) G \\ &= (10-1) 200 \\ &= \underline{\underline{1800 \Omega}} \end{aligned}$$

$$\textcircled{V} (100 \text{ k}\Omega, 20 \text{ V})$$

$$\textcircled{A} \boxed{1 \text{ mA}}$$

$$n = \frac{10^{-3}}{\left(\frac{20}{100 \times 10^3}\right)} = 5$$

$$S = \frac{G}{n-1} = \frac{100 \text{ k}}{5-1}$$

$$\boxed{S = 25 \text{ k}\Omega}$$