

Capacitance (Condensor)

→ Storage device ($\vec{E}$)

$$C = \frac{Q}{V}$$




Unit Farad (F)

$$\mu F = 10^{-6} F$$

$$nF = 10^{-9} F$$

$$pF = 10^{-12} F$$

Parallel Plate Capacitor

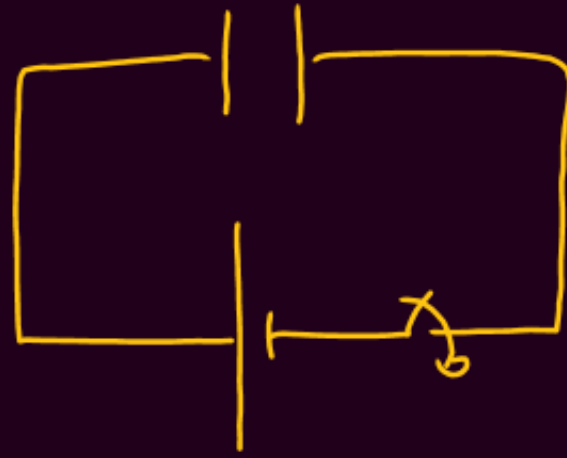

σ = Surface charge density
= charge per unit area

$$\sigma = \frac{q}{A}$$

ϵ_0 = Permittivity of free Space (vacuum) ✓

ϵ = " " Medium

$$\epsilon = \epsilon_0 \epsilon_r = \boxed{\epsilon_0 K}$$

$$\boxed{\epsilon_r = K = \frac{\epsilon}{\epsilon_0}}$$

→ Relative permittivity of medium

→ Dielectric constant

→ unitless

→ Dimensionless

$$\boxed{K \geq 1}$$


$K=1$ vacuum

$K \approx 1$ Air

$K \rightarrow \infty$ metals

$$\frac{1}{4\pi\epsilon_0} = 9 \times 10^9 \quad \frac{\text{N-m}^2}{\text{C}^2}$$
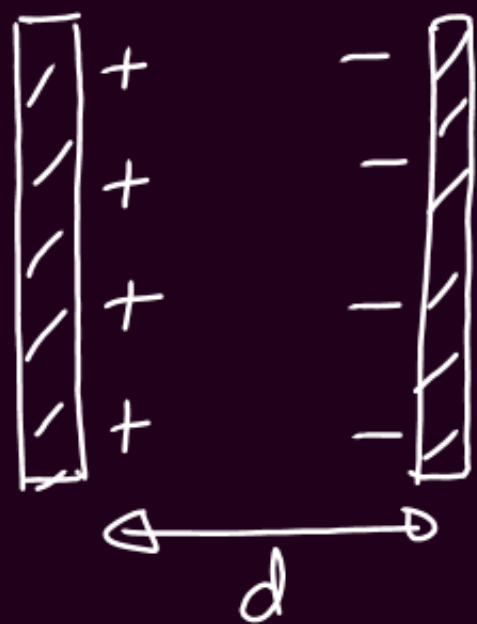
$$\epsilon_0 = 8.85 \times 10^{-12} \quad \frac{\text{C}^2}{\text{N-m}^2}$$



$$E_{\text{out}} = 0$$

$$E_{\text{in}} = \frac{\sigma}{\epsilon_0} = \frac{q}{\epsilon_0 A}$$

Air $\rightarrow \epsilon_0$



$$E_m = \frac{E_0}{x}$$

$$E = \frac{q}{\epsilon_0 A} = \frac{V}{d}$$

$$\frac{q}{V} = \frac{\epsilon_0 A}{d}$$

Air capacitor

$$C = \frac{\epsilon_0 A}{d}$$


$$C = \frac{\epsilon_0 K A}{d}$$



- $\rightarrow$ Area
- $\rightarrow$ Gap / Sep.
- $\rightarrow$ med.

A = Area of plates

d = Sep. / Gap betⁿ plates

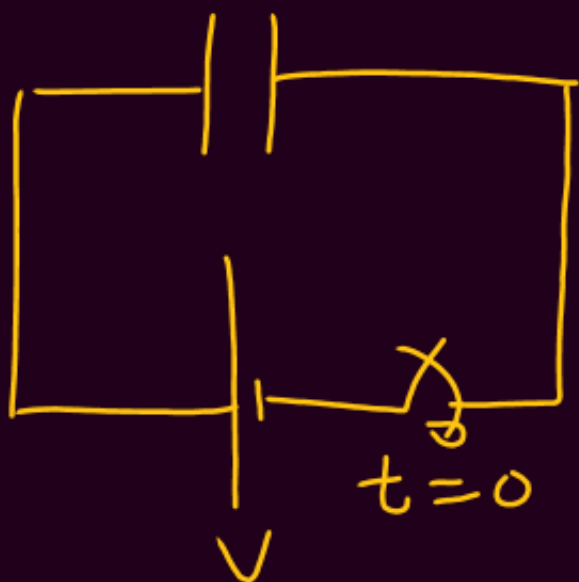

$$\textcircled{1} \quad C = \frac{\epsilon_0 A}{d}$$

$$\textcircled{2} \quad q = CV$$

$$\textcircled{3} \quad \text{W.D. by battery} = qV = CV^2 = \frac{q^2}{C}$$

$$\textcircled{4} \quad U = \frac{1}{2} CV^2 = \frac{q^2}{2C} = \frac{1}{2} qV$$

$$\textcircled{5} \quad E = \frac{\sigma}{\epsilon_0} = \frac{q}{\epsilon_0 A} = \frac{V}{d}$$

$$\textcircled{6} \quad E_{\text{one}} = \frac{\sigma}{2\epsilon_0}$$

$$\textcircled{7} \quad P = \frac{\sigma^2}{2\epsilon_0} = \frac{1}{2} \epsilon_0 E^2$$

$$\textcircled{8} \quad \text{Energy Density} = \frac{\text{Energy}}{\text{Volume}} = \frac{1}{2} \epsilon_0 E^2 = \frac{\sigma^2}{2\epsilon_0}$$

$$= \frac{\frac{1}{2} CV^2}{Ad}$$

$$\textcircled{9} \quad F = \frac{\sigma^2 A}{2\epsilon_0} = \frac{q^2}{2\epsilon_0 A}$$

$$Q \equiv C = \frac{\epsilon_0 K A}{d}$$

$$C = \frac{(8.85 \times 10^{-12})(4)(10 \times 8 \times 10^{-4})}{8 \times 10^{-3}}$$

$$C = 35.4 \times 10^{-12} \text{ F}$$

$$Q \equiv \begin{array}{l} 200 \mu\text{F} \\ 20\text{V} \end{array}$$

$$Q = CV = 4000 \mu\text{C}$$

$$\begin{aligned} U &= \frac{1}{2} CV^2 = \frac{1}{2} (200 \mu) (400) \\ &= 40,000 \mu\text{J} \\ &= \underline{0.04 \text{ J}} \end{aligned}$$

Case Battery Connected ($d \rightarrow 2d$)

① $C_0 = \frac{\epsilon_0 A}{d}$

$$C = \frac{\epsilon_0 A}{2d} = \frac{C_0}{2}$$

② V_0

$$V = V_0$$

③ $q_0 = C_0 V_0$

$$q = \frac{C_0}{2} V_0 = \frac{q_0}{2}$$

④ $U_0 = \frac{1}{2} C_0 V_0^2$

$$U = \frac{1}{2} \left(\frac{C_0}{2} \right) V_0^2 = \frac{U_0}{2}$$

⑤ $E_0 = \frac{V_0}{d}$

$$E = \frac{V_0}{2d} = \frac{E_0}{2}$$

⑥ $F_0 = \frac{q_0^2}{2\epsilon_0 A}$

$$F = \frac{F_0}{4}$$

① $C = \frac{C_0}{2}$

② $q = q_0$

③ $V = \frac{q_0}{(C_0/2)} = 2V_0$

④ $U = \frac{q_0^2}{2(C_0/2)} = 2U_0$

⑤ $E = \frac{V}{d} = E_0$

⑥ $F = F_0$

$$U_0 = \frac{q_0^2}{2C_0}$$

Case Battery connected



$$\textcircled{1} C_0 = \frac{\epsilon_0 A}{d}$$

$$\textcircled{2} V_0$$

$$\textcircled{3} q_0$$

$$\textcircled{4} U_0$$

$$\textcircled{5} E_0 = \frac{V_0}{d}$$



$$C = \frac{\epsilon_0 K A}{d} = K C_0$$

$$V = V_0$$

$$q_0 = (K C_0) V_0 = K q_0$$

$$U = \frac{1}{2} (K C_0) V_0^2 = K U_0$$

$$E = E_0$$

$$\textcircled{1} C = \frac{\epsilon_0 K A}{d} = K C_0$$

$$\textcircled{2} q = q_0$$

$$\textcircled{3} V = \frac{q_0}{K C_0} = \frac{V_0}{K}$$


$$\textcircled{4} U = \frac{q_0^2}{2 (K C_0)} = \frac{U_0}{K}$$

$$\textcircled{5} E = \frac{\sigma}{\epsilon_0 K} = \frac{E_0}{K}$$

$$\left(\frac{V_0 / K}{d} \right)$$

Combination of Capacitance

① Series Combination (Same charge)

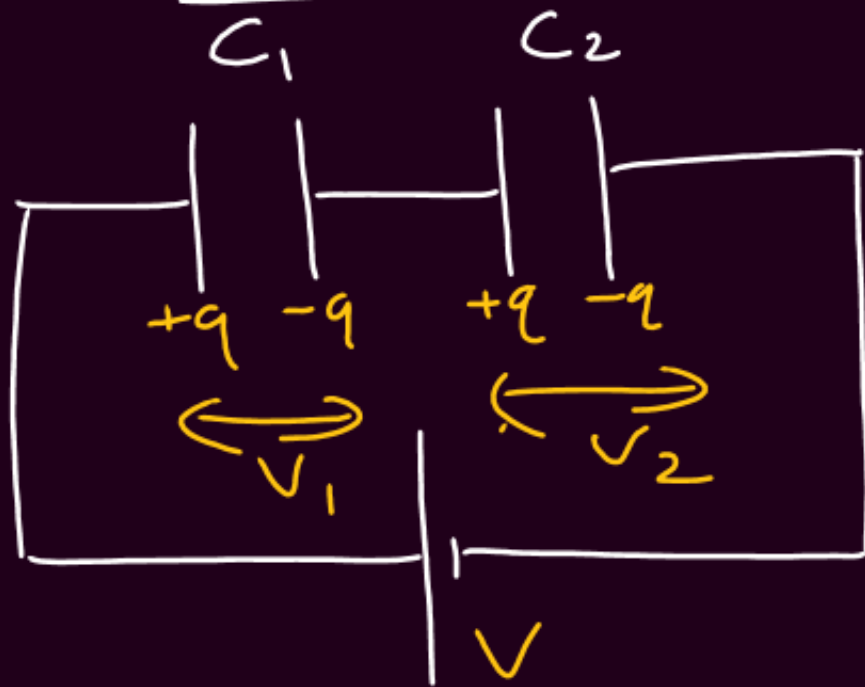

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$C_{eq} < C_1$$
$$C_{eq} < C_2$$

n-identical


$$C_{eq} = \frac{C}{n}$$

$$V = \frac{q}{C}$$

$$V_1 = \frac{V C_2}{C_1 + C_2}$$

$$V_2 = \frac{V C_1}{C_1 + C_2}$$

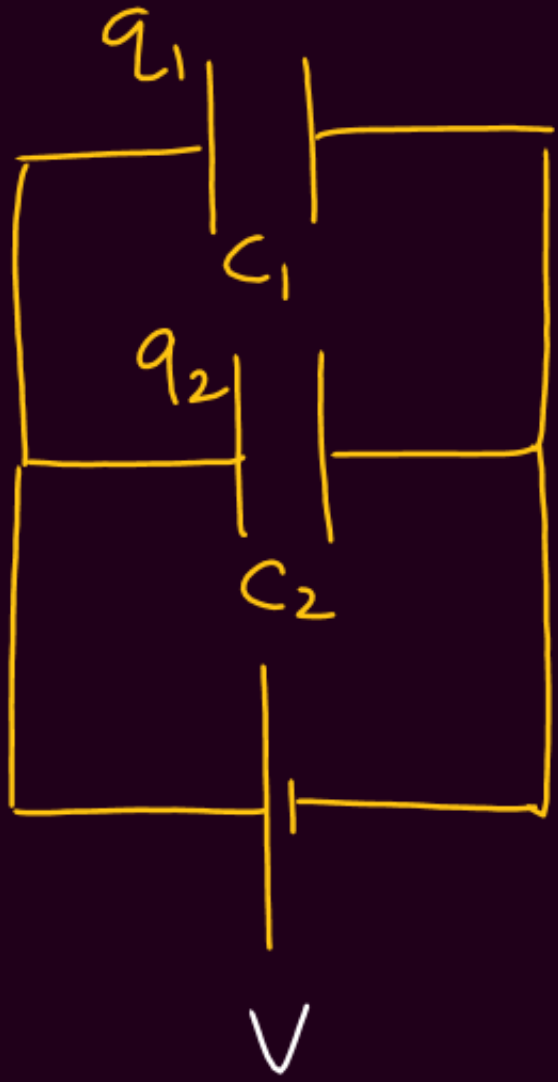② Parallel combination (P.D. is same)
(Voltage)



$$C_{eq} = C_1 + C_2$$


n -identical

$$C_{eq} = nC_0$$


$$q = CV$$

$$q_1 = \frac{q C_1}{C_1 + C_2}$$

$$q_2 = \frac{q C_2}{C_1 + C_2}$$


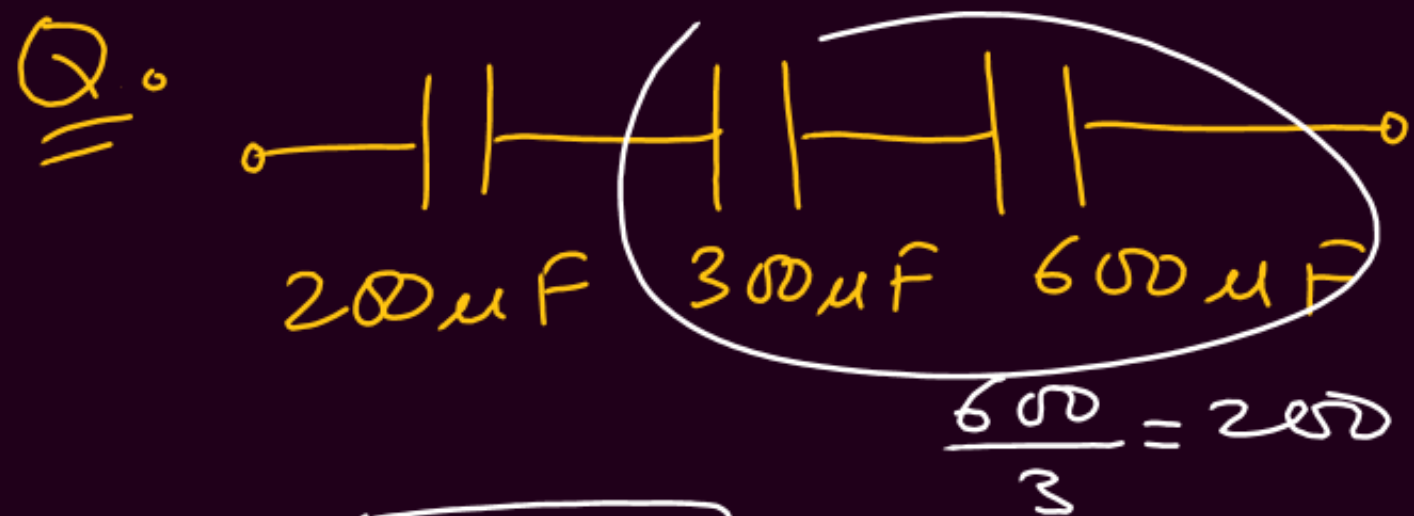


$100\mu F$

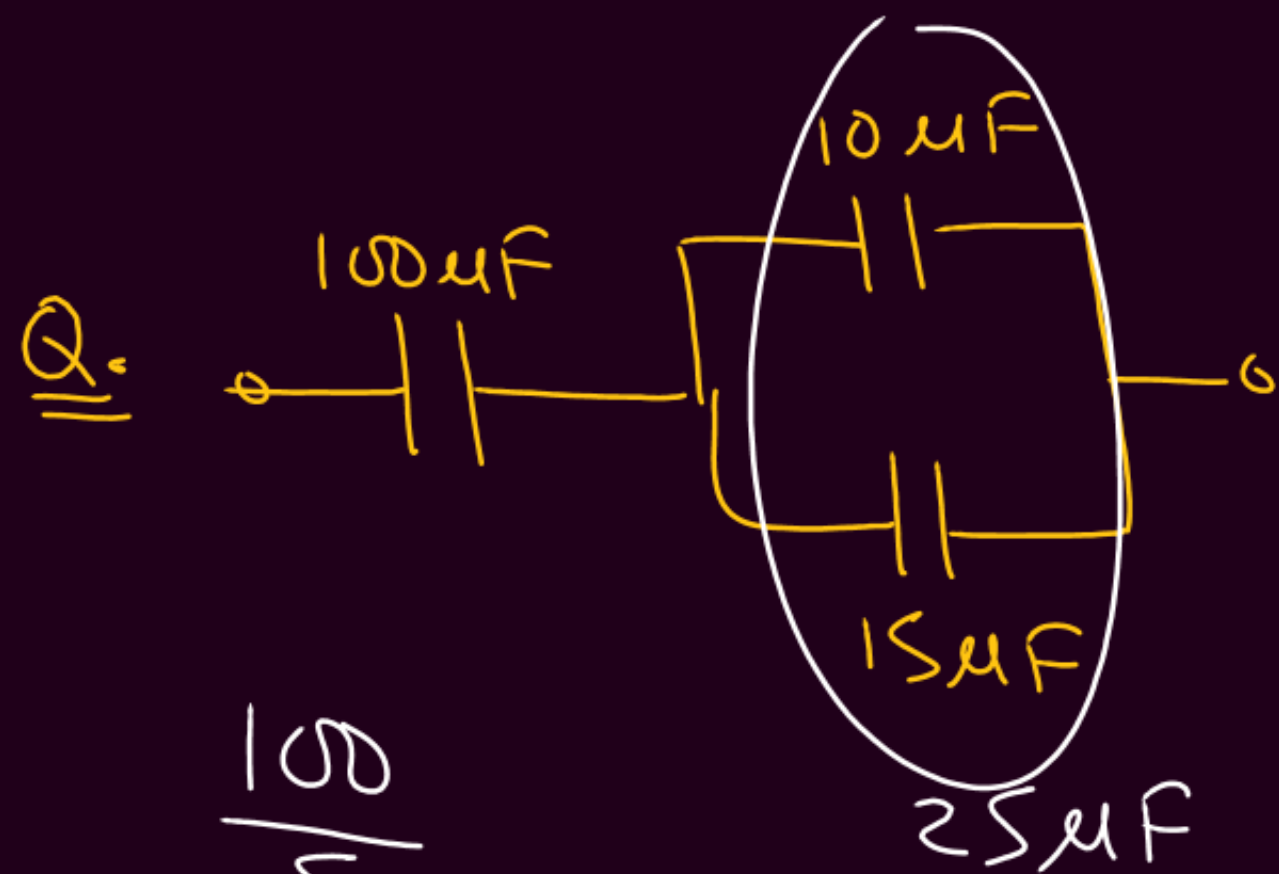


$$\frac{100}{5}$$


$$= 20\mu F$$

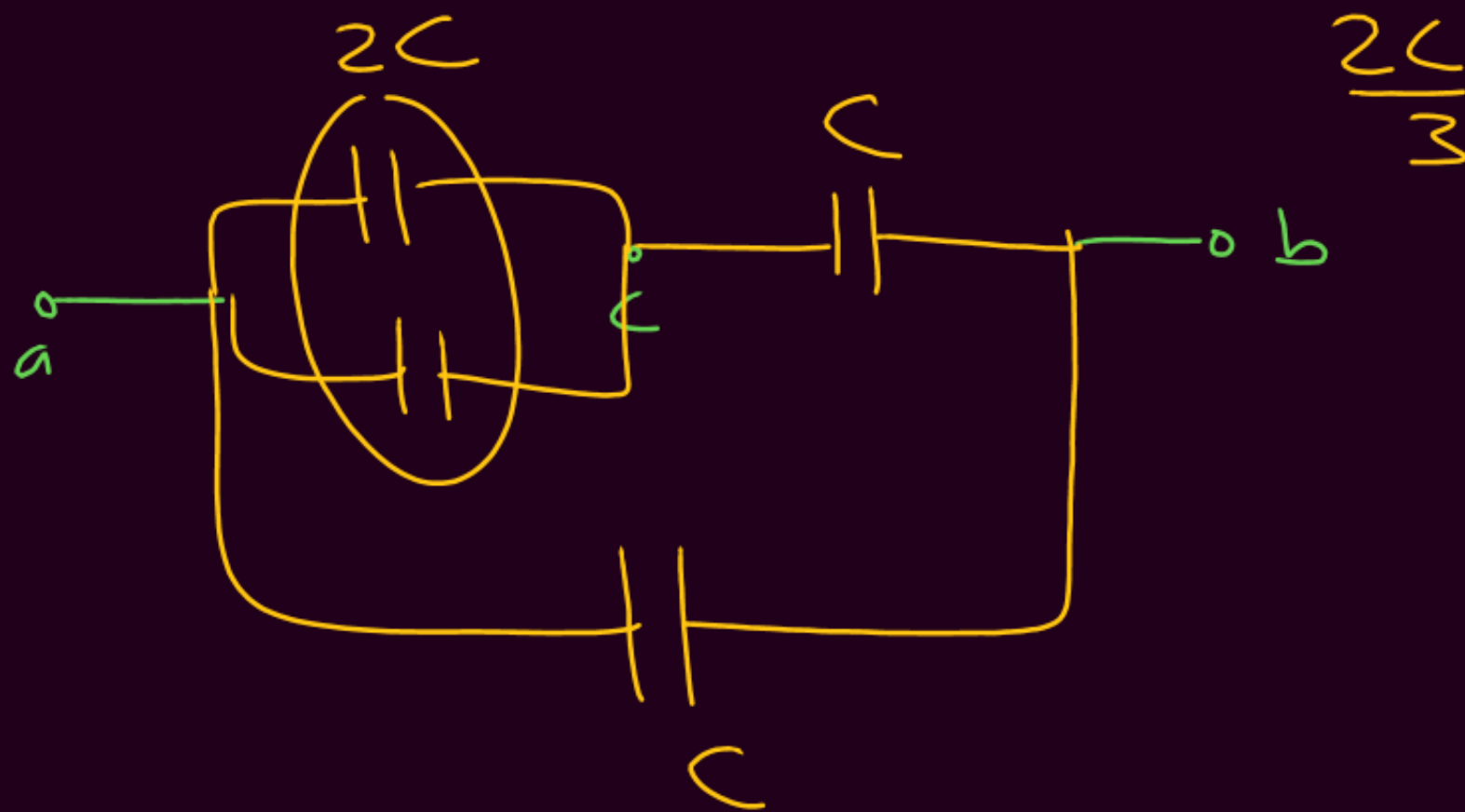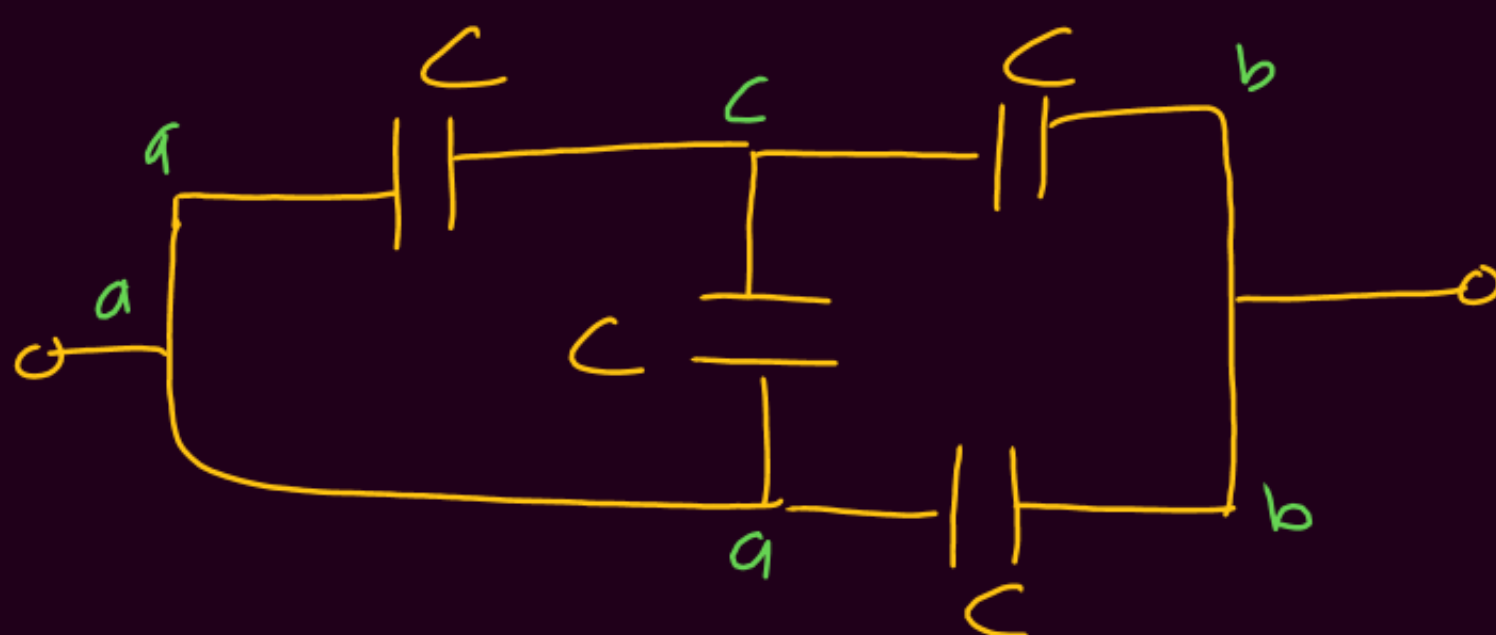
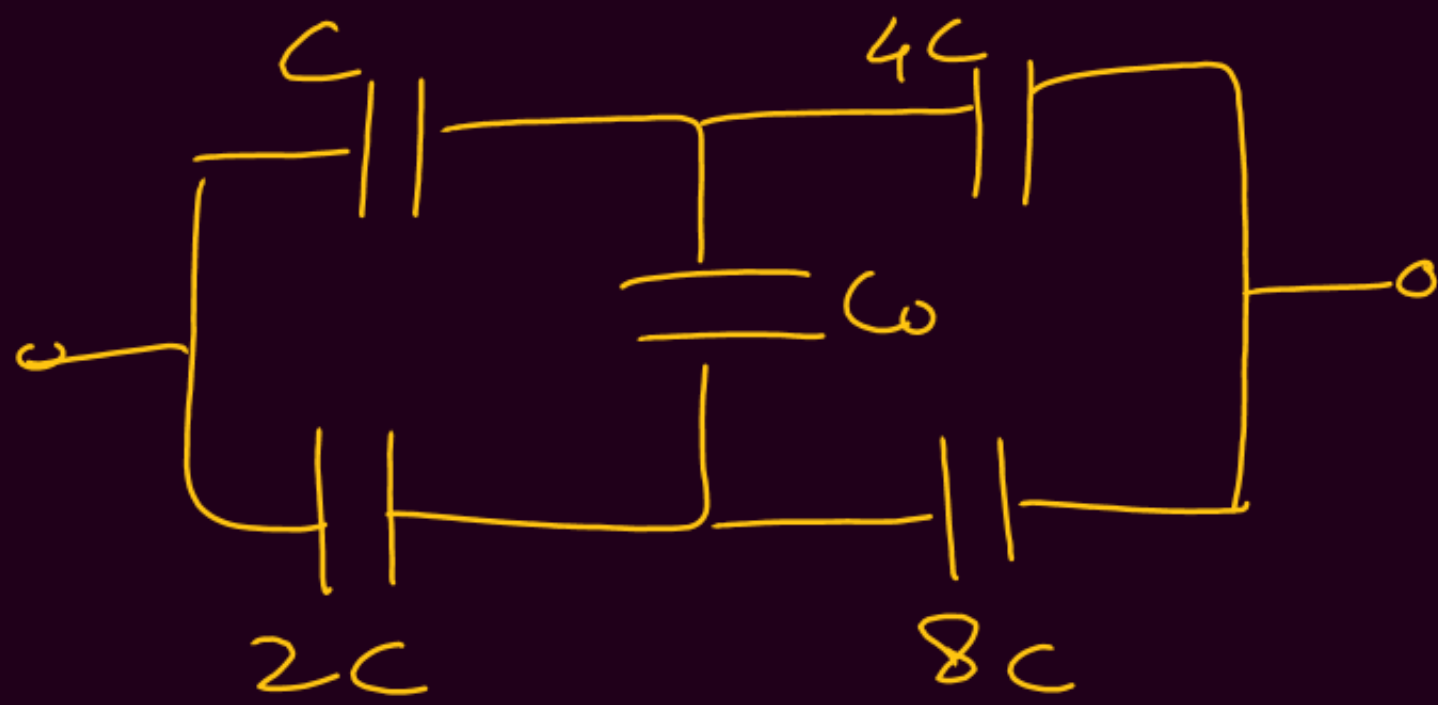
$$C_{eq} = \frac{2C}{3} + C = \frac{5C}{3}$$



B - WSR

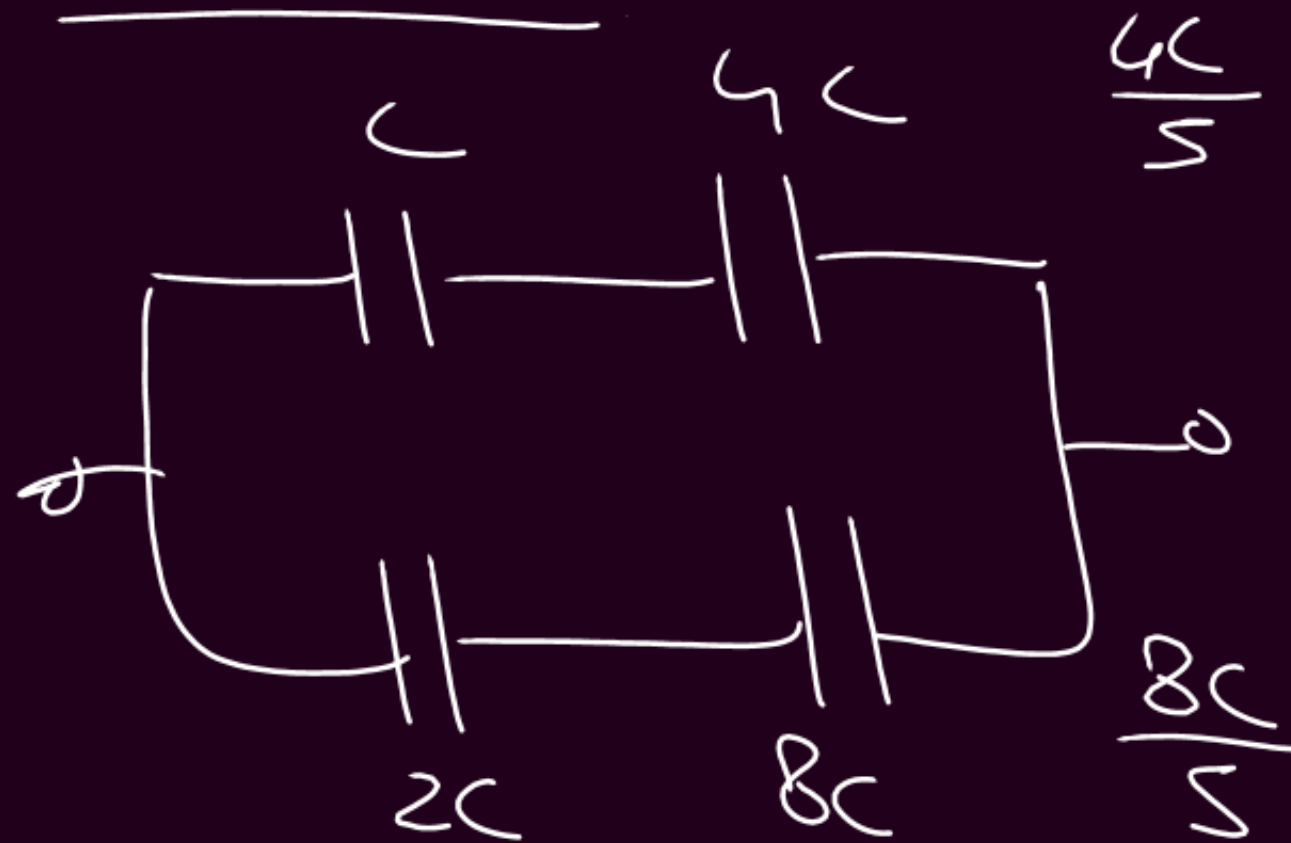

$$C_{eq} = \frac{4C}{5} + \frac{8C}{5} = \frac{12C}{5}$$

Q
100 μ F , 100V

200 μ F , 100V

Unlike polarities together

① Common P.D.

② Final charges

③ Loss of Energy

④ Δq

$$\textcircled{1} V_c = \frac{(200\mu)(100) - (100\mu)(100)}{200\mu + 100\mu} = \frac{100}{3} \text{V}$$

$$\textcircled{2} q_{1f} = C_1 V_c = (100\mu) \frac{100}{3} = \frac{10000}{3} \mu\text{C}$$

$$q_{2f} = C_2 V_c = (200\mu) \frac{100}{3} = \frac{20000}{3} \mu\text{C}$$


$$\textcircled{3} \text{Loss} = \frac{1}{2} \left(\frac{200\mu}{3} \right) (200)(200) = \frac{4}{3} \text{J}$$

④ 200 μ F

$$q_i = (200\mu)(100) = 20000 \mu\text{C}$$

$$q_f = (200\mu) \left(\frac{100}{3} \right) = \frac{20000}{3} \mu\text{C}$$
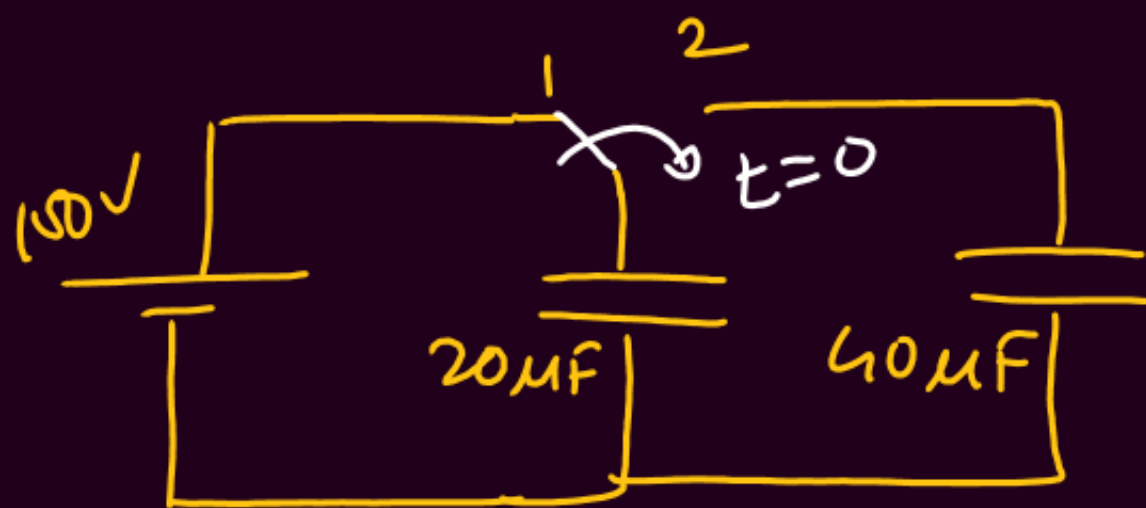
$$\Delta q = \frac{40000}{3} \mu\text{C}$$




$$V_c = \frac{(20\mu)(100) + 0}{20\mu + 40\mu} = \frac{100}{3} \text{ V}$$

$$q_{40} = (40\mu) \left(\frac{100}{3} \right) = \frac{4000}{3} \mu\text{C}$$


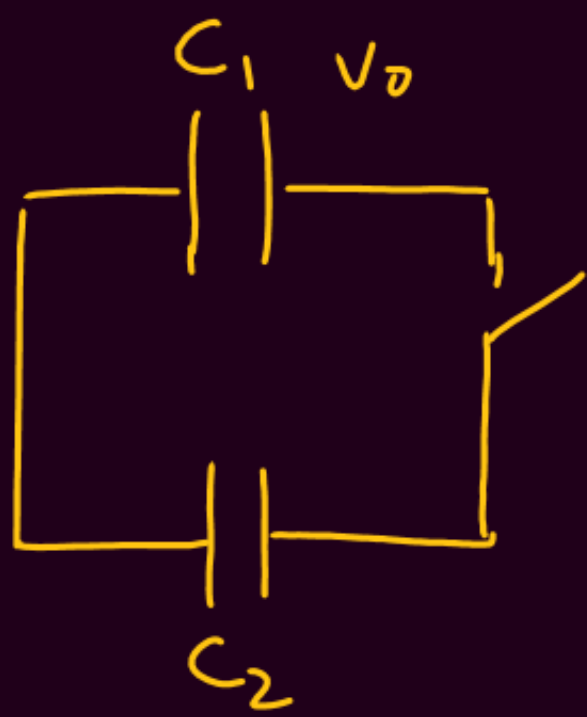
$$\text{fractional loss} = \frac{40\mu}{20\mu + 40\mu} = \frac{2}{3} = 0.67 = \underline{\underline{67\%}}$$





$$\text{fractional loss} = \frac{\text{Loss}}{\text{Initial}} = \frac{\frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_0 - 0)^2}{\frac{1}{2} C_1 V_0^2}$$

$$\text{fractional loss} = \frac{C_2}{C_1 + C_2}$$

Spherical Capacitor



$$\textcircled{1} \quad V = \frac{Q}{4\pi\epsilon_0 R}$$


$$\textcircled{2} \quad C = \frac{Q}{V}$$

$$C = 4\pi\epsilon_0 R$$

Extra



$$C = \frac{4\pi\epsilon_0 ab}{b-a}$$

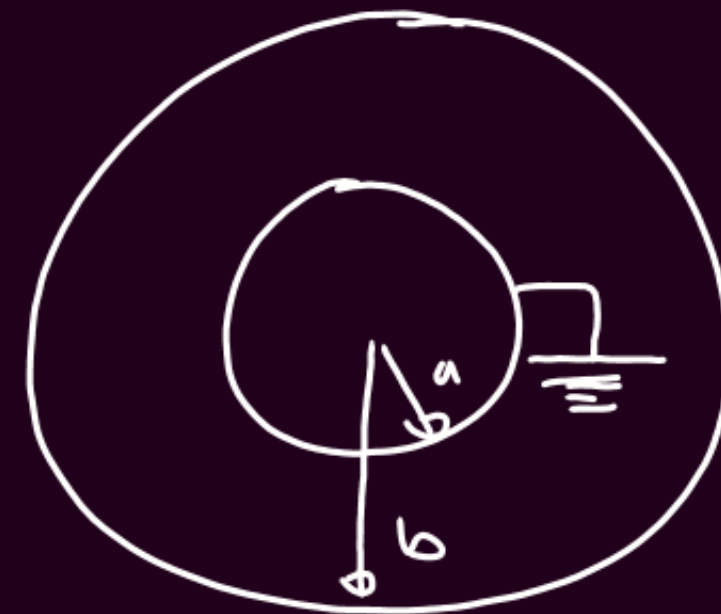

$$C = \frac{4\pi\epsilon_0 b^2}{b-a}$$



$$C = 4\pi\epsilon_0 (a+b)$$

Capacitance of Earth

$$R = 6400 \text{ km}$$

$$C = 4\pi\epsilon_0 R$$

$$C = \frac{6400 \times 10^3}{9 \times 10^9}$$

$$C = 7.11 \times 10^{-4} \text{ F}$$

$$C = 711 \text{ } \mu\text{F}$$

$$\frac{1}{4\pi\epsilon_0} = 9 \times 10^9$$

to form a bigger drop

$$C_0 = 4\pi\epsilon_0 r$$

$$C = 4\pi\epsilon_0 R = 4\pi\epsilon_0 (n^{1/3}) r$$

$$V_0 = \frac{q_0}{4\pi\epsilon_0 r}$$

$$V = \frac{(n) q_0}{4\pi\epsilon_0 (n^{1/3}) r}$$

$$(27)^{1/3} = 3$$

$$(64)^{1/3} = 4$$

$$(1000)^{1/3} = 10$$

$$(27)^{2/3} = (3)^2 = 9$$

1000 drops (identical) } Coalesce
each 10 μ F & 20V


$$C_{\text{new}} = (1000)^{1/3} (10 \mu\text{F}) = 100 \mu\text{F}$$


$$V_{\text{new}} = (1000)^{2/3} (20) = \underline{2000\text{V}}$$

1) A & C are touched & separated

2) B & C ——— " ———

3) A & B ——— " ———

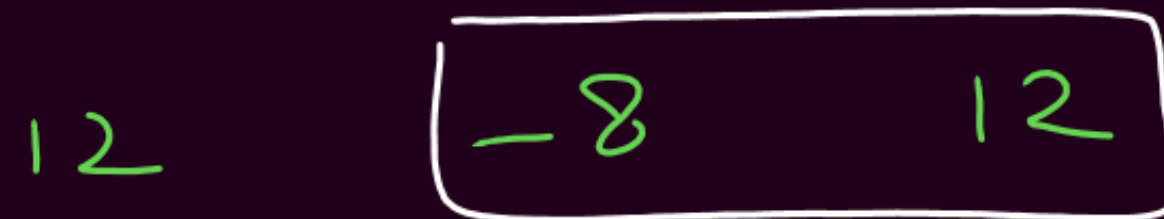

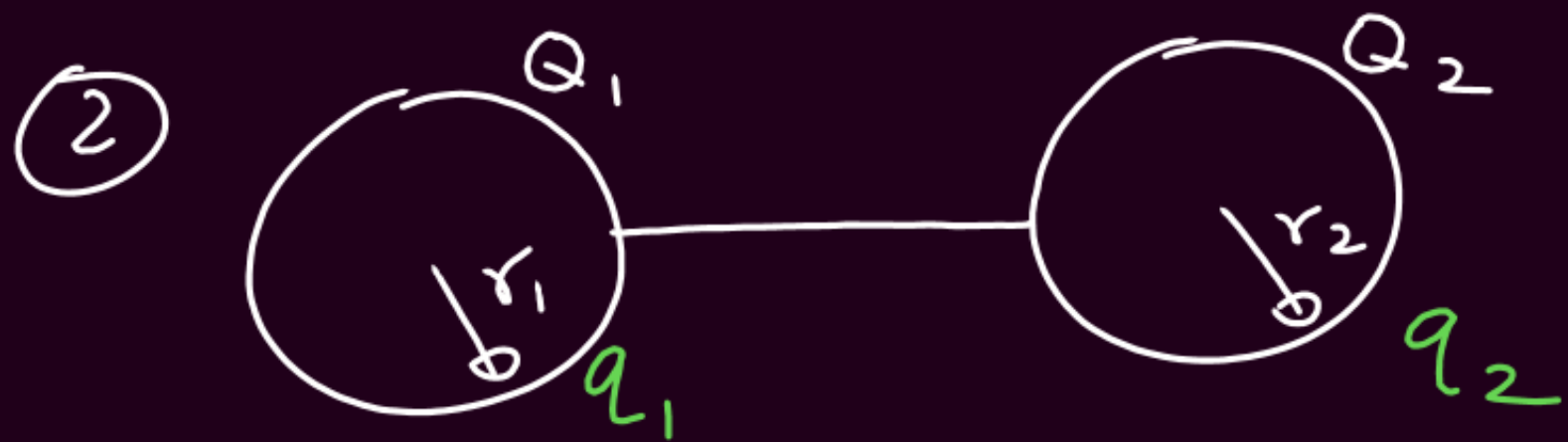

① Finally $\frac{q_1}{4\pi\epsilon_0 r_1} = \frac{q_2}{4\pi\epsilon_0 r_2}$

② Conservation of Charge

$$q_1 + q_2 = Q_1 + Q_2$$

$$\sigma_1 = \frac{q_1}{4\pi r_1^2}$$


$$\frac{\sigma_1 r_1^2}{r_1} = \frac{\sigma_2 r_2^2}{r_2}$$

Same Potential

$$\frac{q_1}{r_1} = \frac{q_2}{r_2}$$

$$\sigma_1 r_1 = \sigma_2 r_2$$

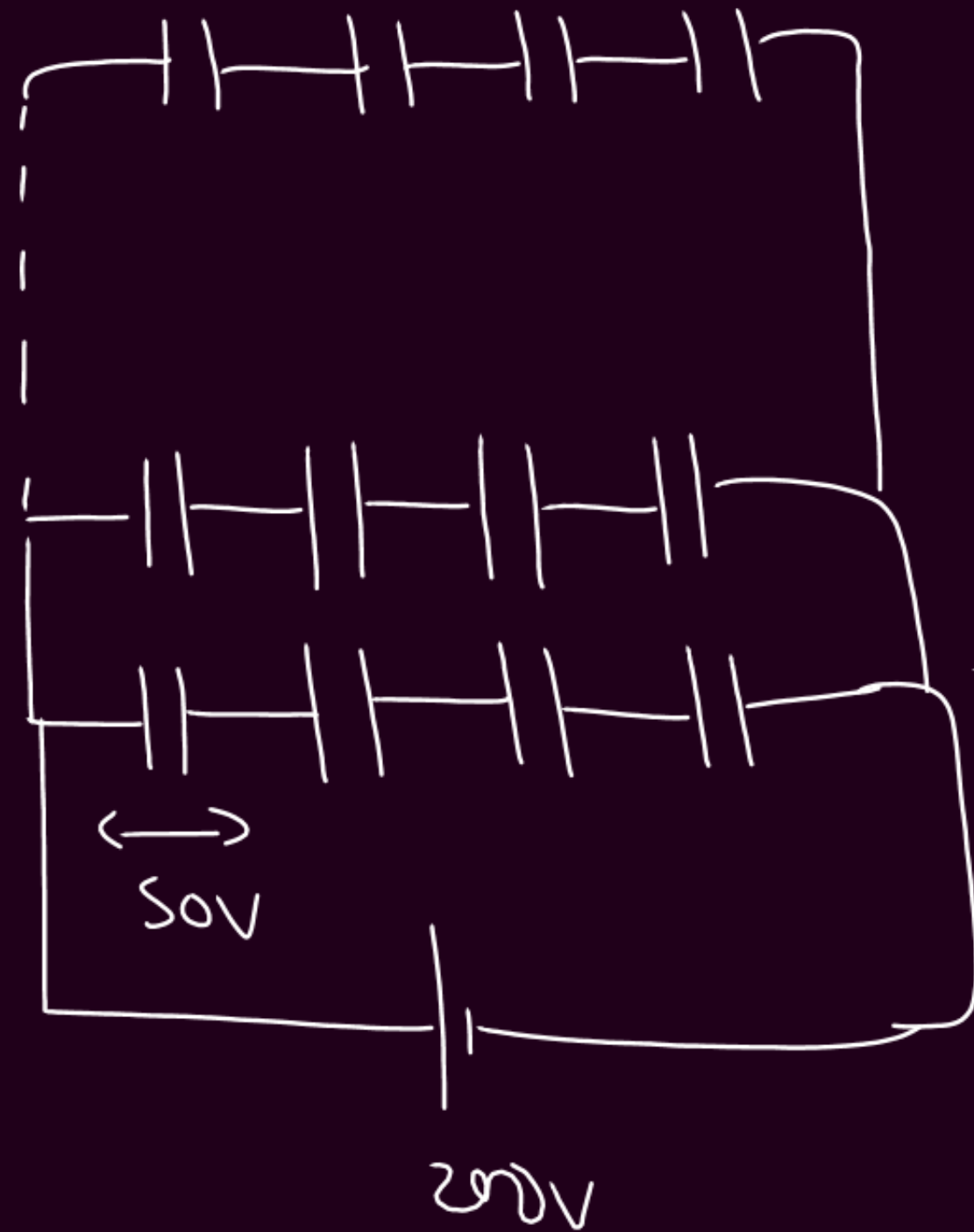Q $[100\mu F, 50V]$ withstand
 $[200\mu F, 200V]$ req



$$n(25) = 200\mu F$$


$$n = 8 \text{ rows}$$

4 in a row

Total 32

$$\frac{100\mu}{4} = 25\mu F$$

Dielectric

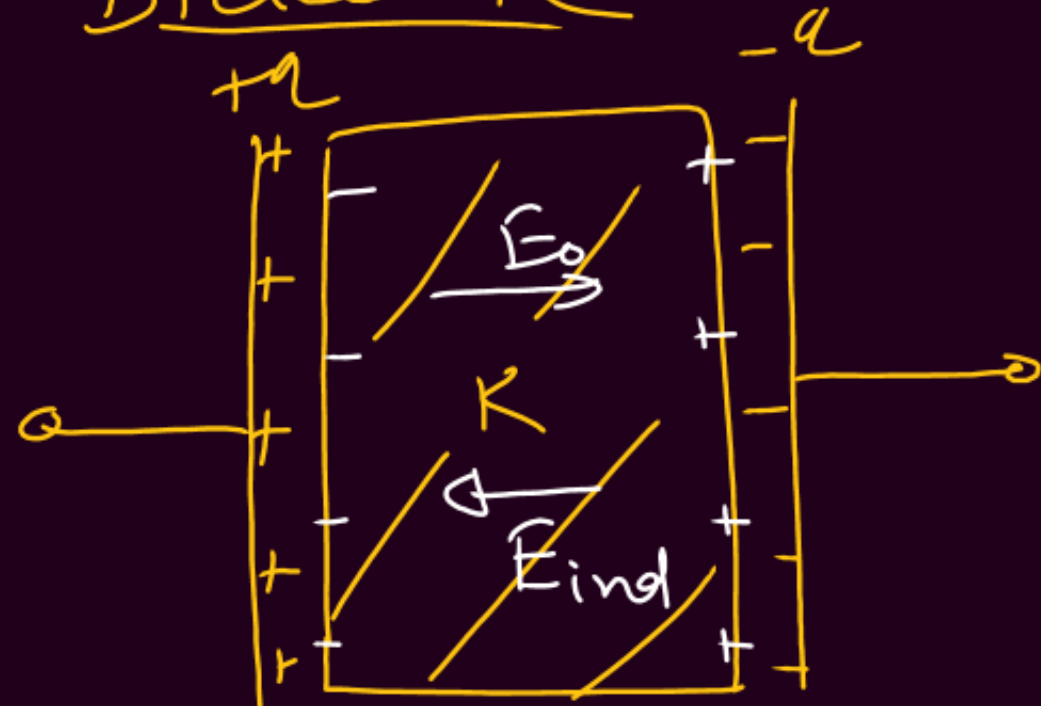

① Field in Air = $E_0 = \frac{\sigma}{\epsilon_0} = \frac{q}{\epsilon_0 A}$

② Field in med. = $E_{net} = \frac{E_0}{K}$

$$\vec{E}_{net} = \vec{E}_0 + \vec{E}_{ind}$$

$$\frac{E_0}{K} = E_0 + E_{ind}$$

$$E_{ind} = -E_0 + \frac{E_0}{K}$$


$$\vec{E}_{ind} = -\vec{E}_0 \left(1 - \frac{1}{K}\right)$$


$$q_{ind} = -q \left(1 - \frac{1}{K}\right)$$

①  $C = \frac{\epsilon_0 A}{d}$


②  $C = \frac{\epsilon_0 K A}{d}$

③  $C = \frac{\epsilon_0 (K_1 A_1 + K_2 A_2 + K_3 A_3)}{d}$

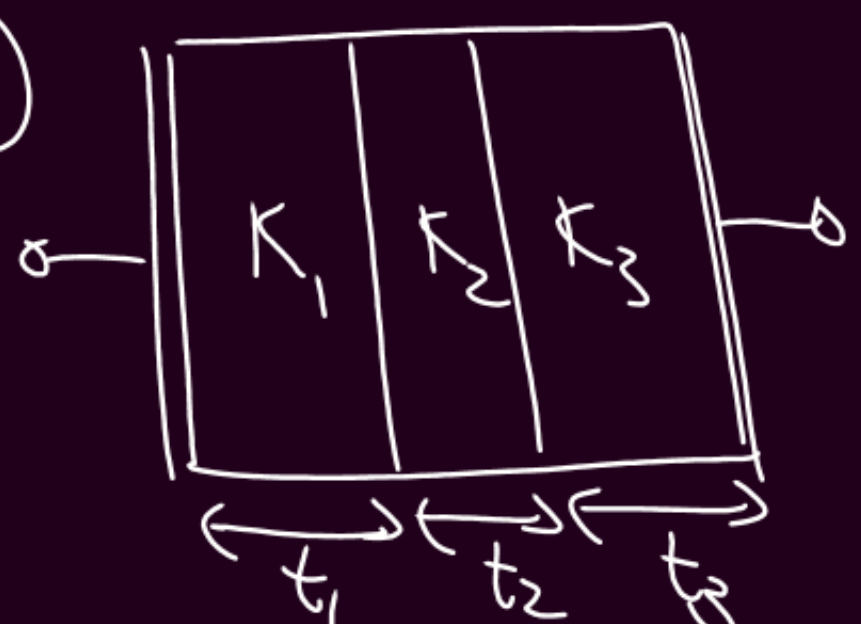
④  $C = \frac{\epsilon_0 A}{\left(\frac{t_1}{K_1} + \frac{t_2}{K_2} + \frac{t_3}{K_3} \right)}$

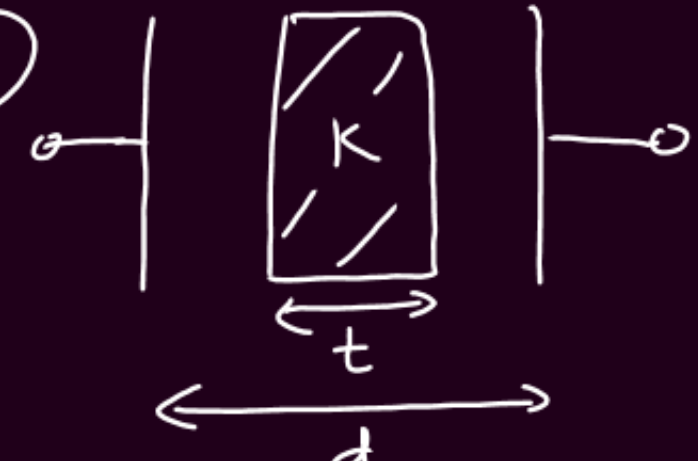⑤  $C = \frac{\epsilon_0 A}{(d-t) + \frac{t}{K}}$


⑥ Thick metal Plate

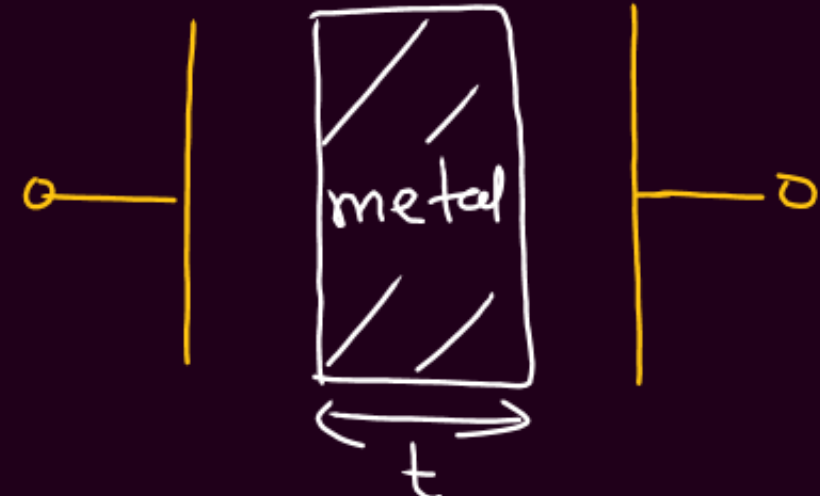 $C = \frac{\epsilon_0 A}{d-t}$

⑦ Thin metal plate

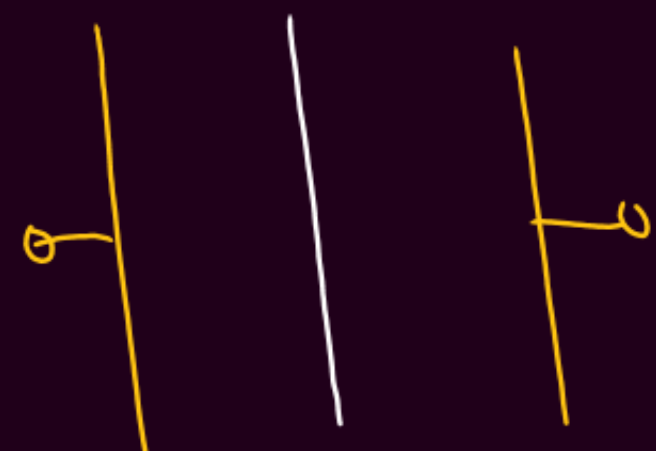 $C = \frac{\epsilon_0 A}{d}$


Q.

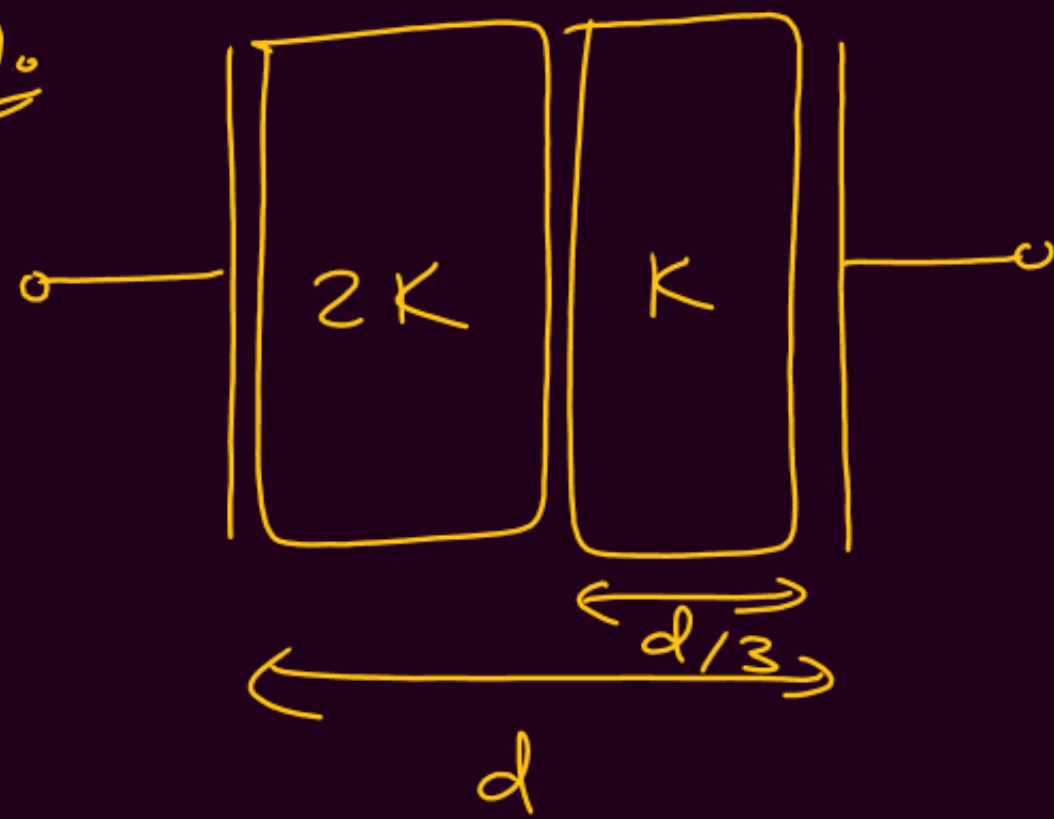

$$C = \frac{\epsilon_0 A}{\frac{2d}{3(2K)} + \frac{d}{3(K)}}$$

$$C = \frac{3\epsilon_0 K A}{2d}$$

Q.

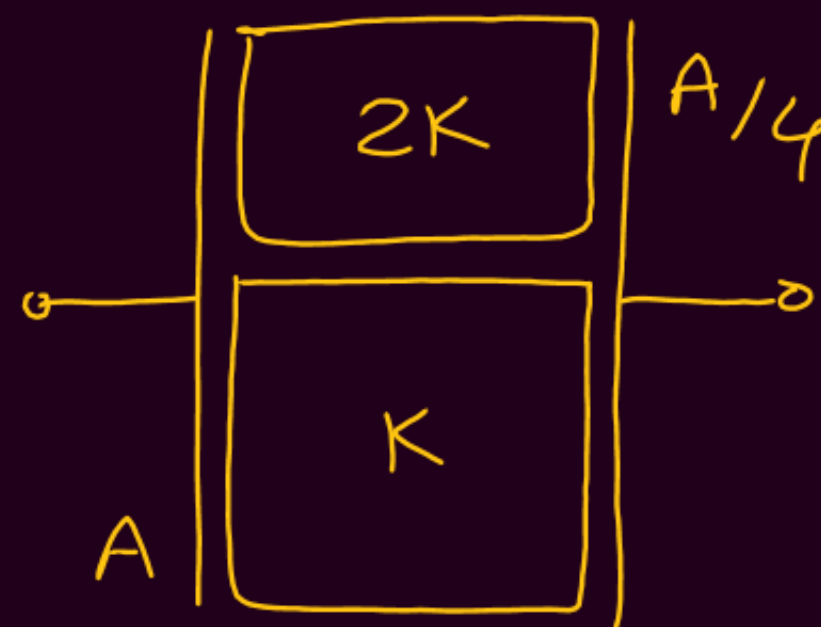

$$C = \frac{\epsilon_0 \left[2K \left(\frac{A}{4} \right) + K \left(\frac{3A}{4} \right) \right]}{d}$$

$$C = \frac{5\epsilon_0 K A}{4d}$$

Q.

$$4\mu F = \frac{\epsilon_0 A}{5}$$


$$6\mu F = \frac{\epsilon_0 A}{(5-2) + \frac{2}{K}}$$



$$6 = \frac{20}{3 + \frac{2}{K}}$$

$$18 + \frac{12}{K} = 20$$


$$\frac{12}{K} = 2$$

$$\boxed{K=6}$$

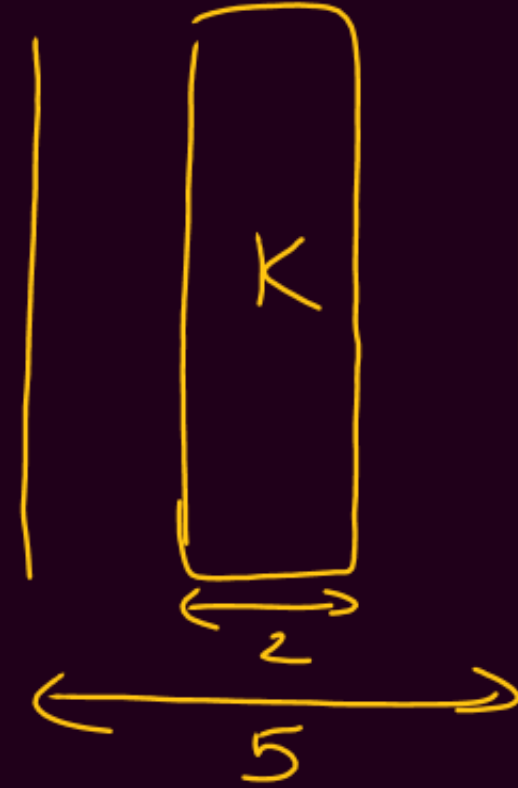

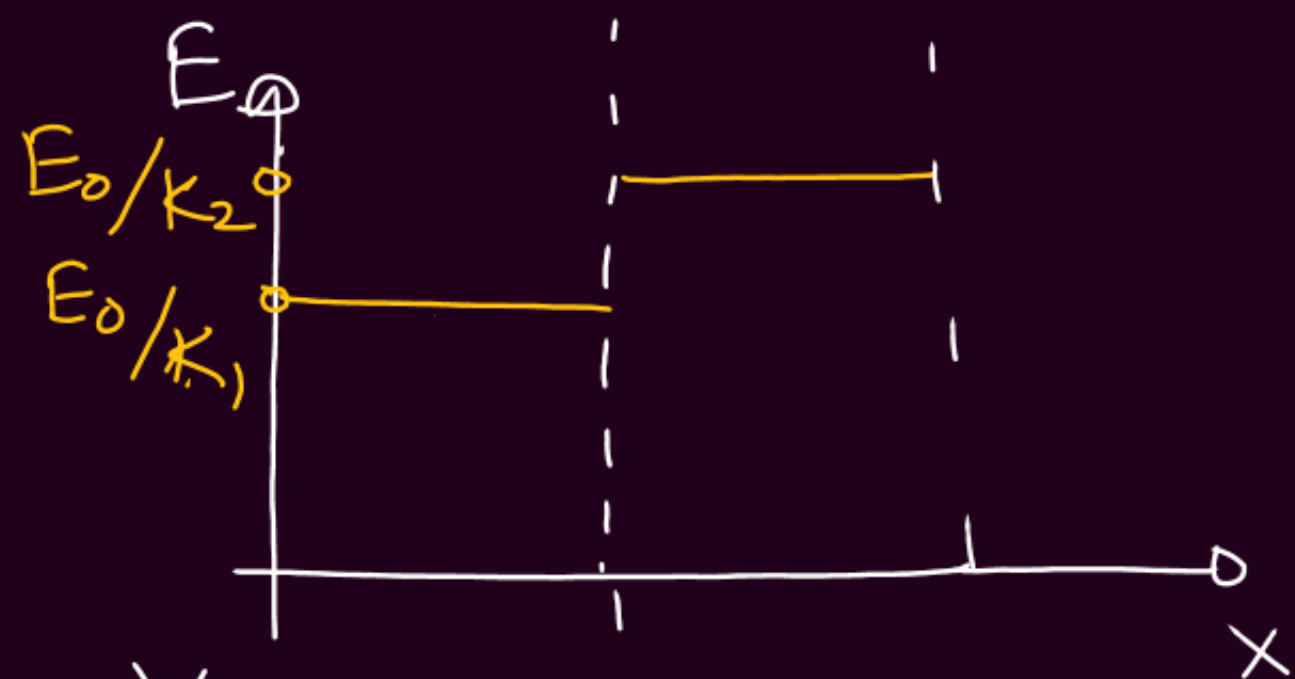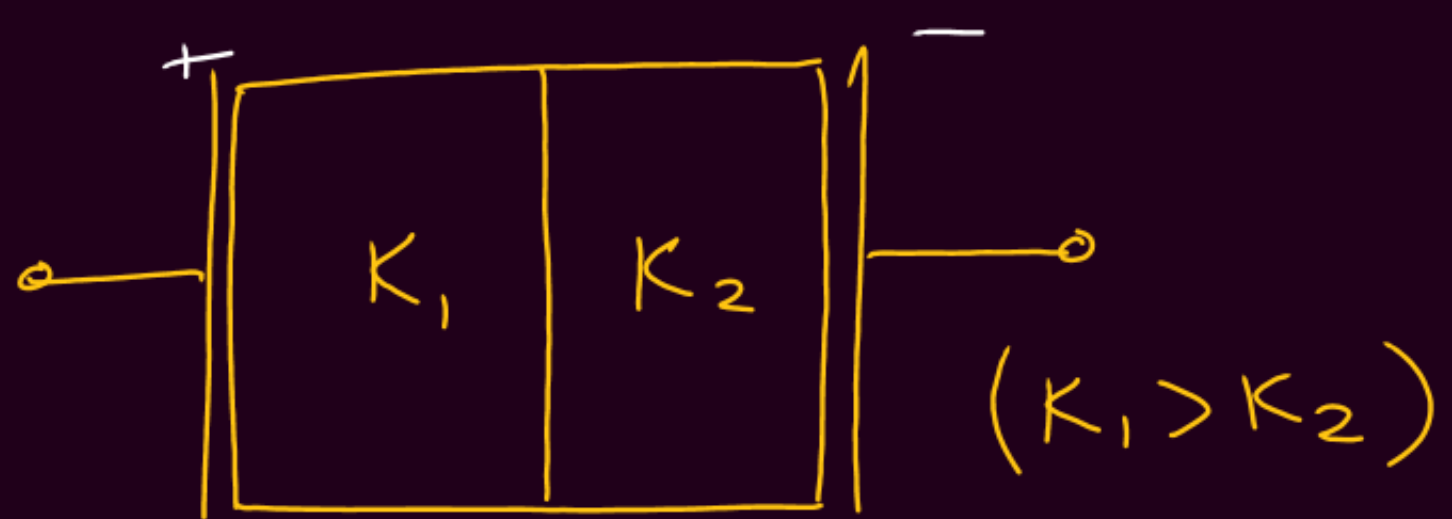


$$E = \frac{E_0}{K}$$

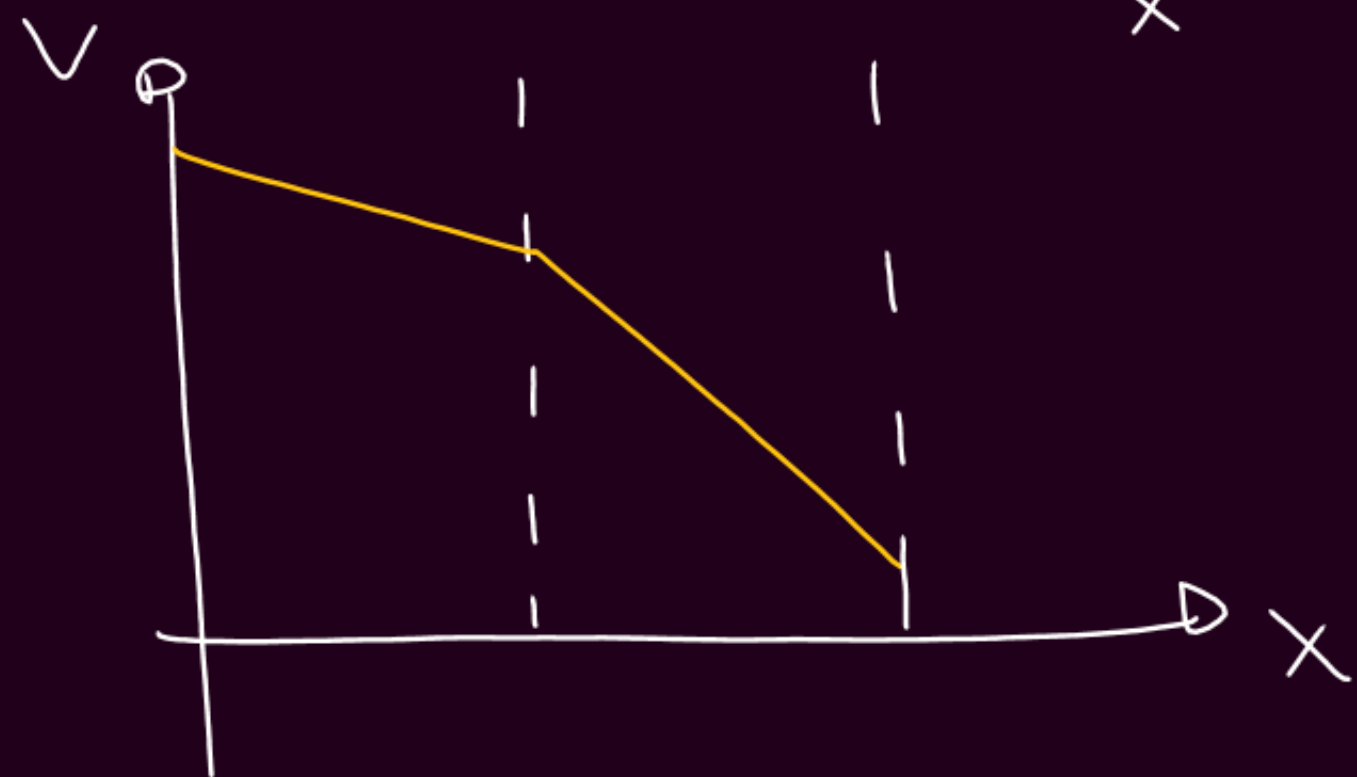

$$E = -\frac{dV}{dx}$$


Key
① Series

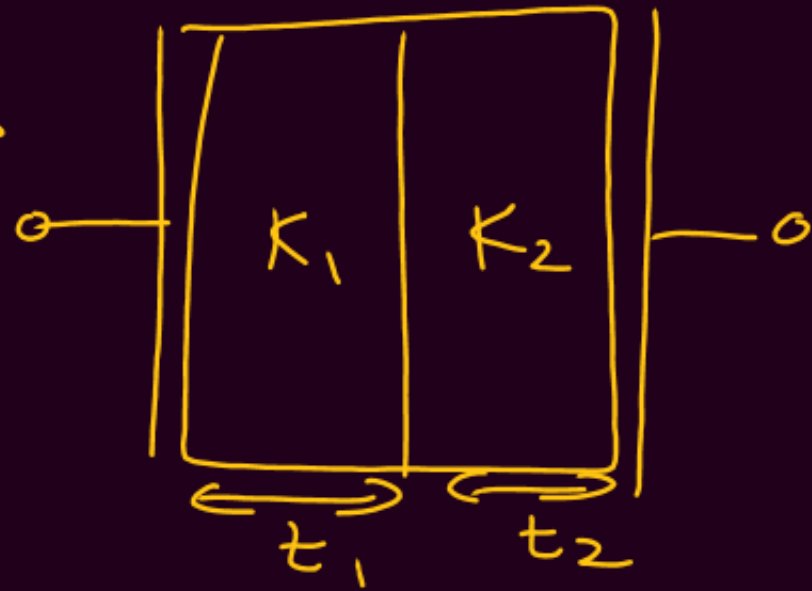

$$\frac{\epsilon_0 K_{eq} A}{t_1 + t_2} = \frac{\epsilon_0 A}{\frac{t_1}{K_1} + \frac{t_2}{K_2}}$$


$$K_{eq} = \frac{t_1 + t_2}{\frac{t_1}{K_1} + \frac{t_2}{K_2}}$$

② Parallel

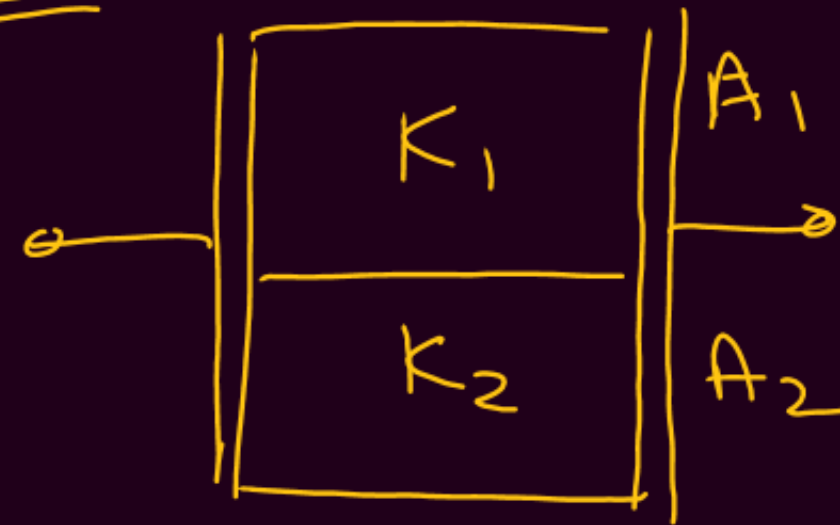


$$\frac{\epsilon_0 K_{eq} (A_1 + A_2)}{d} = \frac{\epsilon_0 (K_1 A_1 + K_2 A_2)}{d}$$
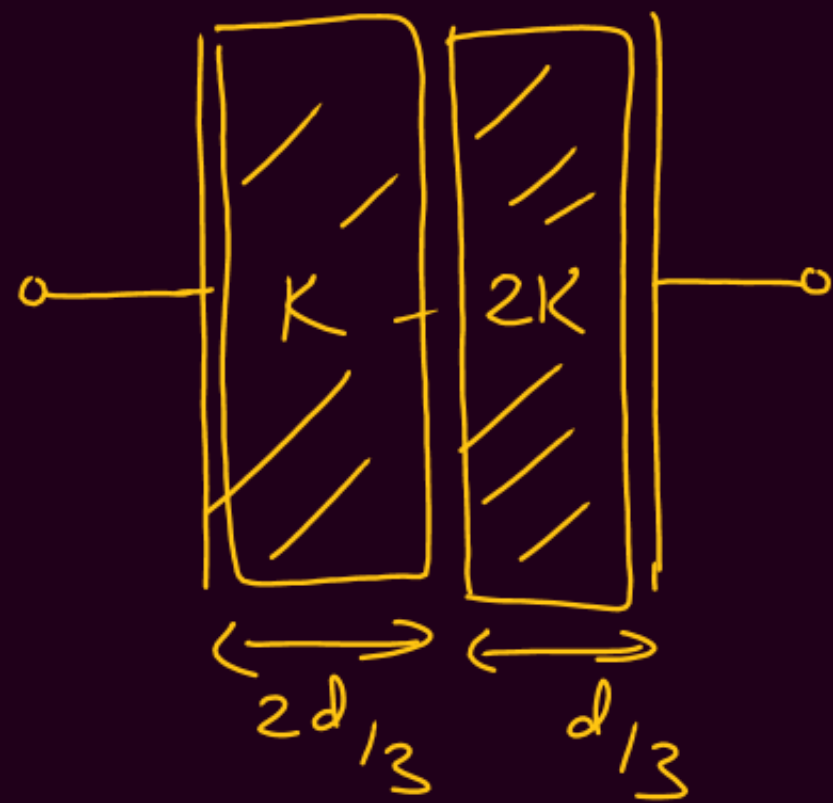
$$K_{eq} = \frac{K_1 A_1 + K_2 A_2}{A_1 + A_2}$$




$$\frac{\epsilon_0 K_{eq} A}{d} = \frac{\epsilon_0 A}{\frac{2d/3}{K} + \frac{d/3}{2K}}$$
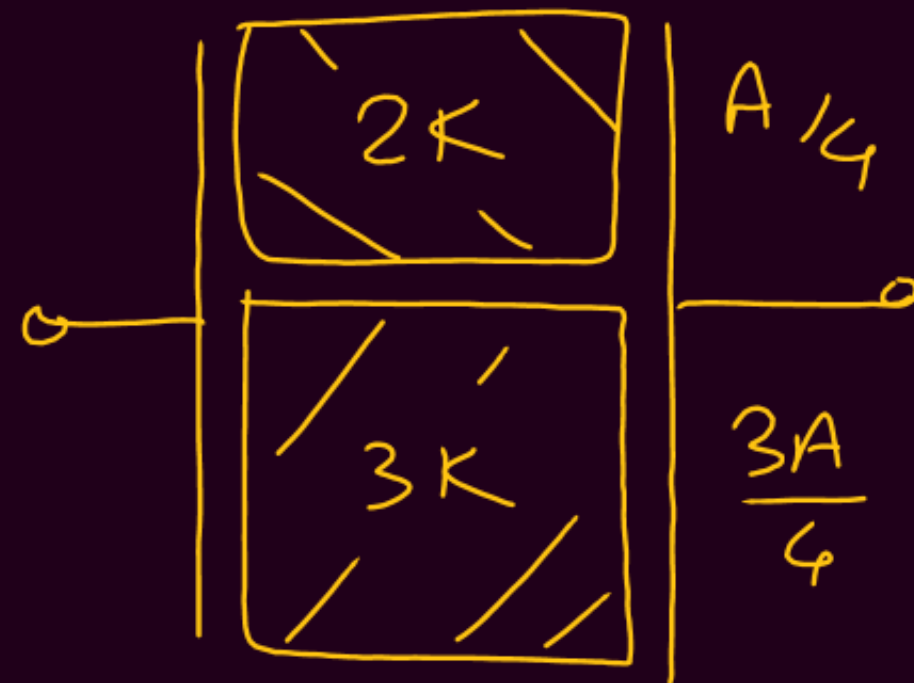
$$K_{eq} = \frac{K}{\frac{2}{3} + \frac{1}{6}} = \frac{6K}{5}$$



$$\frac{\epsilon_0 K_{eq} A}{d} = \frac{\epsilon_0 \left(2K \frac{A}{4} + 3K \frac{3A}{4} \right)}{d}$$

$$K_{eq} = \frac{11}{4} K$$

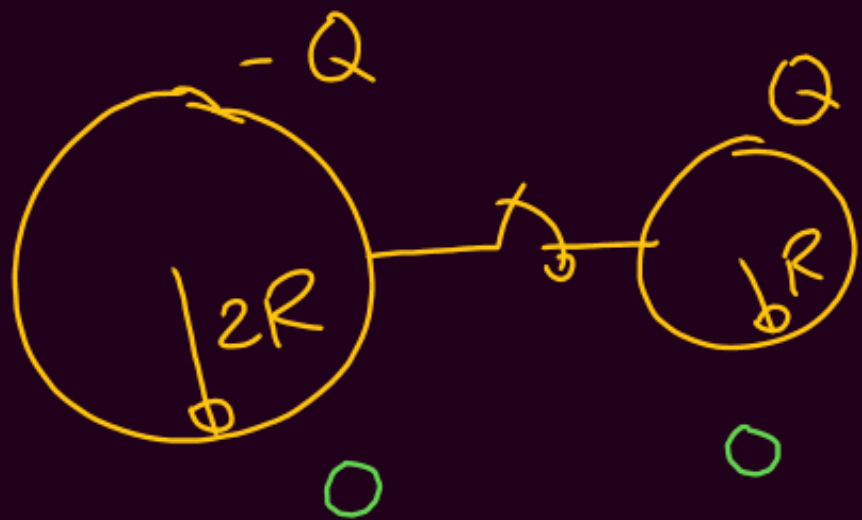

①

$$\frac{q_1}{2R} = \frac{q_2}{R}$$

$$q_1 = 2q_2$$


②


$$q_1 + q_2 = 2Q + (-Q)$$

$$2q_2 + q_2 = Q$$

$$q_2 = \frac{Q}{3}$$

$$q_1 = \frac{2Q}{3}$$

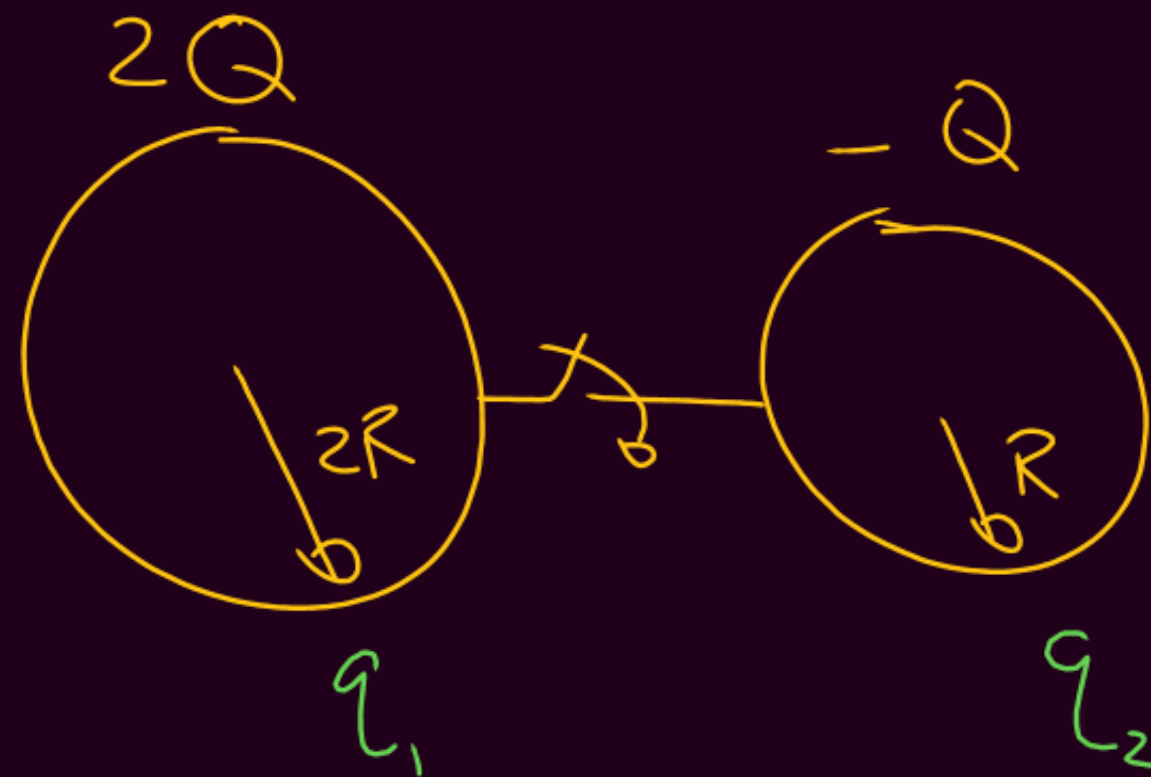

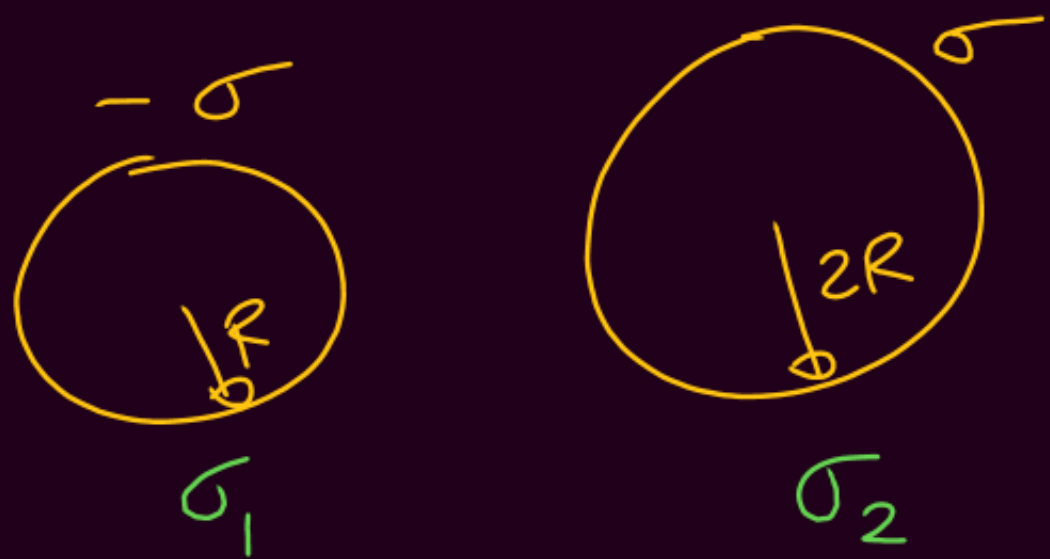

$$\textcircled{1} \quad \sigma_1 R = \sigma_2 (2R)$$

$$\boxed{\sigma_1 = 2\sigma_2}$$

$$\textcircled{2} \quad \sigma_1 (4\pi R^2) + \sigma_2 4\pi (2R)^2 = -\sigma (4\pi R^2) + \sigma 4\pi (2R)^2$$

$$\sigma_1 + 4\sigma_2 = -\sigma + 4\sigma$$

$$2\sigma_2 + 4\sigma_2 = 3\sigma$$


$$6\sigma_2 = 3\sigma$$

$$\boxed{\sigma_2 = \frac{\sigma}{2}}$$

$$\boxed{\sigma_1 = \sigma}$$

R-C Circuit (Extra)

① Charging of Capacitor

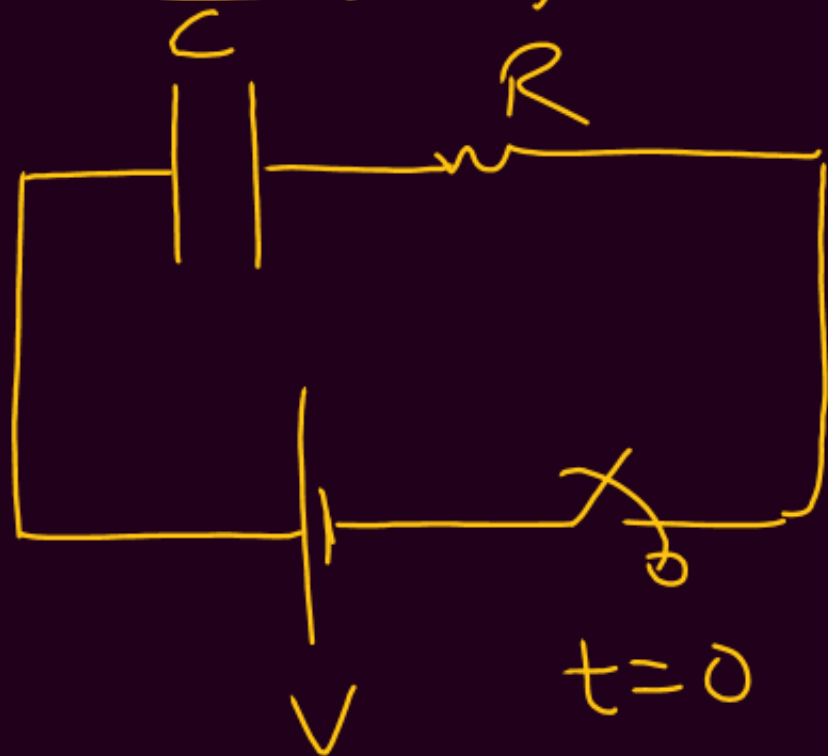


$$① \quad V = \left(\frac{q}{C} \right) + iR$$

$$② \quad \text{Time Constant} \quad \boxed{\tau = RC}$$

$$⑤ \quad \frac{1}{2} CV^2 = \text{Heat}$$

③ Initially ($t=0$)

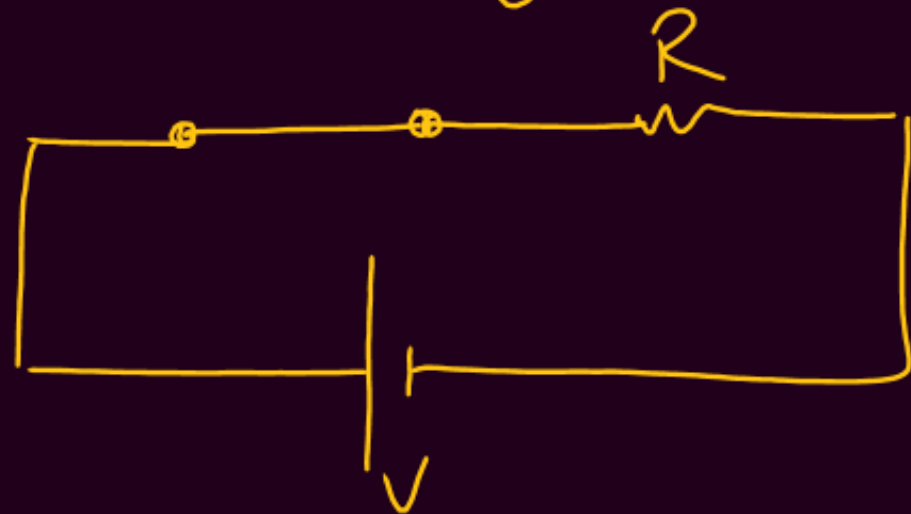

$$q=0$$

$$i_{\max} = \frac{V}{R}$$



④ Finally ($t \rightarrow \infty$)



$$q_{\max} = CV$$

$$i=0$$

⑥

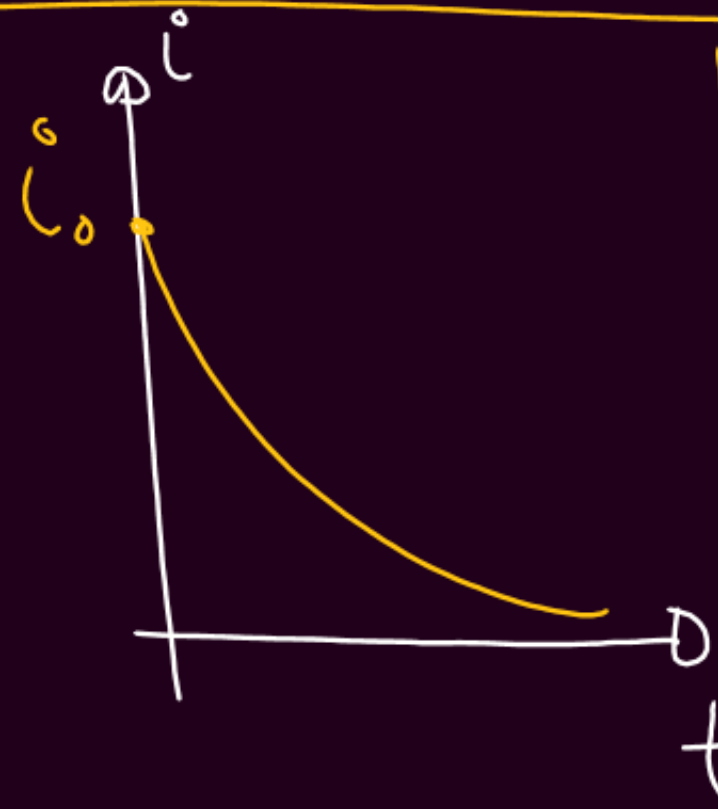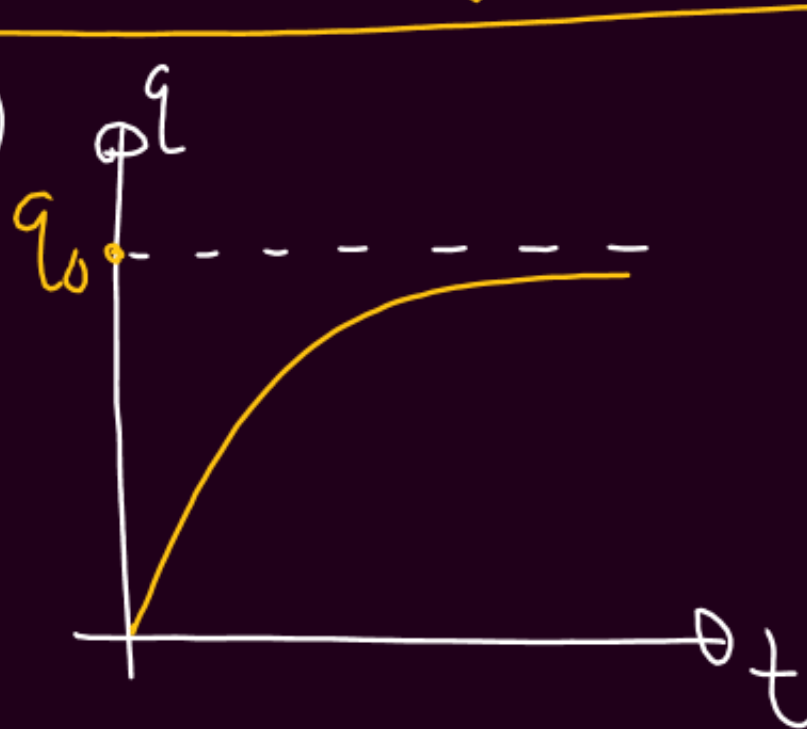


⑦ Half Life

$$t_{1/2} = \tau \ln(2)$$

$$\boxed{t_{1/2} = (0.7) \tau}$$

Q.

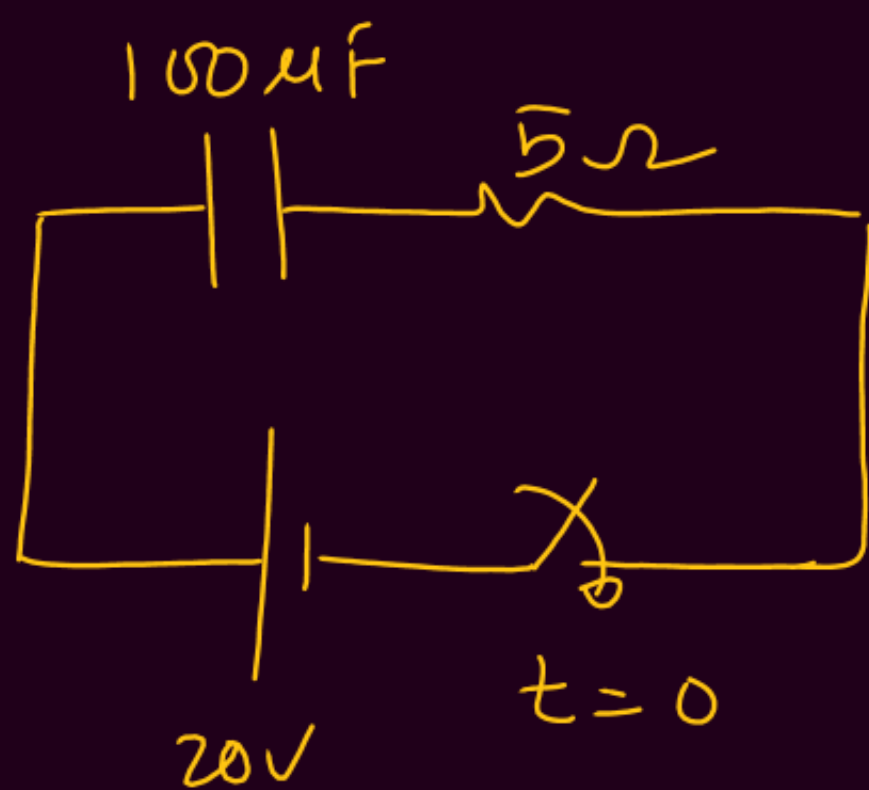

$$\textcircled{1} \tau = 5(100\mu) = 500\mu s = 0.5 \text{ ms}$$

$$\textcircled{2} i_{\max} = \frac{V}{R} = \frac{20}{5} = 4 \text{ A}$$

$$\textcircled{3} q_{\max} = CV = (100\mu)(20) = \underline{2000\mu C}$$

$$\textcircled{4} q = ? \quad \text{when } i = 3 \text{ A}$$

KVL

$$V = \frac{q}{C} + iR$$

$$20 = \frac{q}{100\mu} + (3)(5)$$

$$5 = \frac{q}{100\mu}$$

$$\boxed{q = 500\mu C}$$





$$\textcircled{5} i = ? \quad \text{when } q = 1200\mu C$$

$$20 = \frac{1200\mu}{100\mu} + i(5)$$

$$8 = i(5)$$

$$i = \frac{8}{5} = 1.6 \text{ A}$$

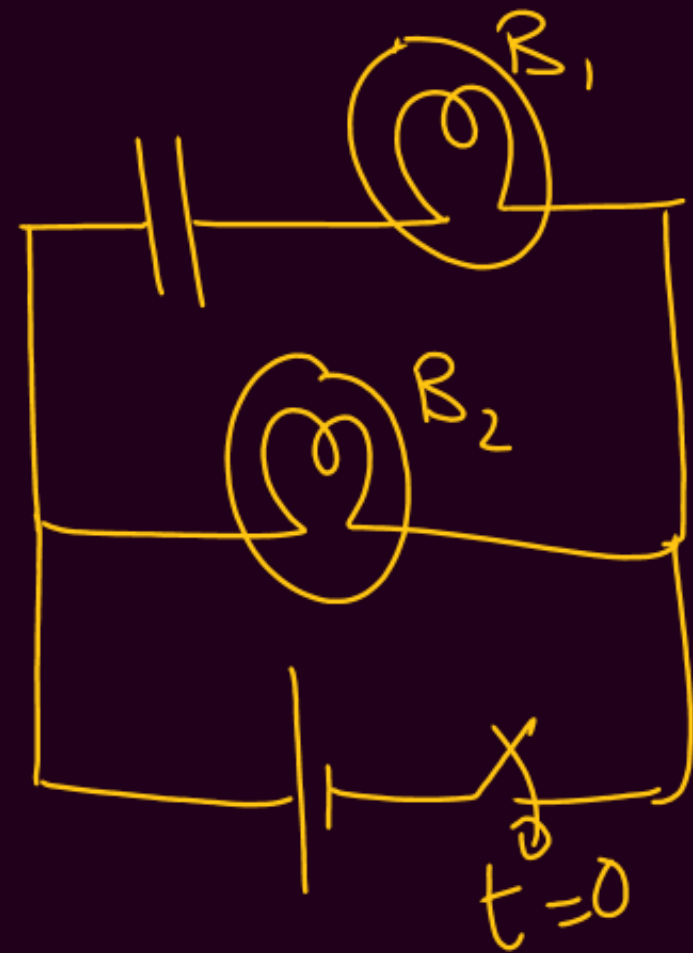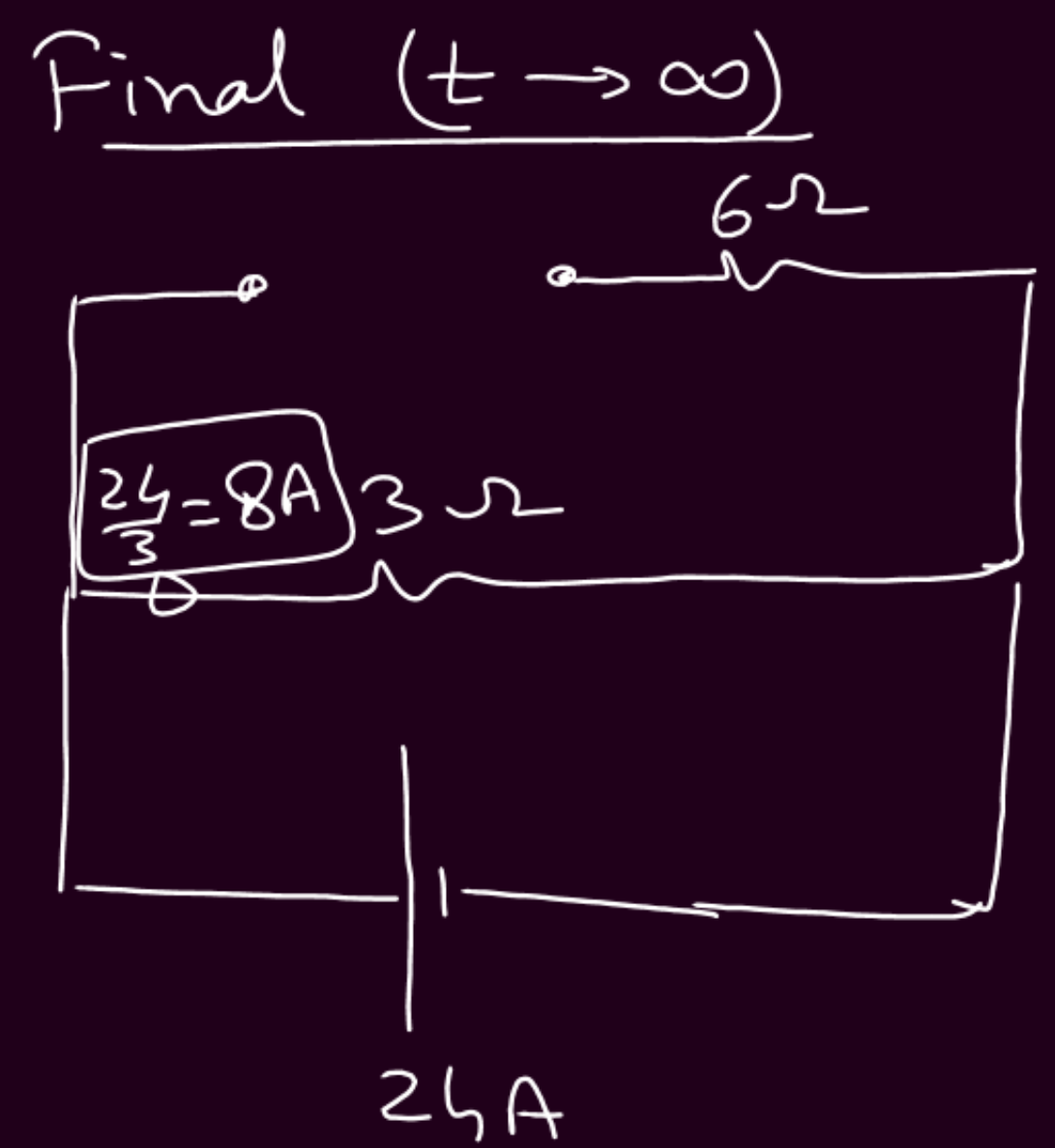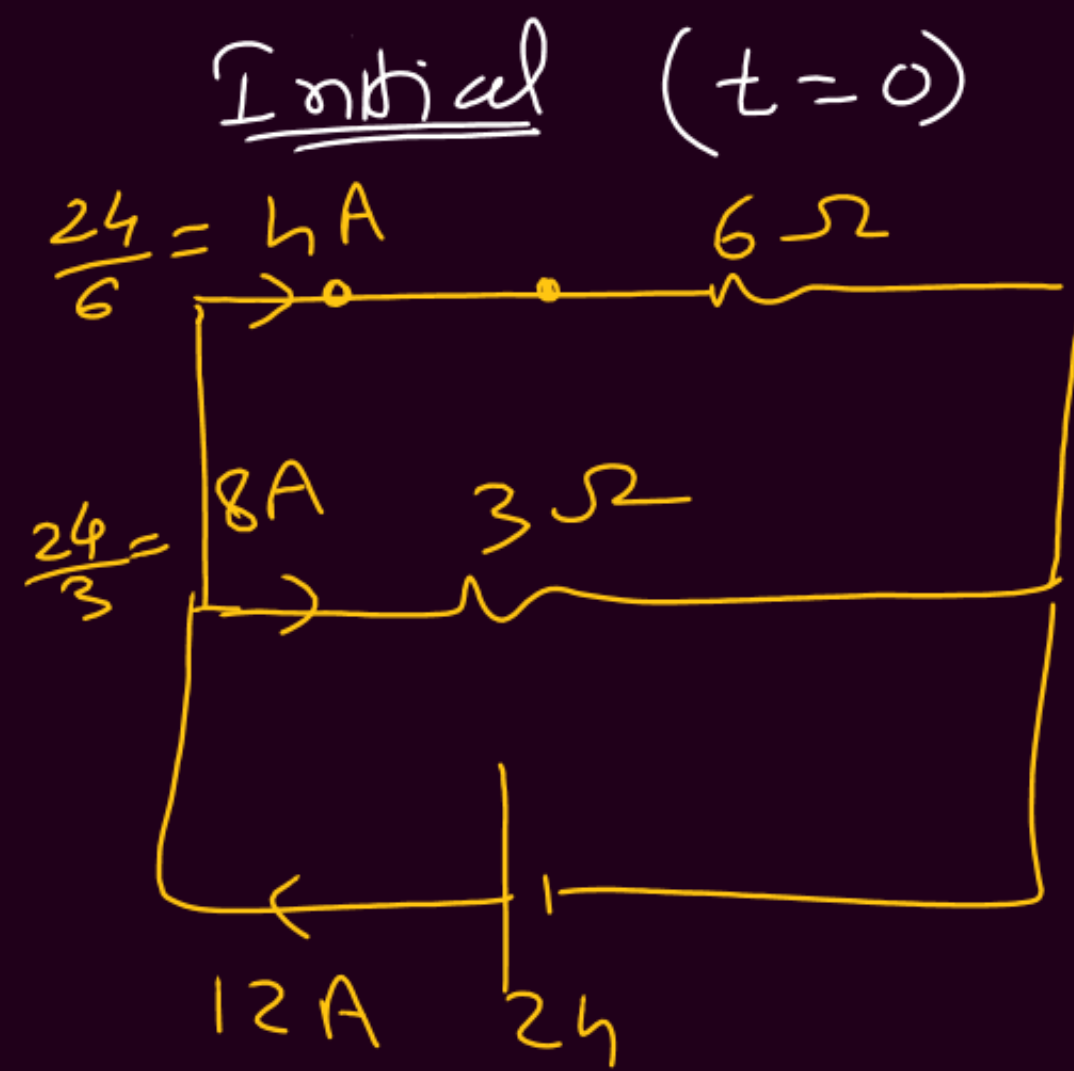
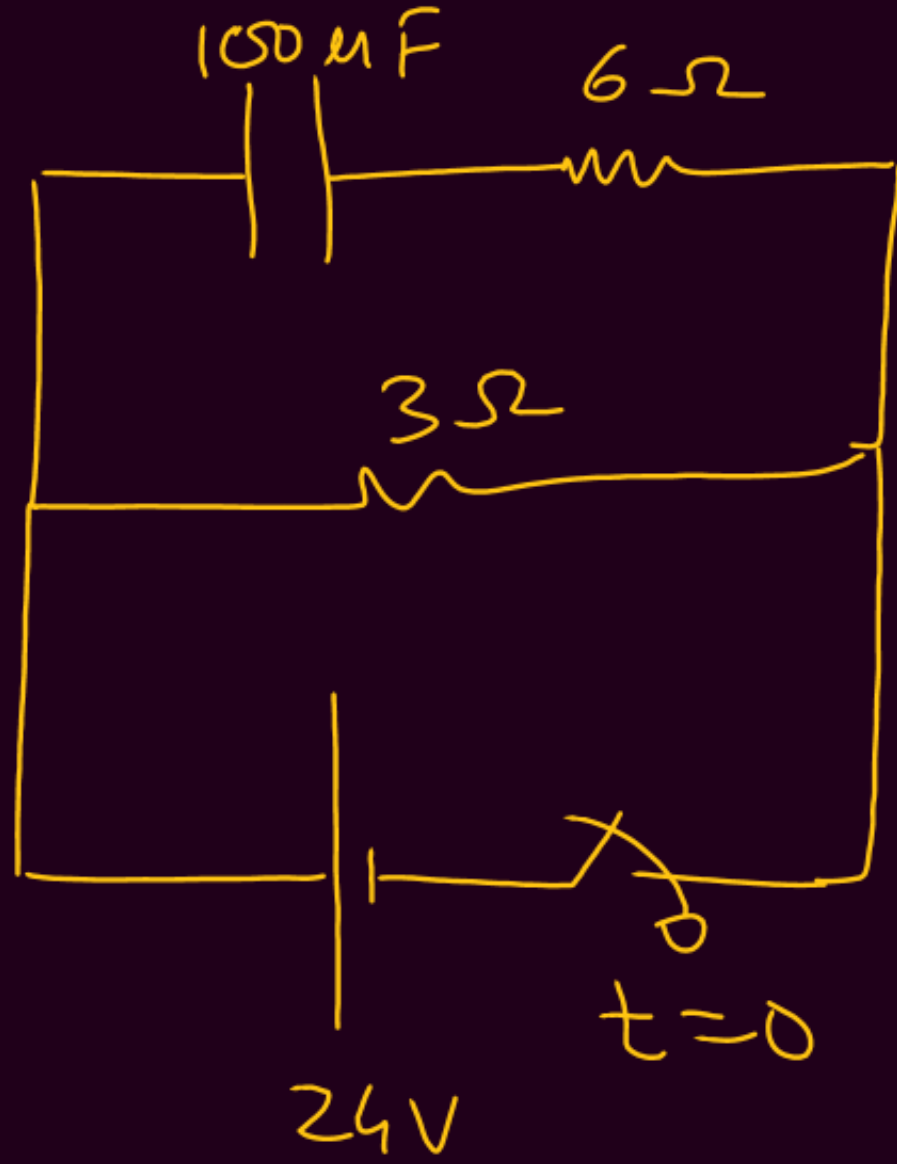
$$\begin{aligned} \textcircled{6} \text{Heat} &= \frac{1}{2} CV^2 \\ &= \frac{1}{2} (100\mu) (20)^2 \\ &= 2 \times 10^{-2} \text{ J} \\ &= \underline{0.02 \text{ J}} \end{aligned}$$




identical Bulbs



$B_2 = \text{const.}$

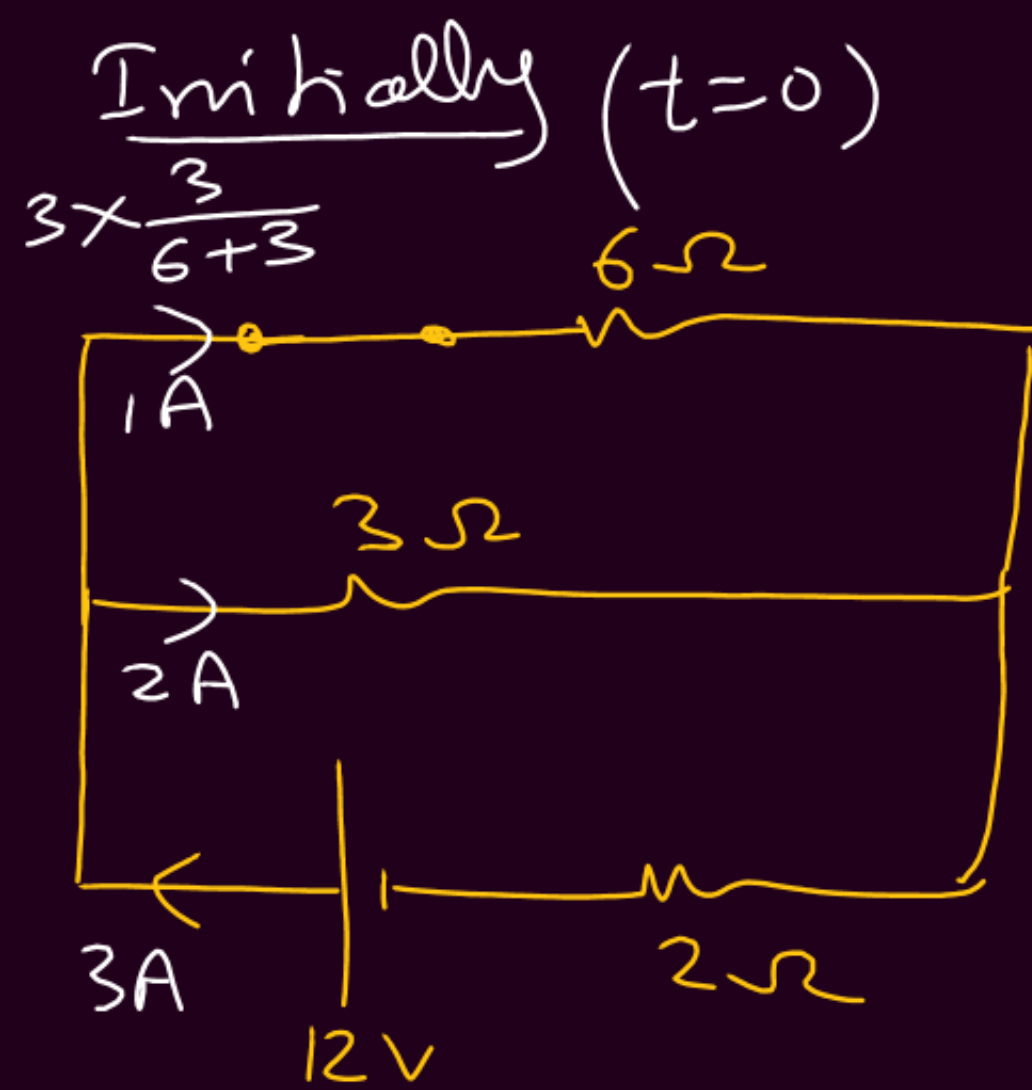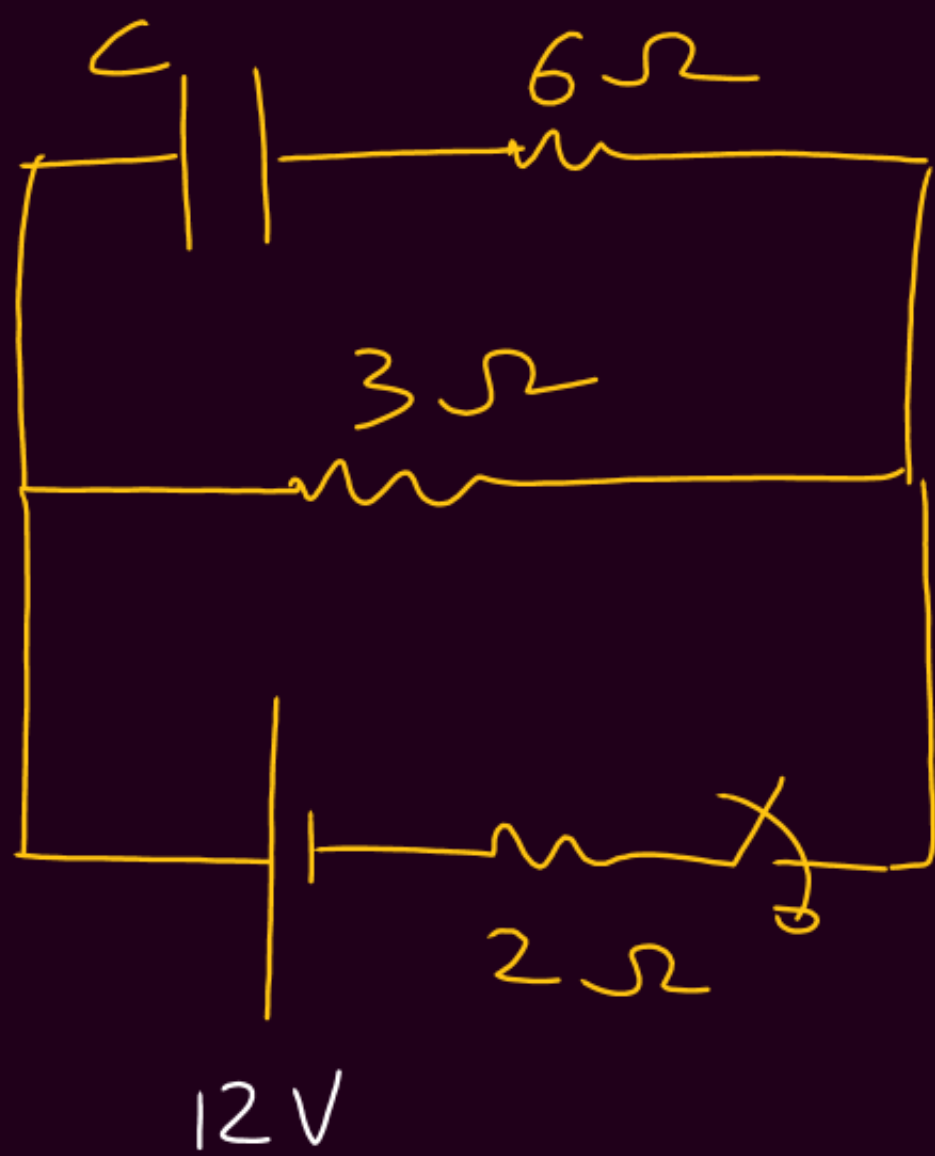$B_1 \rightarrow \downarrow \text{cont. \& '0'}$




$$R_{eq} = 4\Omega$$

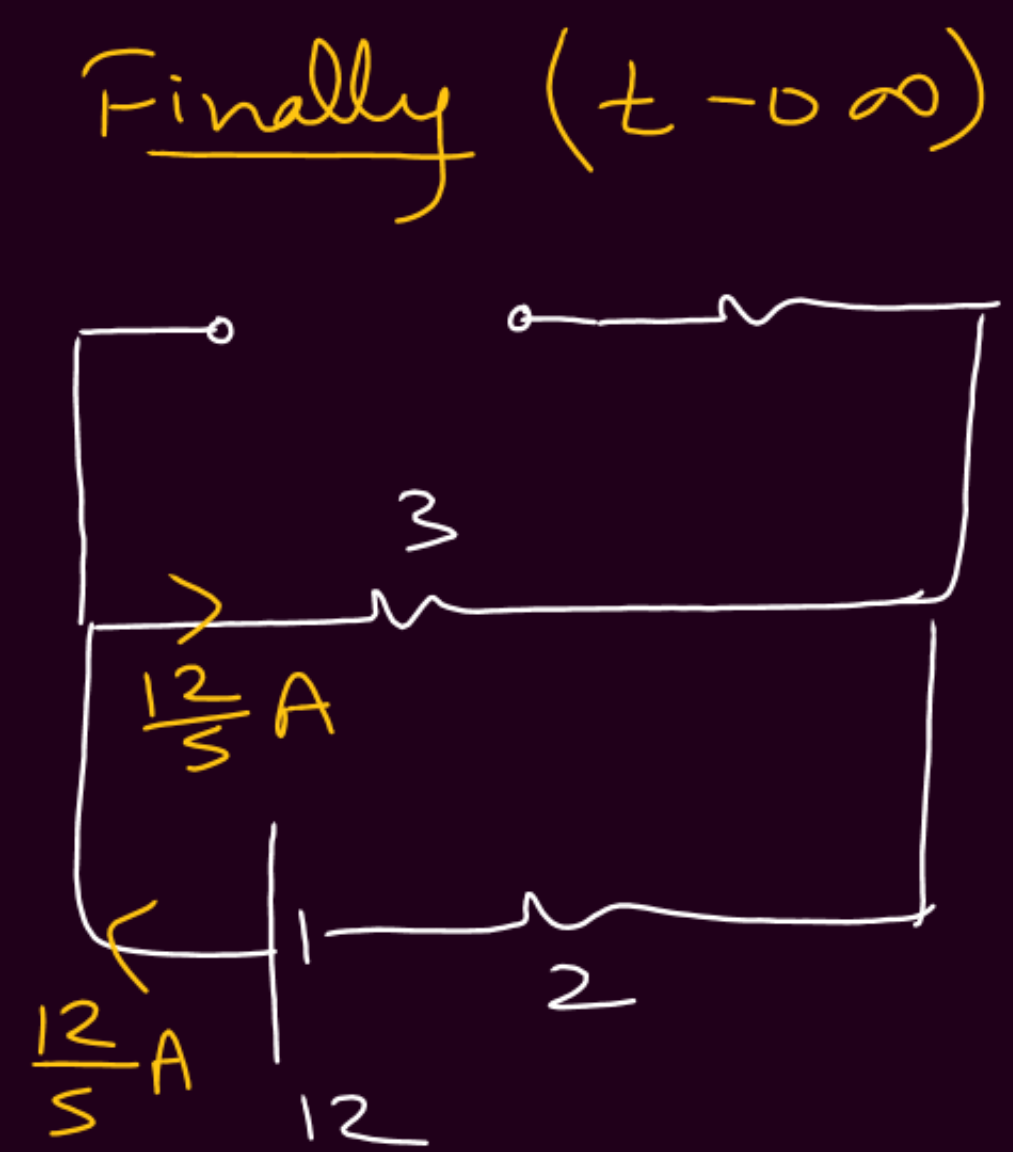

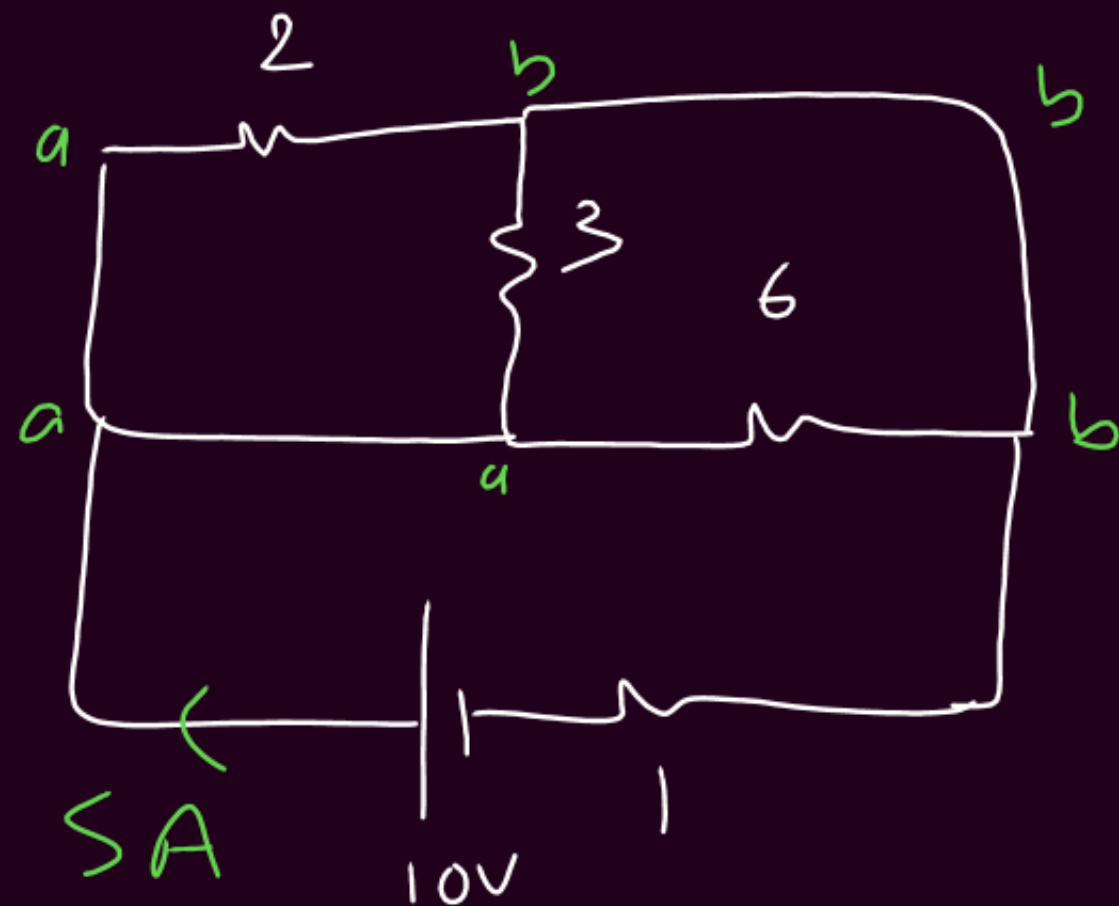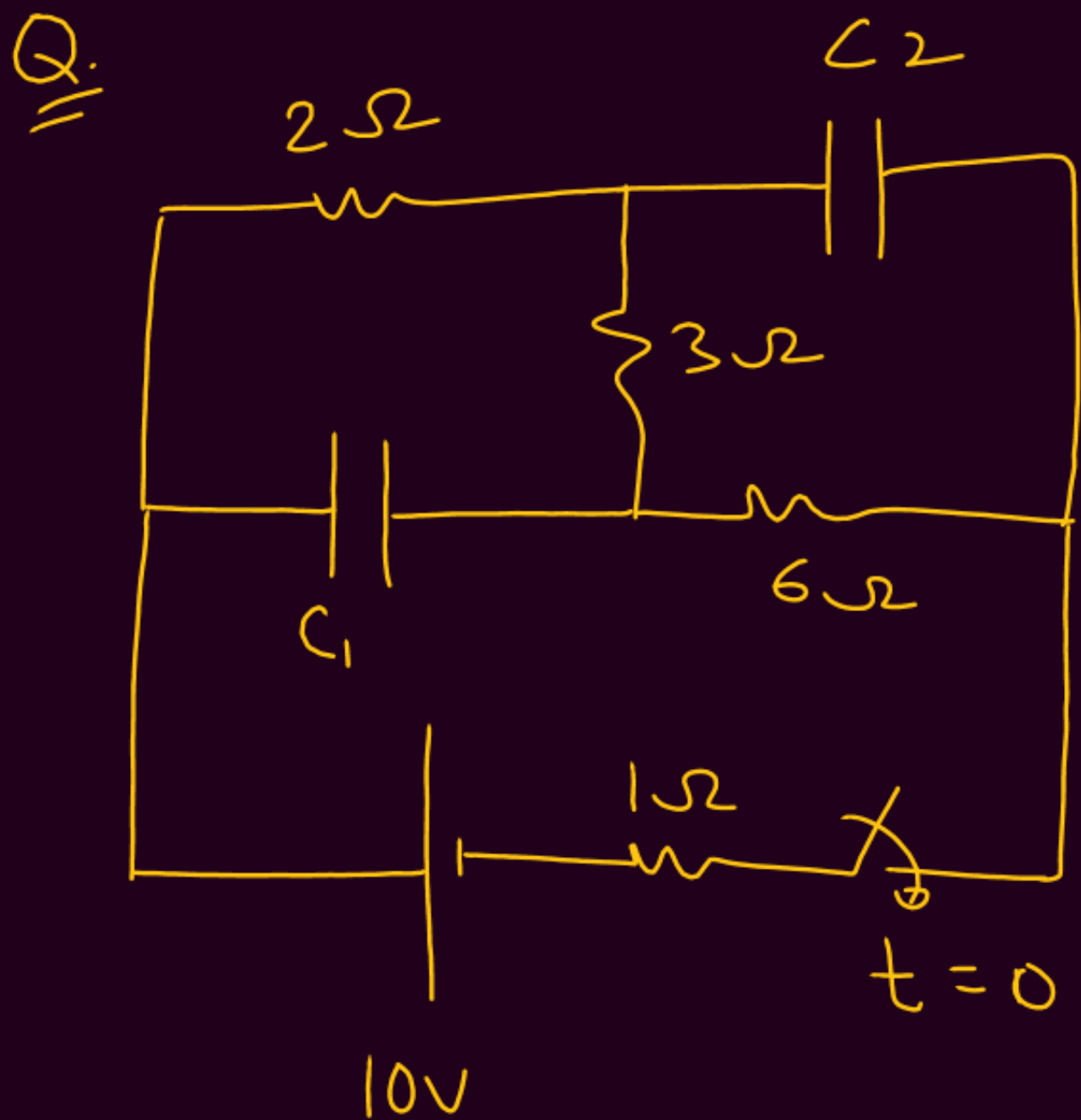


$$R_{eq} = 2\Omega$$

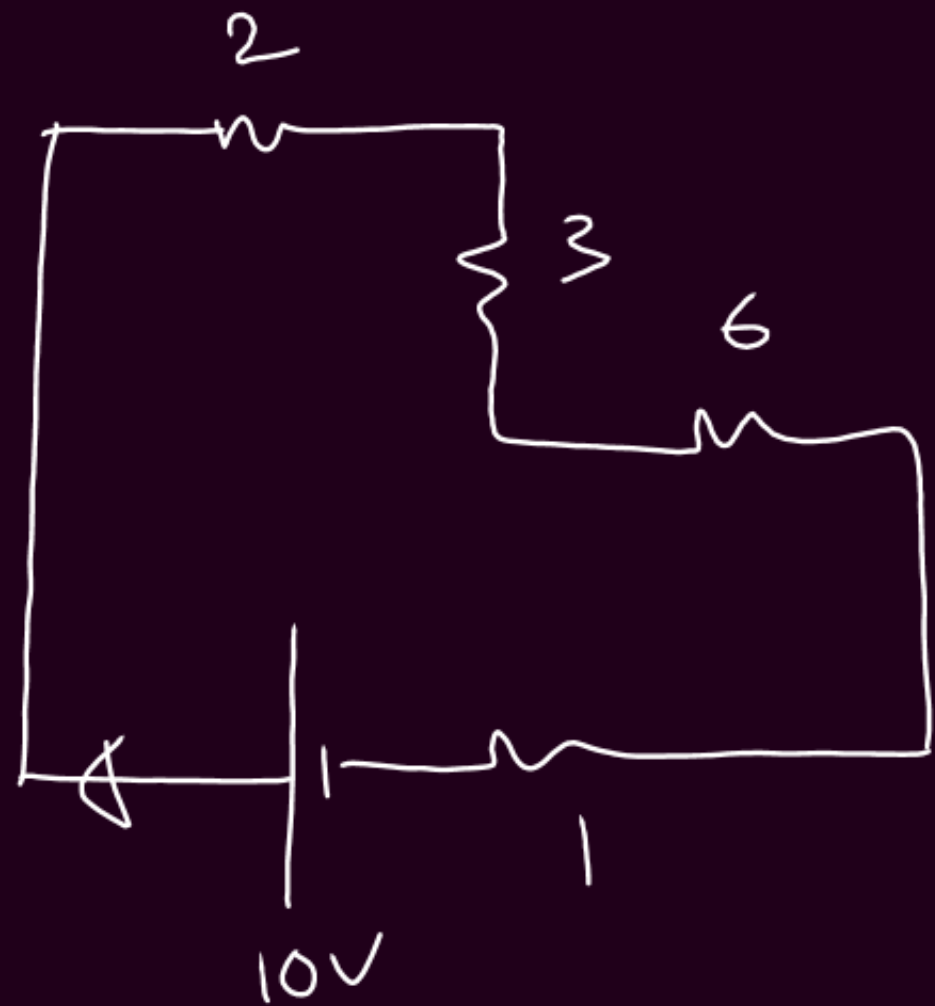

$$i = \frac{10}{2+3+6+1} = \frac{10}{12} A$$

(II) Discharging

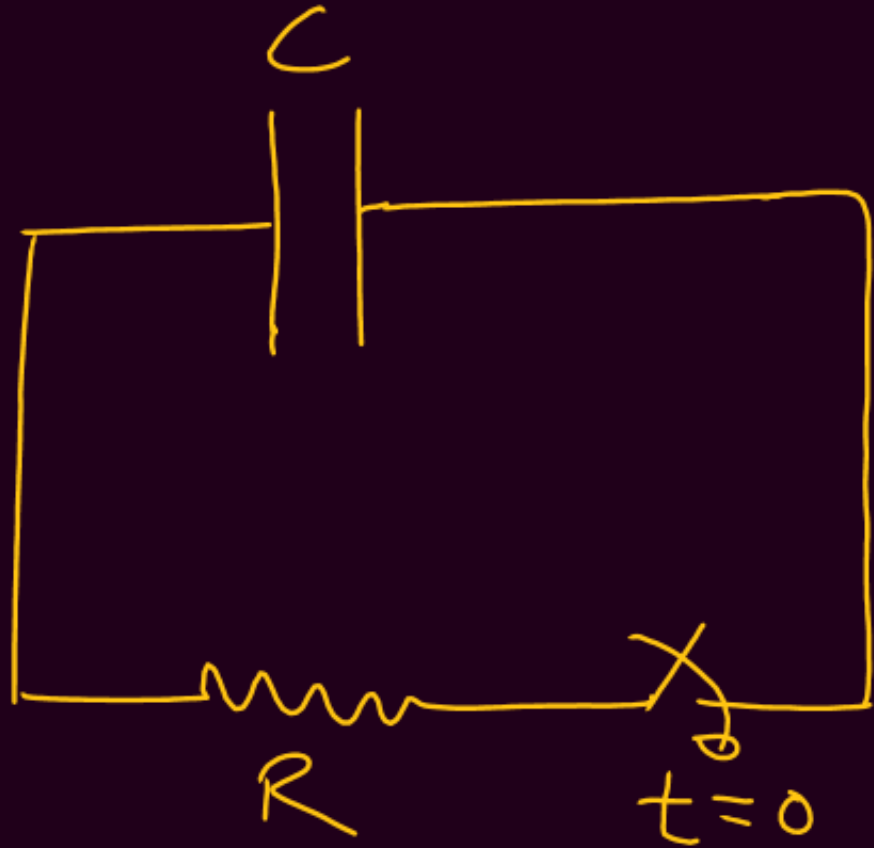



$$\textcircled{1} \quad \frac{1}{2} C V_0^2 = \frac{q_0^2}{2C} = \text{Heat}$$


$$\textcircled{2} \quad \text{Time const. } \boxed{\tau = RC}$$

(3) KVL

$$\boxed{\frac{q}{C} = iR}$$

(4)

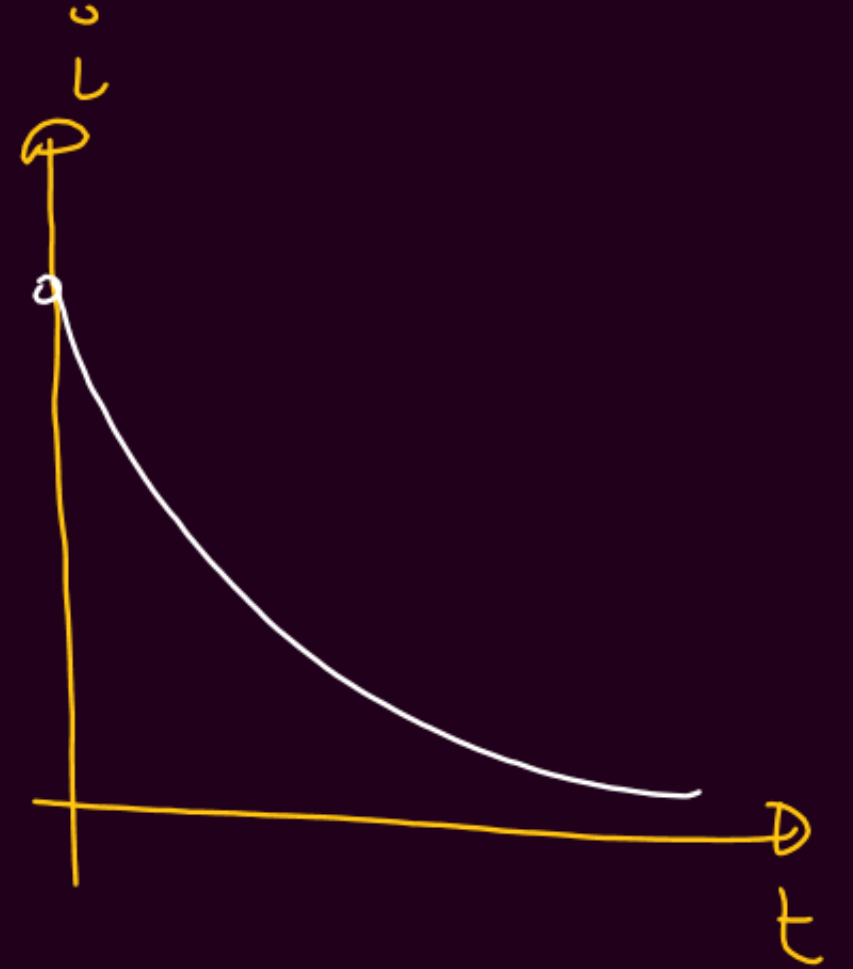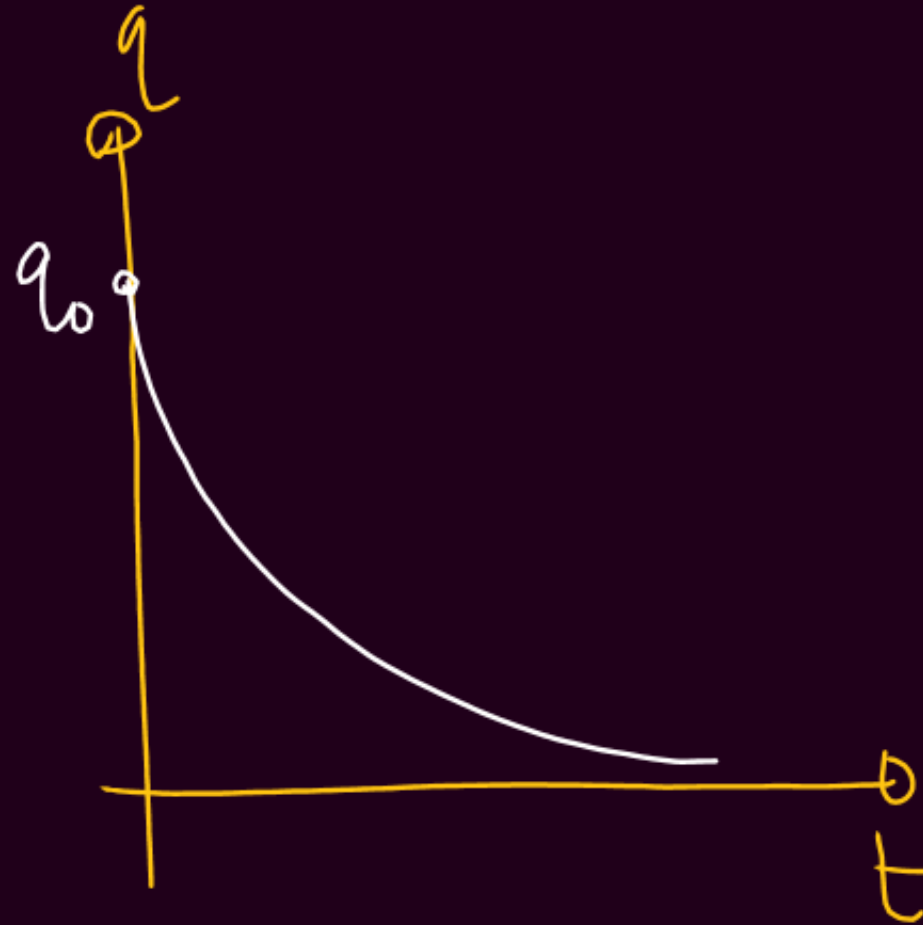

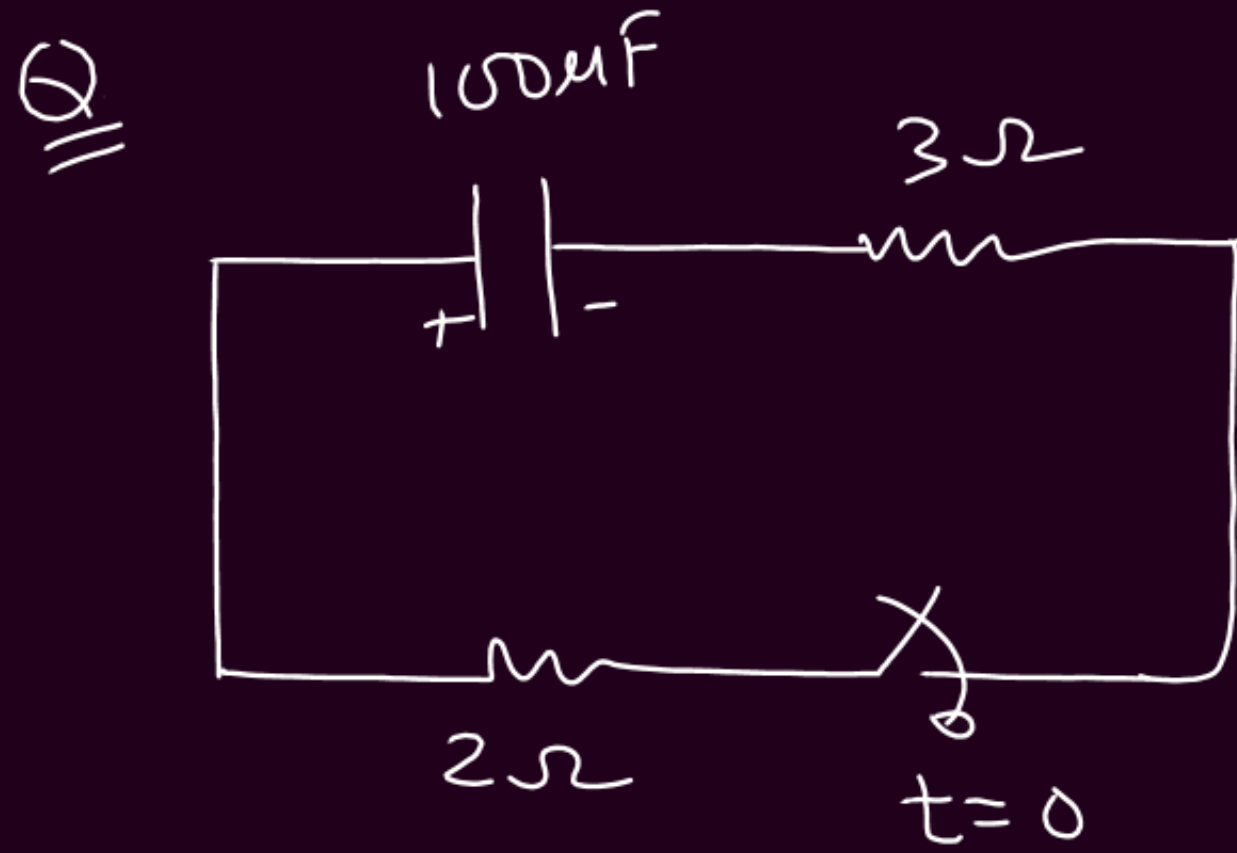

$$\dot{I}_1 R_1 = \dot{I}_2 R_2$$

$$\dot{I}_1 = \dot{I} \frac{R_2}{R_1 + R_2}$$

$$\textcircled{1} \quad \frac{H_1}{H_2} = \frac{2}{3}$$

$$\textcircled{2} \quad \text{Heat} = \frac{1}{2} CV^2 = \frac{1}{2} (100\mu)(200)^2$$

$$= \underline{\underline{2J}}$$

$$H_{2\Omega} = (2) \times \frac{2}{2+3}$$

Dielectric strength

→ E_{max}

Lightening