

Alternating Current

→ Generator / Dynamo

$$\phi = NBA \cos(\omega t)$$

$$\mathcal{E} = NBA\omega \sin(\omega t)$$

$$i = \frac{NBA\omega}{R} \sin(\omega t)$$

$$i = i_0 \sin(\omega t)$$

Sinusoidal

i_0 → peak value

$2i_0$ → peak to peak

ω → Angular freq

$$\omega = 2\pi f = \frac{2\pi}{T}$$


India $\begin{cases} 220V \\ 50Hz \end{cases}$

Avg over cycle → 0

Avg over $\left. \begin{array}{l} \text{+ Half cycle} \end{array} \right\} i_{av} = \frac{2i_0}{\pi}$

RMS
(Effective)

$$i_{rms} = \frac{i_0}{\sqrt{2}}$$

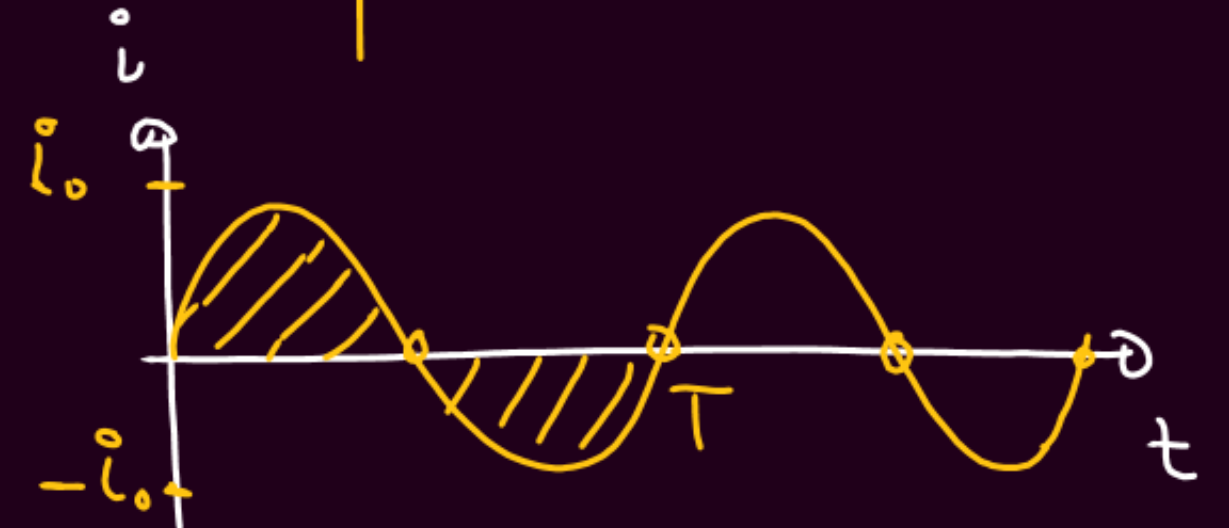

Q. Bulb
Supply 220V, 50Hz

off in a sec $\rightarrow$ 100 times


Q. Avg value of i in Half cycle may be

① +

② -

③ 0

④ All of these

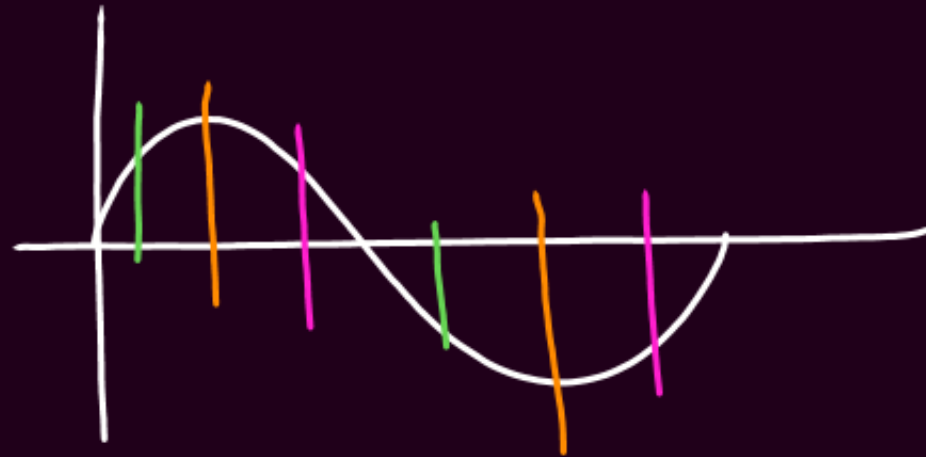

Q. $i = 10 \sin(50\pi t + \frac{\pi}{3})$ A

$\rightarrow$ peak = 10 A

$\rightarrow$ RMS = $\frac{10}{\sqrt{2}} = 5\sqrt{2}$ A

$\rightarrow$ Avg of $\oplus$ Half = $\frac{20}{\pi}$ A

$\rightarrow$ initial current $i = 10 \sin(\frac{\pi}{3})$
($t=0$)

$i = 10 \left(\frac{\sqrt{3}}{2}\right) = 5\sqrt{3}$ A

$\rightarrow t = \frac{1}{100}$ s $i = 10 \sin\left(\frac{\pi}{2} + \frac{\pi}{3}\right) = 10 \cos\left(\frac{\pi}{3}\right)$
 $= \underline{5A}$

Q. $i = 10 \sin\left(100\pi t + \frac{\pi}{6}\right) \text{ A}$

$t = ?$ when i is max

$$(100\pi t) + \frac{\pi}{6} = \frac{\pi}{2}$$

$$100\pi t = \frac{\pi}{3}$$

$$t = \frac{1}{300} \text{ s}$$

Q. $\boxed{100 \text{ V, } 50 \text{ Hz}}$

Avg. value of
⊕ Half =

$$\frac{2}{\pi} (100\sqrt{2}) = \frac{200\sqrt{2}}{\pi}$$

$$\left. \begin{aligned} i &= i_0 \sin(\omega t + \phi) \\ i &= i_0 \cos(\omega t + \phi) \end{aligned} \right\}$$

Peak

$$i_0$$

$$\omega$$

freq

$$\frac{\omega}{2\pi}$$

$$\begin{aligned} i &= i_0 \sin(\omega t) \cos(\omega t) \\ &= \frac{i_0}{2} \sin(2\omega t) \end{aligned}$$

$$\frac{i_0}{2}$$

$$2\omega$$

$$\frac{2\omega}{2\pi}$$

$$\left. \begin{aligned} i &= i_0 \sin^2(\omega t) \\ i &= i_0 \cos^2(\omega t) \end{aligned} \right\}$$

$$i_0$$

$$2\omega$$

$$\frac{2\omega}{2\pi}$$

$$i = a \sin(\omega t) + b \cos(\omega t)$$

$$\frac{\text{Peak}}{\sqrt{a^2 + b^2}}$$

ω

$$i_{rms} = \frac{i_p}{\sqrt{2}}$$

DC + AC

$$i = a + b \sin(\omega t)$$

$$(a + b)$$

ω

$$i_{rms} = \sqrt{a^2 + \frac{b^2}{2}}$$

Q. $i = 8 \sin(\omega t) + 6 \cos(\omega t)$

RMS ?

$$\text{peak} = \sqrt{8^2 + 6^2} = 10$$

$$\text{RMS} = \frac{10}{\sqrt{2}} = 5\sqrt{2}$$

Q. $i = 10 \sin(100\pi t) \cos(100\pi t)$

$$\begin{aligned} \text{peak} &= \frac{10}{2} \\ &= 5 \end{aligned}$$

$$\omega = 2(100\pi)$$

$$f = \frac{200\pi}{2\pi} = 100 \text{ Hz}$$

Q.

$$i = 3 + 4 \sin(100\pi t)$$




$$\text{RMS} = \sqrt{3^2 + \frac{4^2}{2}} = \sqrt{17}$$

$$[\sin(\omega t)]_{av} = 0$$


$$[\sin(\omega t)]_{av, \oplus \text{ half}} = \frac{2}{\pi}$$

$$[\sin^2(\omega t)]_{av} = \frac{1}{2}$$

$$\sqrt{[\sin^2(\omega t)]_{av}} = [\sin(\omega t)]_{rms} = \frac{1}{\sqrt{2}}$$

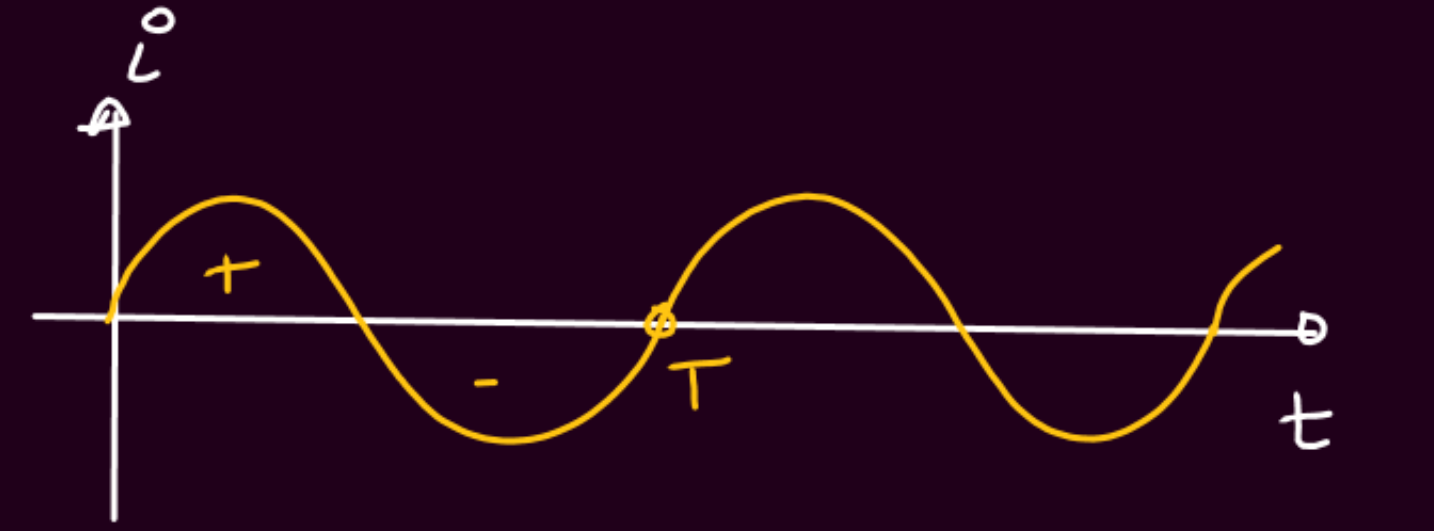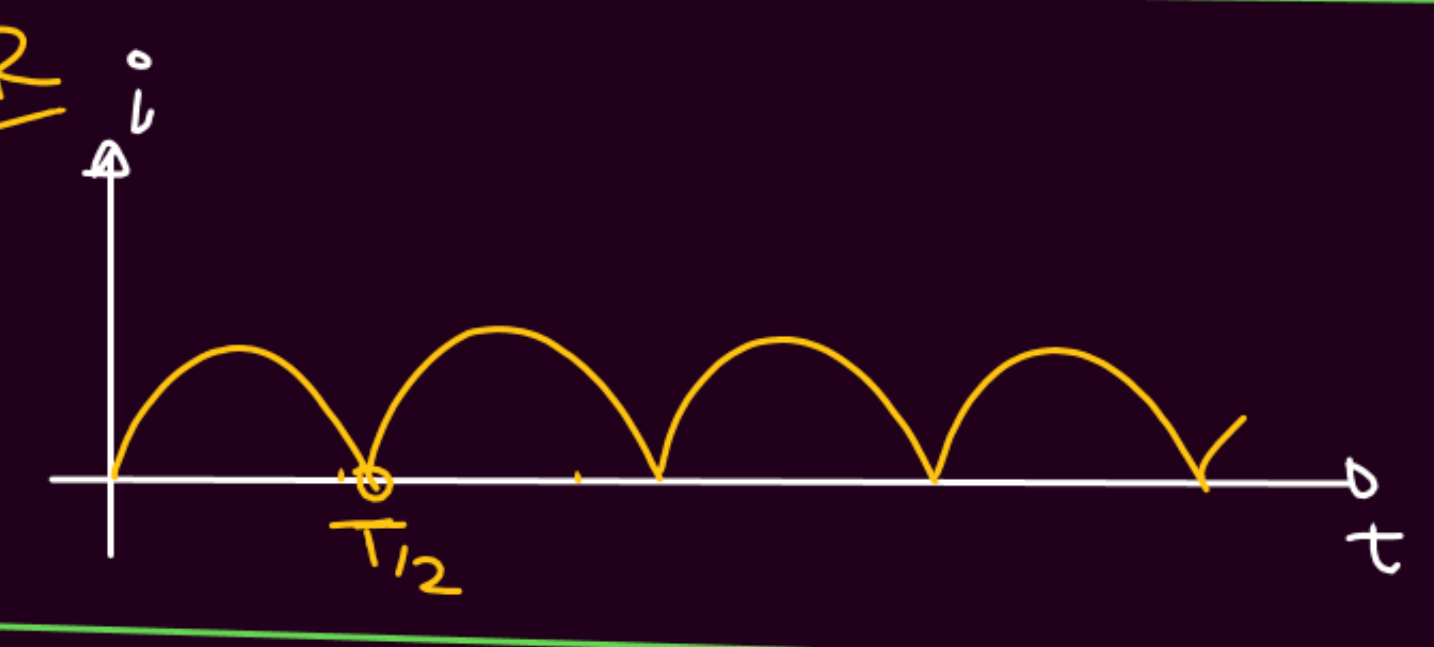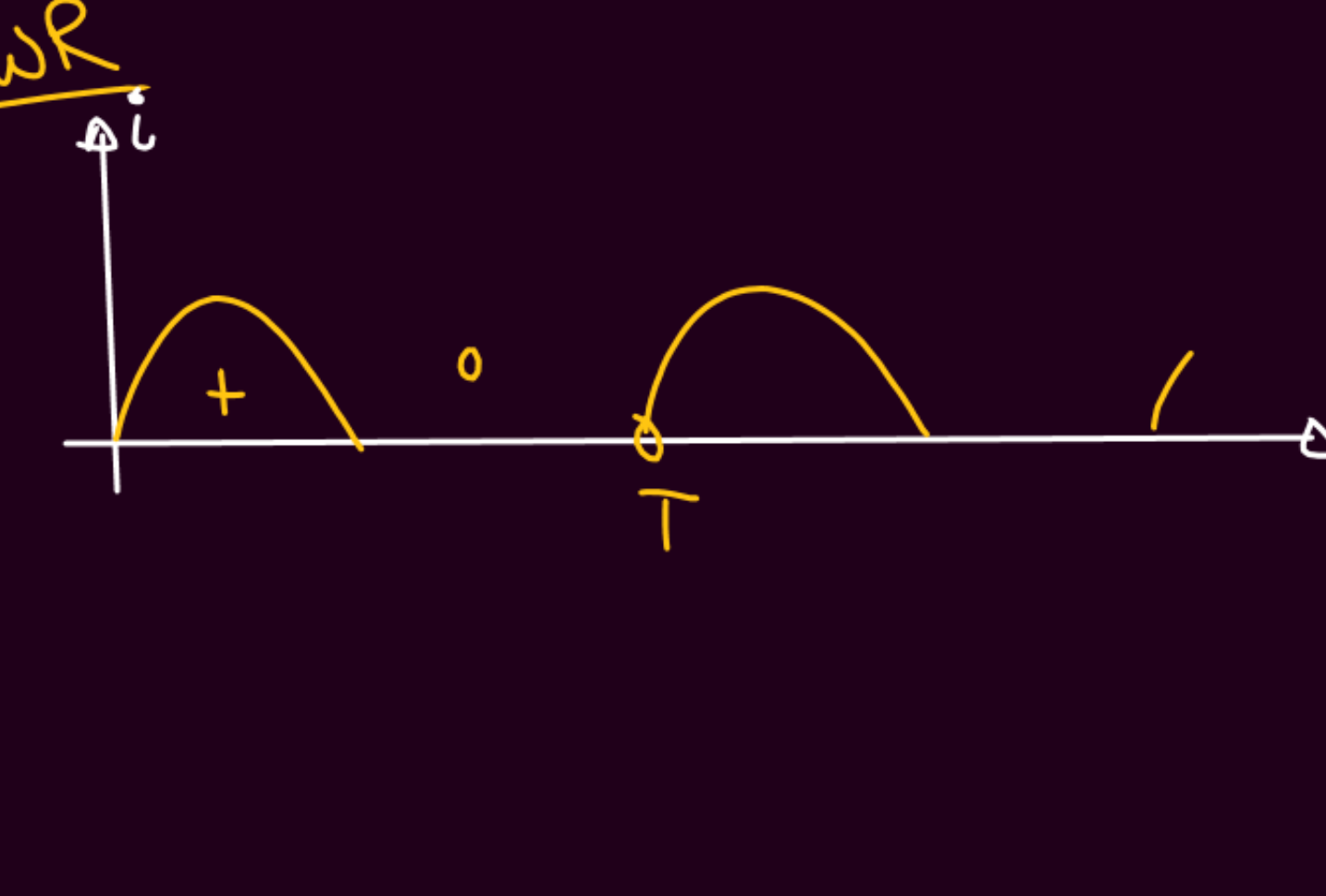AC	<u>Avg.</u>	RMS	Time Period	freq
	0	$\frac{i_0}{\sqrt{2}}$	T	f
<u>FWR</u> 	$\frac{2i_0}{\pi}$	$\frac{i_0}{\sqrt{2}}$	$\frac{T}{2}$	2f
<u>HWR</u> 	i_0	$\frac{i_0}{2}$	T	f

Extra

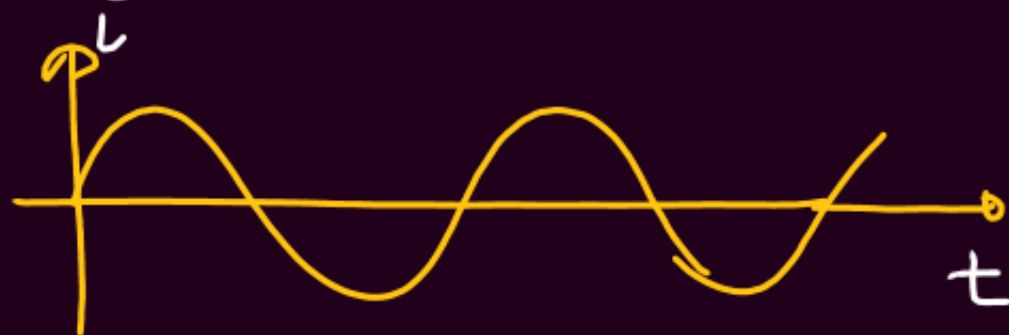


RMS

$$\frac{i_0}{\sqrt{2}}$$

Avg of $\oplus$ Half

$$\frac{2i_0}{\pi}$$


Square

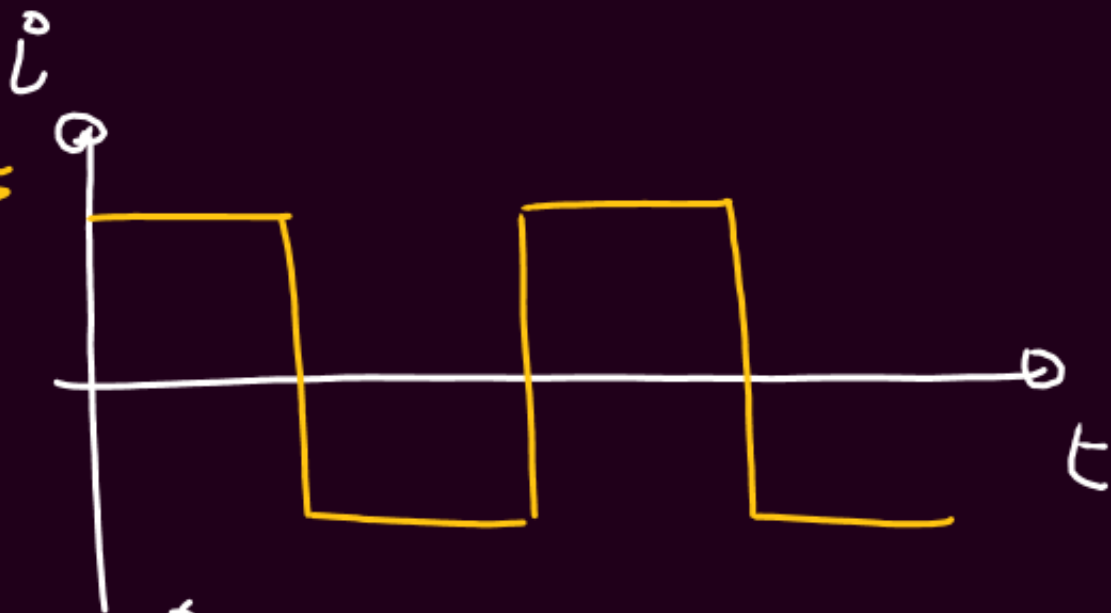

$$i_0$$


$$i_0$$

Triangular
Saw tooth

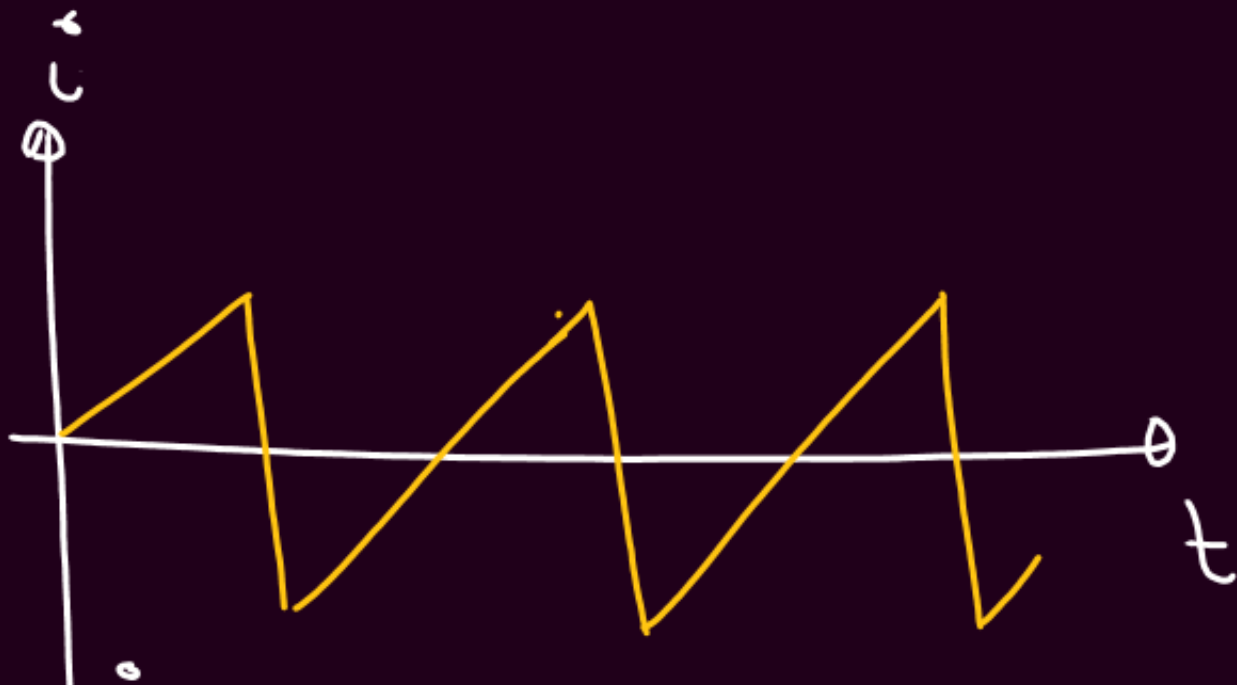


$$\frac{i_0}{\sqrt{3}}$$

$$\frac{i_0}{2}$$

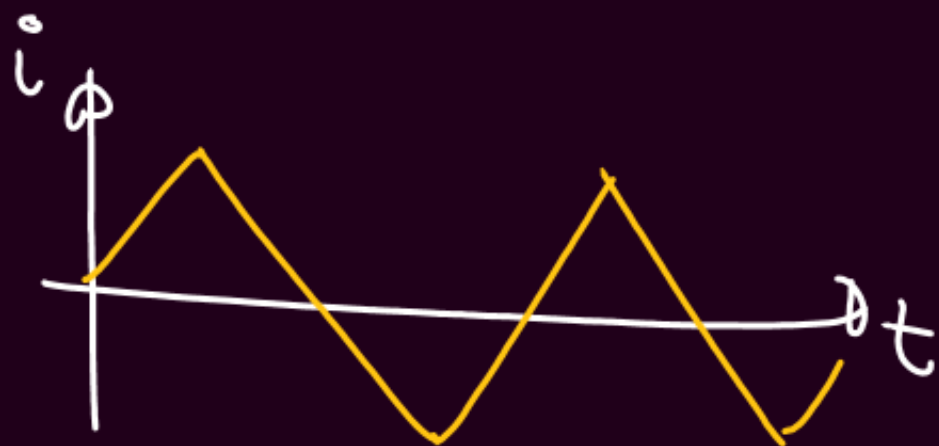


Pure R

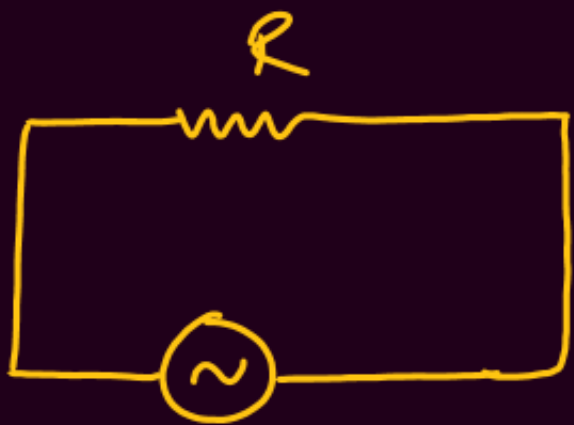

① Instantaneous

$$V = iR$$

② Phasor

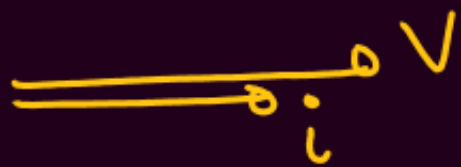

③ if $i = i_0 \sin(\omega t)$
 $V = V_0 \sin(\omega t)$

④ $V_0 = i_0 R$

⑤ $P_{\text{inst}} = V_0 i_0 \sin^2(\omega t)$

if V & i $\rightarrow \omega$

then power $\rightarrow 2\omega$


⑥ $P_{\text{av}} = \frac{V_0 i_0}{2} = V_{\text{rms}} i_{\text{rms}}$

$$P_{\text{av}} = i_{\text{rms}}^2 R$$

DC meters

e.g. $\rightarrow$ moving coil galvanometer

Deflection $\boxed{\theta \propto i}$

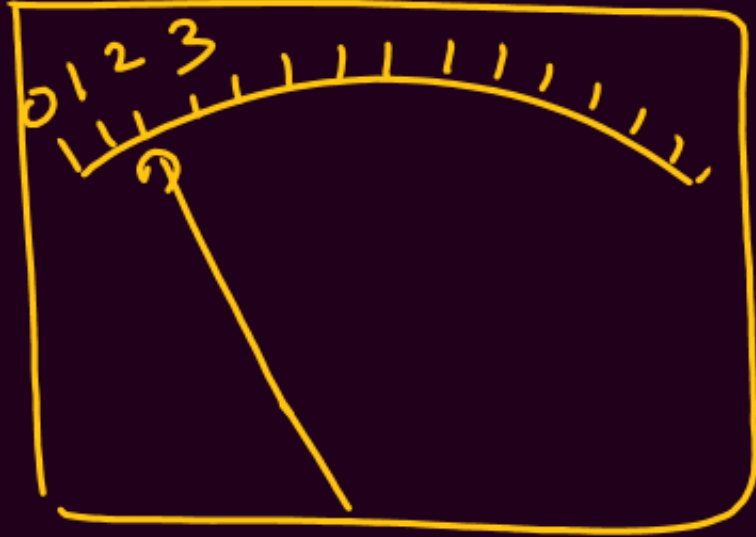


Linear Scale

if DC $\rightarrow$ used in AC $\rightarrow$ '0'

AC meter

Hot wire Instruments $\rightarrow P_{av} \propto i^2$


$$[\theta \propto i^2]$$

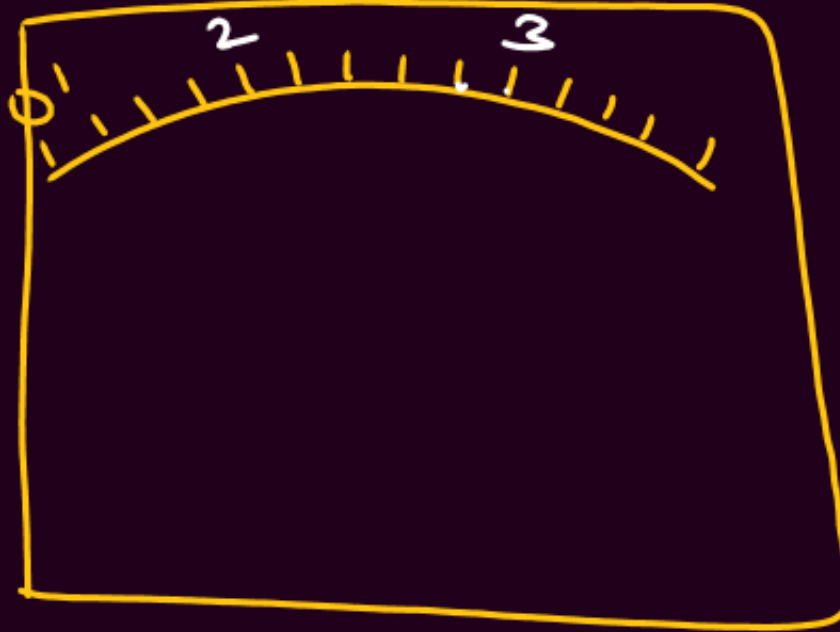

Non-linear Scale

it can be used $\rightarrow$ AC
 $\rightarrow$ DC


AC meter $\rightarrow$ "RMS"

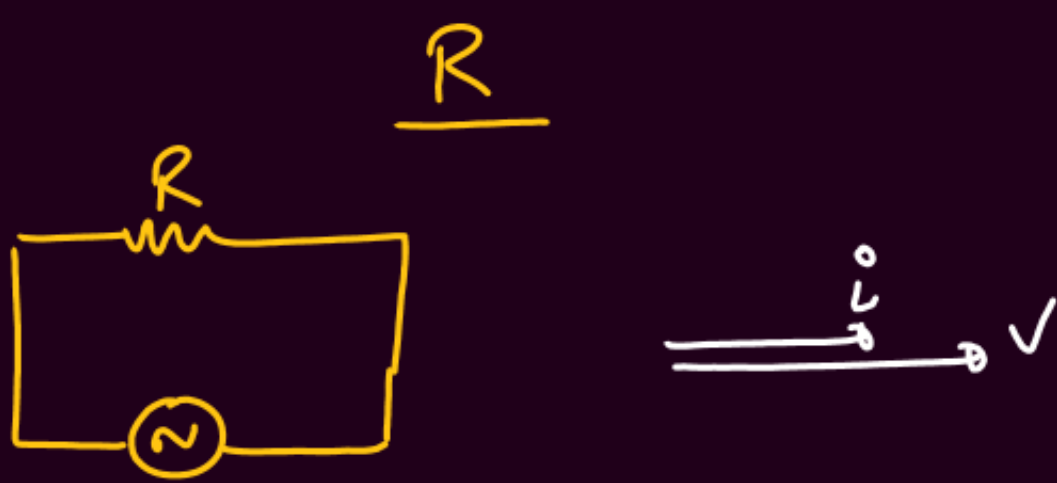

V & i → in same phase



V_L leads i by $\frac{\pi}{2}$

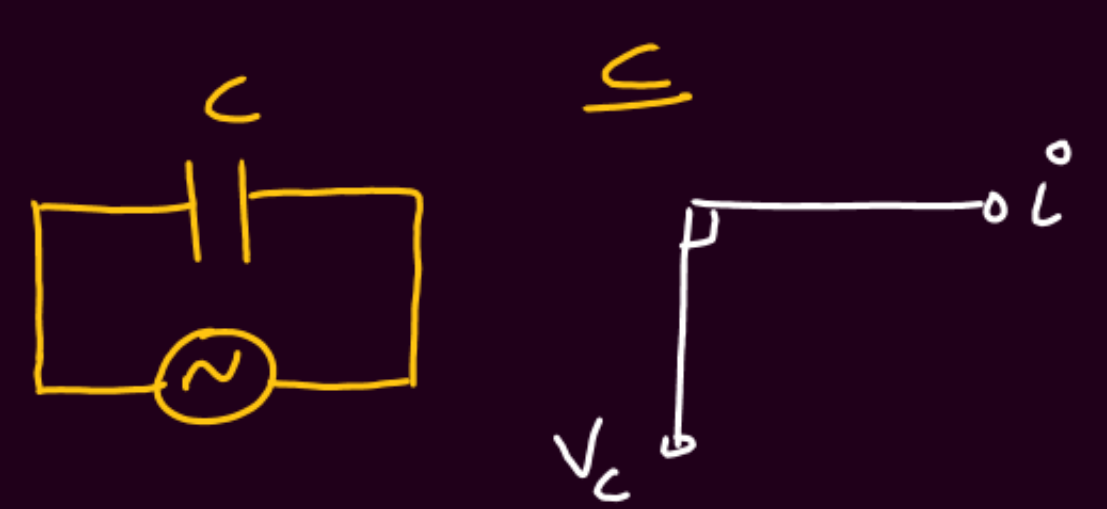

V_C lags i by $\frac{\pi}{2}$

Impedance

$$Z = R$$

$$V_0 = i_0 R$$

$$V = V_0 \sin(\omega t)$$

$$i = i_0 \sin(\omega t)$$

Inductive Reactance

$$Z = X_L = \omega L$$

$$V_0 = i_0 X_L$$

$$V = V_0 \sin(\omega t)$$

$$i = i_0 \sin(\omega t - \pi/2)$$

Capacitive Reactance

$$Z = X_C = \frac{1}{\omega C}$$

$$V_0 = i_0 X_C$$


$$V = V_0 \sin(\omega t)$$

$$i = i_0 \sin(\omega t + \pi/2)$$

R

$$P_{inst} \rightarrow 2W$$

$$P_{av} = i_{rms}^2 R$$

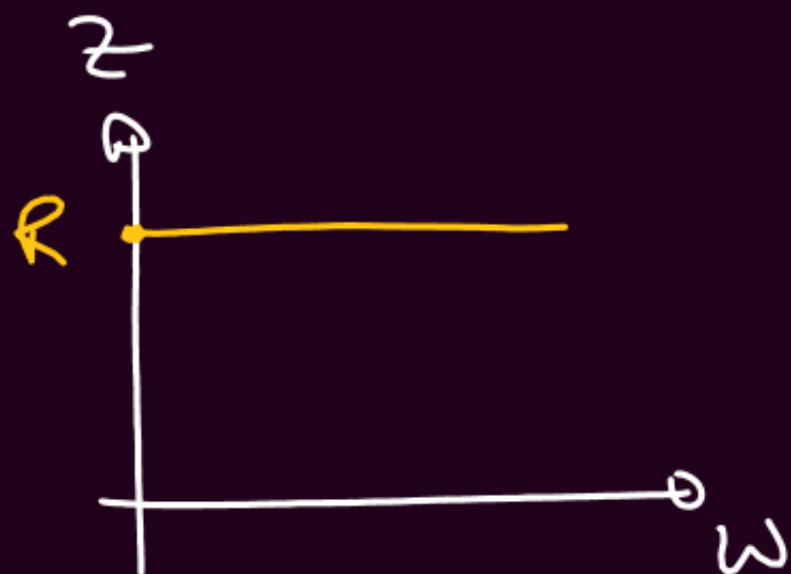


$$i_o = \frac{V_o}{R}$$

L

$$P_{inst} \rightarrow 2W$$

$$P_{av} = 0$$

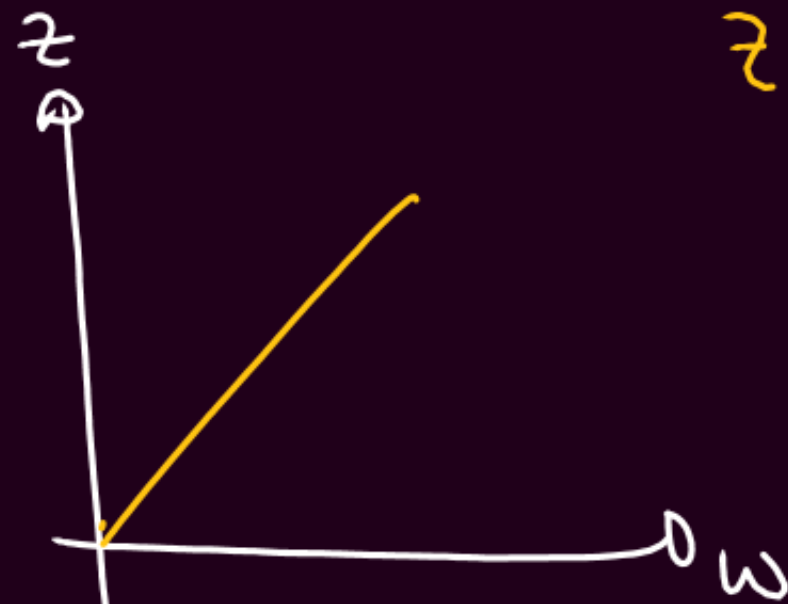Inductor & Capacitor are non-dissipative elements
 $Z = \omega L$




$$i_o = \frac{V_o}{\omega L}$$

L $\rightarrow$ Low pass filter

C

$$P_{inst} \rightarrow 2W$$

$$P_{av} = 0$$

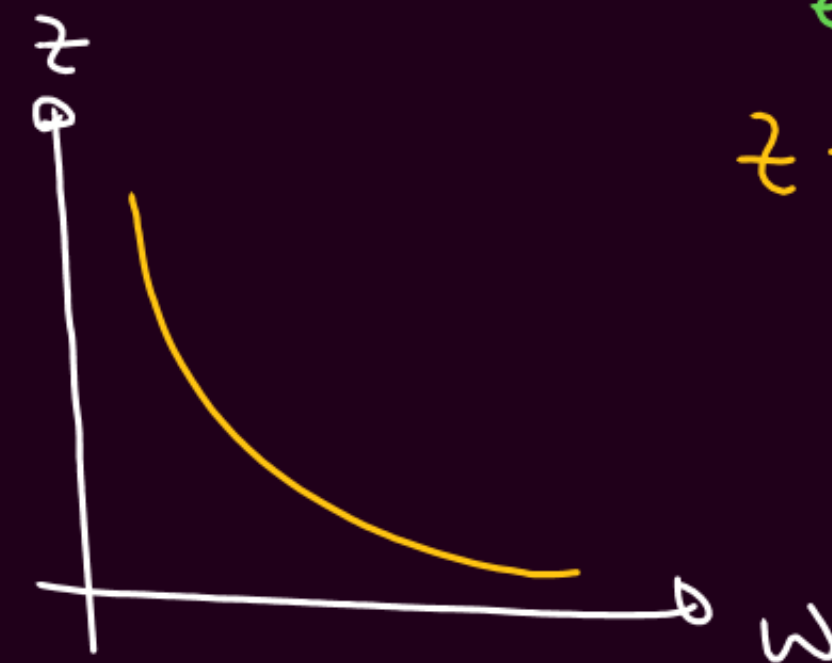


$$Z = \frac{1}{\omega C}$$

$$i_o = V_o \omega C$$

C $\rightarrow$ High pass filter

Q.

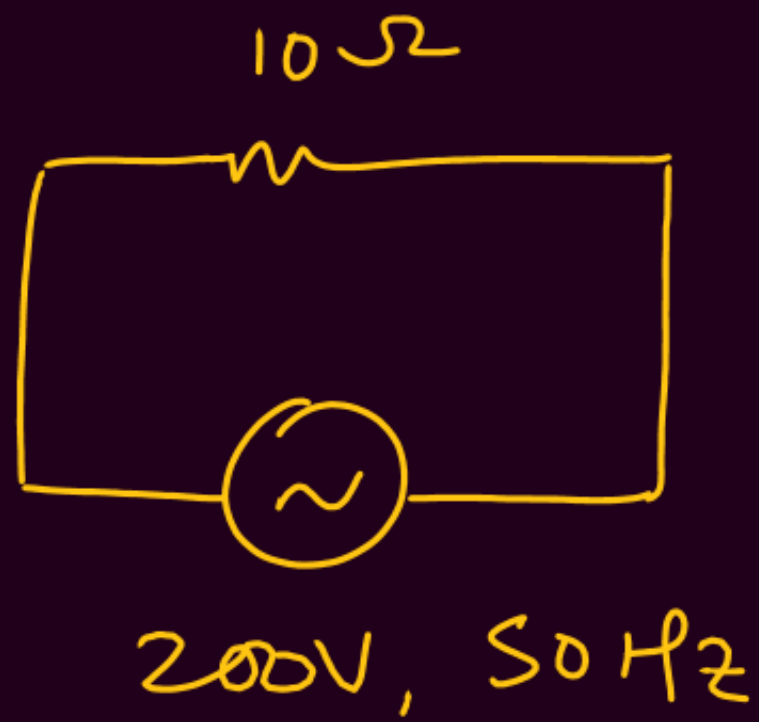

① $i_{peak} = ?$

$$V_o = i_o R$$


$$200 = i_o (10)$$

$$i_o = 20 \text{ A (rms)}$$

$$i_{peak} = 20\sqrt{2} \text{ A}$$

②
$$P_{av} = i_{rms}^2 R$$
$$= (20)^2 (10)$$
$$= 4000 \text{ W}$$

Q

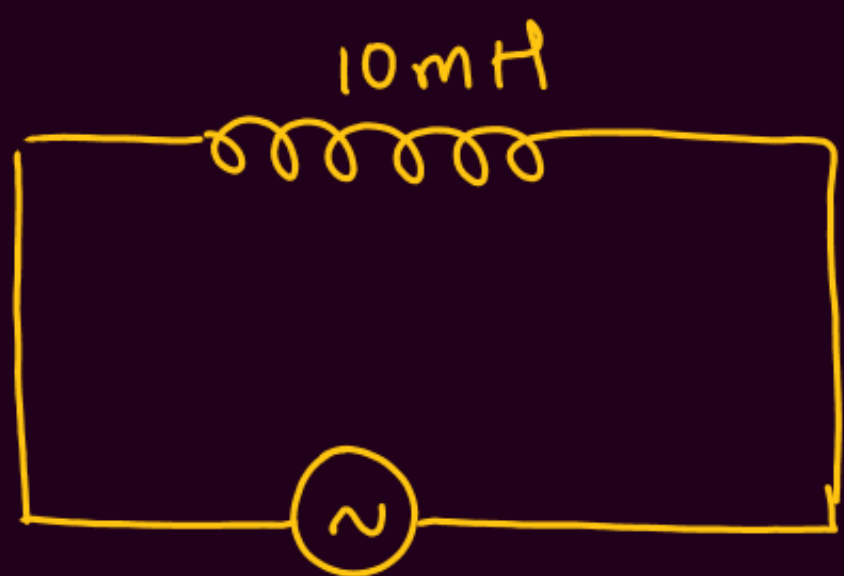


$$V = 100 \sin(200t)$$

$$\begin{aligned} \textcircled{1} \quad X_L &= \omega L \\ &= (200)(10 \times 10^{-3}) \\ &= 2 \Omega \end{aligned}$$

$$\begin{aligned} \textcircled{2} \quad V_o &= \dot{I}_o X_L \\ 100 &= \dot{I} (2) \\ \dot{I} &= 50 \text{ A (peak)} \end{aligned}$$

$$\textcircled{3} \quad P_{av} = 0$$

Q.

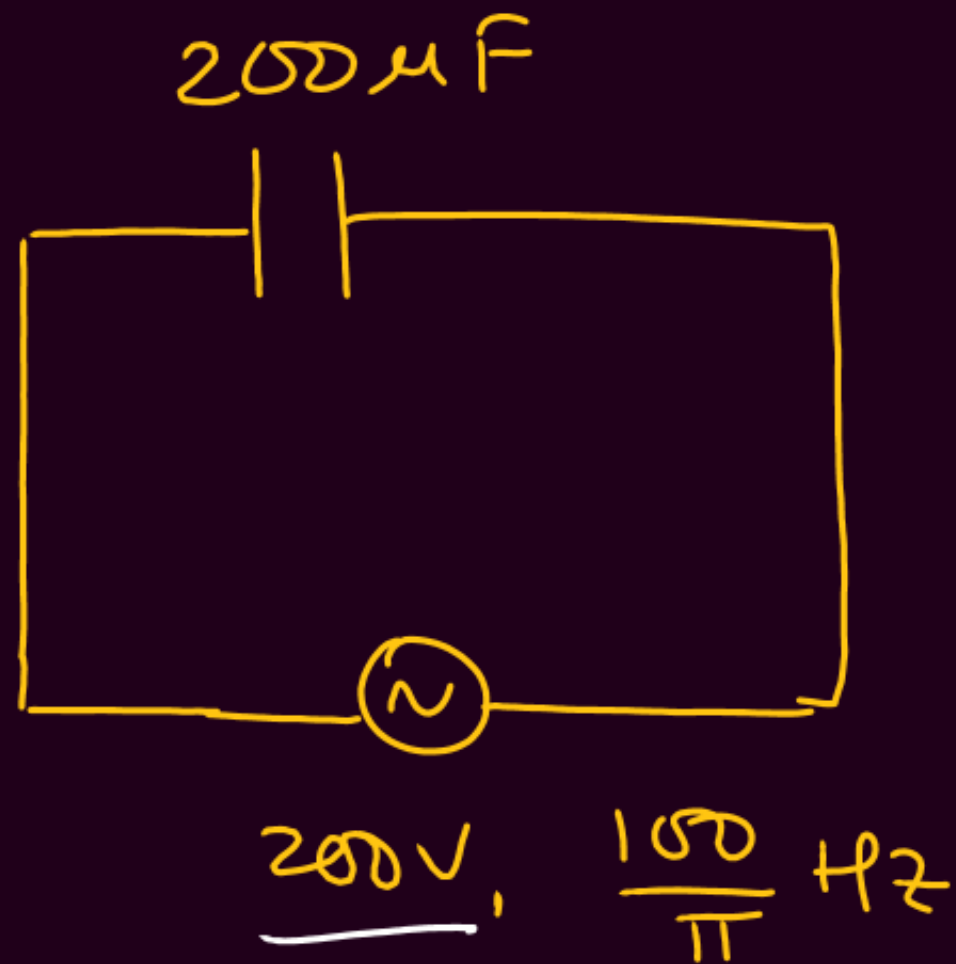

③


$$V = I^{\circ} X_C$$

$$200 = I^{\circ} (25)$$

$$I^{\circ} = 8 \text{ A} \quad (\text{rms})$$

$$\textcircled{1} \quad \omega = 2\pi \left(\frac{100}{\pi} \right) = 200 \text{ rad/s}$$
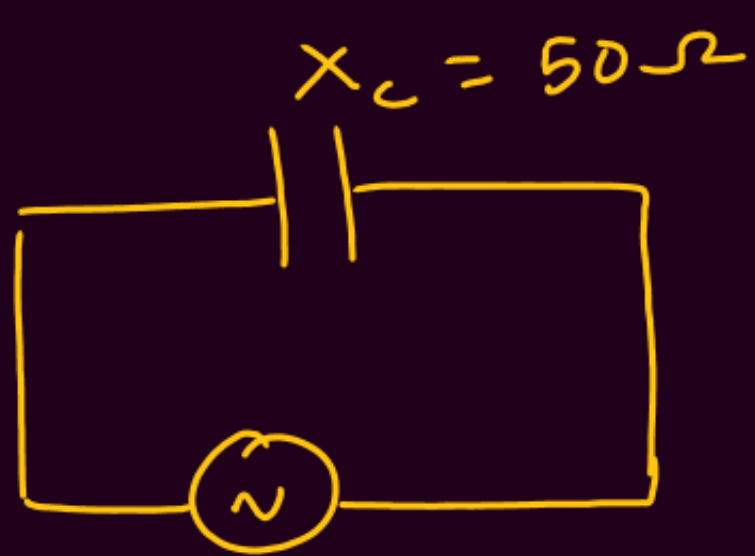
$$\textcircled{2} \quad X_C = \frac{1}{\omega C} = \frac{1}{200 \times 200\mu} = 25 \Omega$$



$$v = 100 \sin\left(\omega t + \frac{\pi}{6}\right)$$

$$i_o = \left(\frac{100}{50}\right) \sin\left(\omega t + \frac{\pi}{6} + \frac{\pi}{2}\right)$$

$$i_o = 2 \sin\left(\omega t + \frac{2\pi}{3}\right)$$

$$i_o = 2 \cos\left(\omega t + \frac{\pi}{6}\right)$$

$$\underline{\underline{Q.}} \quad v = 100 \sin(50\pi t) \quad \text{V}$$

$$i_o = 2 \cos(50\pi t) \quad \text{A}$$


$$P_{av} = ?$$

$$\phi = \pi/2$$

$$P_{av} = 0$$

$\therefore i_o$ leads v by $\pi/2$

$\therefore C$

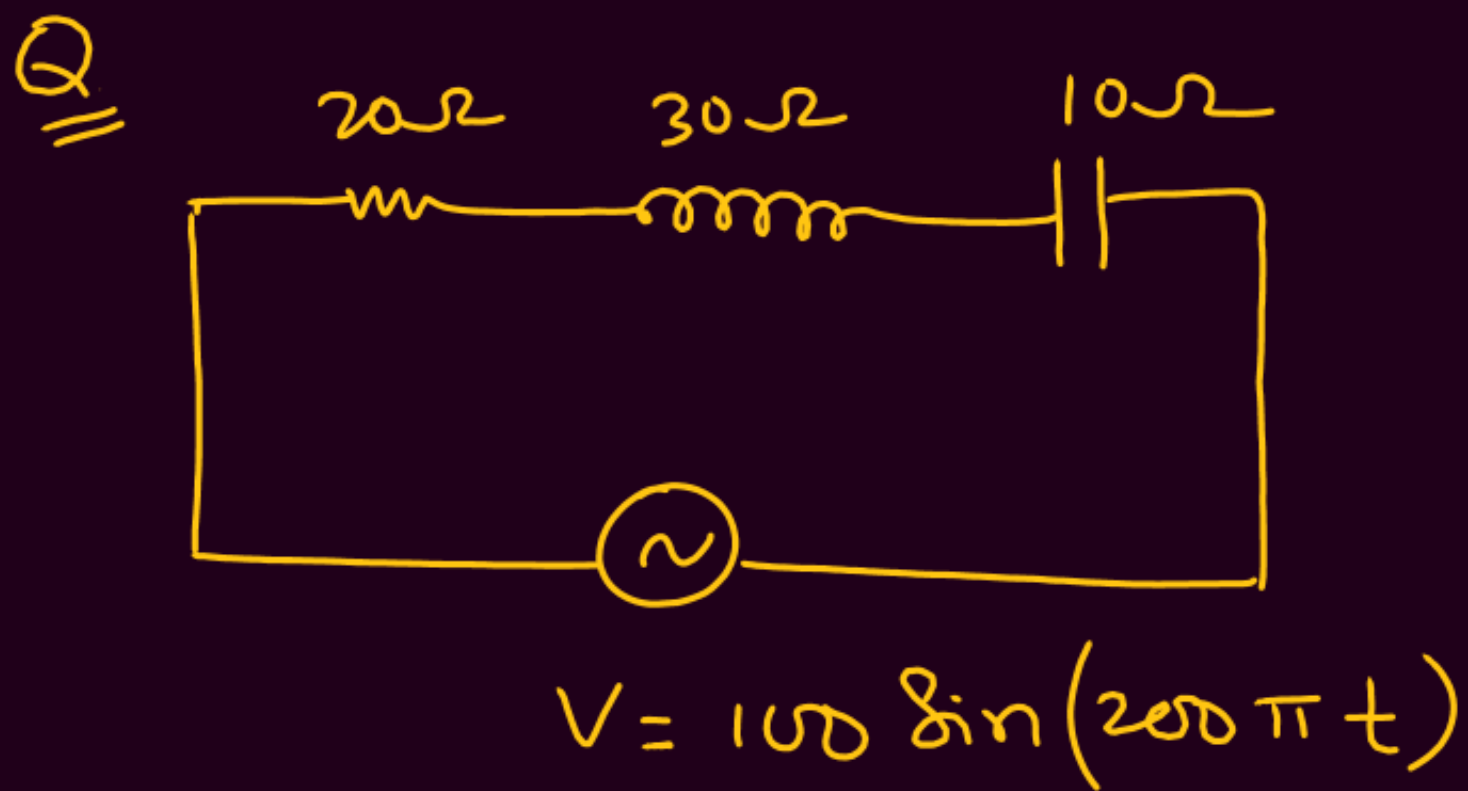

$$\textcircled{1} \quad Z = \sqrt{20^2 + (30 - 10)^2} = 20\sqrt{2} \, \Omega$$

$$\textcircled{2} \quad I_0 = \frac{V_0}{Z} = \frac{100}{20\sqrt{2}} = \frac{5}{\sqrt{2}} \, \text{A}$$

$$I_{\text{rms}} = \frac{5}{\sqrt{2}\sqrt{2}} = \underline{\underline{2.5 \, \text{A}}}$$

$$\textcircled{3} \quad \cos \phi = \frac{20}{20\sqrt{2}} = \frac{1}{\sqrt{2}}$$

$$\textcircled{4} \quad 45^\circ$$

$$\textcircled{5} \quad \text{Wattless} = 2.5 \sin 45^\circ$$



$$V = 100 \sin(200t) \text{ volt}$$

$$X_L = \omega L = 200(100 \times 10^{-3}) = 20 \Omega$$


$$X_C = \frac{1}{\omega C} = \frac{1}{200 \times 200 \times 10^{-6}} = 25 \Omega$$

$$Z = \sqrt{10^2 + (20 - 25)^2} = 5\sqrt{5}$$

$$i_{rms} = \frac{100}{\sqrt{2}(5\sqrt{5})} = \frac{20}{\sqrt{10}} \text{ A}$$

$$\begin{aligned} P_{av} &= i_{rms}^2 R \\ &= \left(\frac{20}{\sqrt{10}}\right)^2 (10) \\ &= 400 \text{ W} \end{aligned}$$

Q:

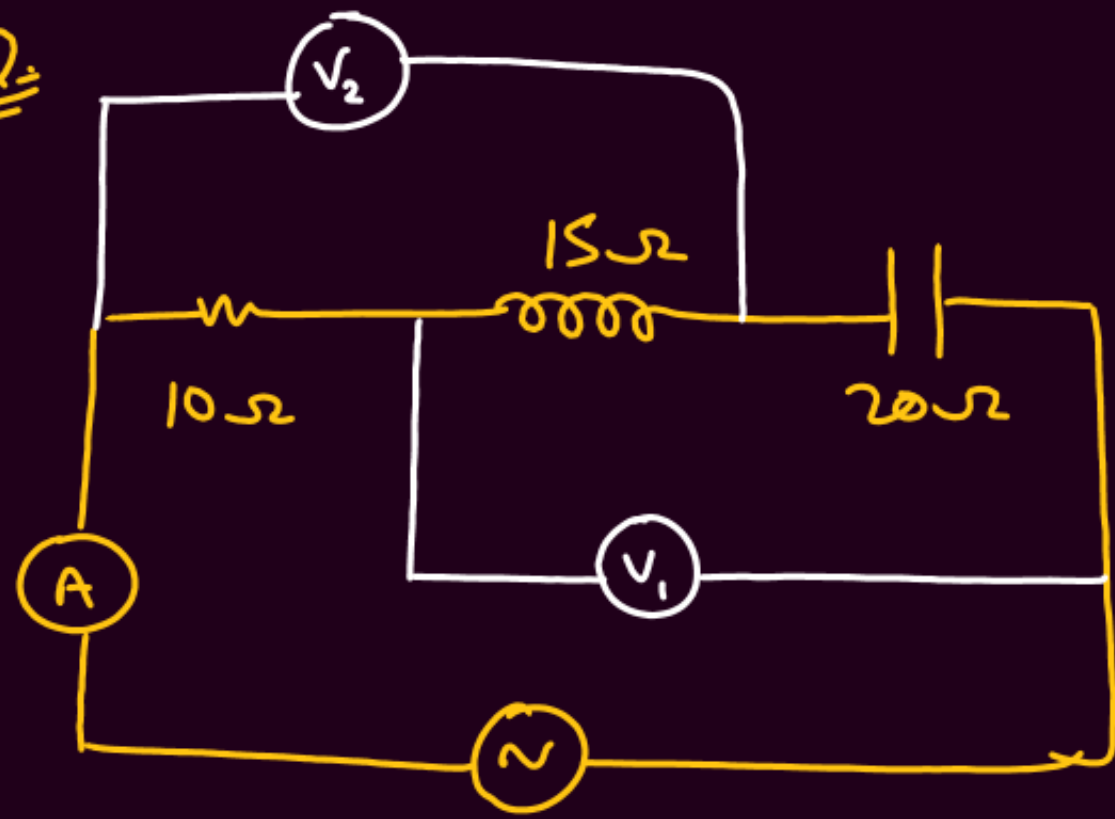

$I = 2\text{ A}$

$V_L = 2(15) = 30\text{ V}$

$V_C = 2(20) = 40\text{ V}$

$V_R = 2(10) = 20\text{ V}$



$30\text{ V} = V_L$





$20\text{ V} = V_R$



30

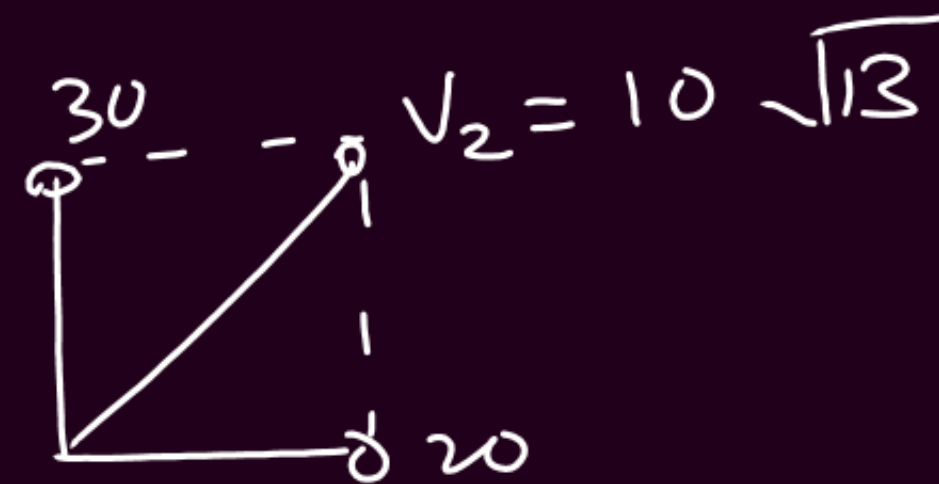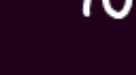

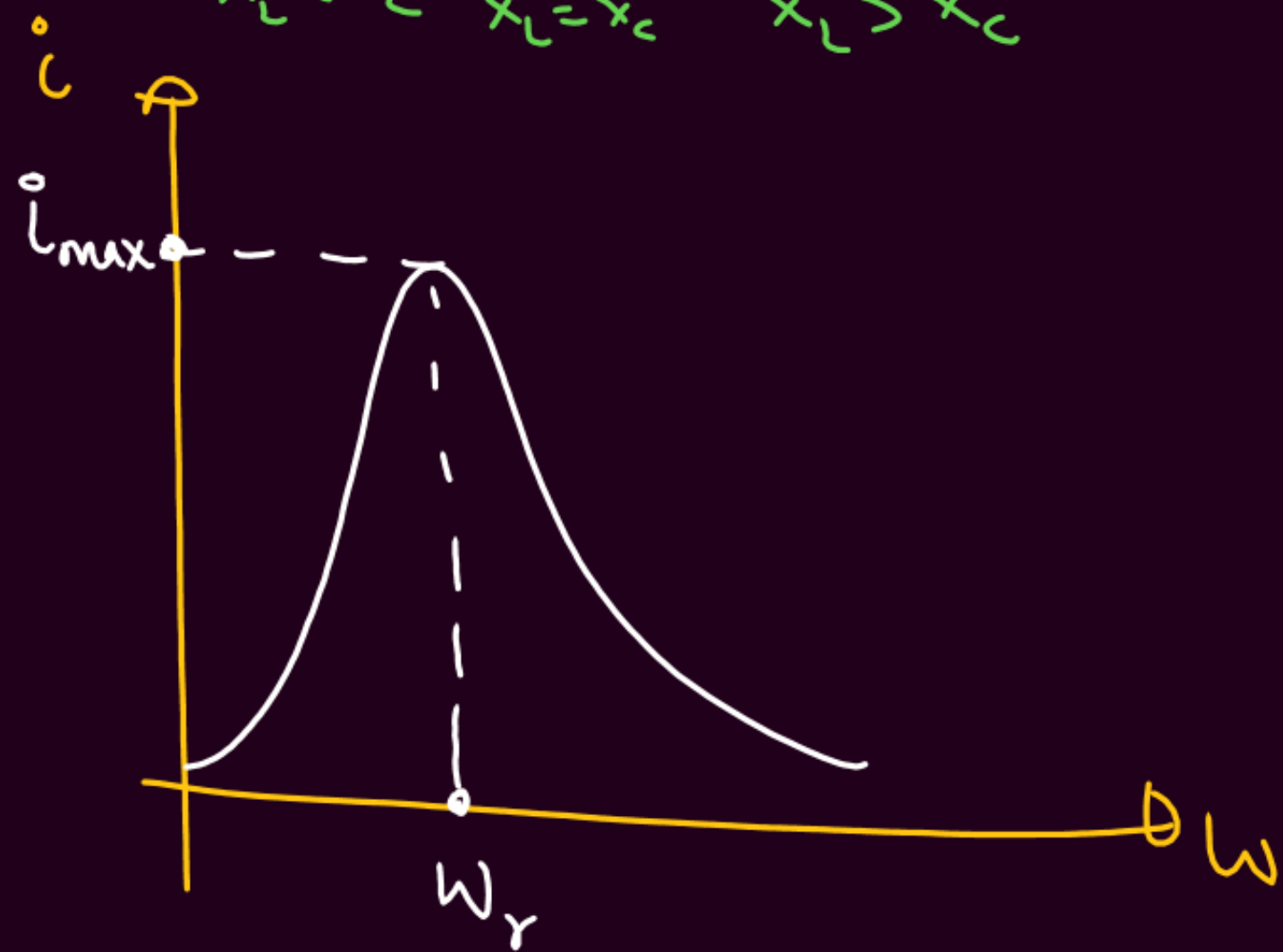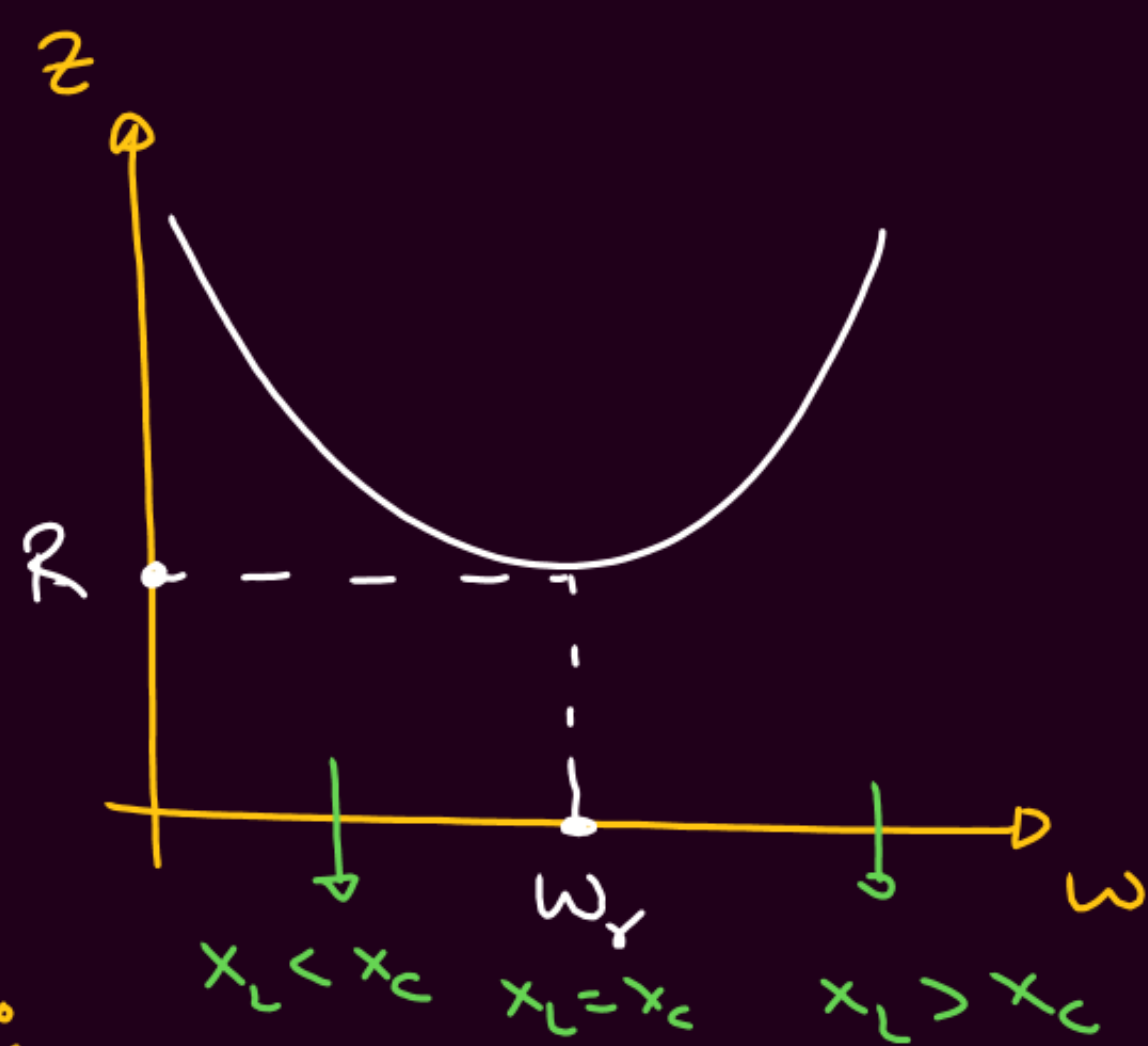

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$i_0 = \frac{V_0}{Z}$$

① if $\omega \rightarrow 0$

$$Z \rightarrow \infty$$

$$i \rightarrow 0$$

② if $\omega \rightarrow \infty$

$$Z \rightarrow \infty$$

$$i \rightarrow 0$$

③ $Z_{min} = R$

$$i_{max} = \frac{V_0}{R}$$

When $X_L - X_C = 0$

$$X_L = X_C$$

$$\omega_r L = \frac{1}{\omega_r C}$$

Resonant
freq.

$$\boxed{\omega_r = \frac{1}{\sqrt{LC}}}$$

$$\textcircled{1} \quad \omega = \omega_r$$

$$X_L = X_C$$


$$\phi = 0$$



Same phase

$$\textcircled{2} \quad \omega < \omega_r$$


$$X_L < X_C$$

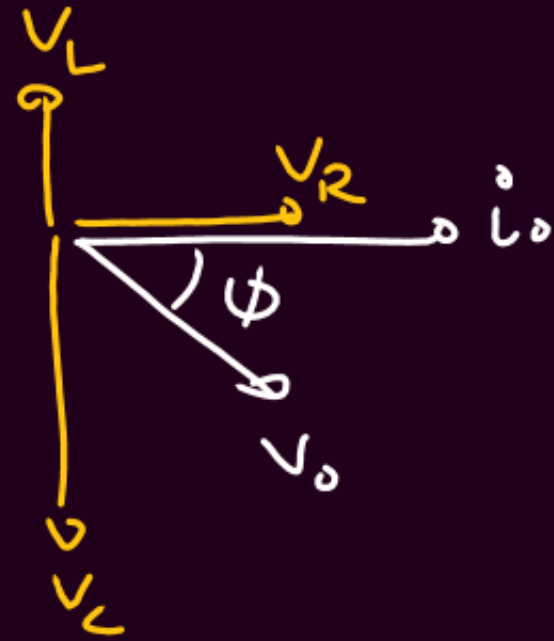

i_0 leads V_0

$$\textcircled{3} \quad \omega > \omega_r$$

$$X_L > X_C$$

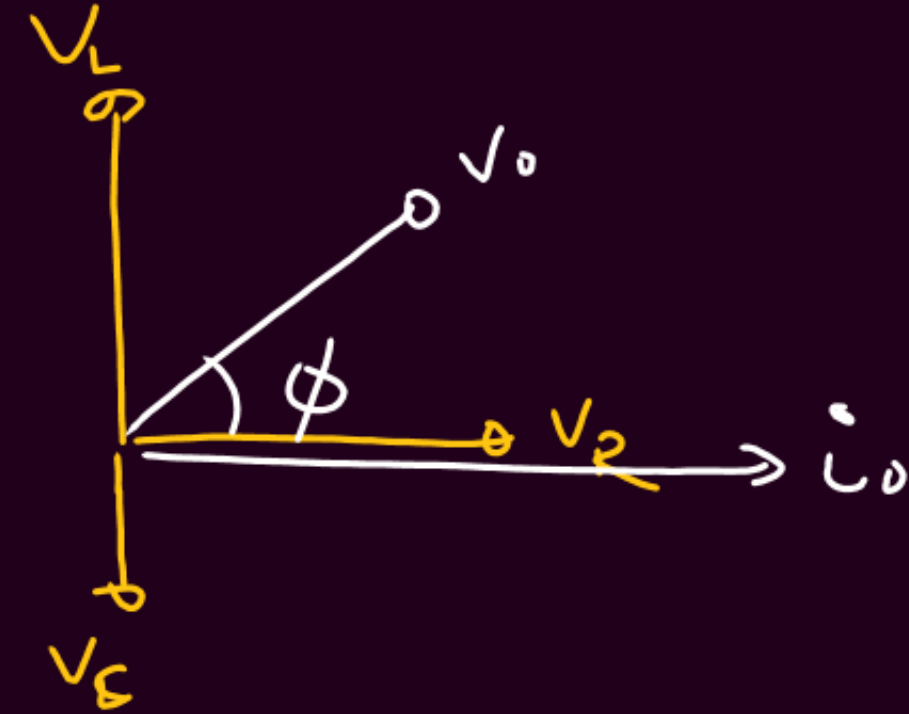

V_0 leads i_0

Resonance

① $i_{\max}$

② $Z_{\min} = R$

③ $X_{L_r} = X_{C_r} = \sqrt{\frac{L}{C}}$

④ $\omega_r = \frac{1}{\sqrt{LC}}$

⑤ $f_r = \frac{1}{2\pi\sqrt{LC}}$

⑥ $T = 2\pi\sqrt{LC}$

⑦ $\tan \phi = 0$


⑧ $\phi = 0$ v & i same in same phase

⑨ $\cos \phi = 1$

⑩ $P_{av} \rightarrow \max$

ωL

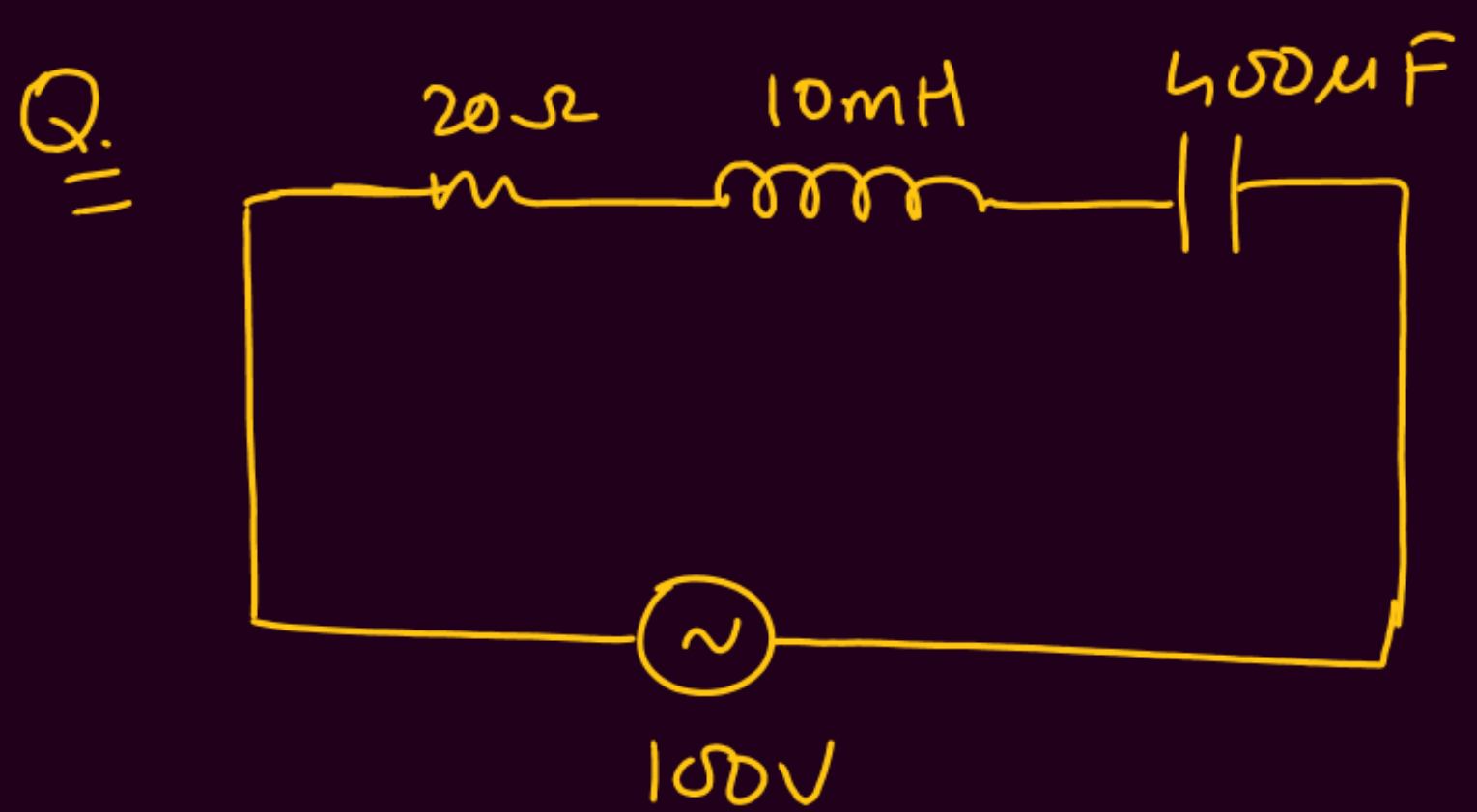$\frac{1}{\sqrt{LC}} L = \sqrt{\frac{L}{C}}$




$$\textcircled{1} f_r = \frac{1}{2\pi \sqrt{10 \times 10^{-3} \times 400 \times 10^{-6}}}$$

$$= \frac{1}{2\pi (2) \times 10^{-3}} = \frac{250}{\pi} \text{ Hz}$$

$$\textcircled{2} P_{av} = i_{rms}^2 R$$

$$= \left(\frac{100}{20} \right)^2 (20) = \underline{500 \text{ W}}$$

Q

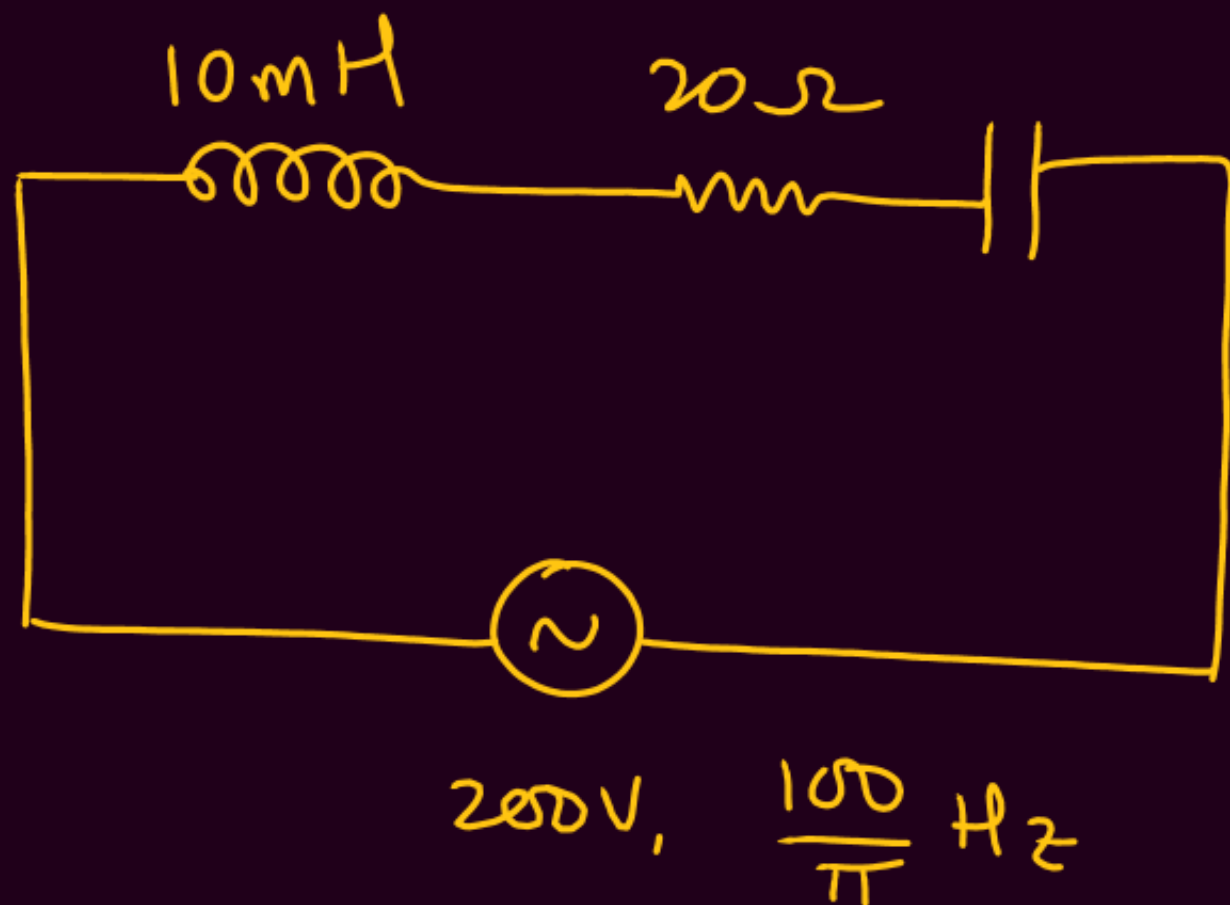

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$


$$\frac{100}{\pi} = \frac{1}{2\pi\sqrt{LC}}$$

$$LC = \frac{1}{200 \times 200}$$

$$C = \frac{1}{200 \times 200 \times 10 \times 10^{-3}} = \frac{1}{400}$$

$$C = \frac{10^6}{400} \mu F = 2500 \mu F$$



R-L

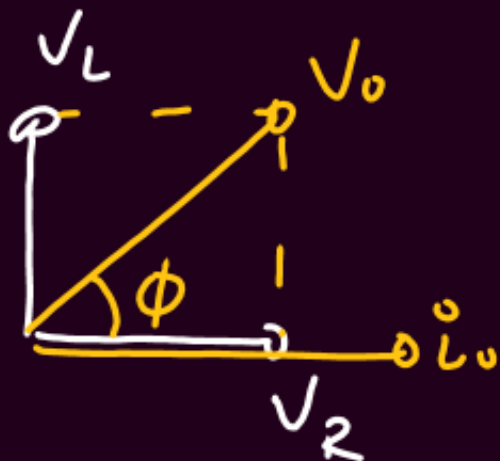


$$Z = \sqrt{R^2 + X_L^2}$$

$$V_0 = \sqrt{V_R^2 + V_L^2}$$

V leads i

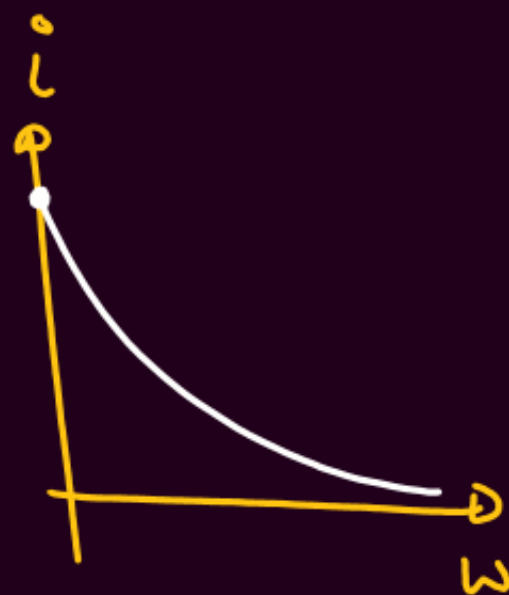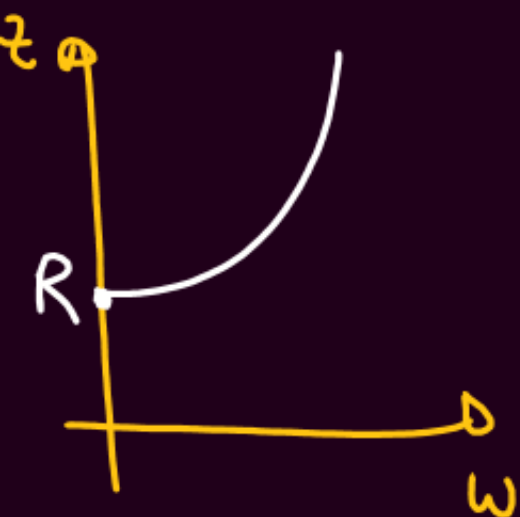



R-C

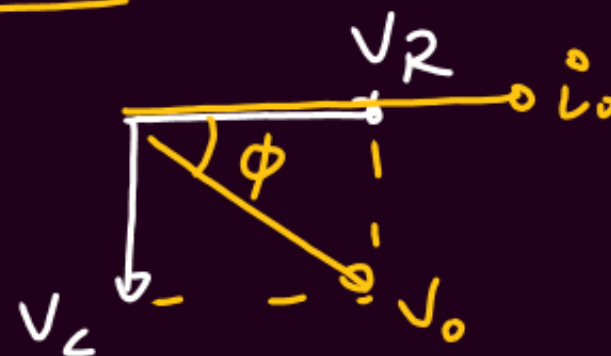

$$Z = \sqrt{R^2 + X_C^2}$$

$$V_0 = \sqrt{V_R^2 + V_C^2}$$

i leads V

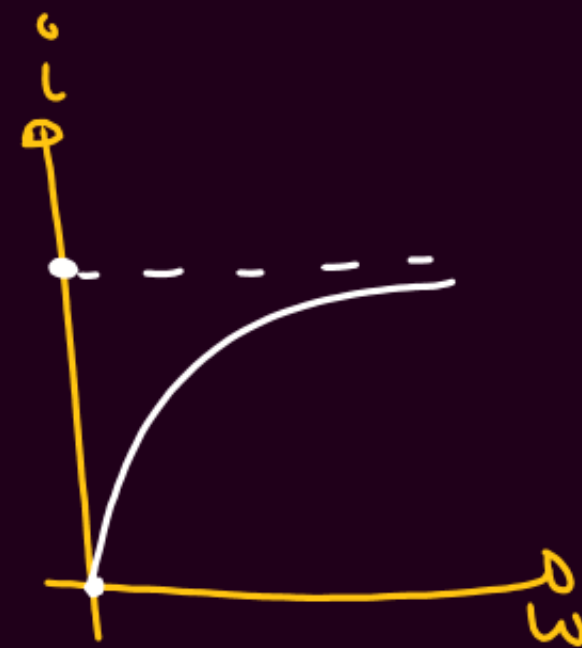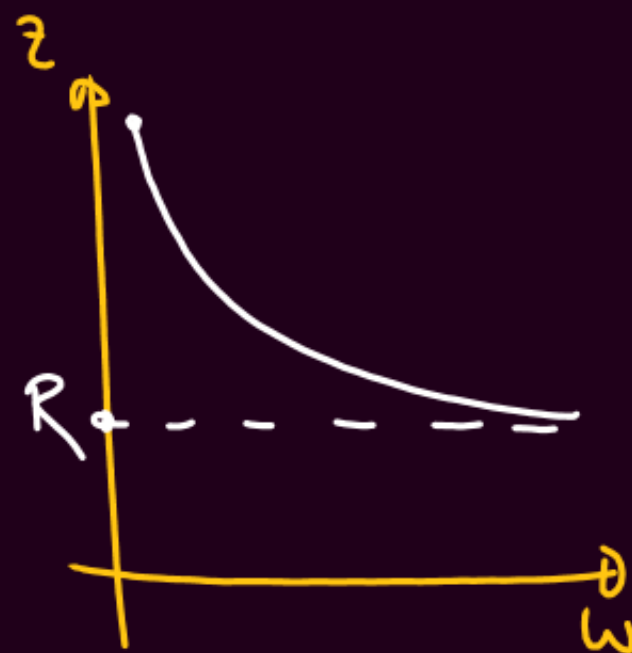



L-C



$$Z = |X_L - X_C|$$

$$V_0 = |V_L - V_C|$$


$\phi = \pm \pi/2$

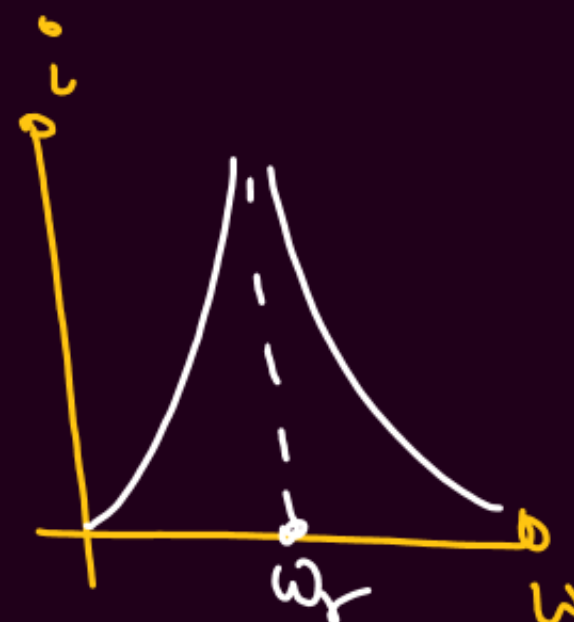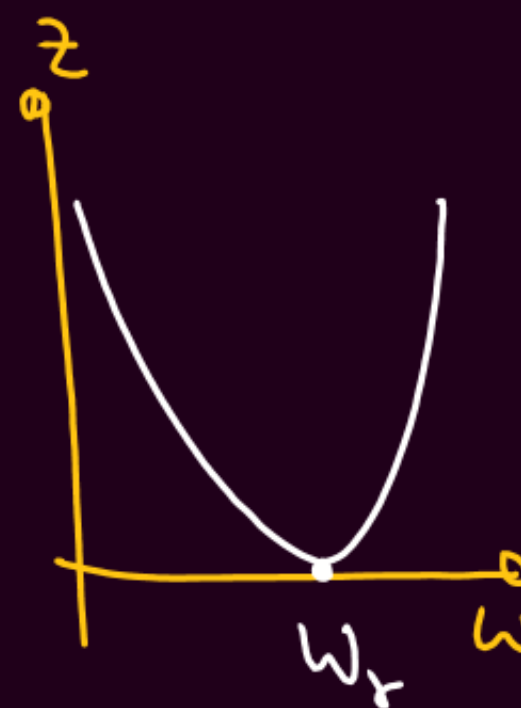

Q. Choke coil.

100 V DC $\rightarrow$ 5 A

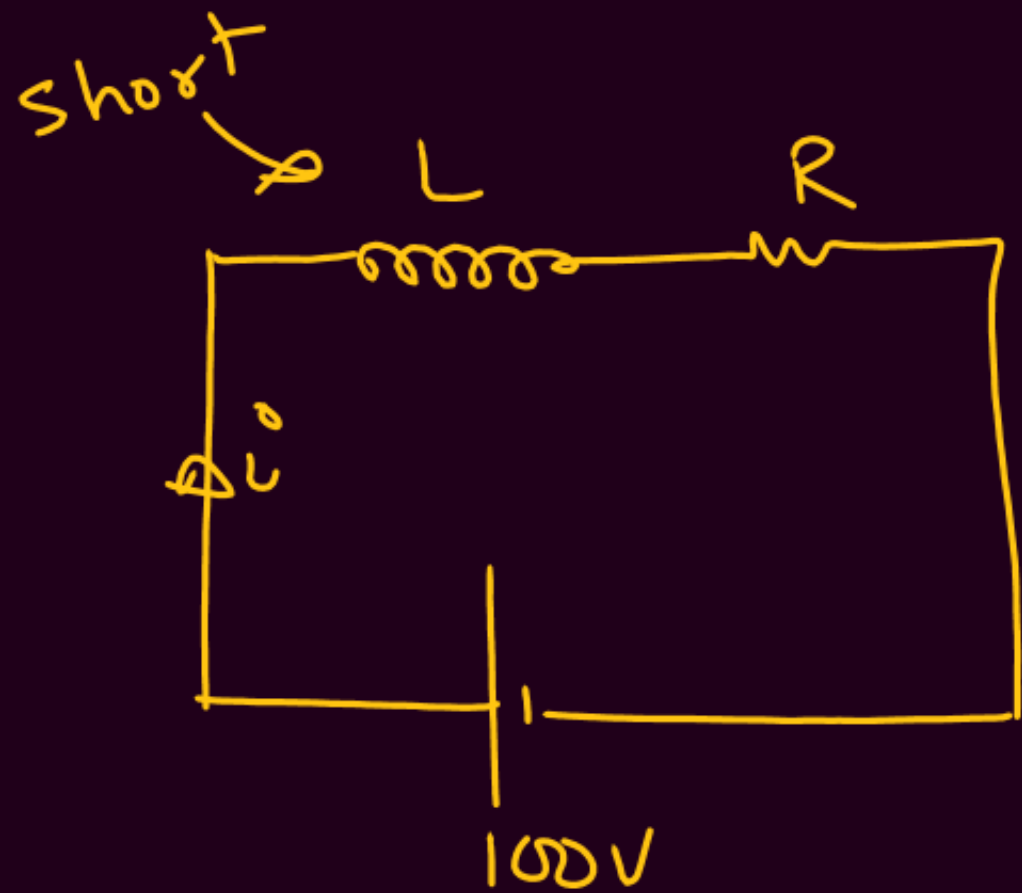100 V, $\frac{100}{\pi}$ Hz $\rightarrow$ 2 A



$$i = \frac{V}{R} \quad \bigg| \quad R = 20\Omega$$
$$5 = \frac{100}{R}$$



$$\frac{V_0}{i_0} = Z = \sqrt{R^2 + (\omega L)^2}$$

$$\frac{100}{2} = \sqrt{20^2 + (200L)^2}$$

$$50 = 20 \sqrt{1^2 + (10L)^2}$$

$$\frac{25}{4} = 1 + 100L^2$$

$$\frac{21}{4} = 100L^2$$

$$L^2 = \frac{21}{400}$$

$$L = \frac{\sqrt{21}}{20} \text{ H}$$

Q. If i lags V
(possibility)

✓ 1) L

2) C

✓ 3) LC

✓ 4) RL

5) RC

✓ 6) RLC



$L \uparrow$

$X_L \uparrow$

$Z \uparrow$

$i \downarrow$

Brightness $\downarrow$

Skin Effect

→ AC

→ multiple strands


$$i = 3 \sin(\omega t) + 4 \sin(\omega t + \frac{\pi}{3})$$

rms = ?

$$i_{\text{peak}} = \sqrt{3^2 + 4^2 + 2(3)(4) \cos \frac{\pi}{3}}$$

$$= \sqrt{37}$$

$$r_{\text{ms}} = \sqrt{\frac{37}{2}}$$

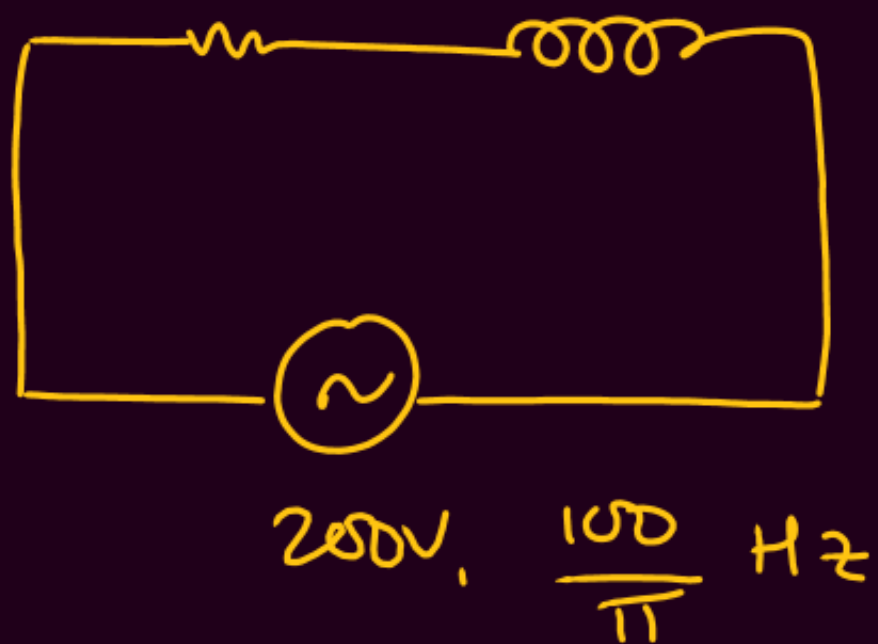

if $V_R = 100V$

① $\phi = ?$

② $V_L = ?$

① $\cos \phi = \frac{V_R}{V_0} = \frac{100}{200} = \frac{1}{2}$

$\phi = \pi/3$


② $V_0^2 = V_R^2 + V_L^2$

$(200)^2 = 100^2 + V_L^2$

$V_L^2 = 200^2 - 100^2$

$V_L = 100 \sqrt{2^2 - 1^2}$
 $= \underline{100\sqrt{3} V}$

PYQ

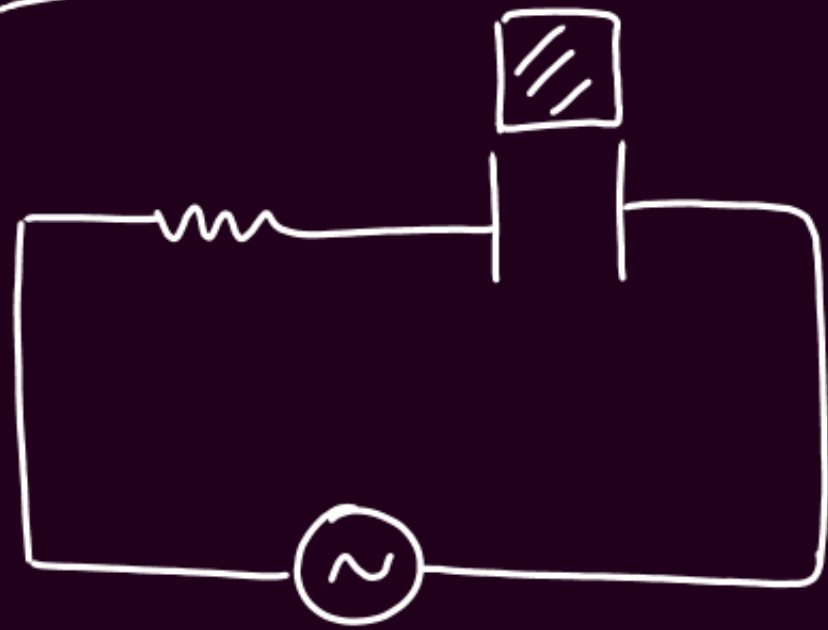

① Air filled

② Mica filled

1) $i_1 < i_2$

2) $V_{C1} > V_{C2}$

Mica

$C \rightarrow KC \uparrow$

$X_C \downarrow$

$Z \downarrow$

$i_0 \uparrow$

$$X_C = \frac{1}{\omega C}$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$i_0 = \frac{V_0}{Z}$$

$$V_0^2 = V_R^2 + V_C^2$$


Const. $(i_0 R)^2 +$

$\uparrow \quad \downarrow$

Quality factor $Q = \frac{\omega_r}{\Delta\omega} = \frac{\omega_r L}{R} = \frac{X_{Lr}}{R} = \frac{X_{Cr}}{R}$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

i (Sharpness)

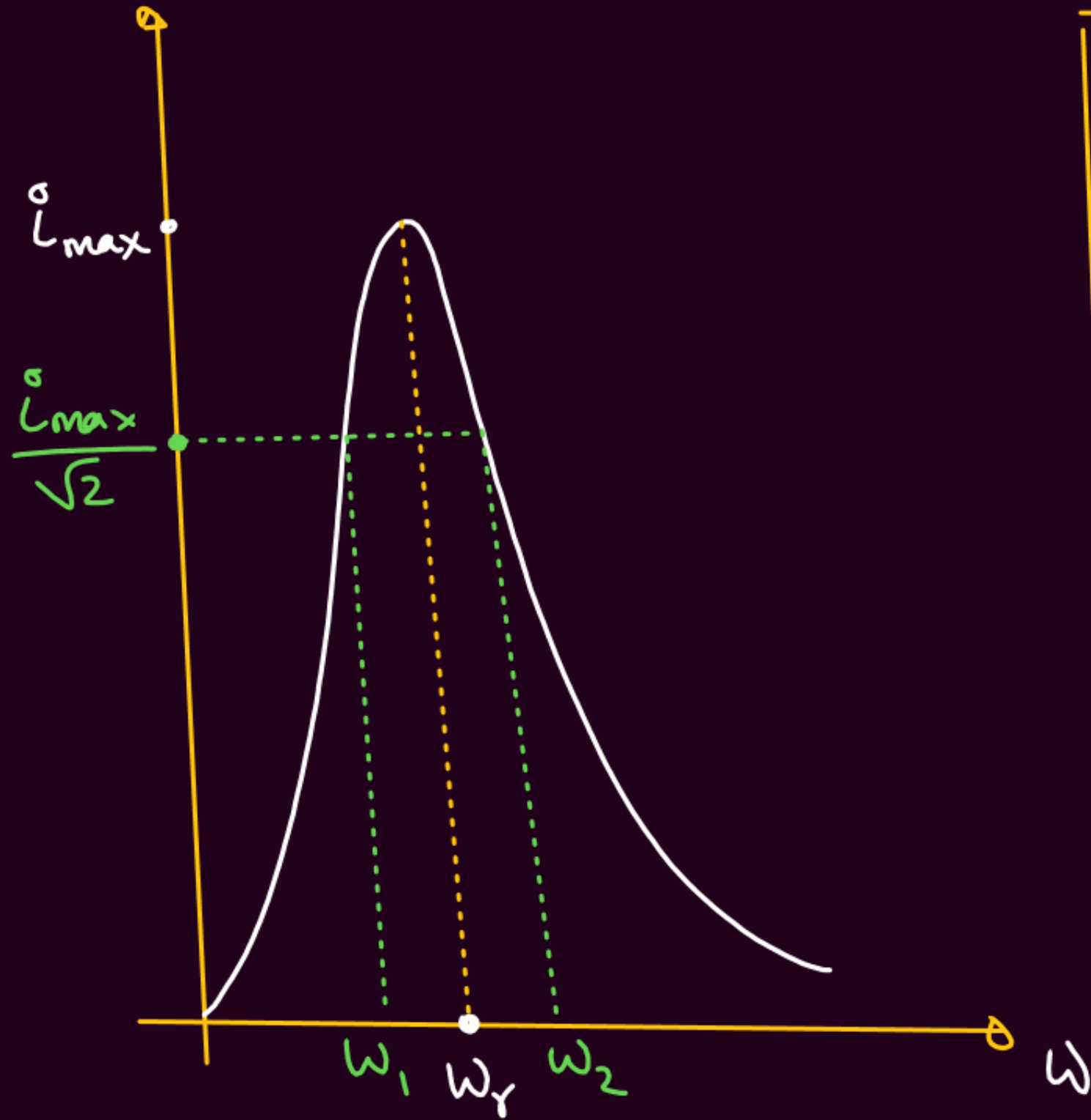

"Half Power"

$$P_{\max} = i_{\max}^2 R$$

$$P_{\text{Half}} \rightarrow \frac{1}{2} P_{\max}$$

$$(1) i = \frac{i_{\max}}{\sqrt{2}}$$

$$Z_{\min} = R$$

$$(2) Z = R\sqrt{2}$$



$$(3) X_L - X_C = R$$

$$(4) \phi = 45^\circ$$

$$(5) \text{P.F.} = \cos \phi = \frac{1}{\sqrt{2}}$$

(5) Bandwidth

$$\Delta f = f_2 - f_1 = \frac{\omega_2 - \omega_1}{2\pi}$$

$$(6) \Delta\omega = \frac{R}{L}$$

(7) Sharpness / Quality Q


$$R \downarrow \quad L \uparrow \quad C \downarrow$$

(26) $L = 5H$
 $C = 80\mu F$
 $R = 40\Omega$
 $V = 230V$

ω_1 / ω_2

$$\omega_r = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5 \times 80 \times 10^{-6}}} = \frac{1}{\sqrt{400 \times 10^{-6}}}$$
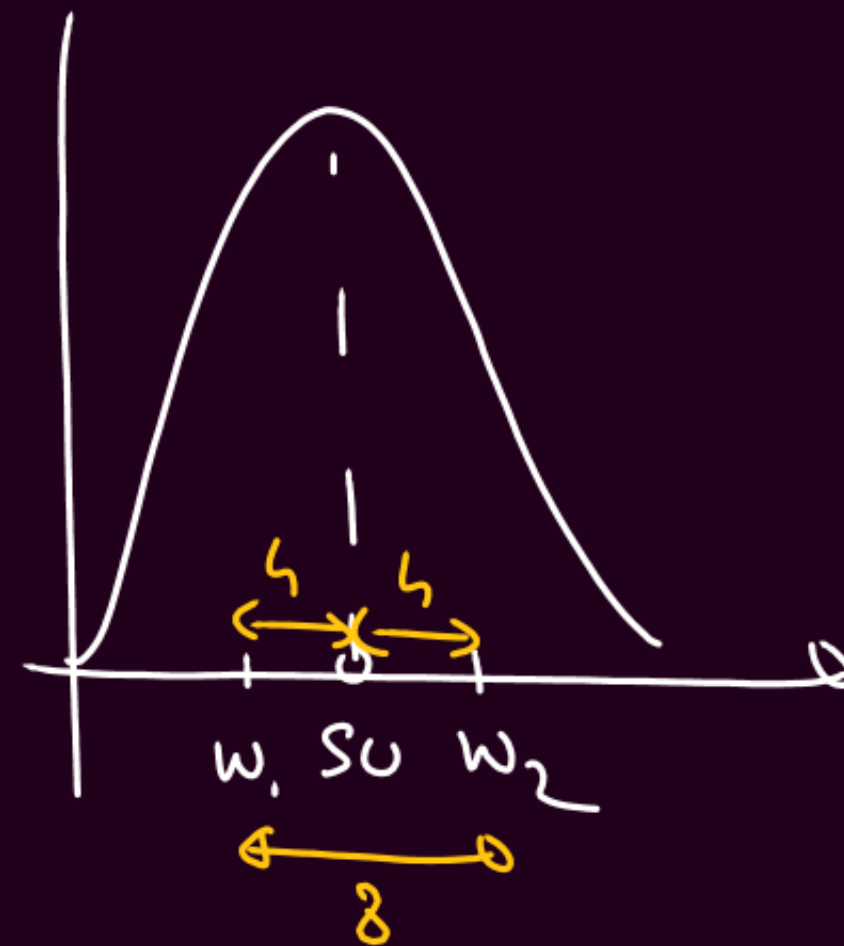
$$= \frac{1}{2 \times 10 \times 10^{-3}} = \frac{100}{2} = 50 \text{ rad/s}$$



$$\Delta\omega = \frac{R}{L} = \frac{40}{5} = 8 \text{ rad/s}$$

